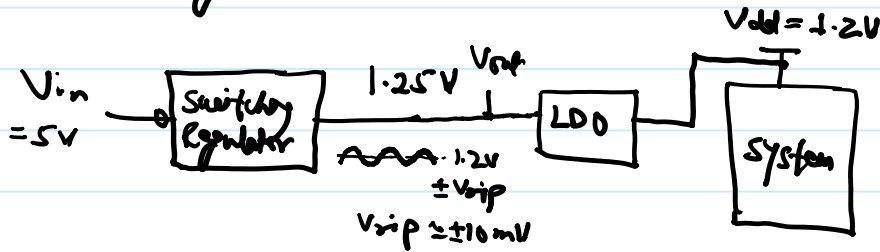



## Applications of LDOs

# Regulator with lower  $V_{in} - V_{out} \rightarrow$  dropout


# Sub-regulated LDOs


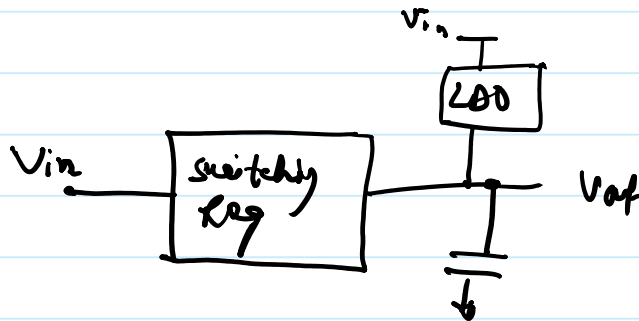
# Parallel supply → to handle higher load current and fast transients



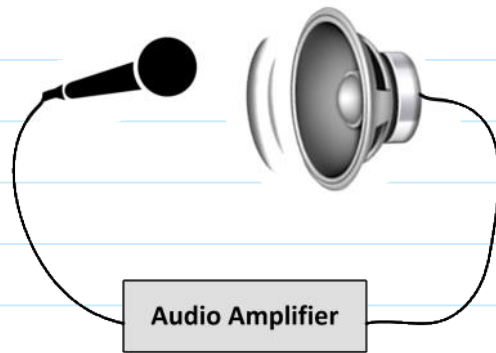
# Overview of Feedback System and Stability



Positive Feedback  $\rightarrow$  unstable
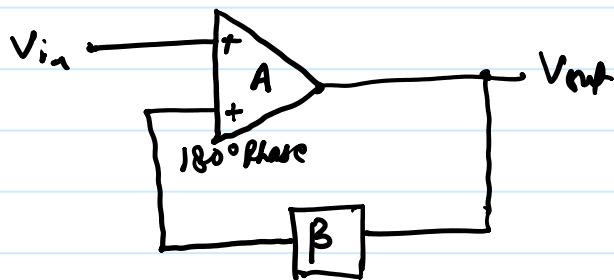
# Air conditioner  $\rightarrow$  negative Feedback (Stable)



$$\frac{V_{out}}{V_{in}} = \frac{A}{1 + A\beta} \quad A\beta = -1$$


$$\frac{V_{out}}{V_{in}} \rightarrow \infty$$

$A\beta \rightarrow$  Loop Gain

$\beta \rightarrow$  feedback factor

$A \rightarrow$  feedforward gain

## First Order System

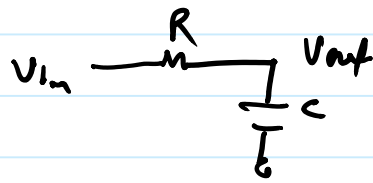

$$\omega_p = \frac{1}{RC}$$

$$H(s) = \frac{1}{1 + s/\omega_p}$$

$$|H(s)| = \frac{1}{\sqrt{1 + (\omega/\omega_p)^2}}$$

$$\angle H(s) = -\tan^{-1}\left(\frac{\omega}{\omega_p}\right)$$

$$|H(s)| = \frac{\omega_p}{\omega} \quad \text{for } \omega \gg \omega_p$$

$$|H(s)| \text{ (dB)} = -20 \log_{10}\left(\frac{\omega}{\omega_p}\right)$$

$$\omega = 10\omega_p$$

$$|H(s)| = -20 \text{ dB}$$

$$\angle H(s) = -45^\circ \quad \text{for } \omega = \omega_p$$

$$\angle H(s) \approx -85^\circ \quad \text{for } \omega = 10\omega_p$$

# Bode Plot

