

Lecture-42 & 43

EE5325 Power Management Integrated Circuits

Dr. Qadeer Ahmad Khan

Integrated Circuits and Systems Group
Department of Electrical Engineering
IIT Madras



EE5325 Power Management Integrated Circuits
Integrated Circuits and Systems Group, Department of EE, IIT Madras

1

Limitations of Analog Controller

- The compensation network is usually designed with RC and for 1MHz or lower frequencies, the value of capacitor is large and kept off-chip
- The discrete nature of compensator makes it difficult to track any variation in loop parameters (L, C, R)
- Does not provide reconfigurability

TABLE 1. OUTPUT FILTER COMBINATIONS

L (μ H)	C (μ F)	Pole (kHz)	Pole with 20% Tolerance (kHz)	Result
10	4.7	23.2	29.0	Unstable
15	4.7	19.0	23.7	Marginally stable
22	4.7	15.7	19.6	Stable
10	10	15.9	19.9	Stable
6.8	10	19.3	24.1	Marginally stable
4.7	10	23.2	29.0	Unstable
2.2	22	22.9	28.6	Unstable
4.7	22	15.7	19.6	Stable
6.8	22	13.0	16.3	Stable

Ref: Optimizing Low-Power DC/DC Designs – External versus Internal Compensation, Michael Day, Texas Instruments



EE5325 Power Management Integrated Circuits
Integrated Circuits and Systems Group, Department of EE, IIT Madras

2

Digital Control of DC-DC Converters




Why Digital Control?

- Unlike the analog control, digital control provides the flexibility of tuning filter coefficients and can be easily reconfigured
- Fully integrated solution - no off chip compensation
- The loop can be designed to adapt any changes in both on-chip and off-chip components due to aging, process, temperature or vendor selection
- Easily scalable with the process-blocks can be synthesized



Digitally Controlled DC-DC Converter

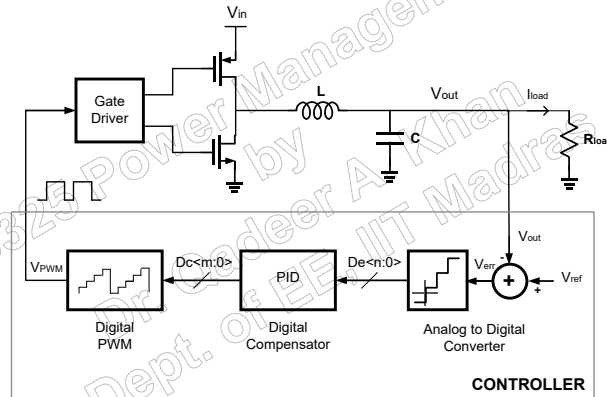- The error voltage is digitized and processed in digital compensator (digital filter)
- The analog PWM is replaced with digital PWM



Constraints on ADC

- The resolution of ADC depends upon the regulation specification
- $V_{out} = 1V$, if regulation specification is 0.1% $\rightarrow \Delta V = 1mV$
 - Requires a 10Bit ADC
- Conversion rate depends upon PWM switching Frequency, ideally it should be less than one clock period
 - A slow ADC might interfere with the loop dynamic and degrade phase margin




Analog-to-Digital Converter (ADC) Architectures




Windowed ADC

- Designing a high resolution ADC is complex and power consuming
- Since the output is a fixed voltage and need to be regulated around reference voltage, a windowed ADC can be used
- This reduces the no. of bins without degrading the regulation
- The range of ADC is restricted to small input
 - If LSB = 1mV then ADC can be designed to resolve few LSBs
 - For example, window size = 6mV \rightarrow requires only levels means 3-bit ADC will give the accuracy of 10-bit

 

Non-Uniform Quantization

 - A windowed ADC saturates under any transient at the output hence loop goes into non-linear – poor transient response
- A non-uniform quantize can be used. The quantization level is small around zero error ($V_{out} = V_{ref}$) and increased gradually as V_{out} move away




Ref: Haitao Hu et al, "Nonuniform A/D Quantization for Improved Dynamic Responses of Digitally Controlled DC-DC Converters", IEEE Transactions on Power Electronics, July 2008



ADC Architectures - VCO Based ADC

 - The VCO is used as the Active load of transconductor
- The two VCOs operate at same frequency if $V_{out} = V_{ref}$
- Any error in the output voltage causes difference in the two frequencies
- Digital error can be generated by counting the no. of VCO clock cycles
- Overall gain = $A_{gm} \cdot K_{vco} \rightarrow$ provides good DC regulation




Ref: Xiao, J.; Peterchev, A.; Zhang, J.; Sanders, S., "A 4 μ A-quiescent-current dual-mode buck converter IC for cellular phone applications" IEEE International Solid-State Circuits Conference, 2004. Digest of Technical Papers. ISSCC-2004



Delay Line Based ADC

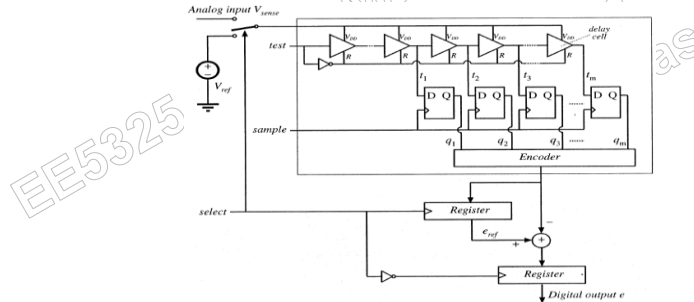- V_{ref} and V_{out} is converted into delay and phase difference is measured
- Uses single delay line and V_{ref} is sampled and calibrated in order to cancel any variation due to PVT
- Poor PSRR
 - Since V_{ref} and V_{out} are sampled at different instance any noise in the VDD may introduce error



Ref: Patella, B.J.; Prodic, A.; Zirger, A.; Maksimovic, D., "High-frequency digital PWM controller IC for DC-DC converters", IEEE Transactions on Power Electronics, Volume 18, Issue 1, Jan 2003




EE5325 Power Management Integrated Circuits
Integrated Circuits and Systems Group, Department of EE, IIT Madras

11

Improved Delay Line Based ADC

 - V_{ref} and V_{out} use separate delay lines and sampled at same instance → good PSRR
- Uses differential input pairs to bias the delay lines in order to reduce the dependency on V_{ref} → VCDL characteristic does not change across different V_{out}



Ref: Lukic, Z.; Rahman, N.; Prodic, A., "Multibit Sigma-Delta PWM Digital Controller IC for DC-DC Converters Operating at Switching Frequencies Beyond 10 MHz", IEEE Transactions on Power Electronics, Sept. 2007



EE5325 Power Management Integrated Circuits
Integrated Circuits and Systems Group, Department of EE, IIT Madras



12

Digital Pulse-Width Modulator (DPWM) Architectures



DPWM Resolution - Limit Cycle Oscillation

  - The resolution of DPWM should be higher than the resolution of ADC to avoid limit cycle oscillation
 - 1 LSB change in duty cycle should cause lesser change in V_{out} than 1 LSB of ADC
- If DPWM resolution is less, the ADC does not find any zero-error bin
- The output oscillates around the regulated dc voltage.
 - The amplitude of oscillation depends upon DPWM resolution




Peterchev, A.V.; Sanders, S.R., "Quantization resolution and limit cycling in digitally controlled PWM converters", IEEE Transactions on Power Electronics, Volume 18, Issue 1, Jan 2003




Counter Based DPWM

- Uses a high frequency clock to Count the PWM clock period
- The Counter output is compared with the error code and duty cycle is reset when counter output crosses the error code
- The step size of duty cycle is given by $\Delta D = \frac{f_{sw}}{f_{clk}}$
- Difficult to realize as max frequency is limited by the technology
 - If ADC LSB = 1mV, then 1 LSB of DPWM should cause less than 1mV change in Vout to avoid limit cycling → if DC-DC is switching at 1MHz then it may require high frequency clock of few GHz

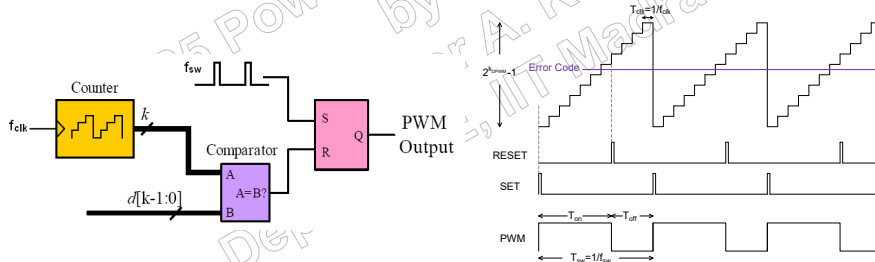

DLL Based DPWM

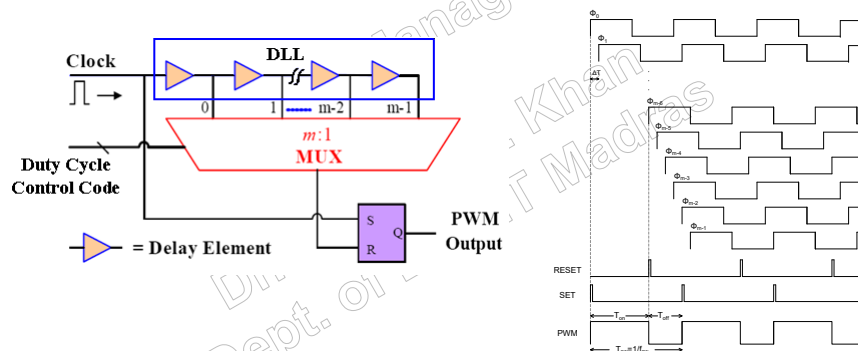- Does not require high frequency clock → relatively low power consumption
- Use multiple phase to reset the duty cycle
- The duty cycle step size is defined by $\Delta D = \frac{1}{m}$; m is the no. of phases




Increasing the resolution of DPWM

- The resolution of counter based and delay in DLL based DPWM is limited by the technology or power consumption
- Dithering is generally used to increase the resolution
- Causes low frequency ripple at the output voltage → depends on resolution

Fixed Ripple Frequency Dither

2-bit LSB	2 ² switching cycles				Sequence average
	0	2	3	1	
00	0	0	0	0	0
01	0	0	0	1	1/4
10	0	0	1	1	1/2
11	0	1	1	1	3/4

 

$$D_{C1}=0.1, D_{C2}=0.2$$

$$D_{C1}+1/4 \text{ LSB} = (3 \cdot D_{C1} + 1 \cdot D_{C2})/4$$


$$= (0.3 + 0.2)/4 = 0.125$$

$$\rightarrow \Delta D = 0.125 - 0.1 = 0.025$$

4x resolution


Variable Ripple Frequency Dither (reduce ripple)

2-bit LSB	2 ² switching cycles				Sequence average
	0	2	3	1	
00	0	0	0	0	0
01	0	0	0	1	1/4
10	0	1	0	1	1/2
11	0	1	1	1	3/4

 

Delta-Sigma Based PWM Control

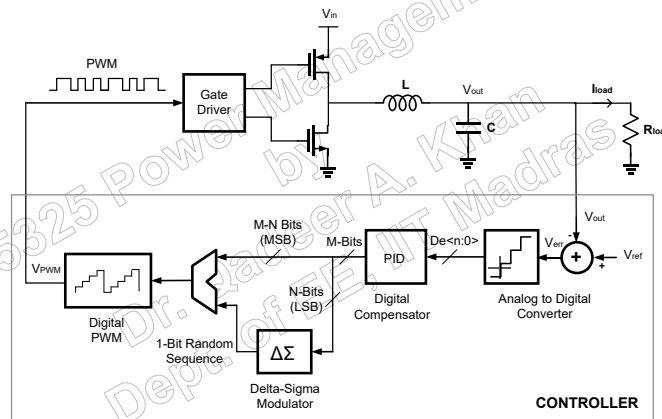- The low frequency dither tones is randomized by using delta-sigma modulator
- Relatively slower as compared to standard dithering



Adaptive Compensation



Need for Adaptive Compensation

- The control loop can be made self compensated by automatic tuning of filter parameters
- Provides robustness over wide variation of operating condition and component values → Plug and Play
- Gain, Phase Margin and values of internal and external components (L, C, R_{on}, R_{esr} etc.) can be monitored continuously



Tuning Methods


Middlebrooke's Method

- Based on Middlebrooke's injection technique
- Middlebrooke's Technique: Does not require to break the loop
- Crossover frequency can be determined by the injection signal frequency at which loop gain becomes unity
- Loop TF is given by

$$T = \frac{-V_y}{V_x}$$

$$f_c = f_{inj}, \quad \left| T(e^{j\omega_{inj}T}) \right| = 1 \Rightarrow \|V_y\| = \|V_x\|$$
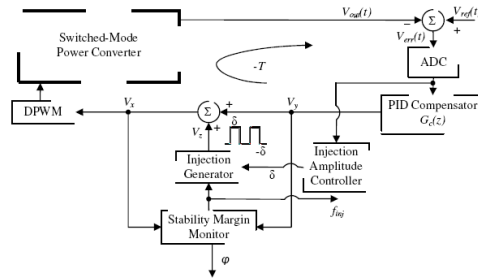
$$\varphi = \varphi_m = \angle V_y(f_{inj}) - \angle V_x(f_{inj})$$



Ref: J. Morroni, R. Zane, D. Maksimovic, "An Online Phase Margin Monitor for Digitally Controlled Switched Mode Power Supplies" Power Electronics Specialist Conference, 2008




EE5325 Power Management Integrated Circuits
Integrated Circuits and Systems Group, Department of EE, IIT Madras

21

Middlebrooke's Method (Contd.)

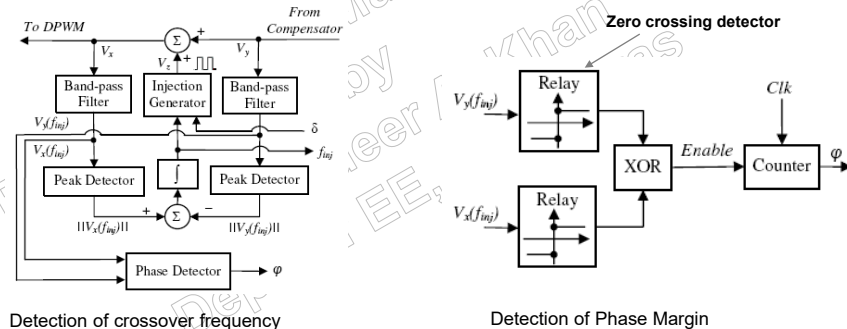- The injected signal is variable frequency square wave therefore requires narrow BPF to get rid of higher harmonics
- Peak Detector is used to determine the amplitude of V_x and V_y and compared
- Phase Margin is determined as the phase difference between two signal



EE5325 Power Management Integrated Circuits
Integrated Circuits and Systems Group, Department of EE, IIT Madras

22


Correlation Based Method

- Uses PRBS generator to determine the impulse response and transfer function is determined by DFT
- PRBS is shaped in pre-emphasis filter which boost the output above the noise floor of ADC in order to reduce the quantization effect
- Cross correlation to obtain the impulse response is computed using Fast Walsh-Hadamard Transform (FWHT)



Correlation Based Method (Contd.)

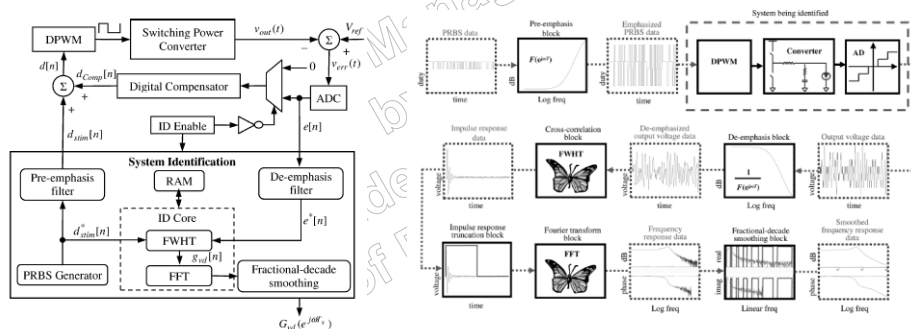- PRBS is shaped in pre-emphasis filter which boost the output above the noise floor of ADC in order to reduce the quantization effect
- Cross correlation to obtain the impulse response is computed using Fast Walsh-Hadamard Transform (FWHT)



M. Shirazi, J. Morroni, A. Dolgov, R. Zane, D. Maksimovic, "Integration of Frequency Response Measurement Capabilities in Digital Controllers for DC-DC Converters", IEEE Transaction on Power Electronics, 2008



Limit Cycling Oscillation Based Tuning

- The method enforces the limit cycle oscillations by reducing the resolution of DPWM under test mode
- The oscillations at the output are analyzed to measure the loop parameters
- The loop is turned into Integral to measure the oscillations

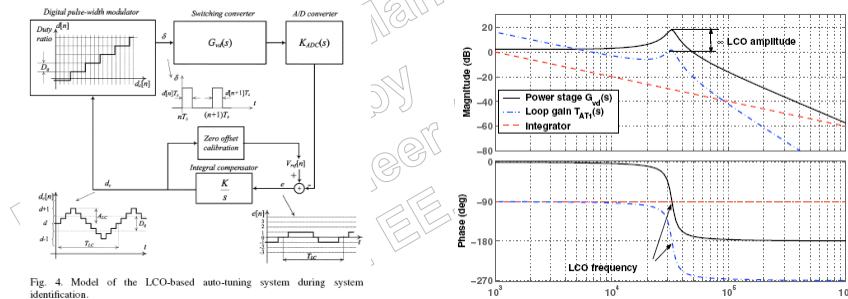


Fig. 4. Model of the LCO-based auto-tuning system during system identification.

Z. Zhao, A. Prodic, "Limit-Cycle Oscillation Based Auto-Tuning System for Digitally Controlled DC-DC Power Supplies", IEEE Transaction on Power Electronics, 2007



Limitations with Digital Control

- ADC is not a big constraint for DC-DC as there are numerous architectures available which can easily meet the requirement
- Designing high resolution of DPWM is a challenging task for faster loop bandwidth as dithering slows down the loop
- All the Adaptive Compensation techniques reported in papers require test signal during normal operation → normal operation is disturbed or amplitude of test signal should be low enough → reduced accuracy
- The existing adaptive compensation techniques can't be used in dynamic supply applications such as RF Power Amplifier and Class-H audio where supply is modulated with RF envelope or audio signal → test signal might fall into the signal frequency





Simplified Tuning Techniques



Measurement Method

  - The technique works in two steps
- In test mode during the startup, a short pulse is applied at the power stage and oscillations are measured → ω_0 is determined
- Once the ω_0 is known, duty cycle is modulated with a sine wave of frequency ω_0 and amplitude is measured at the output → gives Q_0



Measurement Method

$$\text{Loop T.F.}, T(s) = \frac{V_{in}}{V_m} G_c(s) H_{LC}(s)$$

$$H_{LC}(s) = \frac{w_0^2}{s^2 + \frac{w_0}{Q_0}s + w_0^2}$$

$$w_0 = \frac{1}{\sqrt{LC}} \sqrt{1 + \frac{R_{loss}}{R_{load}}} \quad \text{and} \quad Q_0 = \sqrt{LC} \sqrt{\frac{1 + \frac{R_{loss}}{R_{load}}}{\frac{L}{R_{load}} + CR_{loss}}}$$

$$\text{if } G_c(s) = \frac{s^2 + \frac{w_0}{Q_0}s + w_0^2}{s}$$

$$\text{Loop T.F.}, T(s) = \frac{V_{in}}{V_m} G_0 \frac{1}{s}$$

Loop becomes a single pole system

$$\text{under no load condition } (R_{load} \rightarrow \infty)$$

$$w_0(I_{load} = 0) = \frac{1}{\sqrt{LC}} \quad \text{and} \quad Q_0(I_{load} = 0) = \sqrt{LC} \frac{1}{CR_{loss}}$$

Which we already measured from the test setup

Simplified model of the DC-DC Converter



Estimation of R_{loss} and R_{load}

- After w_0 and Q_0 are estimated, the DC-DC is switched to normal operation mode and other parameters are calculated

For a buck converter, ideally, the output voltage is given by: $V_{out} = D \cdot V_{in}$

But this equation never satisfies due to losses in the power stage \rightarrow duty cycle is always higher than the required to compensate for the losses. The voltage loss can be calculated as:

Ideal Vout – Actual Vout $\rightarrow V_{loss} = D \cdot V_{in} - V_{out}$

If I_{load} is known from the current sensing, R_{loss} and R_{load} can be calculated as:

$$R_{loss} = \frac{V_{loss}}{I_{load}} \quad \text{and} \quad R_{load} = \frac{V_{out}}{I_{load}}$$



Estimation of L and C

The voltage across the inductor is given by:

$$V_L = L \frac{dI_L}{dT}$$



The inductor value can be estimated as:

$$L = \frac{V_{out}}{m_1} \quad \text{or} \quad L = \frac{V_{in} - V_{out}}{m_2}$$

Where m_1 and m_2 are the charging discharging slope of the inductor current

Capacitor can be calculated as:
  
$$C = \frac{1}{L \cdot \omega_0^2 (I_{load} = 0)}$$



Adaptive Compensation

- Now all the values could be fed in the following equation and used to calculate the location of compensation zeroes in the real time.

$$\omega_0 = \frac{1}{\sqrt{LC}} \sqrt{1 + \frac{R_{loss}}{R_{load}}} \quad \text{and} \quad Q_0 = \sqrt{LC} \frac{\sqrt{1 + \frac{R_{loss}}{R_{load}}}}{\frac{L}{R_{load}} + CR_{loss}}$$

- The method tracks the location of complex poles in the real time under any changes due to ESR, Temperature, Process etc without disturbing the normal operation of the DC-DC Converter
- The measured data can also be used to estimate other parameters like efficiency and ON resistances of Power FETs for maintenance purpose




Increasing the Resolution of Digital PWM



Technique for increasing the resolution of PWM

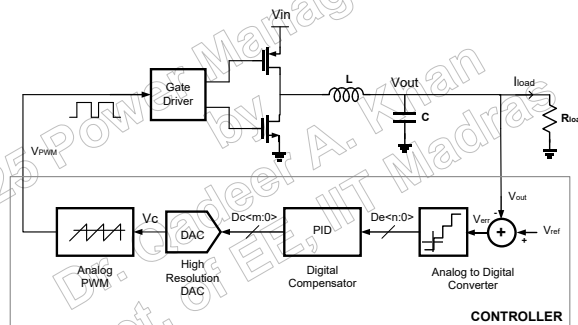- Since Analog PWM provides infinite resolution so the simplest solution would be to use analog PWM instead of Digital
- The Digital Control Word from Compensator output is converted to Analog using high resolution D/A Converter



Modified PWM Controller for High Resolution

