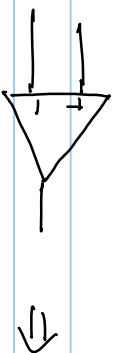



In Order to find the poles.

$$\omega_p = \frac{1}{R_c}$$

We need find nodes with high R & C



$\Rightarrow$

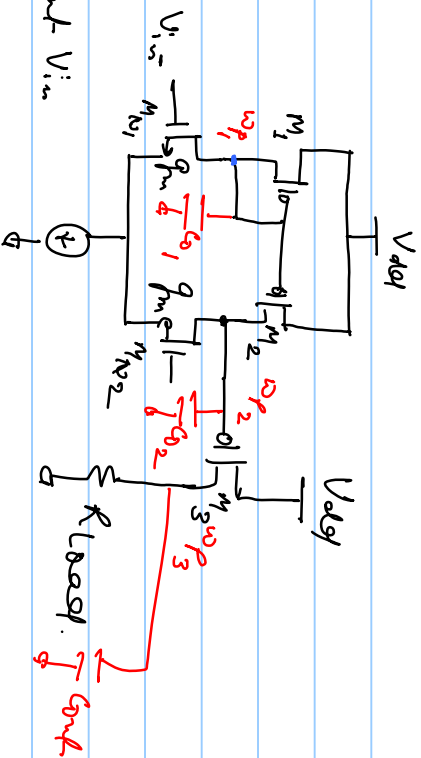

$$V_{out} = A V_{i_n} = g_m R_{out} V_{i_n}$$

$$\omega_{p1} = \frac{1}{C_0 \times R_{01}} = \frac{1}{C_0 \times \left( \frac{1}{g_{m1}} \right)} = \frac{g_{m1}}{C_0} \quad \left( R_{01} \gg \frac{1}{g_{m1}} \right)$$

In saturation, drain current

$$I_{d,s} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{gs} - V_{tn})^2$$

$$g_m = \frac{\partial I_{d,s}}{\partial V_{gs}} = \mu_n C_{ox} \frac{W}{L} (V_{gs} - V_{tn})$$

$V_{ds} \approx 500\text{mV}$  for  $180\text{nm CMOS}$

$$V_{gs} - V_{ds} \approx 100\text{mV}$$

$$I_{d,s} = 10\mu\text{A}, \quad \frac{W}{L} = \frac{10\mu\text{A}}{g_m}$$

$$\mu_n C_{ox} \approx 50\mu\text{A}/\text{V}^2$$

$$g_m = 50\mu\text{A} \times 10 \times 100\text{mV} = 50\mu\text{A}/\text{V}$$

$$\frac{1}{g_m} = 20\text{K}\Omega$$

$$S_{gk} \approx 5 \text{ fF}/\mu\text{m}^2$$

$$C_{01} = 10 \times 5 \text{ fF}/\mu\text{m}^2 = 50 \text{ fF}$$

$$\omega_p \approx \frac{1}{20 \text{ k} \times 50 \text{ fF}} = 1 \text{ G rad/sec}$$

we can ignore  $\omega_{p1}$ .

$$\omega_{p2} = \frac{1}{(R_{02} \| R_{in}) C_{02}}$$

$$\gamma_{01} = \frac{1}{\lambda^{2dL}}, \quad \lambda = \text{channel length modulation}$$

$$\lambda \approx 0.5 - 1 / v \quad \text{for } L = 180 \text{ nm}$$

$$\lambda \propto \frac{1}{L}$$

let's assume  $L = 1 \mu\text{m}$

$$\lambda \approx 0.1 \text{ to } 0.2 / \text{V}$$

assume  $\lambda = 0.1$

$$I_{D1} = 10 \mu\text{A}$$

$$R_{O2} = \frac{1}{0.1 \times 10^{-4}} \approx 1 \text{ M}\Omega$$

$$R_{OIN} = 1 \text{ M}\Omega$$

$$R_{O2} = 500 \text{ k}\Omega$$

$C_{O2}$   $\rightarrow$  we need to find the size of  $M_3$

Assume Max. load current =  $10 \mu\text{A}$

$M_3$  has to be in saturation.

$$V_{DD} = 1.8 \text{ V} \pm 0.2$$

$$V_{DD\_min} = 1.6 \text{ V}$$

$$V_{out\_max} = 1.5 \text{ V}$$

$$V_{drop\_out} = V_{DS_{min}} = 100 \text{ mV}$$

$\frac{W}{L}$  should be determined for

$$(V_{gs} - V_{th}) \leq 100 \text{ mV} \quad \& \quad I_d = 10 \text{ mA}$$

$$I_d = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{gs} - V_{th})^2$$

$$10 \text{ mA} = \frac{1}{2} (50 \mu) \frac{W}{L} (100 \text{ mV})^2$$

$$\frac{W}{L} = \frac{20 \text{ mA}}{50 \mu \times 10^4 \times 10^{-6}}$$

$$\frac{20 \times 10^{-3}}{50 \times 10^{-8}} = \frac{20}{50} \times 10^5 = 40,000$$

$$W = 40,000 \times 0.18 \mu \text{m} = 7200 \mu \text{m}$$

$$W \times L = 7200 \times 0.18 = 1296 \mu \text{m}^2$$

$$g_m = 5 \text{ mS} / \mu \text{m}^2$$

$$g_m = 6.48 \text{ PF}$$

$$\begin{aligned}
 \omega P_2 &= \frac{1}{500 \times 6.48 \text{ PF}} = \frac{1}{5 \times 10^5 \times 6.48 \times 10^{-12}} \\
 &= \frac{10^7}{5 \times 6.48} = 0.03 \times 10^7 = 3 \times 10^5 \\
 &= 300 \text{ krad/sec}
 \end{aligned}$$

$\omega P_2$  can't be ignored.

$$\omega P_3 = \frac{1}{R_{\text{int-Load}}}$$

Assume  $C_{\text{int}} = 10 \text{ pF}$

$$A \approx 1$$

$$\gamma_{03} = \frac{1}{10 \text{ nA}} = 100 \Omega$$

$$R_{\text{load}} = \frac{1.5 \text{ V}}{10 \text{ uA}} = 150 \Omega$$

$$R_{\text{int}} = 100 / 150 = 60 \Omega$$

$$\omega_3 = \frac{1}{R_{\text{int}} \times \text{int}} = 1.67 \text{ k rad/sec.}$$

$\omega_3$  is outside U & B

Assume


$$\text{int} = 10 \mu\text{F}$$

$$\omega_3 = 1.67 \text{ krad}$$

Assume

$$\text{int} = 10 \mu\text{F}$$

$$\omega_3 = 1.67 \text{ krad/sec}$$

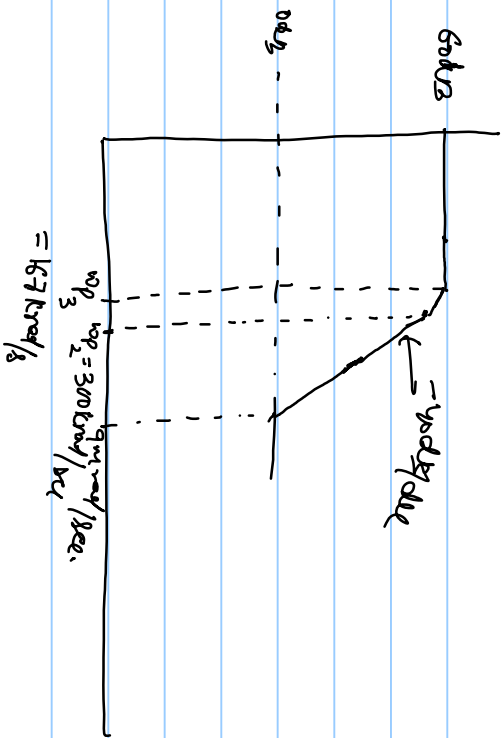

$PM \approx 0 \Rightarrow$  unstable.

for  $60^\circ$  phase margin

$\omega_{ng5}$  should be  $\frac{\omega_{p3}}{1.7}$

$\omega_{p2}$  (compensated) should be  $\frac{\omega_{ng5}}{60 \text{ dB}}$

$$\omega_{ng4} = \frac{16.7 \text{ dB}}{1.7} = 10 \text{ dB}$$



$\omega_2$  (uncompensated) = 100 rad/sec.

$$\omega_2 = \frac{1}{500 \times (C_1 + C_2)} = 100 \text{ rad/sec,}$$

$$C_1 + C_2 = \frac{1}{5 \times 10^5 \times 100} = \frac{10^{-7}}{5}$$

$$= \frac{100}{5} \times 10^{-9} = 20 \text{ nF}$$