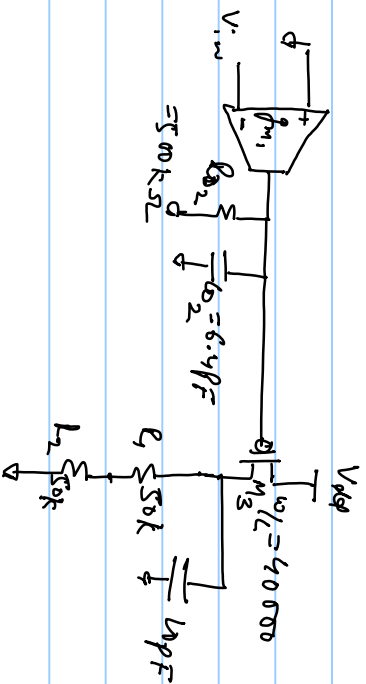


Let's assume, $C_{int} = 10\text{pF}$ and $Z_{load} = 0$ ($R_{load} = \infty$)



$$\omega_{p2} = 300k \text{ rad/sec}$$

$$\omega_{p3} = \frac{1}{40k (10\text{pF})} = 2.5 \text{ Mrad/sec}$$

$$I_d = \frac{1}{2} \mu_{\text{ox}} \frac{W}{L} (V_{gs} - V_{th})^2$$

$$15\mu\text{A} = \frac{1}{2} (50\mu\text{A}) (40000) (V_{gs} - V_{th})^2$$

$$\frac{30}{50k \cdot 40000} = (V_{gs} - V_{th})^2 \Rightarrow V_{gs} - V_{th} = \sqrt{\frac{30}{150k \cdot 40000}} = 3.87 \text{ mV}$$

$$g_m = 7.7 \text{ mA/V}$$

$$r_{o3} = \frac{1}{\lambda I_{D1}} = \frac{1}{15 \mu} = 66.67 \text{ k}$$


$$R_{out} = 100 \text{ k} \parallel 66.67 \text{ k} = 40 \text{ k} \Omega$$

$$A_3 = g_{m3} \times R_{out} = 40 \times 7.7 = 308$$

$$A_2 = g_{m1} \times R_{o2} = 50 \mu \times 500 \text{ k} \\ = 25$$

$$A_0 = 7700 = 7700 \text{ dB}$$
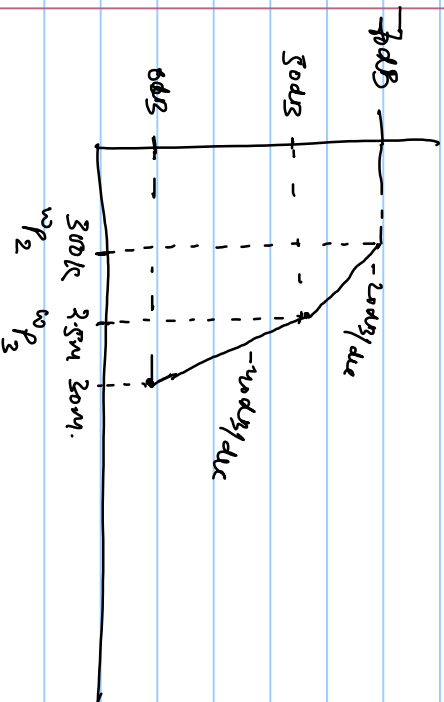
$$\beta_{A_0} = \frac{7700}{2} \approx 7000$$



Phase Margin ≈ 0 unstable.

compensate by adding C_c at ω_{p2}

Phase Margin = 60°

$$\text{angle} = \frac{\omega_{p3}}{1.7} = \frac{3.5 \text{ M}}{1.7} = 1.44 \text{ M rad/sec} / \text{sec.}$$

$$\omega_{p2} (\text{uncompensated}) = \frac{1.44 \text{ M}}{\beta A_0} \approx 400 \text{ rad/sec}$$


$$\omega_{p2} = \frac{1}{R_{02}(\omega_{z1}C_c)} = 400 \text{ rad/sec.}$$

$$\omega_{z1}C_c = \frac{1}{500k \times 400} = \frac{1}{2 \times 10^8} = \frac{10^{-8}}{2} = 5 \text{ nF}$$

$$C_c = 5 \text{ nF}$$

5nF is quite large to implement on-chip
so we look for alternate way of reducing the
capacitor size.


Miller compensation

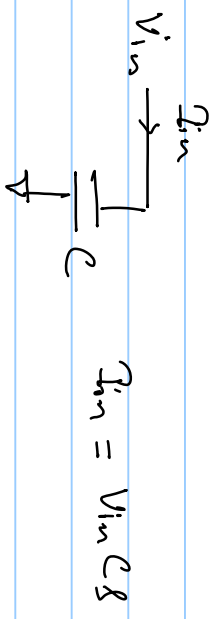


$I_{in} \rightarrow k \cdot I_{in}$

Two possibilities:

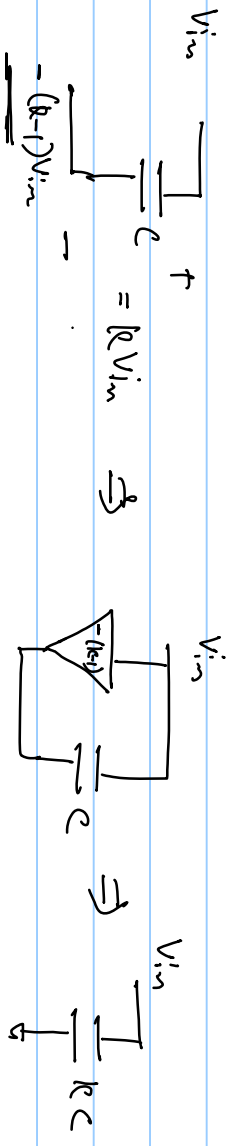- ① Increase $C \rightarrow kC$
- ② Decrease $V_{in} \rightarrow kV_{in}$



Miller Effect

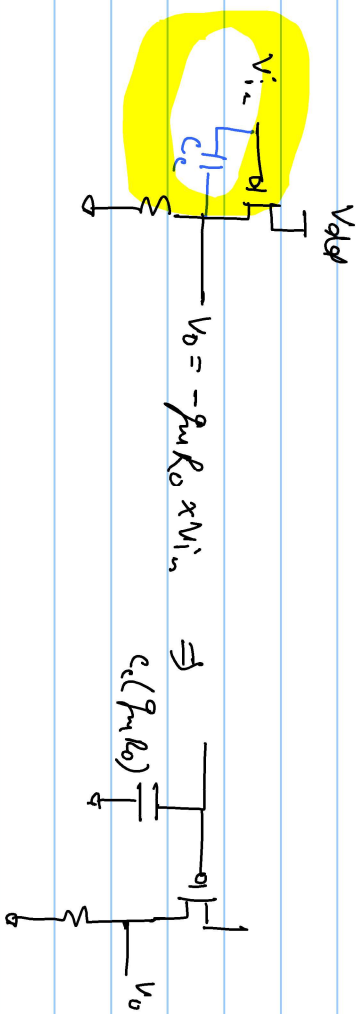

If $\beta \mu_{Ro}$ is large then C_c is quite small.

Assume previous case, C_c required was $5nF$

$$\beta \mu_{Ro} = 300$$

$$C_c = \frac{5nF}{300} = 18.6pF$$

$$C_c = 18.6pF$$