



If f_{uLo} is large also C_c is quite small.

Assume previous case, C_c required was $5nF$

$$f_{uLo} = 300$$


$$C_c = \frac{5nF}{300} = 16.67pF$$

$$C_c = 16.67pF$$

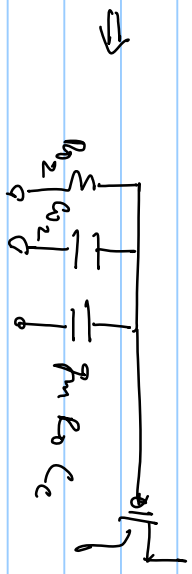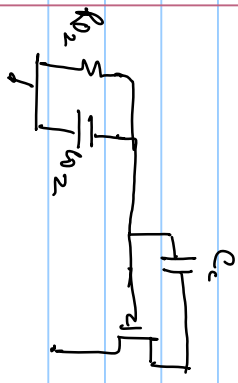

$$g_m R_0 C_c \gg \omega_2$$

Right Half Plane Zero

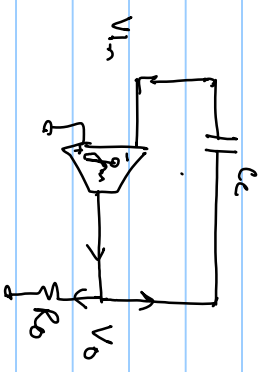


$$(V_o - V_{in}) g_c + \frac{V_o}{R_0} = -V_{in} g_m$$

$$V_o g_c - V_{in} g_c + \frac{V_o}{R_0} = -V_{in} g_m$$

$$V_o \left(\frac{1}{R_o} + g_c \right) = V_{in} (g_c - g_m)$$

$$\frac{V_o}{V_{in}} = \frac{g_c - g_m}{\frac{1}{R_o} + g_c}$$
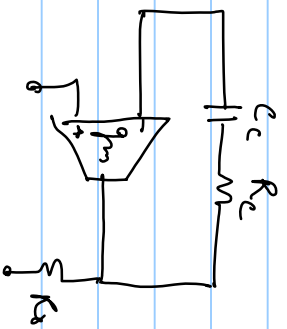
$$z_{\text{zero}} = \frac{g_m}{g_c} \quad \text{R.H.P.}$$




$$z_{\text{zero}} = \frac{1}{\left(\frac{1}{g_m} - R_e \right) C_e}$$

$$R_e > \frac{1}{g_m}$$

zero \rightarrow L.H.P.


Uncompensated poles

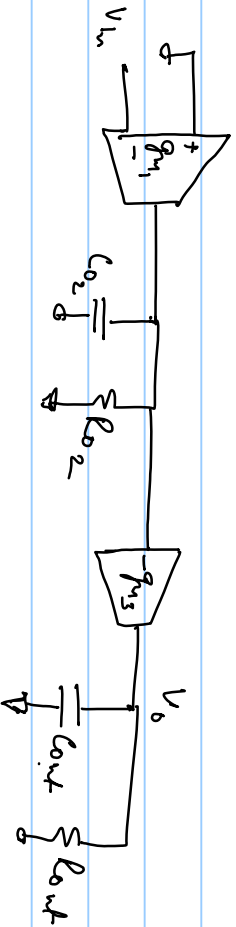


$$\omega_{p1} = \frac{1}{R_{b2} C_{c2}} \quad \omega_{p2} = \frac{1}{R_{out} C_{out}}$$

$$g_{ain} (A_{o2}) = g_{m1} R_{b2} g_{m3} R_{out}$$


Affel Miller Compensation

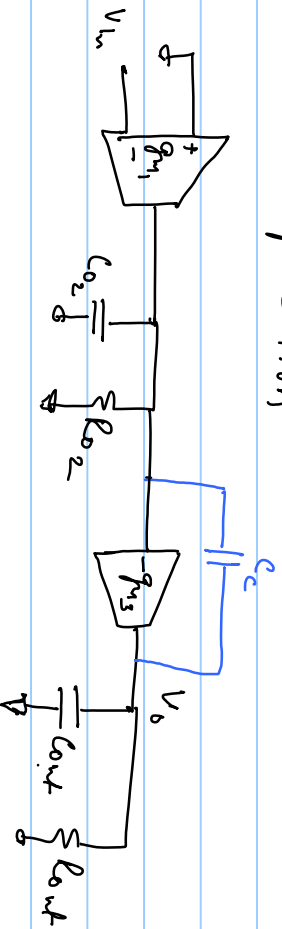

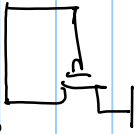


$$R_{out} = \frac{1}{g_m} = \frac{R_L}{g_m R_L} = \frac{1}{g_m}$$

Intrinsic gain = $g_m R_o$

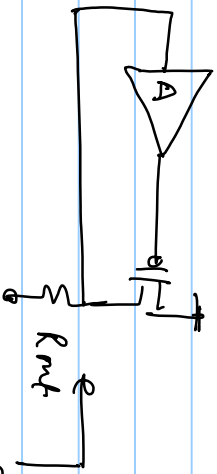
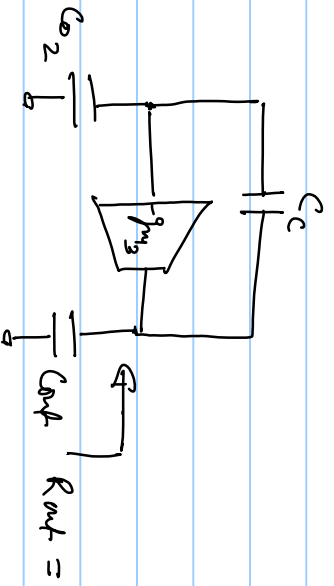
$$R_{out} \approx \frac{R_{out}}{A g_m R_L}$$




$$P = \frac{C_c}{C_c + C_{c2}}$$

Transconductance

$$g_{m3}' = g_{m3} \times \frac{C_c}{C_c + C_{c2}}$$

Compensated pole at ω_{p2}
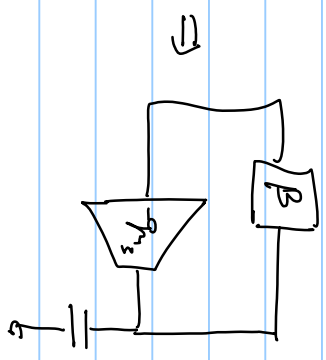
$$\omega_{p2}' = \frac{g_{m3}}{C_{out} + \frac{C_{c2} C_c}{C_c + C_{c2}}}$$



If $c_e \gg c_o$


Pole splitting

$$\omega_p' = \frac{g_{m3}}{C_{o2} + C_{out}}$$

Compensated ω_p

$$\omega_{p1}' = \frac{1}{R_{o2} (C_{o2} + g_{m3} R_{out} C_e)}$$
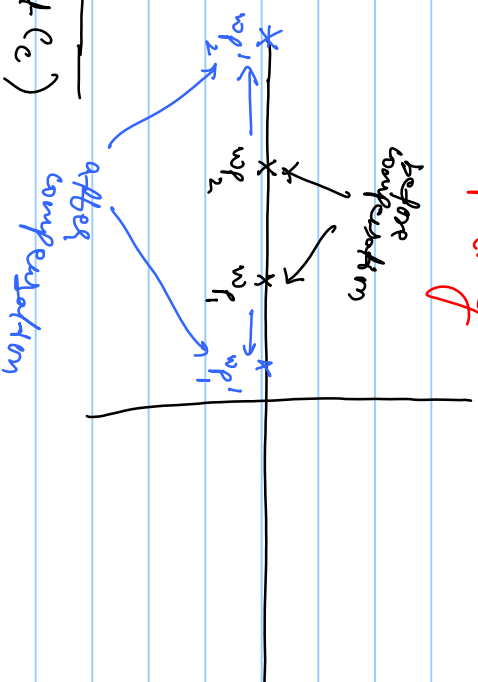
$$\omega_{p2} \approx \frac{1}{R_{o2} g_{m3} R_{out} C_e}$$



Phase Margin after compensation.

$$\begin{aligned} \omega_{mfg} &= \omega_{p2}' \times (\text{dc loop gain}) \\ &= \omega_{p2}' (R A_{o2}) \end{aligned}$$

assume.

$$\beta = 1$$

$$A_D = g_{m2} R_{o2} g_{m3} R_{o3}$$

$$\omega_{p1}' = \frac{1}{R_{o2} \times g_{m3} R_{o3} C_c}$$

$$\omega_{ngb} = \frac{g_{m2} R_{p2} g_{m3} R_{p3} C_c}{R_{p2} \times g_{m3} R_{p3} C_c} = \frac{g_{m2}}{C_c}$$

$$\omega_2 = \frac{g_{m3}}{C_c}$$

$$\text{Phase Margin} = 180^\circ - \tan^{-1} \omega_{ngb} \frac{1}{\omega_{p1}'} - \tan^{-1} \omega_{ngb} \frac{1}{\omega_{p2}'} - \tan^{-1} \omega_{ngb} \frac{1}{\omega_2}$$

90°

$$= 90^\circ - \tan^{-1} \frac{g_{m2}/C_c}{g_{m3}/(R_{o2} + R_{p1})} - \tan^{-1} \frac{g_{m2}/C_c}{g_{m3}/C_c}$$

Phase shift due to R.N.P. zero

$$\phi_2 = -\tan^{-1} \frac{q_{m2}}{q_{m3}}$$

$$q_{m3} \gg q_{m2}$$

$$\phi_2 \approx 0$$