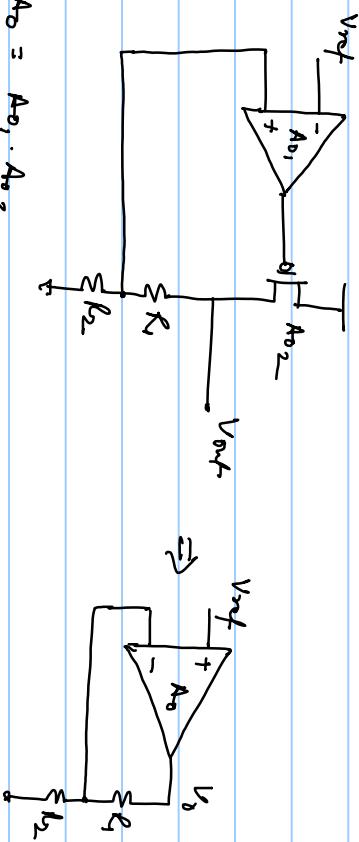


Sources of Error in Regulators

1. Loop Gain
2. V_{ref}
3. Mismatch in feedback resistor (error in /β)
4. Offset



Closed loop gain

$$= \frac{A_o}{1 + \beta A_o} = \frac{1}{\beta} \quad \text{if } \beta A_o \gg 1$$

(1)

Example :

$$\text{if } \beta = \frac{1}{2}$$

$$V_{ref} = 0.6 V$$

$$V_0 = 1.2 V$$

$$V_0 = \frac{A_0}{1 + \beta A_0} V_{ref}$$

assume $A_0 = 150$

$$V_0 = \frac{150 \times 0.6}{1 + 50} = \frac{150 \times 0.6}{51} = 1.17 V$$

$$\text{Error} = -0.023 V \approx 2\%$$

In order to reduce error, we should have less βA_0 or for smaller β
 A_0 must be increased (\Rightarrow exp.)

(2)

Vref.

$$V_0 \approx \frac{V_{ref}}{\beta}$$

any error in V_{ref} will directly affect your V_{out} .
Error is more for smaller β_B .

③ Mismatch in feedback resistors.

$$\beta_B = \frac{R_2}{R_1 + R_2}$$

$$V_{out} = \frac{V_{ref}}{\beta_B}$$

Assume, R_2 & R_1 have ΔR error.

$$R_2 \rightarrow R_2 + \Delta R$$


$$R_1 \rightarrow R_1 - \Delta R$$

$$\beta'_B = \frac{R_2 + \Delta R}{R_1 + R_2} = \frac{R_2}{R_1 + R_2} \left(1 + \frac{\Delta R}{R_2}\right)$$

$$= \beta_B (1 + \Delta \beta)$$


$$V_o = \frac{V_{ref}}{\beta'_B}$$
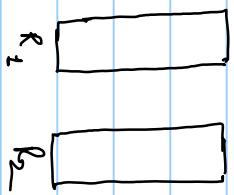
$$\begin{cases} V_{out} \\ K_1 - \Delta R \\ K_2 + \Delta R \end{cases}$$





④)

offset


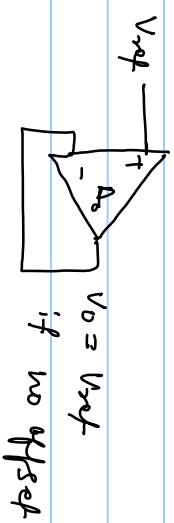


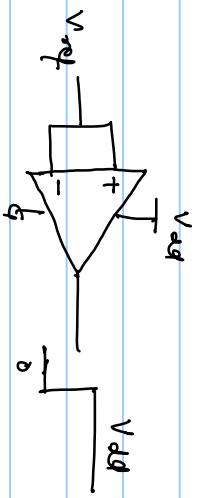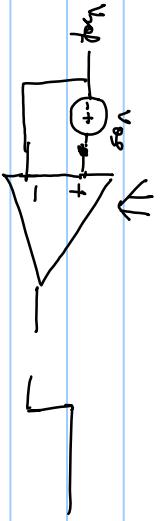But $V_o = V_{ref} + \Delta V$ in presence of offset
 $\Delta V = \pm \frac{\Delta V}{A_o} \rightarrow$ input referred offset.



(unten)

zu
sehr
ger


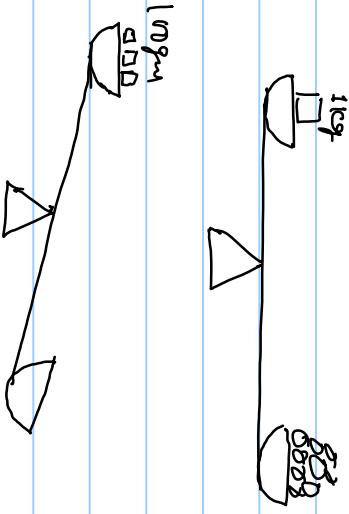
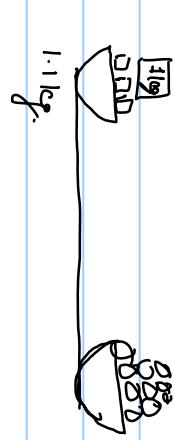


zu
ger



zu
ger

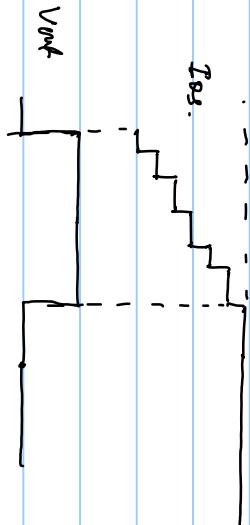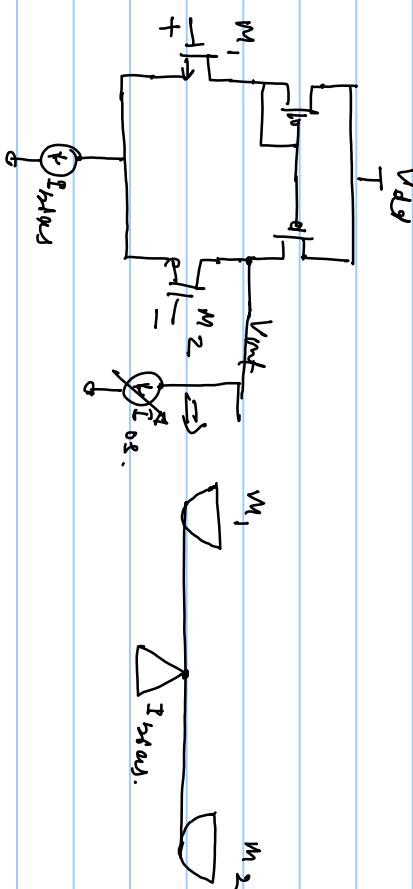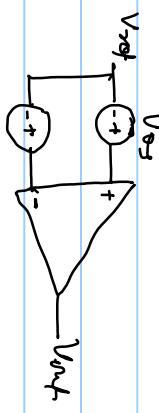offset correction. (static offset cancellation)



2nd method.

