

$$V_o = D \cdot V_{DD}$$

for ideal transformer

$$P_o = P_{DD}$$

$$V_{DD} I_{DD} = V_o \cdot I_o$$

$$I_{DD} = D \cdot I_o$$


$V_o = D \cdot V_{DD}$ is only true under no-load condition

$I_{DD} = D \cdot I_o$ is true for all conditions.


Efficiency of a switching converter

$$\eta = \frac{P_{out}}{P_{in}} = \frac{V_o \cdot I_o}{V_{dd} \cdot I_{dd}}$$

$\frac{D \cdot V_{dd} \cdot I_{dd}}{D}$

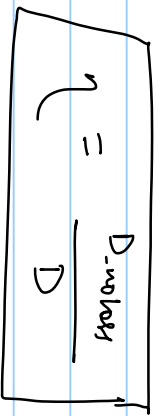

True only for conduction losses.

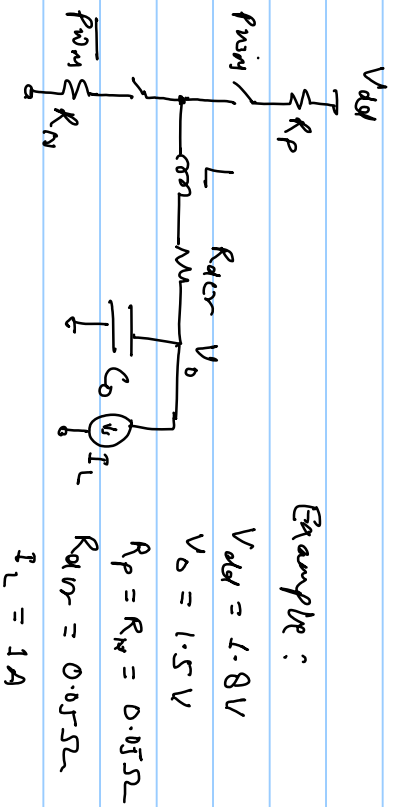

$$V_o = D \cdot V_{\text{dd}} - V_{\text{body}}$$

$$V_{\text{body}} = I_L \left(D \cdot R_p + (1-D) R_n + R_{\text{dcr}} \right) \\ = 1 \text{ A} (0.05 + 0.85) = 100 \text{ mV}$$

$$1.5 = D(1.8) - 100 \text{ mV}$$

$$\Rightarrow D = \frac{1.6}{1.8} = 0.888$$

$$D_{\text{no-load}} = \frac{1.5}{1.8} = 0.833$$

$$\Rightarrow \Delta D = 0.055 \approx 5.5\%$$

$$I_{\text{dd}} = 0.888 \times 1 \text{ A} = 0.888 \text{ A}$$

$$P_{\text{dd}} = 1.8 \times 0.888 = 1.6 \text{ W}$$

$$P_o = 1.5 \text{ W}$$

$$\eta = \frac{1.5}{1.6} = 93.75\%$$

$$\eta = \frac{P_{\text{out}}}{D} = \frac{0.833}{0.88} \approx 93.75\%$$

Efficiency of LDO

$$\eta = \frac{1.5}{1.8} = 83.33\%$$

Nms answer

$$V_0 = 0.9V$$


$$0.9 = D(1.8) - 150mV$$

$$D = \frac{1}{1.8} = 0.555$$


$$\eta = \frac{0.5}{0.555} \approx 90\%$$

for LDO


$$\eta = 50\%$$

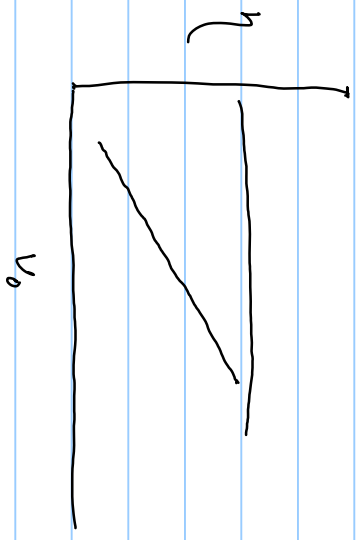

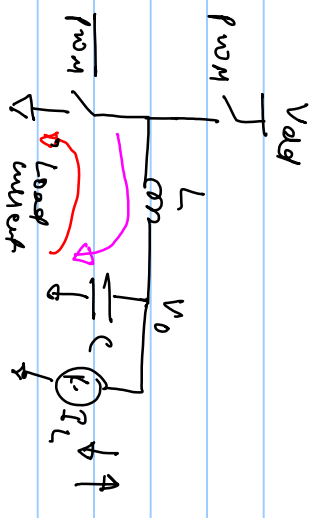Synchronous vs. non-synchronous switching regulator.



Synchronous
Bi-directional

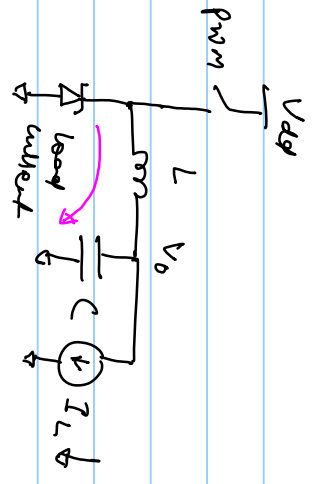


non-synchronous


Control Techniques

PWM control → Voltage mode control

↘ Current mode control


Voltage mode control

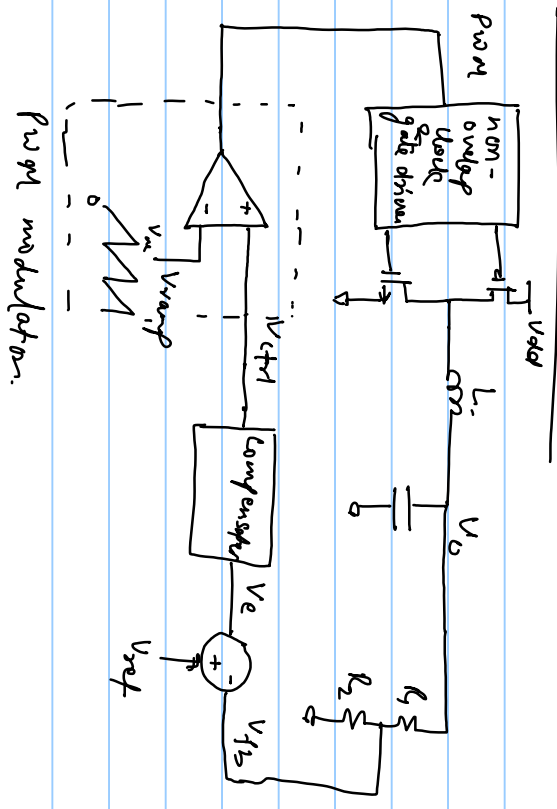

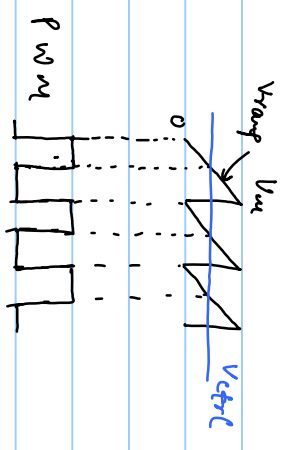

$$D = \frac{V_{CH}}{V_m}$$

Current mode control

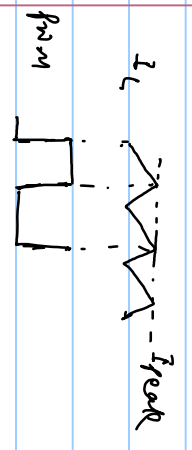

no external Vmp is used.