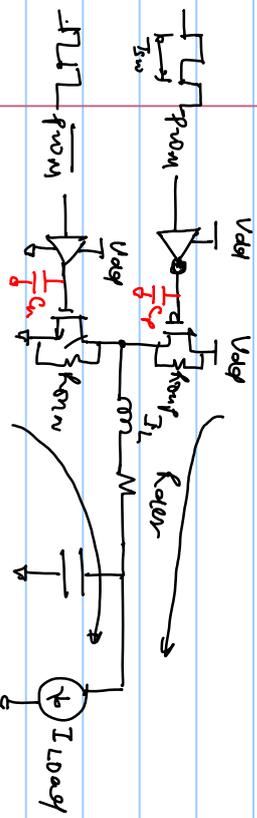


## Losses in switching d-c-dc converters



$P_{sw}$  &  $P_{con}$  are non-overlapped.

① Conduction Loss.  $\rightarrow$  resistive loss

$$P_{cond} = I_{rms}^2 \cdot R$$

$$P_{cond} = I_L^2 (D \cdot R_{on} + (1-D) \cdot R_{on} + R_{diode})$$

② Gate Switching Loss.

$$P_{\text{gate-sw}} = C_p V_{\text{dd}}^2 F_{\text{sw}} + C_n V_{\text{dd}}^2 F_{\text{sw}} \quad F_{\text{sw}} = \frac{1}{T_{\text{sw}}}$$

$$= (C_p + C_n) V_{\text{dd}}^2 F_{\text{sw}}$$

not a function of load current (Fixed loss for constant  $V_{\text{dd}}$  &  $F_{\text{sw}}$ )

$$C_p = C_n = 10 \text{ pF}$$

$$V_{\text{dd}} = 1.8 \text{ V}$$


$$F_{\text{sw}} = 1 \text{ MHz}$$

$$P_{\text{gate-sw}} = 20 \text{ pF} \times (1.8)^2 \times 10^6 = 64.8 \text{ mW}$$

if  $F_{\text{sw}} = 10 \text{ MHz}$

$$P_{\text{gate-sw}} = 648 \text{ mW}$$

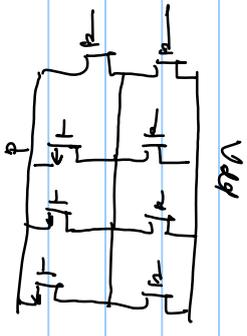[ switching frequency must be reduced at light load for high efficiency ]



Segmented FET

used smaller FETs in parallel instead of single large FET

Turn OFF nmos of nMOSFETs as load current reduces.

Let's say, we have 10 FETs.

10 in parallel = 10pF cap.

1 FET → 1pF

$$f_{\text{gate-sws}} = C_{\text{red}} V^2 f_{\text{red}} \quad \text{reduced } f \text{ (FFreq)}$$


(segmented FET)

③ Load Time Switching Delay




if  $M_p$  &  $M_n$  are turned ON simultaneously then



$$I_{\text{dload}} = \frac{V_{\text{dd}}}{1000 \Omega} = \frac{1.8 \text{ V}}{0.1} = 18 \text{ A} \rightarrow \text{reliability issues.}$$

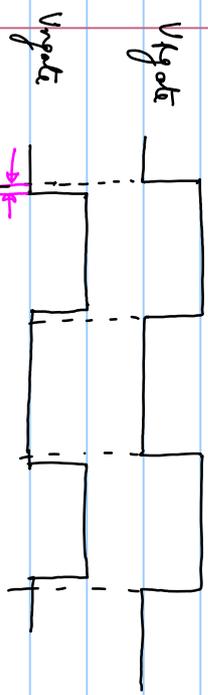We need to make sure both  $M_N$  &  $M_P$  are not on simultaneously.  
 → use non-overlapped PWM signals  
 (Break before make)



(both  $M_N$  &  $M_P$  are OFF)

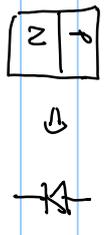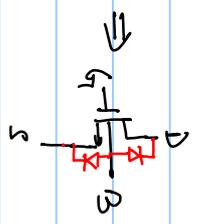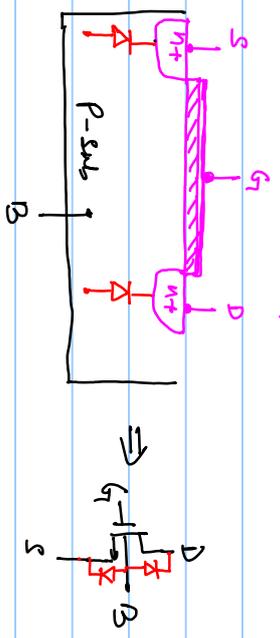

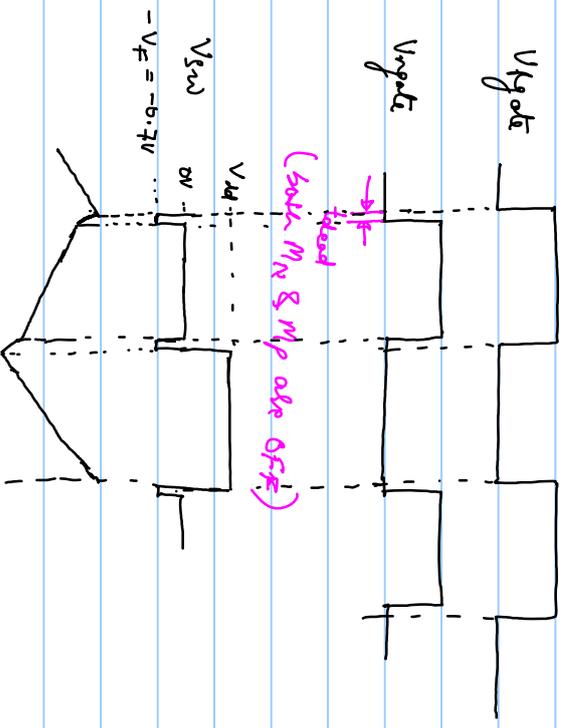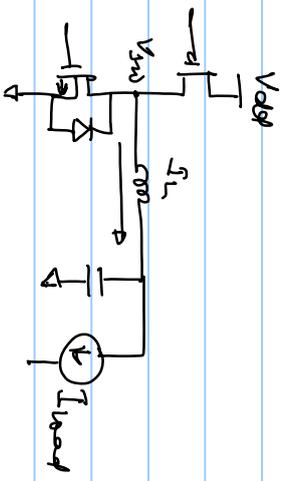

If ripple current is negligible compared to  $I_{load}$ .

then

$$P_{load\_sw} = V_F \times I_{load} \left( \frac{t_{dead}}{T_{sw}} \right) \times 2$$

$$P_{load\_sw} = 2V_F I_{load} \frac{t_{dead}}{T_{sw}}$$

Assume,  $V_F = 0.7V$

$$I_{load} = 1A$$

$$T_{sw} = 1\mu s$$

$$t_{dead} = 10ns$$

$$P_{load\_sw} = 2 \times 0.7 \times 1 \times \frac{10ns}{1\mu s}$$

$$= \frac{1.4}{100} = \frac{1400mW}{100} = 14mW$$

If  $t_{dead} = 1ns$

$\Rightarrow$  we should minimize  $t_{dead}$  to increase efficiency.  
 $P_{load\_sw} = 1.4mW$