
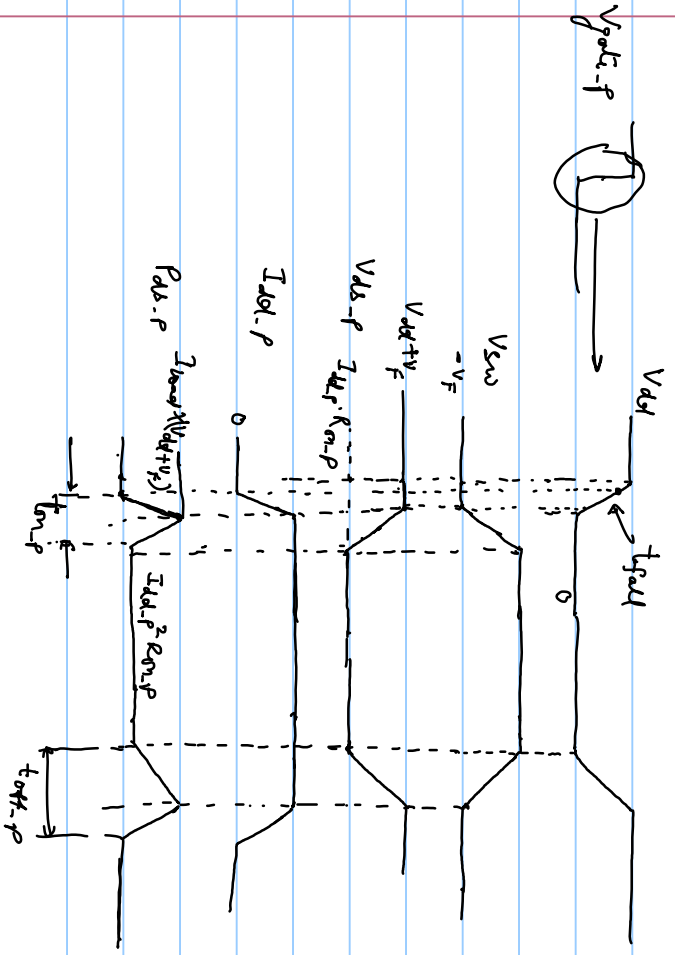


# Hard Switching Losses

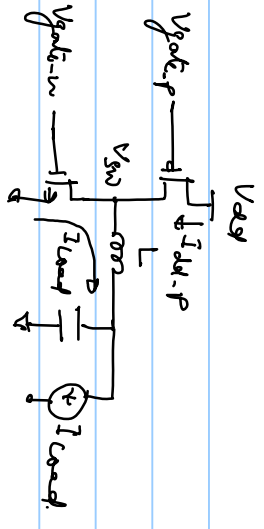


$P_{sw}$  = average power during  $t_{on-p}$  &  $t_{off-p}$

$$= \frac{1}{2} \times t_{on-p} \times I_{load} (V_{dd} + V_F) + \frac{1}{2} \times t_{off-p} \times I_{load} (V_{dd} + V_F)$$

$V_{dd} \gg V_F$

$$\approx \frac{1}{2} (t_{on-p} + t_{off-p}) I_{load} V_{dd} = \frac{1}{2} (t_{on-p} + t_{off-p}) F_{sw} I_{load} \cdot V_{dd}$$

### Magnetic Loss

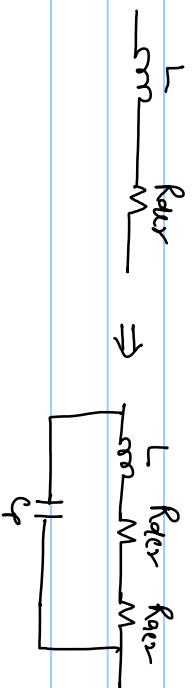

Rair  $\rightarrow$  magnetic losses (core loss, skin effect loss due to ac current)  
 Rair  $\rightarrow$  resistive loss due to rms current (winding resistance)


$$\text{rms loss} = I_{L-rms}^2 \times R_{dc}$$

$$\text{ac loss} = I_{L-ac}^2 \times R_{ac} = P_{ac}$$

$\downarrow$   
 inductor ripple current  
 (no dc content)

$$Q = \frac{wL}{R_{dc} + R_{ac}}$$

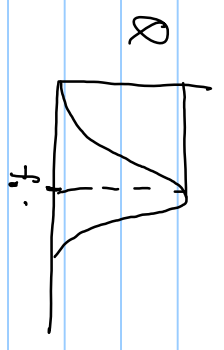$\downarrow$   
 measured data  
 dominant at high freq.




Choose  $f_{sw} \approx f_0$  for better efficiency.


$$P_{\text{loss}} = P_{\text{cond}} + P_{\text{gate-sim}} + P_{\text{dead-time}} + P_{\text{sw}} + P_{\text{rc}} + P_{\text{Q}}$$

$I_{\text{rms}}^2 R$  (conduction loss)  $\downarrow$   $C V^2 f$  (gate drive loss)  $\downarrow$   $\frac{2 t_{\text{dead}}}{T_{\text{sw}}} \times V \times I$  (dead time loss)  $\downarrow$   $\frac{1}{2} (t_{\text{rise}} + t_{\text{fall}}) V_{\text{ds}} \cdot I$  (hold switching loss)  $\downarrow$   $I_{\text{dc}}^2 R_{\text{rc}}$  (RC loss)  $\downarrow$   $V_{\text{ds}} \cdot I_{\text{Q}}$  (Quiescent loss)

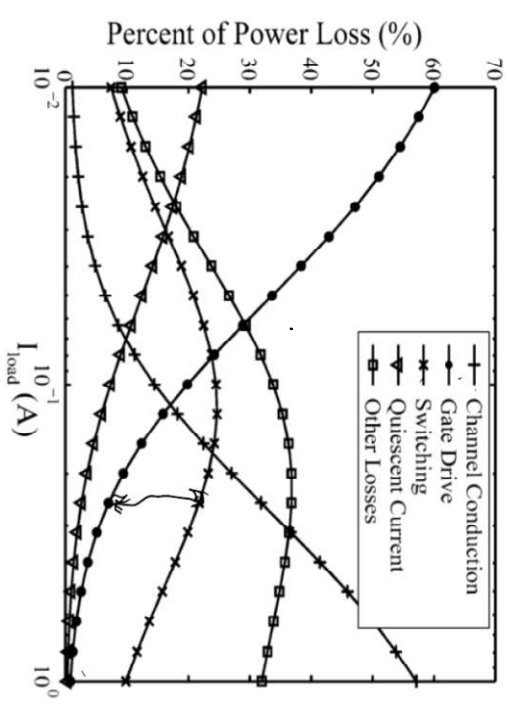( $I_{\text{Q}}$  → current associated with controller)



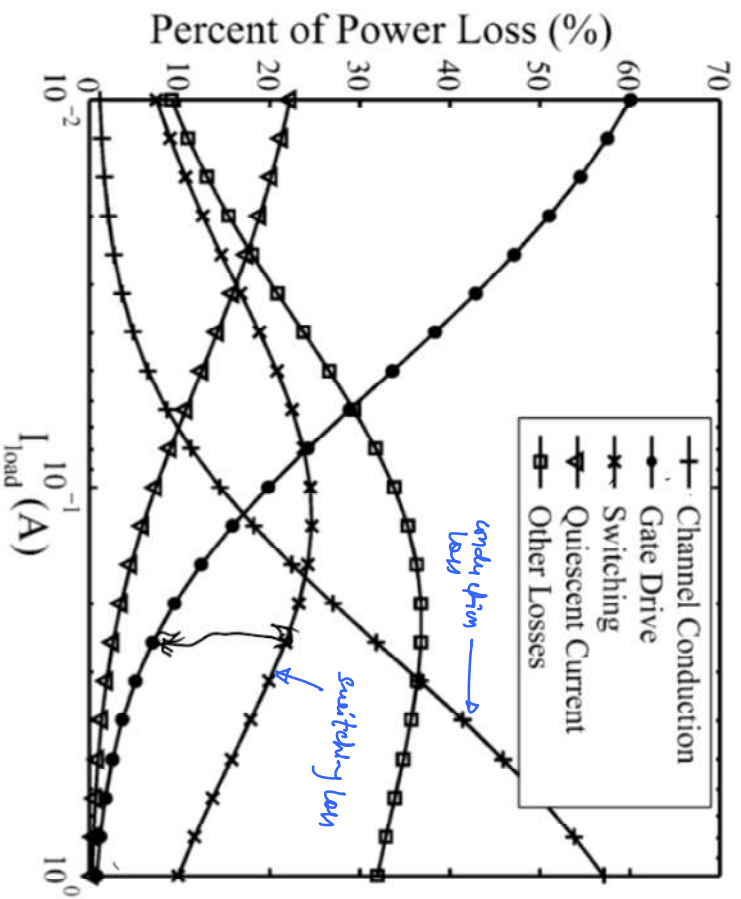Ref: M. D. Mulligan, et al "A constant-frequency method for improving light-load efficiency in synchronous buck converters," IEEE Power Electron. Lett., vol. 3, no. 1, pp. 24-29, Mar. 2005.



Ref: M. D. Mulligan, et al "A constant-frequency method for improving light-load efficiency in synchronous buck converters," IEEE Power Electron. Lett., vol. 3, no. 1, pp. 24-29, Mar. 2005.