

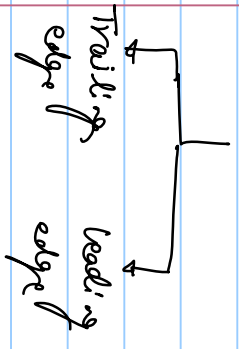
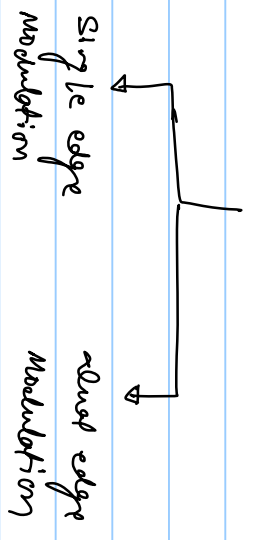


PWM Modulator

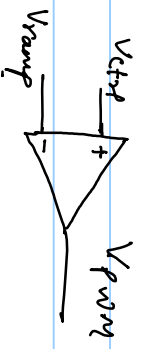


Trailing Edge Modulation

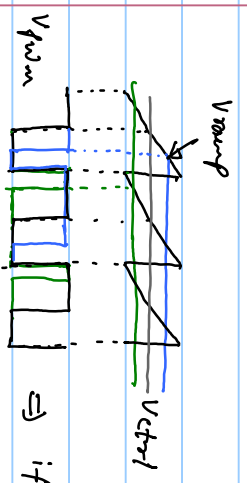


⇒ if duty cycle is changed then only trailing edge moves while leading edge is fixed

Leading Edge Modulation

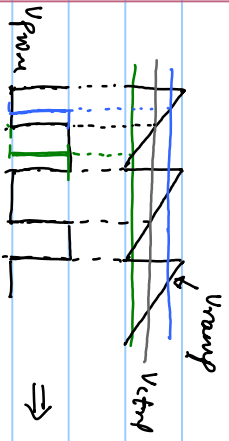


⇒ if duty cycle is changed then leading edge moves while trailing edge is fixed.

Sharp Edge Modulation

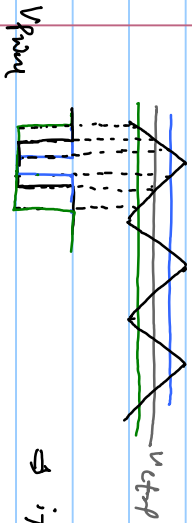


⇒ if duty cycle is changed then both edges move.

Dc-Dc Control Techniques

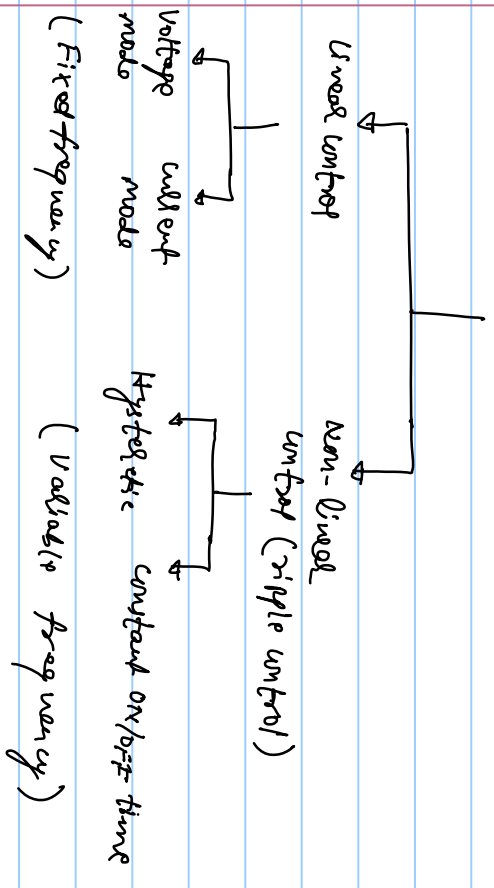

Voltage Mode Control

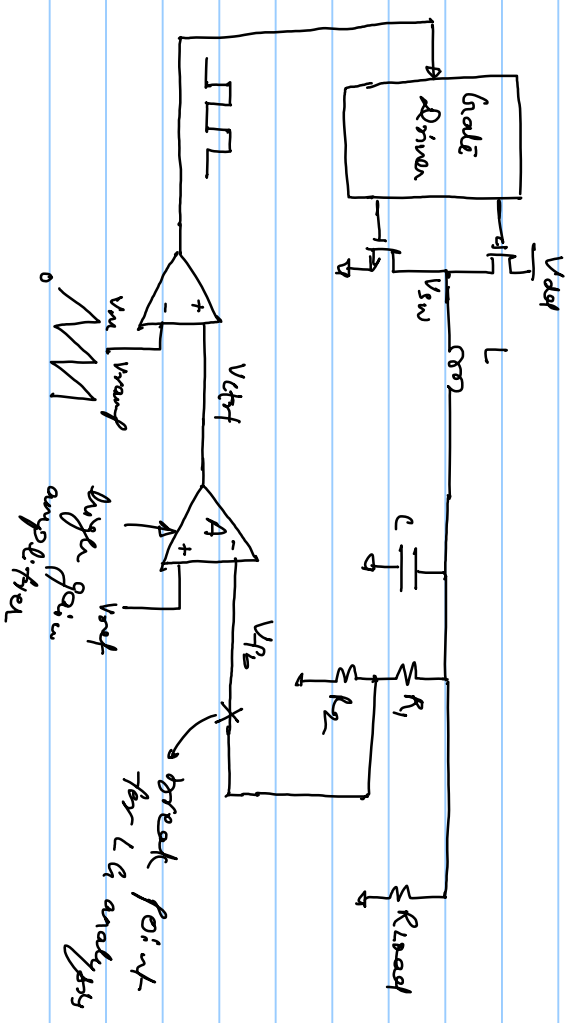

Loop gain analysis is required for stability.

Step-1 Break the loop

Step-2 Find the transfer function of each stage in the loop.

① feedback factor

$$H_{FB}(s) = \beta = \frac{R_2}{R_1 + R_2}$$

② Amplifier

$$H_{amp}(s) = A$$


③ Pw m modulation

$$Gain = \frac{\partial D}{\partial V_{ch}}$$

$$D = \frac{V_{ch}}{V_m} \Rightarrow \frac{\partial D}{\partial V_{ch}} = \frac{1}{V_m}$$

$$G_{pwm} = \frac{1}{V_m}$$

4) Gate Drive + Switches

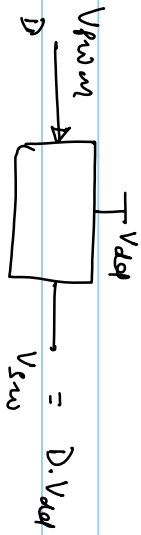


$$V_{gw} = D \cdot V_{dd}$$

$$\frac{\partial V_{gw}}{\partial D} = V_{dd}$$

Grüner-stage = V_{dd} .

5) LC filter

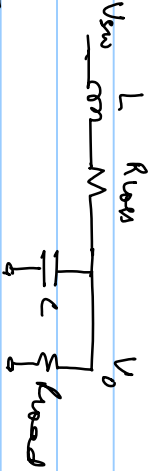

$$H_L(s) = \frac{V_o(s)}{V_{gw}(s)}$$

$$\frac{V_o}{V_{gw}} = \frac{Z_2}{Z_1 + Z_2} = \frac{1}{Y_2 Z_1 + 1} = \frac{1}{(sC + \frac{1}{R_{load}})(sL + R_{load}) + 1}$$

$$= \frac{1}{s^2 L C + R_{load} C s + \frac{L}{R_{load}} s + \frac{R_{load}}{R_{load}} + 1}$$

$$= \frac{1/LC}{s^2 + s \left(\frac{R_{load}}{L} + \frac{1}{R_{load} C} \right) + \left(\frac{R_{load}}{R_{load}} + 1 \right) \frac{1}{LC}}$$

$R_{load} \ll R_{load}$

$$H_L(s) = \frac{1/LC}{s^2 + s \left(\frac{R_{load}}{L} + \frac{1}{R_{load} C} \right) + \frac{1}{LC}}$$

$$\omega_0 = \sqrt{\frac{1}{LC}}$$

$$\frac{\omega_0}{Q_0} = \frac{R_{load}}{L} + \frac{1}{R_{load} C}$$

$$\begin{aligned} \beta_0 &= \frac{\omega_0}{\frac{L\omega_0}{R_{\text{load}}} + \frac{1}{R_{\text{load}} C}} = \frac{1/\sqrt{LC}}{\frac{C R_{\text{load}} + L/R_{\text{load}}}{L C}} \\ &= \frac{\sqrt{LC}}{C R_{\text{load}} + L/R_{\text{load}}} \end{aligned}$$