

$$\omega_{\text{cgs}} < \frac{\omega_0}{D_0}$$

for -20dB gain margin

$$\omega_{\text{cgs}} = \frac{\omega_0}{10 D_0}$$

$$\frac{V_o(s)}{V_{in}(s)} = L_{\text{comp}}(s) = \beta H_{\text{comp}}(s) H_{\text{drv}}(s) H_z(s)$$

$$= \beta \frac{k_i}{s} \frac{V_{dd}}{V_{in}} H_z(s)$$

$$\beta \frac{V_{dd}}{V_{in}} = K_{\text{uo}}$$

$$L_{\text{comp}}(s) = K_{\text{uo}} \frac{k_i}{s} H_z(s)$$

$$K_{\text{uo}} k_i = \omega_{\text{cgs}} = \frac{\omega_0}{10 D_0}$$

$$k_i = \frac{\omega_0}{K_{\text{uo}} 10 D_0} = \frac{1}{10 K_{\text{uo}}} \left(\frac{R_{\text{uo}}}{1} + \frac{1}{R_{\text{oad}}} \right)$$

For no load,

$$R_{load} = \infty$$

$$k_i = \frac{1}{10 k_{wo}} \left(\frac{R_{load}}{L} \right)$$

Example

$$V_{del} = 1.8V, \quad V_{out} = 1.2V, \quad V_{ref} = 0.6V$$

$$F_{sw} = 1MHz, \quad L = 3.3\mu H, \quad C = 10\mu F$$

$$R_{ds-on} = 50m\Omega, \quad R_{dcr} = 50m\Omega, \quad V_{in} = 1V$$

$$k_{uo} = \frac{V_{del}}{V_{in}} \times \beta = 1.8 \times \frac{1}{2} = 0.9$$

$$R_{low} = R_{ds-on} + R_{dcr} = 100m\Omega$$

$$L = 3.3\mu H$$

$$|k_i| = \frac{1}{10 \times 0.9} \left(\frac{0.1}{3.3\mu H} \right) = 3.367 \text{ krad/sec}$$


Integrator.

$$\frac{g_m}{C_i} = k_i = 3.367 \text{ krad/sec}$$


$$g_m = 10 \mu\text{A/V}$$

$$k_i = \frac{g_m}{C_i} = \frac{10^{-5}}{3.367 \times 10^{-3}} = \frac{1}{3.367} \times 10^{-8}$$

$$= 2.97 \mu\text{F}$$

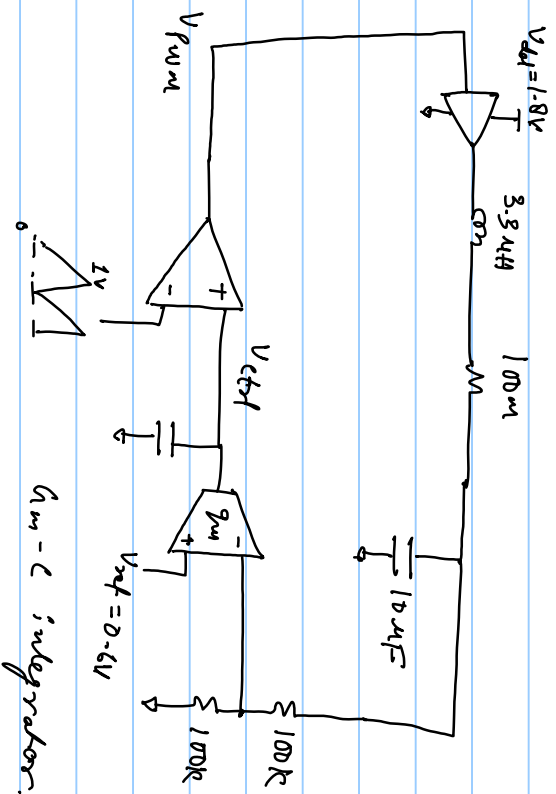

$g_m - C$ integrator.

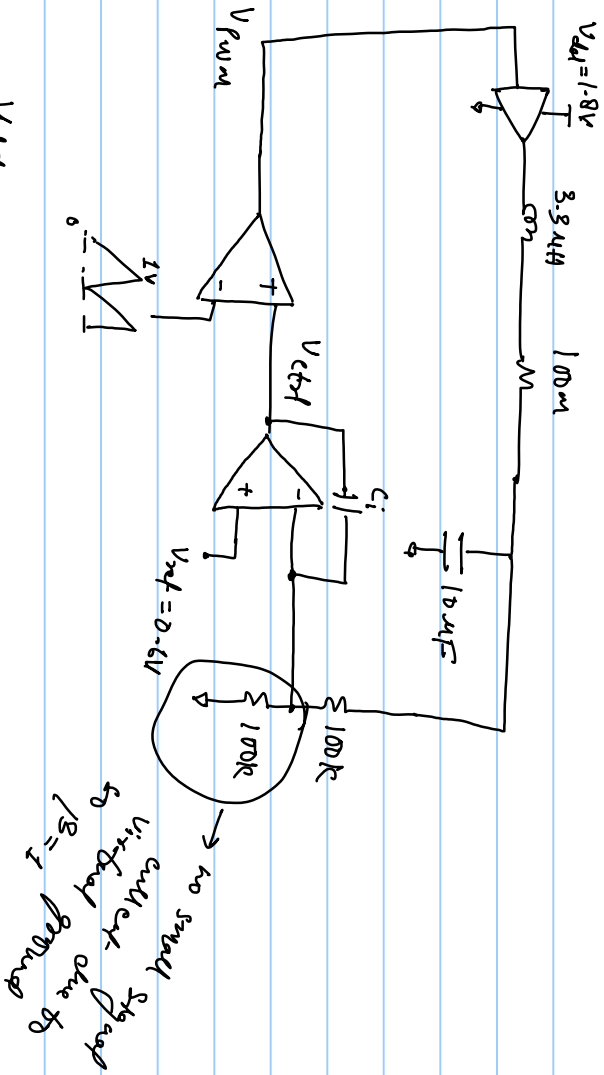

$$I_{curr} = \frac{V_{out}}{V_{in}}$$

$$C_i = 5.94 nF$$

⇒ Integral or type-1 compensation slows down the loop due to lower ω_{cgl} .

⇒ Poor transient response.

⇒ Only suitable for low bandwidth system.
(fixed load ON/OFF system)