

$$\omega_{\text{ugb}} = \frac{2\pi f_{\text{sw}}}{10}$$

$$\omega_{\text{R}} = 0.09 \text{ Mrad/sec} = \frac{1}{R_p C_i}$$

$$C_i = \frac{1}{R_p \omega_{\text{R}}}$$

Assume, $L = 3.3 \mu\text{H}$, $C = 10 \mu\text{F}$

$$V_{\text{dd}} = 1.8 \text{V}, V_{\text{M}} = 1 \text{V}, f_{\text{M}} = 1 \text{M Hz}$$

$$f_{\text{sw}} = 1 \text{M Hz}$$

$$f_{\text{ugb}} = \frac{f_{\text{sw}}}{10} = 100 \text{K Hz}$$

$$\omega_{\text{ugb}} = 2\pi \times 100 \text{K Hz} = 628 \text{K rad/sec.}$$


$$R_p = \frac{2\pi \times 10^5}{0.174 \times 10^6 \times \frac{1}{2} \times 1.8 \times 10^{-3}} = \frac{2\pi \times 10^2}{0.174 \times 0.9} = 4 \text{K}\Omega$$

① type compensator requires one more zero which can be added by having R_{out} in output cap.

② keeping higher f_u requires large $C_i \rightarrow$ large area.

③ Reducing f_u reduces C_i but at the cost of offset.

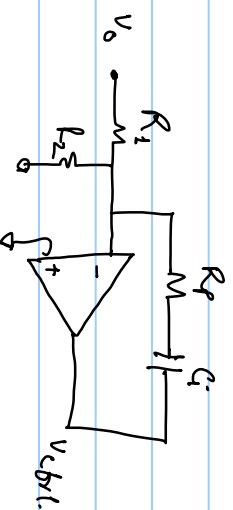Therefore, op-amp-RC compensator is preferred.



$$\text{Hcomp-II} = - \frac{R_p + \frac{1}{sC_i}}{R_1} = - \left[\frac{R_p}{R_1} + \frac{1}{R_1 C_i s} \right]$$

\downarrow \downarrow
 k_p $k_i = \frac{1}{R_1 C_i}$

$$\omega_z = \frac{1}{R_1 C_i}$$

$$R_1 = 100k$$

$k_p = \frac{1}{2}$ of k_p calculated in gm-c compensator.

$$\frac{k_p}{T_1} = 2 \Rightarrow R_p = 200k$$


$$C_1 = \frac{1}{\omega_c \times R_p} = \frac{1}{0.09 \times 10^6 \times 2 \times 10^5}$$

$$= \frac{10^{-11}}{0.18} = 55 \text{ pF}$$

Requires smaller capacitor.

Drawback of type-II compensator with R_{eq} .

\Rightarrow Output ripple is increased.

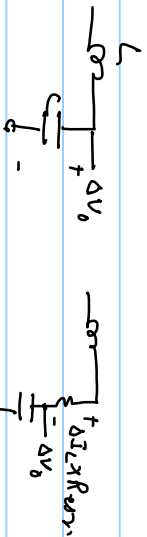


$$\Delta V_{o, \text{total}} = \Delta V_o \times R_{eq} + \Delta V_o$$

This is not preferred for applications requiring smaller ripple.

Therefore we need to add 2nd zero in the compensator.

type-II + one zero = type-III

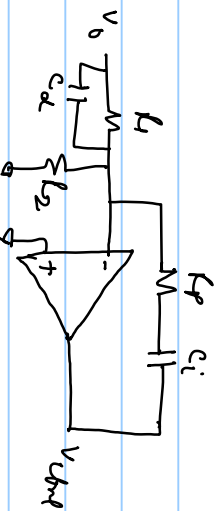

$$H_{\text{comp-III}}(s) = \underbrace{\left(k_p + \frac{k_i}{s}\right)}_{\text{type-II}} \underbrace{\left(1 + \frac{s}{\omega_{z2}}\right)}_{\text{2nd zero}}$$

$$\omega_{z2} = \frac{1}{R_1 C_1}$$

$$k_p + \frac{k_i}{s} = \frac{k_i}{s} \left(1 + \frac{k_p}{k_i} s\right) = \frac{k_i}{s} \left(1 + \frac{s}{\omega_{z1}}\right)$$

$$\omega_{z1} = \frac{k_i}{k_p}$$

$$H_{comp-III}(s) = \frac{k_i}{s} \frac{(1+s/\omega_{z1})(1+s/\omega_{z2})}{s}$$

$$\frac{k_i}{s} \left[1 + \frac{s}{\omega_{z1}} + \frac{s}{\omega_{z2}} + \frac{s^2}{\omega_{z1}\omega_{z2}} \right]$$

$$= \frac{k_i}{s} \left[1 + s \left(\frac{1}{\omega_{z1}} + \frac{1}{\omega_{z2}} \right) + \frac{s^2}{\omega_{z1}\omega_{z2}} \right]$$

$$= \frac{k_i}{\omega_{z1}} \left(1 + \frac{s\omega_{z1}}{\omega_{z2}} \right) + \frac{k_i}{s} + k_i \frac{s}{\omega_{z1}\omega_{z2}}$$

$$= k_p \left(1 + \frac{\omega_{z1}}{\omega_{z2}} \right) + \frac{k_i}{s} + \frac{k_p}{\omega_{z2}} s$$

$$\begin{matrix} P & I & D \\ k_p' & k_i/s & k_d s \end{matrix}$$

