

# Lecture-1

## EE5325 Power Management Integrated Circuits

Dr. Qadeer Ahmad Khan





Integrated Circuits and Systems Group  
Department of Electrical Engineering  
IIT Madras


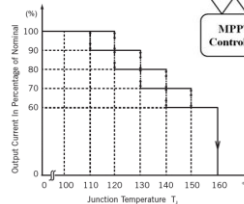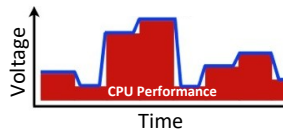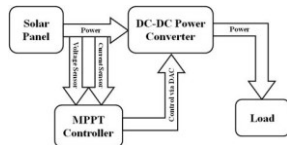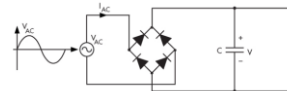
### What is Power Management?

Deals with Efficient and Reliable Power Delivery to a system





- Voltage conversion from one power domain to other
  - DC-DC Conversion (Regulators)
  - AC-DC/DC-AC Conversion (Rectifiers/Inverters)
- Voltage/Current Measurement
  - Voltage and Current Sensing
- Managing Losses or Heat
  - Current de-rating
  - Dynamic Voltage Scaling (DVS)


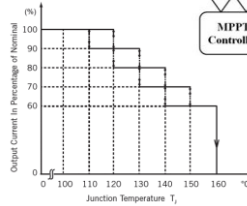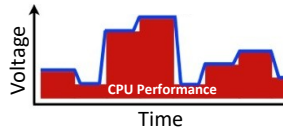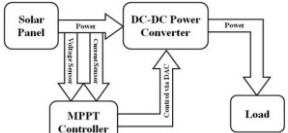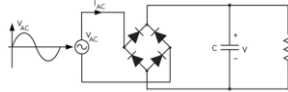
# What is Power Management?

Deals with Efficient and Reliable Power Delivery to a system

- Voltage conversion from one power domain to other
  - DC-DC Conversion (Regulators)
  - AC-DC/DC-AC Conversion (Rectifiers/Inverters)
- Voltage/Current Measurement
  - Voltage and Current Sensing
- Managing Losses or Heat
  - Current de-rating
  - Dynamic Voltage Scaling (DVS)



Achieved by controlling or managing power delivered to load



# Types of Power Management

## High Power:

- 100s to KWatts range powered by direct AC
- Discrete semiconductor devices (FETs, BJTs, diodes) and large passives



## Low/Mid Power:

- mWatts to 10s of Watts powered from battery
- Integrated controller & power FETs with few small external passives



Source: ST Microelectronics



## Types of Power Management

### High Power:

- 100s to KWatts range powered by direct AC
- Discrete semiconductor devices (FETs, BJTs, diodes) and large passives



### Low/Mid Power:

- mWatts to 10s of Watts powered from battery
- Integrated controller & power FETs with few small external passives



Source: ST Microelectronics


VLSI Power Management deals with mainly Low/Mid power applications



EE5325 Power Management Integrated Circuits  
Integrated Circuits and Systems Group, Department of EE, IIT Madras


5

## Need of Integrated Power Management

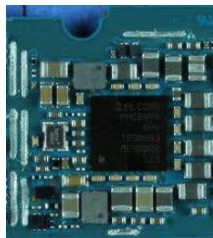

PMIC: 6mm x 6mm, 225 pins

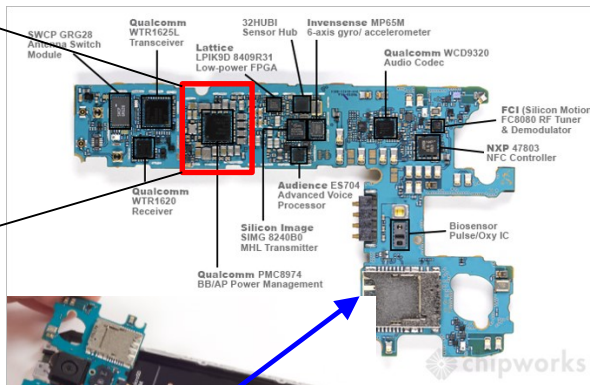- Power demand is increasing while board space is shrinking




Samsung Galaxy S4  
Source: chipworks




EE5325 Power Management Integrated Circuits  
Integrated Circuits and Systems Group, Department of EE, IIT Madras

6

# Application of DC-DC Converters

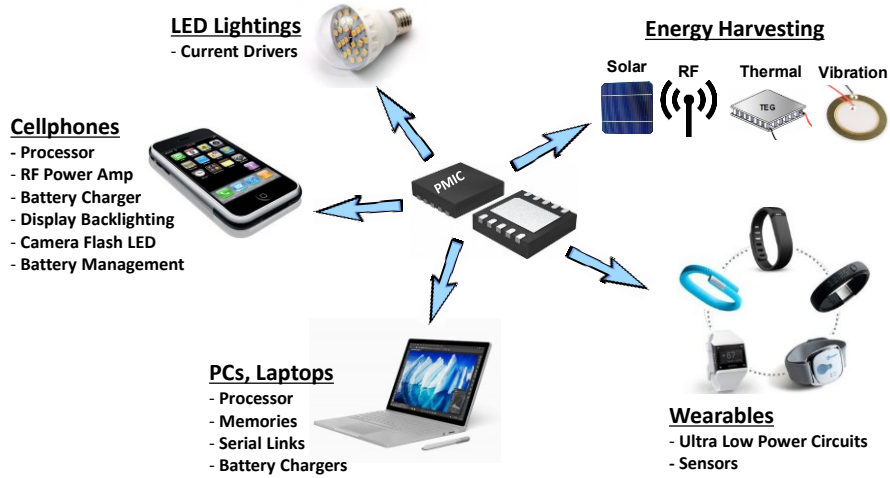

# Application of DC-DC Converters

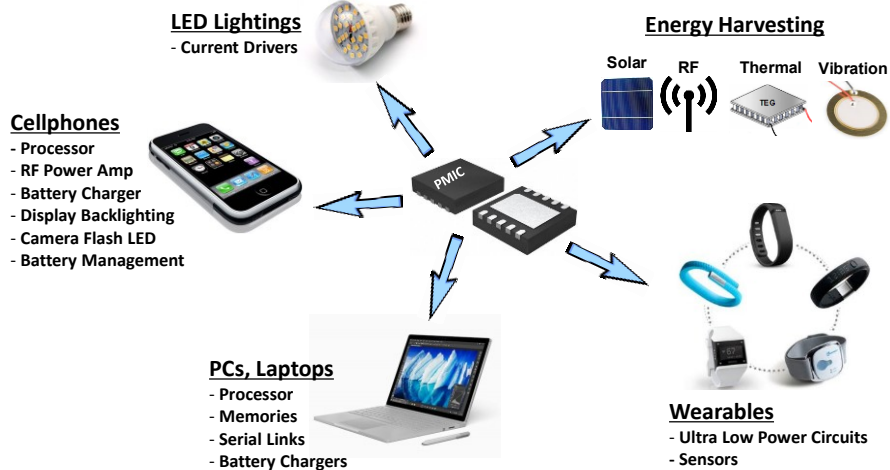

**Power delivery for these applications is mostly met by DC-DC Converters**



## Applications in Self Powered Sensors

- Targeted for ultra low power applications – IoT
- Highly efficient, miniaturized low power converters
- Energy is harvested from freely available sources such as light, vibration, heat, RF


### Structural Health Monitoring

- Powering Sensors from Mechanical Vibration
- Wireless Charging



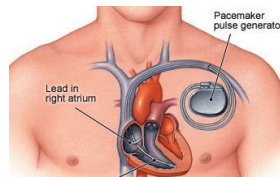
### Implantable Biomedical

- Charging Battery from Heart Beat
- Wireless Charging




### Health Monitoring Systems

- Powering Sensors from Body Heat

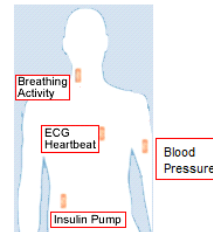

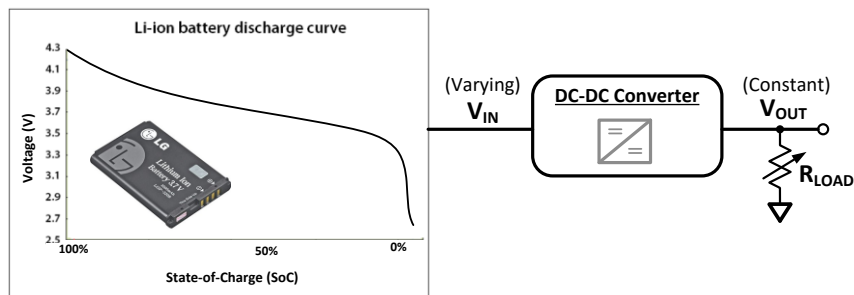
## DC-DC Power Converter

- Converts voltage from one domain to other
- Provides regulated output voltage
  - Under varying conditions (input voltage, output current)



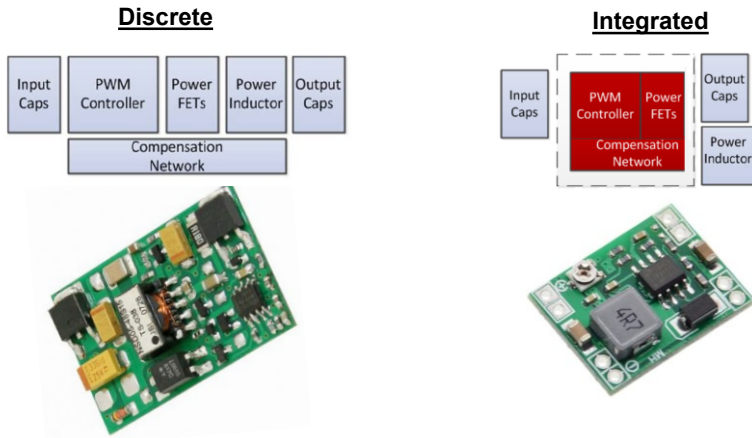
## Discrete Vs. Integrated Power Converters




VLSI Systems mostly use Integrated DC-DC Converters due to limited board space


## DC-DC Converter Types

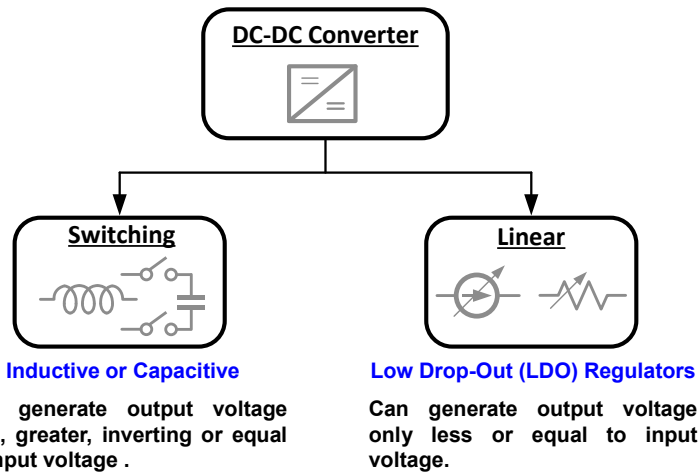

## DC-DC Converter Types

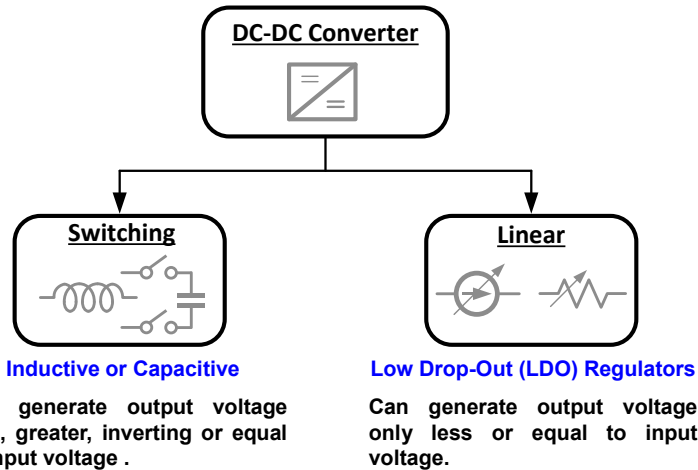


## Switching vs Linear Regulator

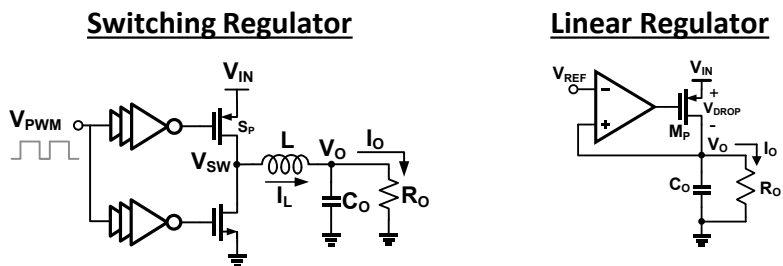

- Regulation achieved by changing on/off time
- Switches are in either linear or cutoff  $\rightarrow$  reduced losses
- High efficiency over wide range of  $V_O/V_{IN}$
- Regulation achieved by dropping voltage
- Switches are in saturation  $\rightarrow$  higher losses
- Poor efficiency when  $V_O/V_{IN}$  ratio is low

# Switching vs Linear Regulator

## Switching Regulator

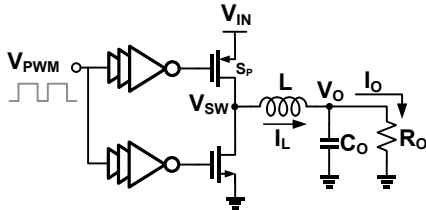

- Regulation achieved by changing on/off time
- Switches are in either linear or cutoff → reduced losses
- High efficiency over wide range of  $V_O/V_{IN}$


**More than 90% of power requirement is met by Switching Converters**


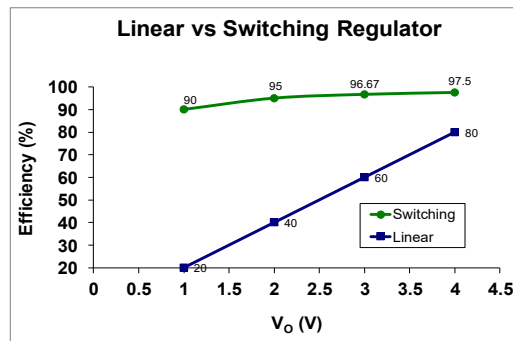
# Switching Vs Linear Regulator

- For  $V_{in} = 5V$ ,  $V_o = 1V$  and  $I_{Load} = 1A$ 
  - 80% power loss in the Linear regulator as compared to 10% in switching regulator
- For  $V_{in} = 5V$ ,  $V_o = 4V$  and  $I_{Load} = 1A$ 
  - 20% power loss in linear regulator as compared to 2.5% in switching regulator


$$\text{Efficiency } (\eta) = \frac{\text{Output Power}}{\text{Input Power}}$$






## Switching vs Linear Regulator

### Switching Regulator

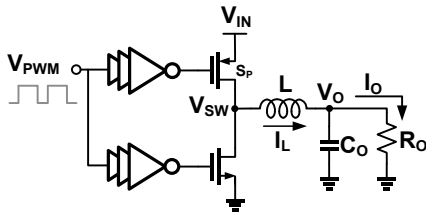

- Regulation achieved by changing on/off time
- Switches are in either linear or cutoff  $\rightarrow$  reduced losses
- High efficiency over wide range of  $V_O/V_{IN}$

### Linear Regulator

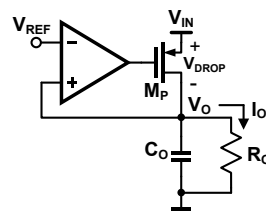

- Regulation achieved by dropping voltage
- Switches are in saturation  $\rightarrow$  higher losses
- Poor efficiency when  $V_O/V_{IN}$  ratio is low

## How to Choose Between Linear Vs Switching

- **Cost**
  - Linear Regulators are cheaper compared to switching
- **Power**
  - In a multi-power domain, linear regulator are preferred over switching regulators for low power domains
  - Switching regulators are preferred for high power applications
- **Conversion Ratio ( $V_{out}/V_{in}$ )**
  - Efficiency of linear regulators is comparable to switching for higher  $V_{out}/V_{in}$  ( $>0.9$ )
  - Switching regulators are preferred when  $V_{out}/V_{in}$  is less
- **Noise**
  - Linear regulators are quiet compared to switching hence preferred over switching for noise sensitive applications such as RF, sensors and other analog circuitries