
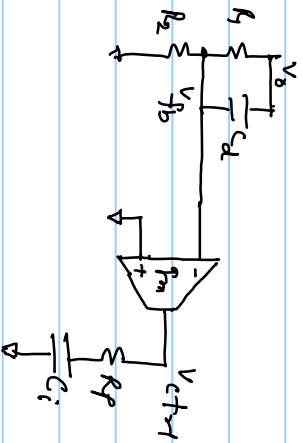


### Type - III Com - C Compensator

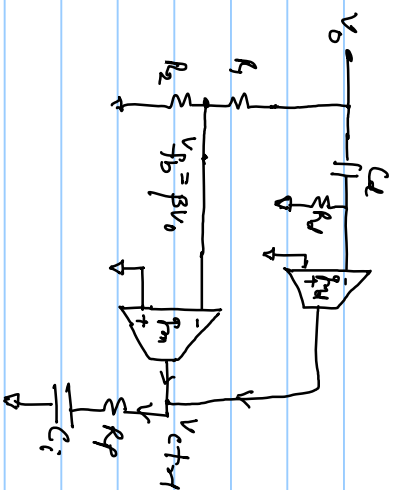

$$\frac{V_{0B}(s)}{V_{0A}(s)} = \frac{R_2 \left( \frac{1}{R_1} + sC_d \right)}{R_2 \left( \frac{1}{R_1} + sC_d \right) + 1} = \frac{Z_2 Y_1}{Z_2 Y_1 + 1}$$

$$\begin{aligned} & \frac{R_2}{R_1} (1 + R_1 C_d s) \\ & \frac{R_2}{R_1} + R_2 C_d s + 1 \\ & = \left( \frac{1 + R_1 C_d s}{1 + \frac{R_1 R_2}{R_1 + R_2} C_d s} \right) \frac{R_2}{R_1 + R_2} \\ & = \beta \left( \frac{1 + R_1 C_d s}{1 + \beta R_1 C_d s} \right) \Rightarrow \text{effect of zero is cancelled out due to pole.} \end{aligned}$$



$$-\left(\frac{R_d C_d s}{1 + R_d C_d s}\right) V_0 \times g_m - \beta V_0 g_m - \frac{V_{c1}}{R_p + \frac{1}{C_1 s}} = 0$$

$$\frac{C_1 s}{1 + R_p C_1 s} V_{c1} = -V_0 \left( \frac{R_d C_d s}{1 + R_d C_d s} g_m + \beta g_m \right)$$

$$\frac{1}{R_d C_d} \gg \omega_{ngt}$$

$$\frac{V_{c1}(s)}{V_0(s)} = \frac{1}{C_1 s} (1 + R_p C_1 s) \left( \frac{R_d C_d s}{1 + R_d C_d s} g_m + \beta g_m \right)$$

$$= \frac{\beta g_m}{c_i s} (1 + R_p c_i s) \left( 1 + \frac{R_d C_d}{\beta} \frac{g_m s}{g_m} \right) = H_{\text{comp-III}}(s)$$

$$k_i = \frac{\beta g_m}{c_i}$$

$$\omega_{z_1} = \frac{1}{R_p c_i} \quad \& \quad \omega_{z_2} = \frac{\beta}{R_d C_d} \left( \frac{g_m}{g_m} \right)$$

$$\beta = \frac{1}{2}, \quad \frac{1}{R_d C_d} = 5 \omega_{ng_0}$$

$$\omega_{z_2} = \frac{5}{2} \omega_{ng_0} \left( \frac{g_m}{g_m} \right)$$

$$\omega_{z_2} = \omega_0$$

$$\omega_0 = 2.5 \omega_{ng_0} \left( \frac{g_m}{g_m} \right)$$

$$\Rightarrow g_{\text{mid}} = 2.5 \left( \frac{\omega_{ng_0}}{\omega_0} \right) (g_m)$$