 


Error Amplifier



- ① Bandwidth of op-amp should be high enough not to interfere with loop gain T.F.


Op-amp $\omega_{gb} \geq 10 \times$ dc ω_{c}

$$A(s) = \frac{A_0}{1 + s/\omega_p}$$

- ② High frequency poles (outside ω_{gb}) in type-III compensator help in suppressing resonance which might occur due to internal poles of op-amp.
- ③ Any op-amp topologies can be used.


Delays associated with PWM modulation

Trailing edge

 

$$T_d = (1-D)T_{sw}$$

Leading Edge

 


$$T_d = D \cdot T_{sw}$$

Pulse Skip Mode (PSM) & Pulse Frequency Modulation (PFM)

→ used in light load condition or when duty cycle is reduced

$D_{min} \rightarrow T_{on-min}$

 


$$T_{on-min} = 50\mu s$$

$$D_{min} = 5\%$$

To operate at below 5% duty cycle, T_{off} must be increased.

 One way is to reduce the switching freq. while keeping T_{on} fixed at T_{on-min} .



For higher resolution

10 Dwin: 0

9 Dwin: 0

8 Dwin: 0

1

1

Dwin: 0

Dwin: 2.0%

" : 3.0%

" :

10.0%

FSM \rightarrow digital way of implementing FSM.

FSM \rightarrow instead of Vhdl controlling the duty cycle, it controls only Toff.

$$T_{off} \rightarrow \frac{1}{I_{load}}$$

