
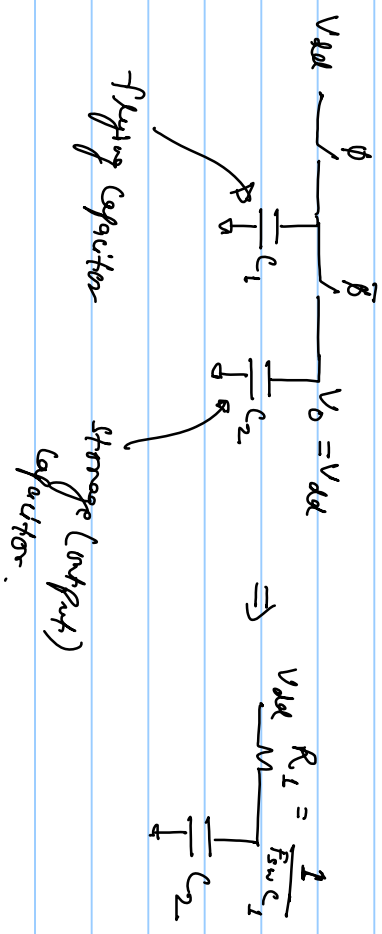


Switched capacitor DC-DC converter

Switched capacitor is used as resistor

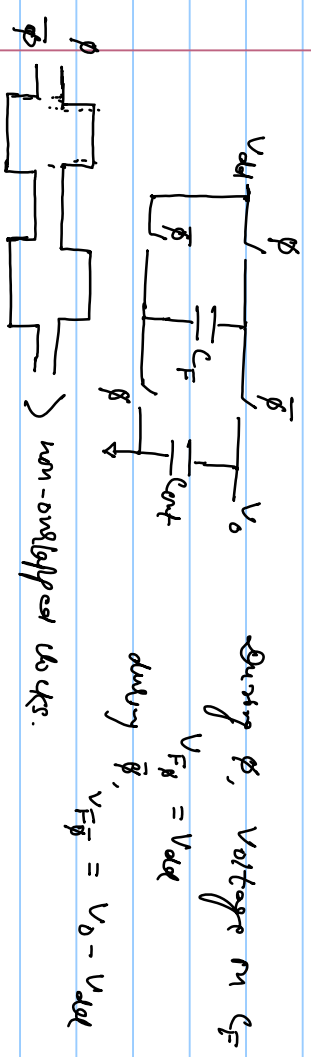

$V_o = 2x V_{dd}$



$$V_{FV} = V_{F\bar{F}}$$

$$V_{dcl} = V_o - V_{dcl}$$

$$\Rightarrow \boxed{V_o = 2V_{dcl}} \Rightarrow \text{ideal case under no load}$$


Under load condition.


$$V_o = 2V_{dcl} - V_{loss}$$

$$V_{loss} \rightarrow I_{load}$$


Open loop operation  $\rightarrow$  output can't be regulated.

Applications in open loop.

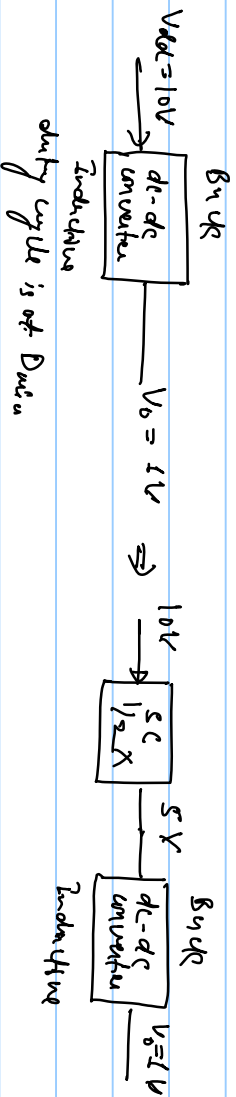

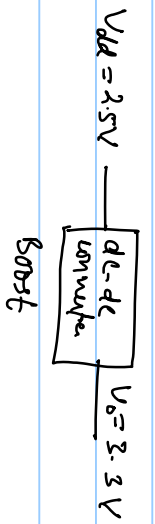


$\Rightarrow$

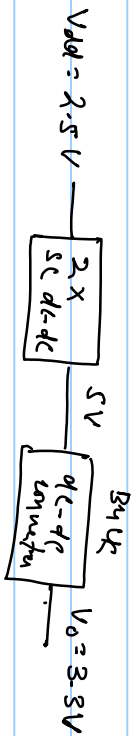


$I_L = \frac{1}{1-D} I_{load}$  (Boost)

- ① Better transient response  $\rightarrow$  no R.H.P zero
- ② Smaller output capacitor or smaller ripple with same cap.
- ③ Improved efficiency because  $I_L = I_{load}$  (Boost)

Regulation Volt in SC dc-dc converter

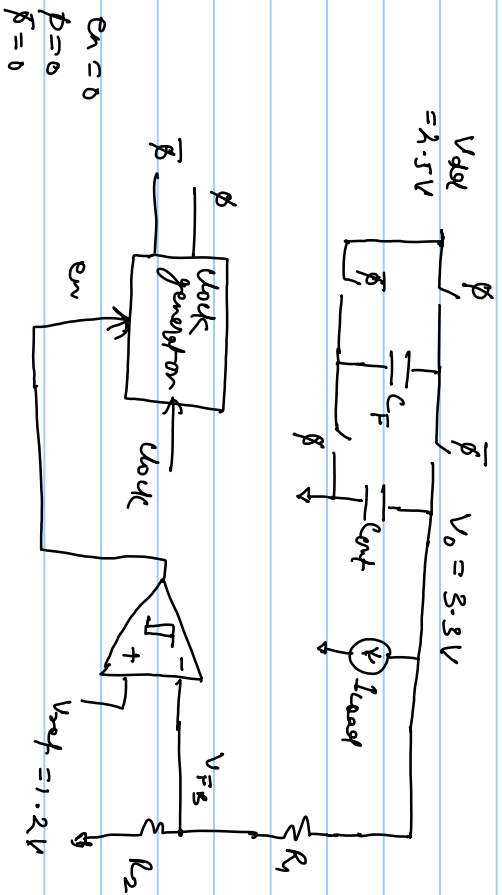

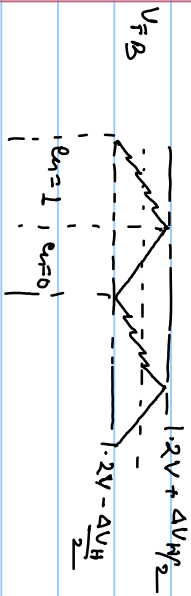$\frac{V_{ref}}{V_o} = \frac{1.2}{3.3} = \beta$



⇒ Similar to PFM operation in inductive dc-dc

In open loop.

$V_o = 5V$ ,  $V_{dd} = 2.5V \rightarrow$  efficient

$V_o = 3.3V$ ,  $V_{dd} = 2.5V$  (closed loop)  $\rightarrow$  inefficient as  $5V - 3.3V = 1.7V$  will be dropped.

