
Switched Capacitor DC-DC Converter

EE5325 VLSI Power Management Circuits

Dr. Qadeer Ahmad Khan

**Integrated Circuits and Systems Group
Department of Electrical Engineering
IIT Madras**



EE5325 Power Integrated Management Circuits
Integrated Circuits and Systems Group, Department of EE, IIT Madras

Switched Capacitor (SC) DC-DC Converter


- Works on a principle of charging and delivering the energy through capacitor
- Concept is similar to switched capacitor DAC
- Voltage can be varied by re-arranging the capacitors in series and parallel
- Can be used to implement Buck, Boost or Buck-Boost converters




EE5325 Power Integrated Management Circuits
Integrated Circuits and Systems Group, Department of EE, IIT Madras

2

Basic Concept

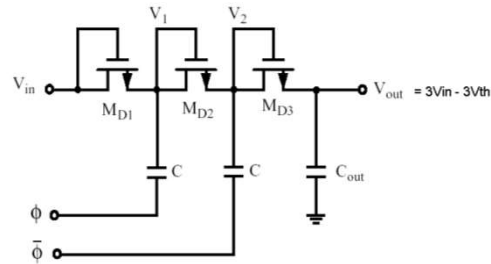


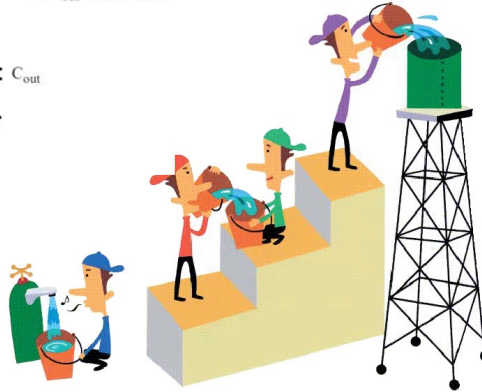- Step 1- $\phi = 0$
 $V1 = Vin - V_{th}$
- Step 2- $\phi = Vin$
 $V1 = 2Vin - V_{th}$
- Step 3- $\phi = 0$
 $V2 = 2Vin - V_{th}$
- Step 4- $\phi = Vin$
 $V2 = 3Vin - 2V_{th}$
- $V_{out} = 3Vin - 3V_{th}$




H-bridge Topology

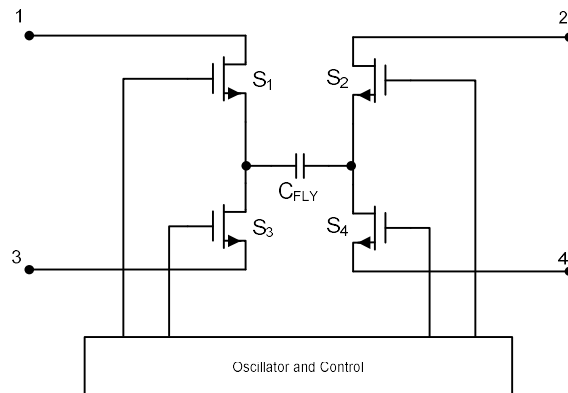
- Buck, Boost or Inverting functions can be achieved depending upon how input and output connects




H-bridge Topology - Boost

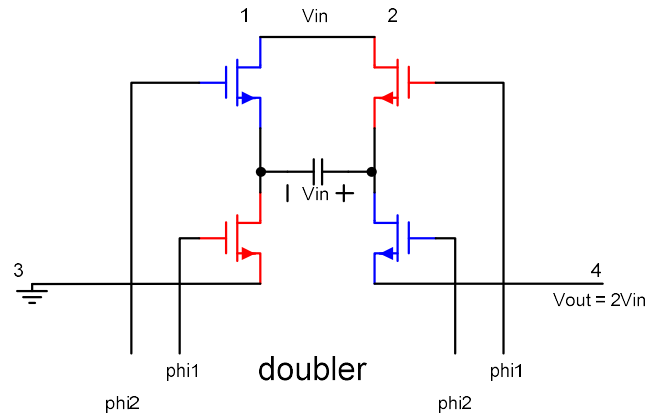

H-bridge Topology - Buck

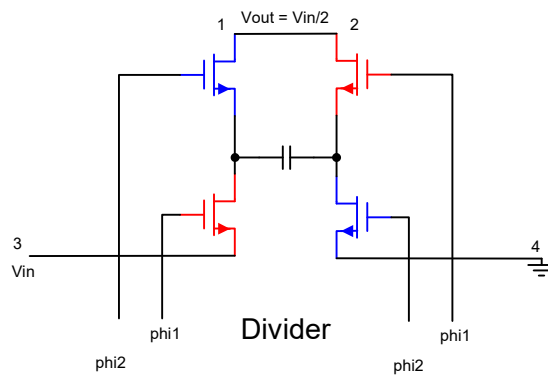


H-bridge Topology - Inverting

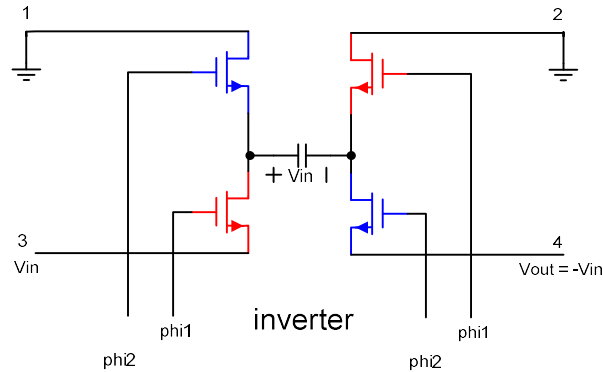


Efficiency of SC DC-DC Converter

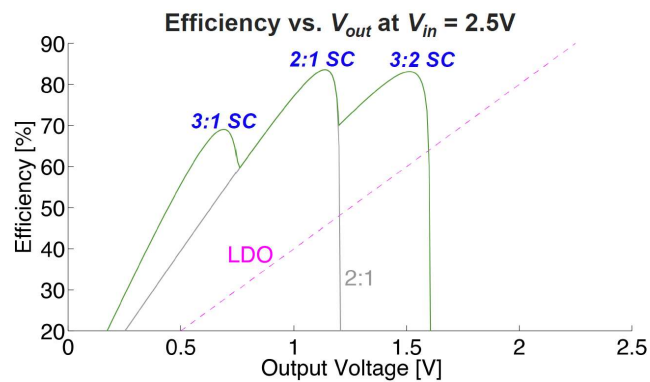
- Efficiency peaks $V_o/V_{in} = \text{Gain}$
- More gain settings are required to achieve higher efficiency across wide V_o/V_{in} range → flatter efficiency curve



LM3352 SC Regulator

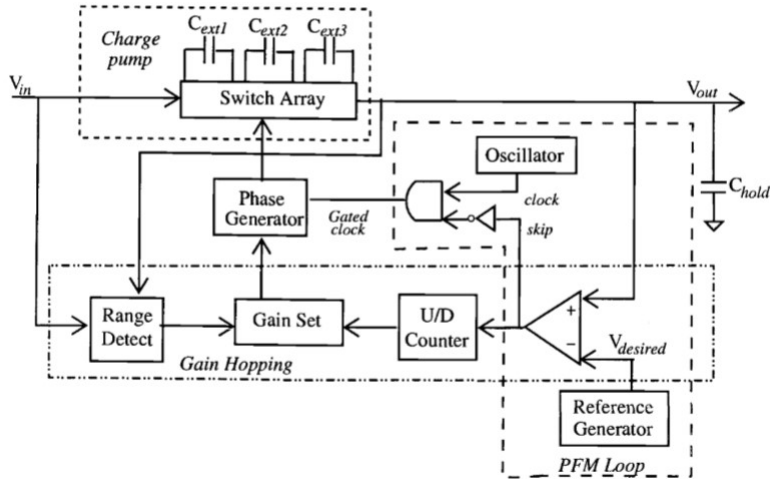

LM3352 SC Regulator - Switches

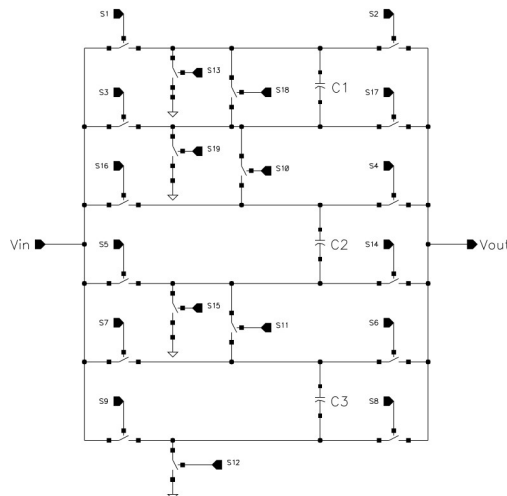

Region	Max. Gain	Min. Gain
1	2/3	1/2
2	2/3	1/2
3	3/4	2/3
4	1	2/3
5	1	3/4
6	1	1
7	4/3	1
8	3/2	4/3
9	2	4/3
10	2	4/3
11	2	2

↑ Buck
↓ Bypass
↑ Boost

