

Time-Based Voltage Regulators

EE5325 Power Management Integrated Circuits

Dr. Qadeer Ahmad Khan

Integrated Circuits and Systems Group
Department of Electrical Engineering
IIT Madras





EE5325 Power Management Integrated Circuits
Integrated Circuits and Systems Group, Department of EE, IIT Madras

1

DC-DC Converter Wish List

- **High Power Density**
 - Higher efficiency to reduce heat dissipation
 - Smaller passive components to reduce board space
 - Shrinking die size by innovative controller and integrating more features on single PMIC

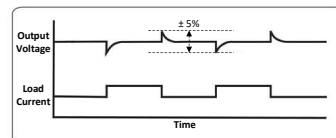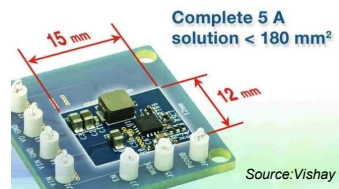- **Stable Supply**
 - High performance controller design




EE5325 Power Management Integrated Circuits
Integrated Circuits and Systems Group, Department of EE, IIT Madras

2

Technology Trends in PMIC

- Scaling semiconductor process technology


- Higher speed Power FETs
- Smaller Size

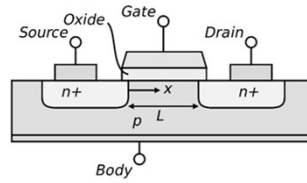


$0.5\mu\text{m} \rightarrow 0.35\mu\text{m} \rightarrow 0.18\mu\text{m}$

- Low parasitic packaging technologies (WLP, BGA)

- Smaller Parasitic

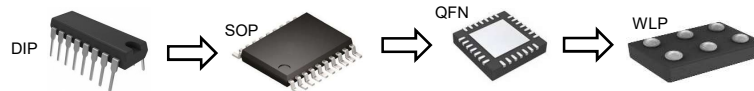

PMIC vs Passive Size

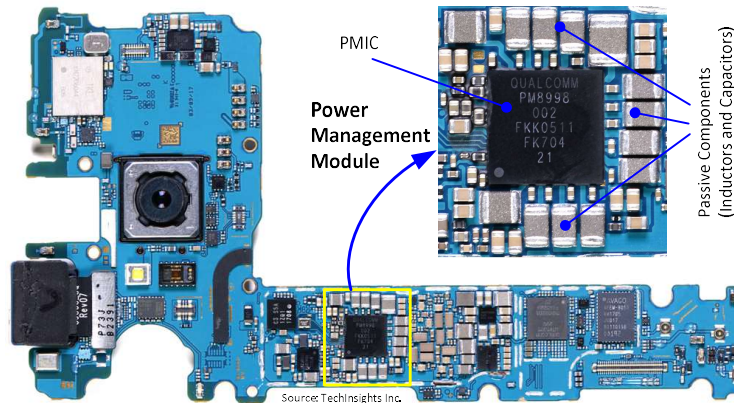

Source: Techinsights Inc.

Samsung Galaxy S8

External Passive components (L and C) occupy 2/3rd of the total power module size




Passive Size Reduction


- Output ripple is a function of inductor (L), capacitor (C) and switching frequency (F_{SW})

$$\Delta V_O = \frac{V_{IN} D(1 - D)}{8F_{SW}^2 LC_O}$$

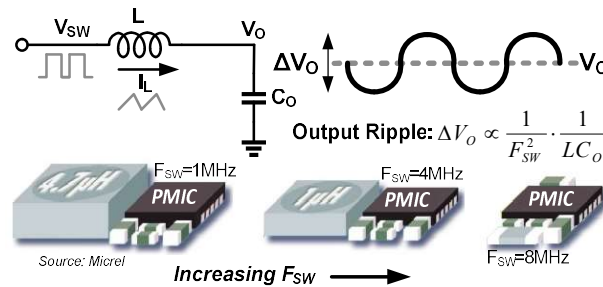- Doubling switching frequency reduces passive components by 4x for the same output ripple




Limitations of Analog Controller

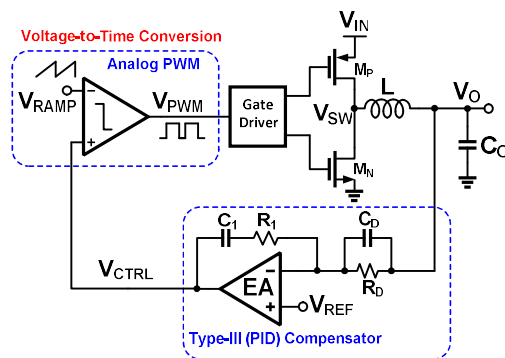

- PID Compensator**
 - Area/power inefficient
- Error Amplifier (EA)**
 - Bandwidth limits transient response
- Ramp Generator**
 - Limits switching frequency
- PWM Comparator**
 - Delay limits output range



Limitations of Analog Controller

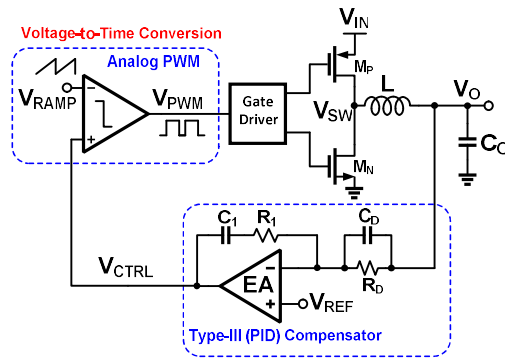


- **PID Compensator**
 - Area/power inefficient
- **Error Amplifier (EA)**
 - Bandwidth limits transient response
- **Ramp Generator**
 - Limits switching frequency
- **PWM Comparator**
 - Delay limits output range

Significant power penalty at high F_{sw}




Digital Controller Design Challenges

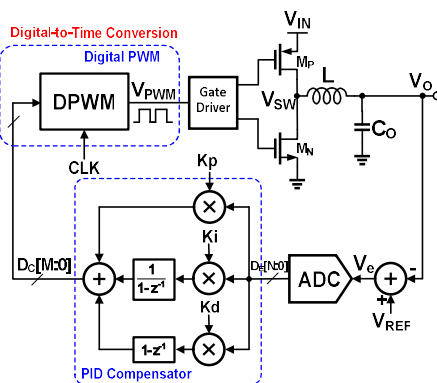

- **Small controller area at low F_{sw}**
- **Non-linear loop dynamics**
 - Steady state is a bounded limit cycle \rightarrow large ripple
- **ADC res. > reg. accuracy**
 - 0.1% accuracy \rightarrow 10bit
- **DPWM res. \approx inverter delay**
 - Large area and power
- **$F_{CLK} \gg F_{sw}$**



Digital Controller Design Challenges

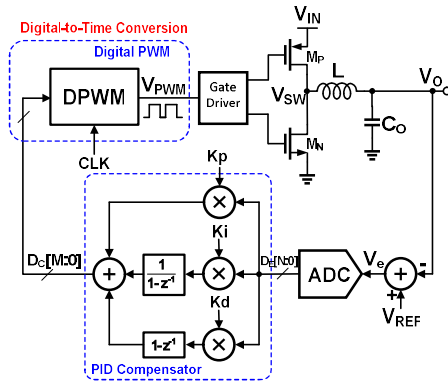


- Small controller area at low F_{sw}
- Non-linear loop dynamics
 - Steady state is a bounded limit cycle \rightarrow large ripple
- ADC res. > reg. accuracy
 - 0.1% accuracy \rightarrow 10bit
- DPWM res. \approx inverter delay
 - Large area and power
- $F_{CLK} \gg F_{SW}$

Significant power & area penalty at high F_{SW}




Time Based Controlled DC-DC Converter

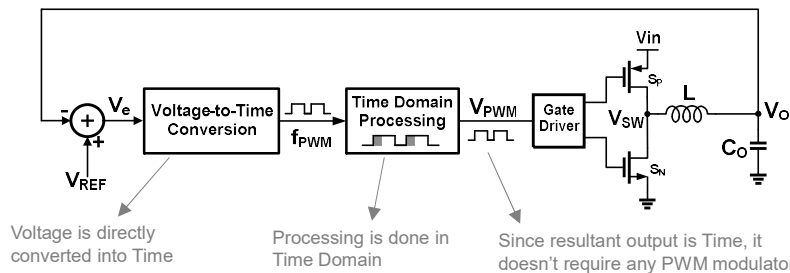

- Preserves benefits of both analog (low power, high accuracy) and digital (process scaling, low voltage operation, area efficient) without using any A/D or error amplifier
- Implicit PWM generation \rightarrow Eliminates PWM modulator hence minimum delay




Time Based Controlled DC-DC Converter

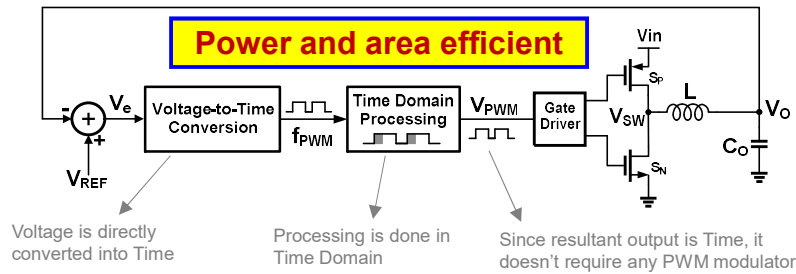

- Preserves benefits of both analog (low power, high accuracy) and digital (process scaling, low voltage operation, area efficient) without using any A/D or error amplifier
- Implicit PWM generation → Eliminates PWM modulator hence minimum delay




VCO as Time-based Integrator

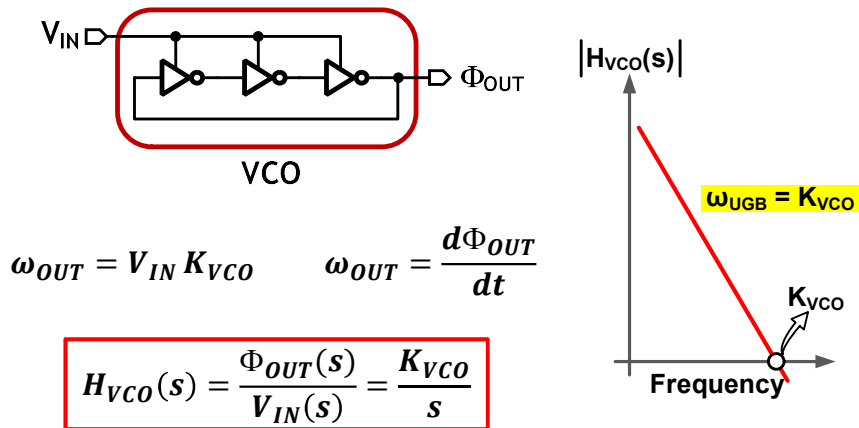

VCO acts as an ideal V-to- Φ integrator




VCO Behavior in Time Domain

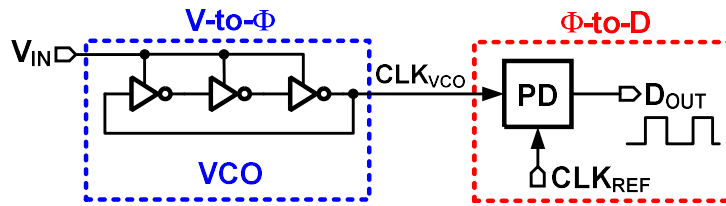

$$\Phi_{D_{OUT}} - \Phi_{CLK_{REF}} = K_{VCO} \int_0^t V_{IN}(\tau) d\tau$$

$$D_{OUT} = \frac{\Phi_{D_{OUT}} - \Phi_{CLK_{REF}}}{2\pi}$$


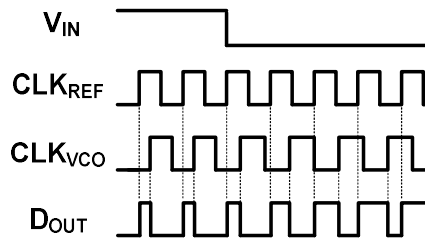
$$D_{OUT} = \frac{K_{VCO}}{2\pi} \int_0^t V_{IN}(\tau) d\tau$$



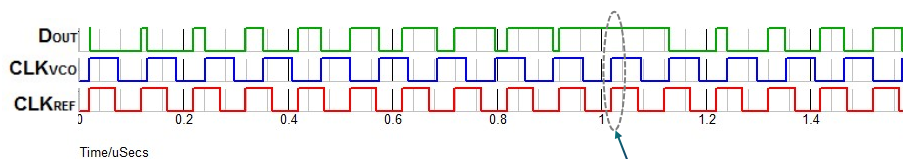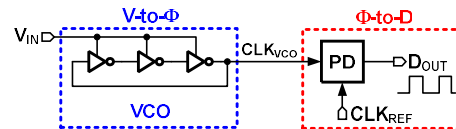Example of Phase Accumulation

$f_o = 10\text{MHz}$ (free running frequency of VCO)
Or $\omega_o = 2\pi \cdot 10\text{MHz}$
 $K_{VCO} = 2\pi \text{Mrad/s/V}$

Then phase difference will become 2π every 10th cycle of the clock





Phase difference becomes 2π



Opamp-RC vs Time Based Integrator



Voltage Based Integrator

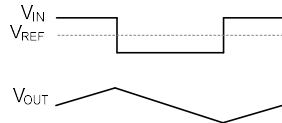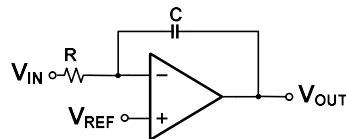- Input voltage is integrated as voltage
- Integral Gain = $1/RC$




Time Based Integrator

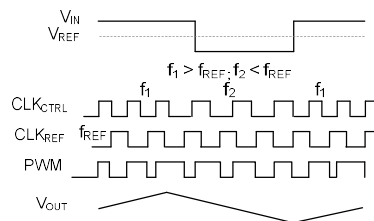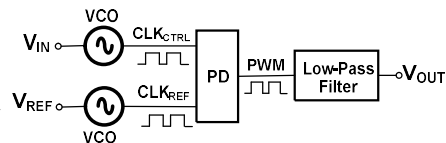- Input voltage is integrated as phase (time) by VCO
- Integral Gain = K_{VCO}



Buck w/ Time-based Type-I Controller

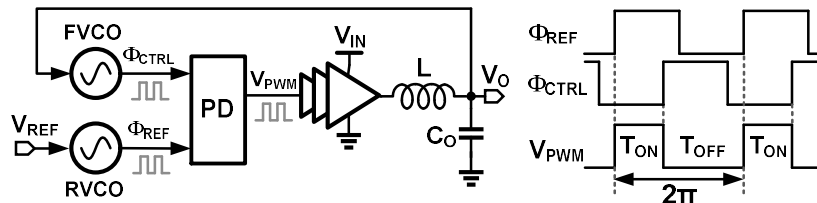

- Acts as a Frequency Locked Loop, FLL
- In steady state : $f_{FVCO} = f_{RVCO} \Rightarrow V_O = V_{REF} = D \cdot V_{IN}$

$$D = \frac{T_{ON}}{T_{ON} + T_{OFF}} = \frac{(\Phi_{CTRL} - \Phi_{REF})}{2 \cdot \pi} = \frac{V_O}{V_{IN}}$$



Time Based PID Controller


$$H_{PID}(s) = K_P + \frac{K_I}{s} + K_D s$$

Need 3 functions to realize time based PID compensator:

1. Time based Integrator \rightarrow VCO
2. Time based Proportional (Gain) \rightarrow ?
3. Time based Differentiator \rightarrow ?




Time-based Proportional Control

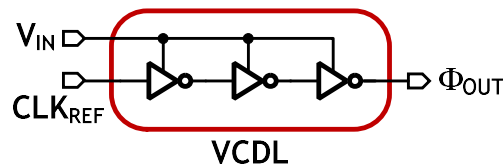

$$\Phi_{OUT} = \Phi_{CLK_{REF}} + K_{VCDL} \cdot V_{IN}$$

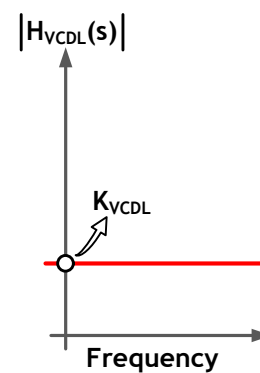
$$H_{VCDL}(s) = \frac{\Phi_{OUT}(s)}{V_{IN}(s)} = K_{VCDL}$$



VCDL acts as an ideal V-to- Φ converter




Time-based Differentiator

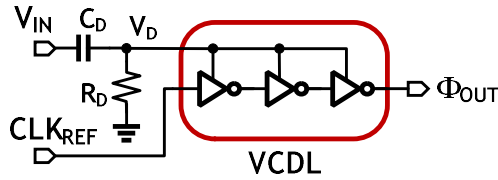

$$\Phi_{OUT} \approx \Phi_{CLK_{REF}} + K_{VCDL} R_D C_D \cdot \frac{dV_{IN}}{dt}$$

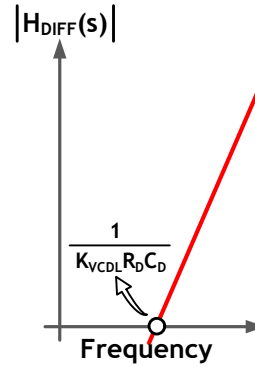
$$H_{DIFF}(s) = \frac{\Phi_{OUT}(s)}{V_{IN}(s)} = K_{VCDL} R_D C_D s$$



H.P. filter + VCDL acts as an ideal V-to-Φ differentiator




Buck Converter with T-PID Controller

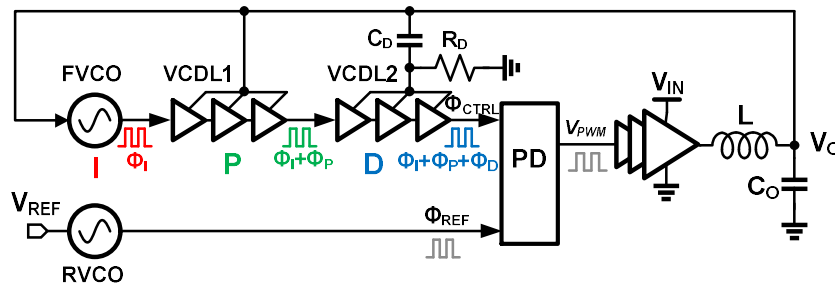

- Integral gain $\rightarrow K_{VCO}$ of FVCO
- Proportional gain $\rightarrow K_{VCDL}$ of VCDL₁
- Derivative gain $\rightarrow R_D C_D$ and K_{VCDL} of VCDL₂



Mapping V-PID to T-PID (1)

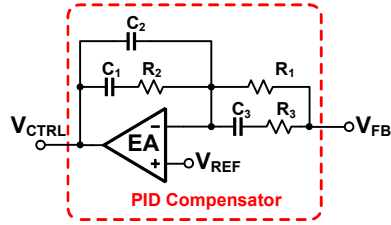

where, $G = \frac{R_2}{R_1}$

$$H^V_{PID}(s) = G \cdot w_{z1} \frac{(1 + \frac{s}{w_{z1}})(1 + \frac{s}{w_{z2}})}{s(1 + \frac{s}{w_p})}$$

Ignoring w_p and simplifying


$$H^V_{PID}(s) = G \cdot \left\{ \left(1 + \frac{w_{z1}}{w_{z2}} \right) + w_{z1} \frac{1}{s} + \frac{1}{w_{z2}} s \right\}$$

Comparing with standard $H_{PID}(s) = K_P + \frac{K_I}{s} + K_D s$

$$K^V_P = G \cdot \left(1 + \frac{w_{z1}}{w_{z2}} \right) \quad K^V_I = G \cdot w_{z1} \quad K^V_D = \frac{G}{w_{z2}}$$



Mapping V-PID to T-PID (1)

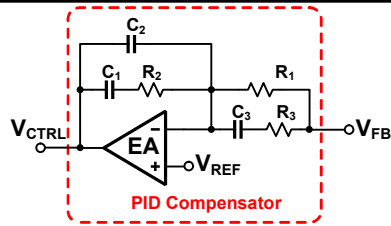

where, $G = \frac{R_2}{R_1}$

$$H^V_{PID}(s) = G \cdot w_{z1} \frac{(1 + \frac{s}{w_{z1}})(1 + \frac{s}{w_{z2}})}{s(1 + \frac{s}{w_p})}$$

Ignoring w_p and simplifying

$$H^V_{PID}(s) = G \cdot \left\{ \left(1 + \frac{w_{z1}}{w_{z2}} \right) + w_{z1} \frac{1}{s} + \frac{1}{w_{z2}} s \right\}$$

Comparing with standard $H_{PID}(s) = K_P + \frac{K_I}{s} + K_D s$

$$K^V_P = G \cdot \left(1 + \frac{w_{z1}}{w_{z2}} \right) \quad K^V_I = G \cdot w_{z1} \quad K^V_D = \frac{G}{w_{z2}}$$

↑
Proportional


↑
Integral

↑
Derivative



Mapping V-PID to T-PID (2)
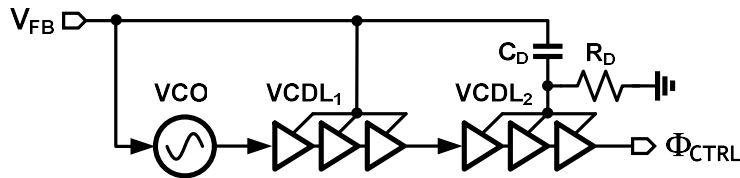
$$H^V_{PID}(s) = G \cdot \left\{ \left(1 + \frac{\omega_{z1}}{\omega_{z2}} \right) + \omega_{z1} \frac{1}{s} + \frac{1}{\omega_{z2}} s \right\}$$



$$H^T_{PID}(s) = K_{VCDL1} + K_{VCO} \frac{1}{s} + K_{VCDL2} R_D C_D s$$

$$K^T_P = K_{VCDL1}$$

$$K^T_I = K_{VCO}$$

$$K^T_D = K_{VCDL2} R_D C_D$$



$$K^V_P = G \cdot \left(1 + \frac{\omega_{z1}}{\omega_{z2}} \right)$$

$$K^V_I = G \cdot \omega_{z1}$$

$$K^V_D = \frac{G}{\omega_{z2}}$$




T-PID Transfer Function

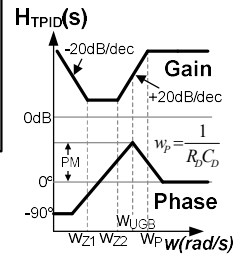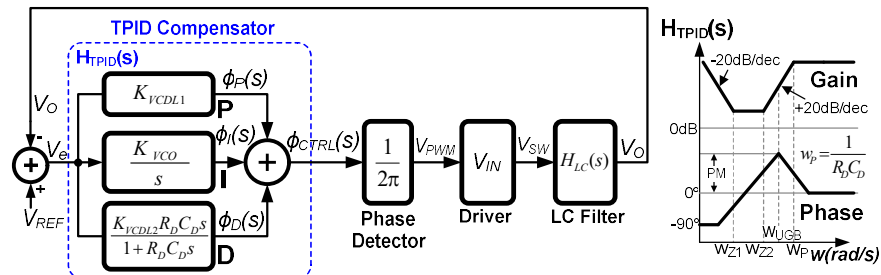

$$K_{VCO} = K_I \quad K_{VCDL1} = K_I \left(\frac{1}{\omega_{z1}} + \frac{1}{\omega_{z2}} \right) \quad K_{VCDL2} = \frac{1}{R_D C_D} \cdot \frac{1}{\omega_{z1} \cdot \omega_{z2}}$$




Circuit Implementation

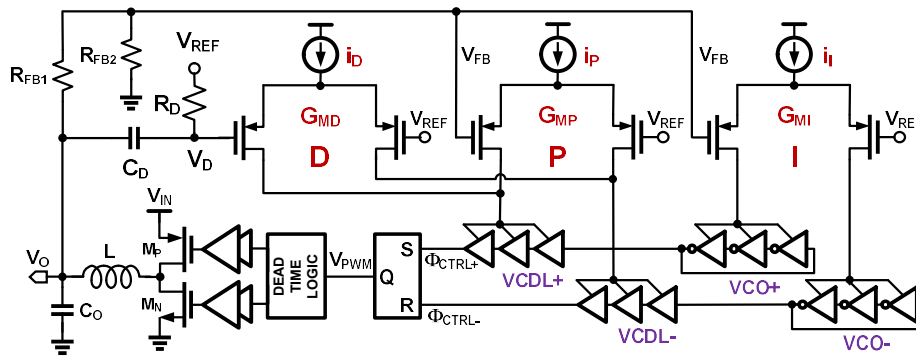

- Phase detector is implemented with SR latch
- Fully differential control eliminates reference clock
- Shared VCDL for proportional and derivative control




Prototype Buck Converter in 180nm CMOS

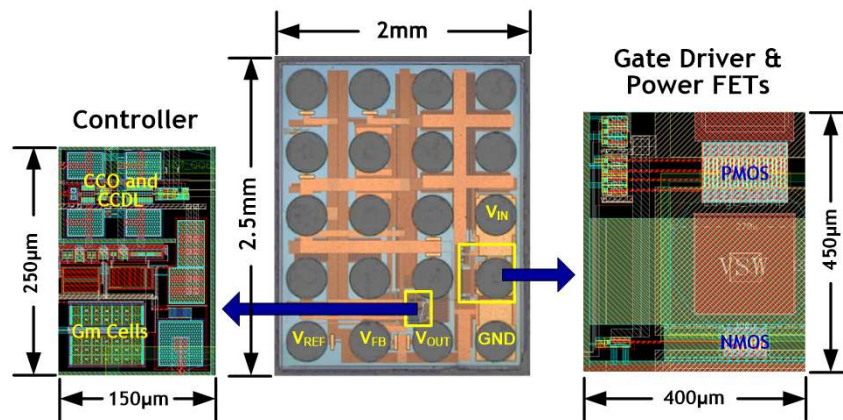


- "A 10–25 MHz, 600 mA buck converter using time-based PID compensator with 2µA/MHz quiescent current, 94% peak efficiency, and 1MHz BW," *Symposium on VLSI Circuits (VLSIC), June 2014.*
- "High frequency buck converter design using time-based control techniques," *IEEE JSSC, Apr. 2015.*




Steady-State Waveforms ($V_O = 1V$)

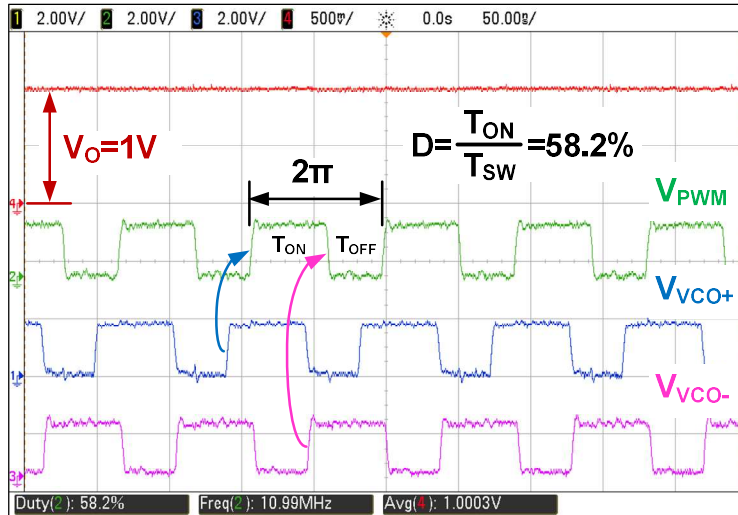


Load Transient Response

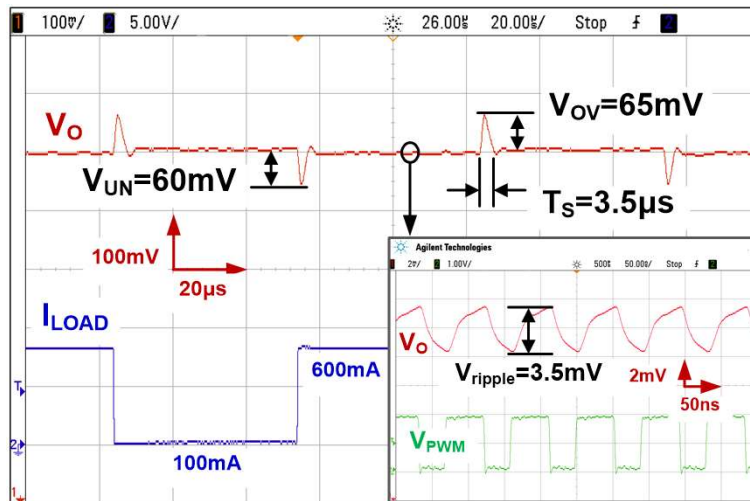

Oscillator Frequency Spectra

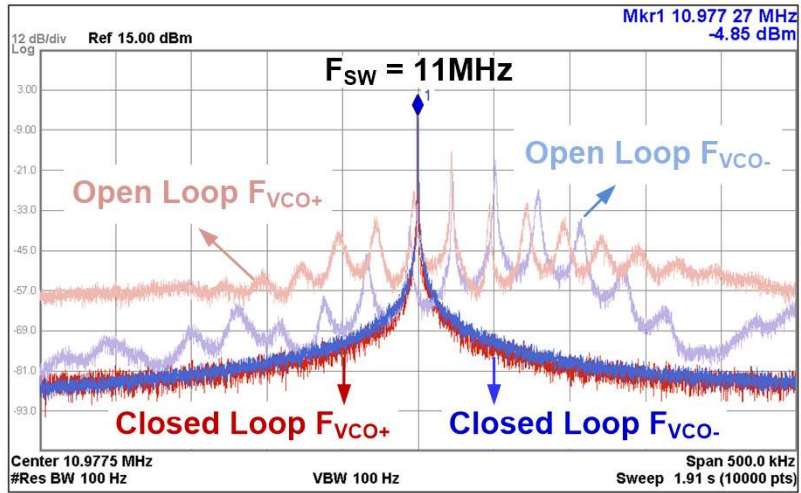

Efficiency vs. Output Current

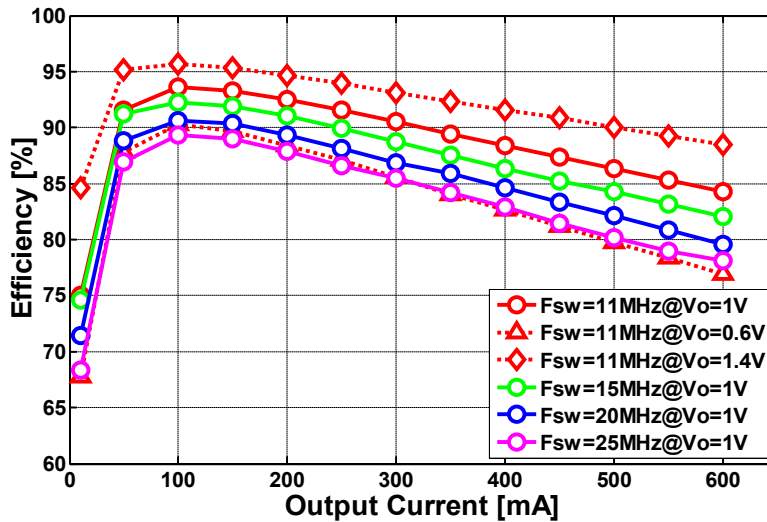


Performance Summary

| Publication | ISSCC 2014 | This Work |
|--------------------|------------------------------|------------------------|
| Control Loop | Voltage mode PID | Time based PID |
| Process | 0.13 μ m CMOS | 0.18 μ m CMOS |
| Supply Voltage | 3.3V | 1.8V |
| Output Voltage | 0.37V – 2.85V | 0.6V – 1.5V |
| F _{sw} | 10MHz(30MHz) | 11-15MHz |
| L / C | 330nH/3.3 μ F(1 μ F) | 220nH/4.7 μ F |
| Max. Load Current | 1.5A@V _o =2.4V | 600mA |
| Settling Time | n/a | 3.5 μ s |
| Output Ripple | n/a | 3.5mV |
| Controller Current | n/a | 23 μ A@11MHz |
| Peak Efficiency | 91.8%(86.6%) | 94%@V _o =1V |
| Active Area | n/a | 0.24mm ² |




Application in Multi-Phase

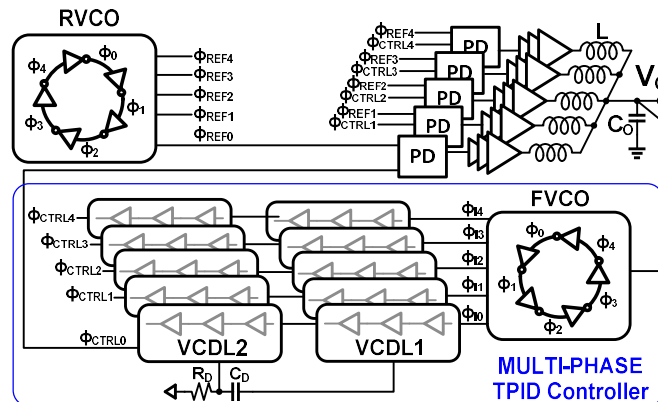- Since VCOs come inherently with multiple phases, different phases from VCOs can be tapped
- All phases use common integrator (VCO) but separate VCDLs



30-70MHz 4-Phase Time-Based Buck

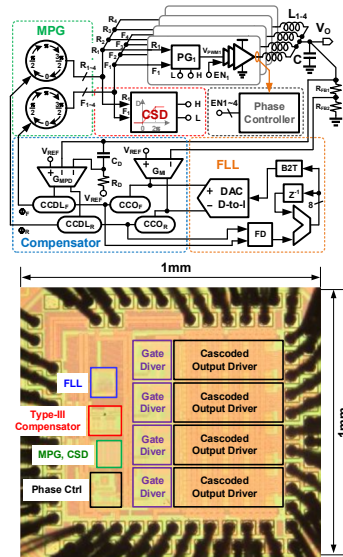

| | This Work | JSSC '05 Hazucha | JSSC '09 P. Li | VLSI' 14 Harish |
|------------------------------------|-----------------------|---------------------|-------------------------|-----------------------|
| Process | 65nm CMOS | 90nm CMOS | 0.5μm CMOS | 22nm CMOS |
| Control | T-PID PWM | Hysteretic | Hysteretic | Digital PWM |
| Synchronization | MPG | Injection | DLL | DPWM |
| Number of Phases | 4 | 4 | 4 | 4 |
| Input Supply [V] | 1.8 | 1.2/1.4 | 4-5 | 1.5 |
| Output Voltage [V] | 0.6-1.5 | 0.9/1.1 | 0.86-3.93 | 1 |
| F _{sw} [MHz] | 30-70 | 233 | 25-70 | 500 |
| Inductance [nH] | 90 | 2.5 | 110-220 | 1.5 |
| Capacitance [nF] | 470 | 6.8 | 8-190 | 10 |
| Load Current [A] | 0.8 | 0.3/0.4 | 1 | N/A |
| Controller Current | 90μA@30MHz | N/A | N/A | N/A |
| Peak Efficiency [%] | 87@V _o =1V | 83.2/84.5 | 83@V _o =3.3V | 68@V _o =1V |
| Power Density [W/mm ²] | 2.5 | 1.93/3.14 | 1.2 | N/A |

- A 1.8V 30-to-70MHz 87% Peak Efficiency 0.32mm² 4-Phase Time-Based Buck Converter Consuming 3uA/MHz Quiescent Current in 65nm CMOS, " *JSSCC-2015*.
- A 4-phase 30-70 MHz switching frequency buck converter using a time-based compensator," *IEEE JSSC, Dec. 2015*



EE5325 Power Management Integrated Circuits
Integrated Circuits and Systems Group, Department of EE, IIT Madras


33

Time-Based Low Drop-Out Regulator (LDO)



Low Drop-Out Regulator


- A conventional low drop-out regulator (LDO) suffers from trade-off between power and area.
- Pole, w_o , worsens the situation particularly under light-load condition due to high output resistance.
- Most of state-of-the art LDOs either consume high quiescent current, large on-chip capacitance or achieve limited bandwidth.
- Reduced bandwidth degrades power supply rejection (PSR) and transient response.

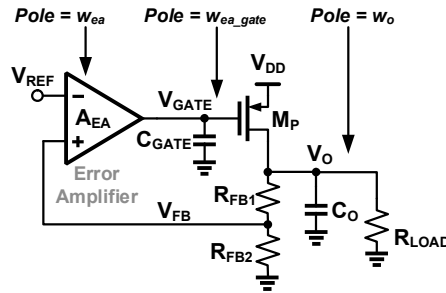

35

Time-Based Error Amplifier

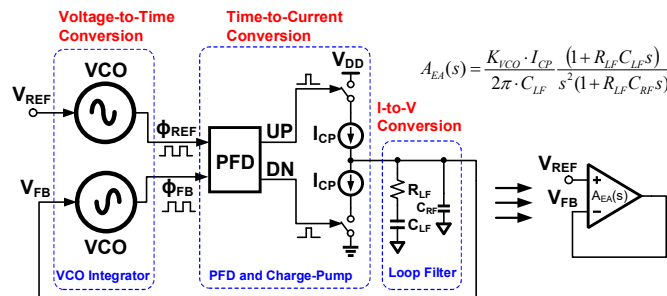- Concept of time-based error amplifier is derived from type-II phase locked loop (PLL).
- A voltage-controlled oscillator (VCO) is used for voltage-to-time/phase conversion which also acts as a phase integrator.
- Under lock condition, $F_{FB}=F_{REF} \rightarrow V_{FB}=V_{REF}$, assuming two VCOs are identical.




36

Time-Based LDO

- Concept of time-based error amplifier can be extended to LDO by adding a pass element, M_p to drive the output load R_L and C_L .
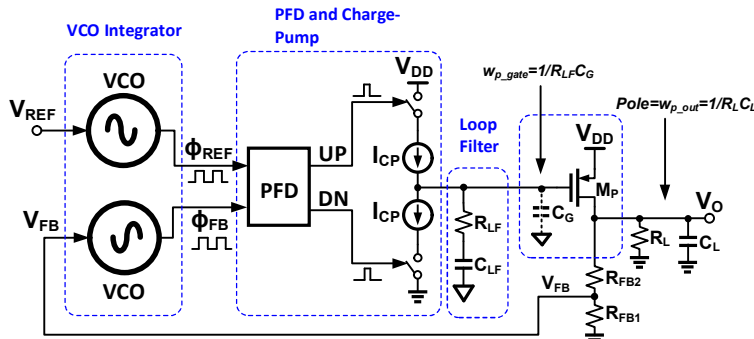
$$H_{LG}(s) = \frac{A_{PE} \cdot \beta \cdot K_{VCO} \cdot I_{CP}}{2\pi \cdot C_{LF}} \cdot \frac{(1 + w_{z_LF})}{s^2(1 + w_{p_gate})(1 + w_{p_out})}$$




37

Time-Based LDO with FF Compensation

- Feed-forward compensation cancels one of the poles (w_{p_gate} and w_{p_out}) and stabilizes the loop
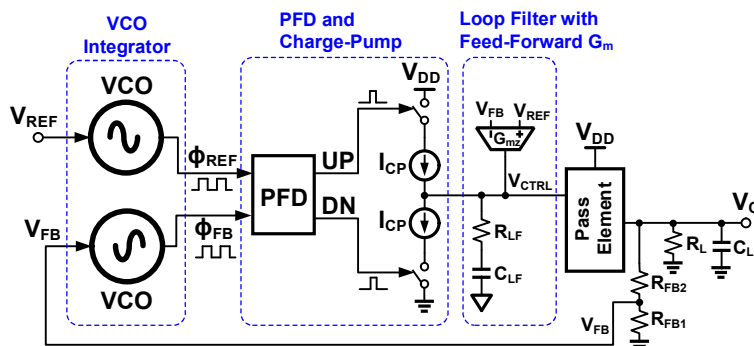
$$H_{LG}(s) = \frac{A_{PE} \cdot \beta \cdot K_{VCO} \cdot I_{CP}}{2\pi \cdot C_{LF}} \cdot \frac{(1 + w_{z_LF})(1 + w_{z_FF})}{s^2(1 + w_{p_out})} \quad w_{z_FF} = \frac{\beta \cdot K_{VCO} \cdot I_{CP}}{2\pi \cdot G_{mz}}$$




Area and Current Efficient Capacitor-Less Low Drop-Out Regulator Using Time-Based Error Amplifier, ISCAS-2018, Florence, Italy, May, 2018.



38

Multi-Phase Time-Based LDO

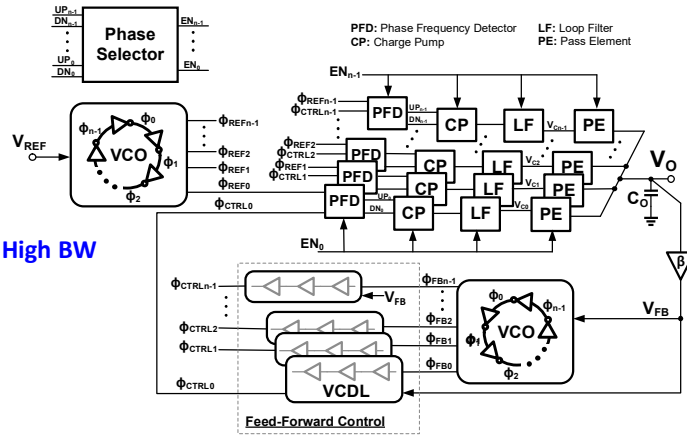- Auto-Reconfigurable → numbers of phases are turned on/off based on load currents
- Seamless transition between number of phases



- Low IQ and High BW




Issues with Time-Based Controller



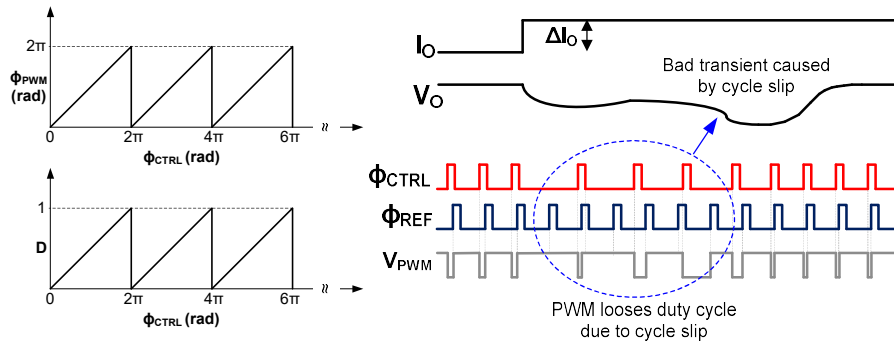
Problem-1: Cycle Slipping

- Since VCO phase folds back after every 2π , it causes duty cycle to reset and losing the duty cycle lock
- Duty cycle slipping may cause instability in the output before it acquires the phase lock again




Solution: How to Avoid Duty Cycle Slip

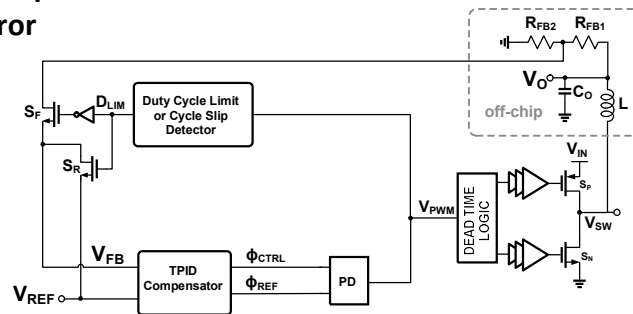- A cycle slip or min/max duty cycle detector can be used
- Once cycle slip is detected, error current to VCOs is made zero by applying V_{REF} to V_{FB}
- VCO phase will not accumulate further when there is no error



CSD Operation

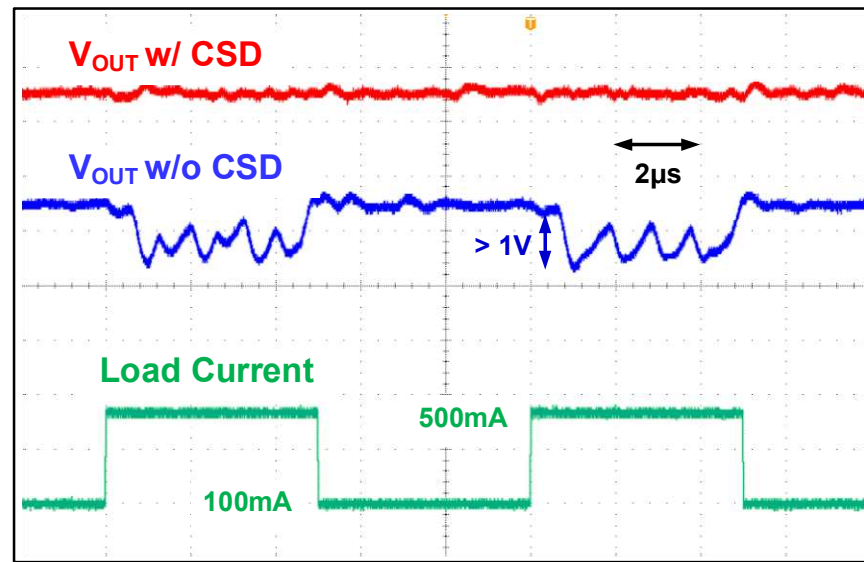

43

Problem-2: Offset Due to VCO Mismatch

- Since any error between frequencies of two VCOs is integrated in phase, mismatch in VCOs will cause offset in input voltage
- Considering 10MHz frequency and K_{VCO} of 1MHz/V, 1% mismatch in VCO will introduce 100KHz offset in frequency
- Assuming offset frequency due to mismatch is Δf_{VCO} , absolute input referred offset voltage can be represented as:

$$V_{OS} = \frac{\Delta f_{VCO}}{K_{VCO}}$$


- 1% between VCOs causes 100mV offset which is 16.67% for $V_{REF}=600mV$.




44

Solution: Offset Cancellation

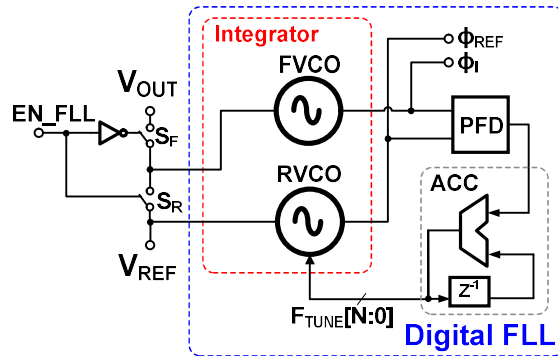- Mismatch between VCOs can be corrected by locking two VCOs to same frequency during startup
- Digital FLL is used for frequency locking
- Any offset in Gm also gets corrected during the calibration



Oscillator Frequency Spectra

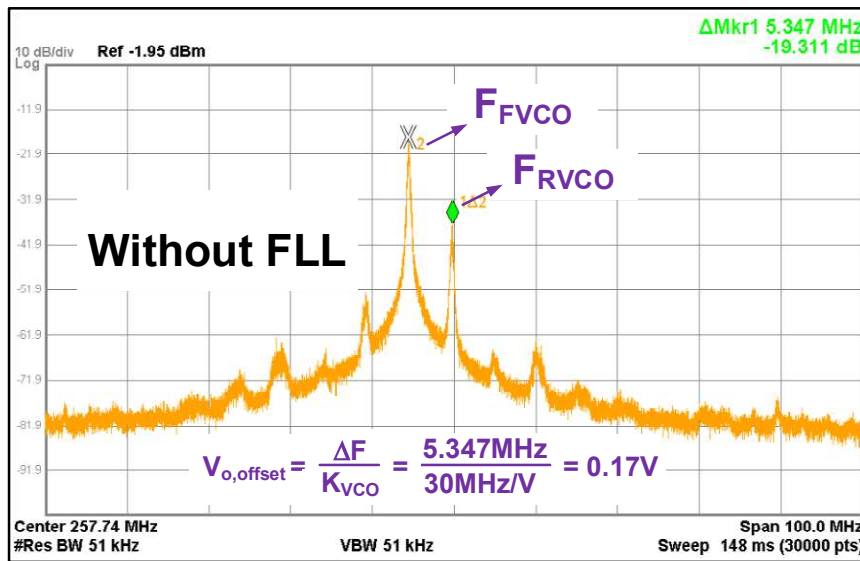

Oscillator Frequency Spectra

