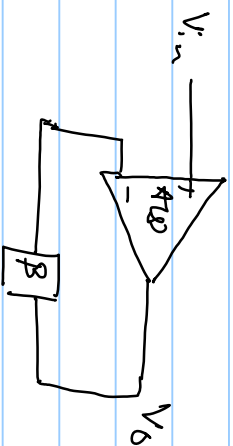


Second order system



$$A(s) = \frac{A_0}{(1 + s/\omega_{p1})(1 + s/\omega_{p2})}$$

$$\frac{V_o}{V_{in}} = \frac{A(s)}{1 + A(s)B} = \frac{A_0 (1 + s/\omega_{p1})(1 + s/\omega_{p2})}{1 + \frac{A_0 B}{(1 + s/\omega_{p1})(1 + s/\omega_{p2})}}$$

$$= \frac{A_0}{(1 + s/\omega_{p1})(1 + s/\omega_{p2}) + A_0 B}$$

$$= \frac{A_0}{(1+\delta/w_1)(1+\delta/w_2) + A_0\beta}$$

$$= \frac{A_0}{1 + \frac{\delta}{w_1} + \frac{\delta}{w_2} + \frac{\delta^2}{w_1 w_2} + A_0\beta}$$

$$= \frac{A_0}{\frac{\delta^2}{w_1 w_2} + \left(\frac{1}{w_1} + \frac{1}{w_2}\right) \delta + (1 + A_0\beta)}$$

$$= \frac{A_0 w_1 w_2}{\delta^2 + (w_1 + w_2) \delta + (1 + A_0\beta) w_1 w_2}$$

$$= \frac{A_0}{1 + A_0\beta} \frac{w_1 w_2}{\delta^2 + (w_1 + w_2) \delta + (1 + A_0\beta) w_1 w_2}$$

$$= \frac{A_0}{1 + A_0\beta} \frac{(1 + A_0\beta) w_1 w_2}{\delta^2 + (w_1 + w_2) \delta + (1 + A_0\beta) w_1 w_2}$$

$$\frac{V_n}{V_n} = K \frac{\omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

$$K = \frac{A_0}{1 + A_0\beta}$$

$$\omega_n^2 = (1 + A_0\beta)\omega_{p1}\omega_{p2} \Rightarrow \omega_n = \sqrt{(1 + A_0\beta)\omega_{p1}\omega_{p2}}$$

$$2\zeta\omega_n = \omega_{p1} + \omega_{p2}$$

$$\zeta = \frac{\omega_{p1} + \omega_{p2}}{2\sqrt{(1 + A_0\beta)\omega_{p1}\omega_{p2}}} = \frac{1}{2\sqrt{1 + A_0\beta}} \sqrt{\frac{\omega_{p1}^2 + \omega_{p2}^2 + 2\omega_{p1}\omega_{p2}}{\omega_{p1}\omega_{p2}}}$$

$$= \frac{1}{2\sqrt{1 + A_0\beta}} \sqrt{\frac{\omega_{p1}}{\omega_{p2}} + \frac{\omega_{p2}}{\omega_{p1}} + 2}$$

Case-1 $\omega_{p1} = \omega_{p2}$

$$\zeta = \frac{1}{2\sqrt{1+A_0\beta}} \quad \cancel{2} = \frac{1}{\sqrt{1+A_0\beta}}$$

$$A_0\beta \gg 1$$

$\zeta \rightarrow 0$ untere Seite.

Case-2 $\omega_{p1} \ll \omega_{p2}$

$$= \frac{1}{2\sqrt{1+A_0\beta}} \sqrt{\frac{\omega_{p1}}{\omega_{p2}} + \frac{\omega_{p2}}{\omega_{p1}} + 2}$$

$$= \frac{1}{2\sqrt{1+A_0\beta}} \sqrt{\frac{\omega_{p2}}{\omega_{p1}}}$$

Assume $\omega_{p2} = \omega_{p1} = (1+A_0\beta)\omega_{p1}$

$$\xi = \frac{1}{2 \sqrt{1+\rho^2}} \sqrt{1+\rho^2} = \frac{1}{2}$$

$$\xi = 0.5$$

Case-3 for $PM = 60^\circ$

$$PM = 180^\circ - 90^\circ - \tan^{-1} \frac{\omega}{\omega/2}$$

$$\tan^{-1} \frac{\omega}{\omega/2} = 90^\circ$$


$$\frac{\omega/2}{\omega/2} = \tan 90^\circ = \frac{1}{\sqrt{3}}$$

$$\omega/2 = \sqrt{3} \omega/2$$


$$\omega/2 = \frac{\omega/2}{1+\rho^2} \Rightarrow \xi = \frac{1}{2 \sqrt{1+\rho^2}} \sqrt{3(1+\rho^2)}$$

$$\xi = 0.65$$

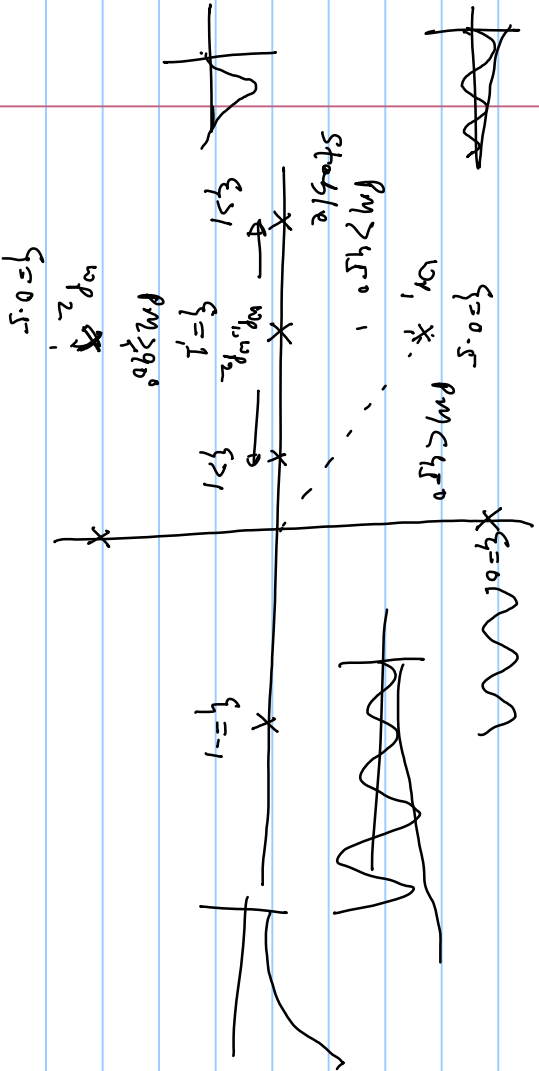Phase Margin $\approx 90^\circ - 180^\circ \zeta$




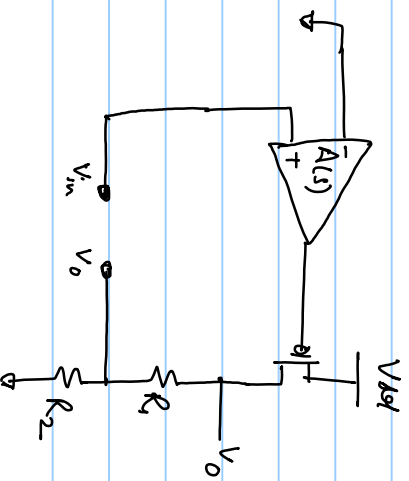
Stabilizing a system
compensation techniques.




How to Analyse the stability (Loop gain analysis)

Step-1 Break the loop.


Step-2 Find poles (and zeroes)

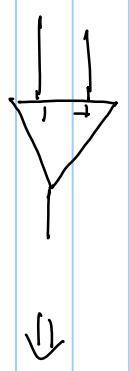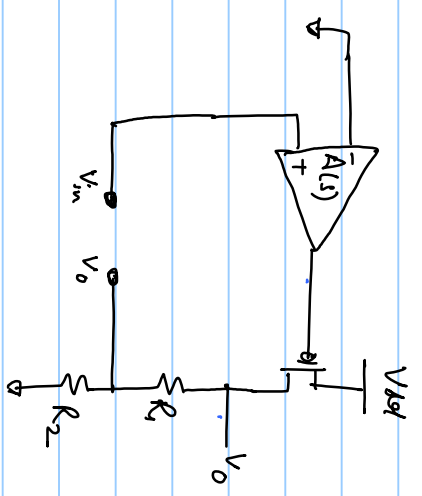


\Rightarrow

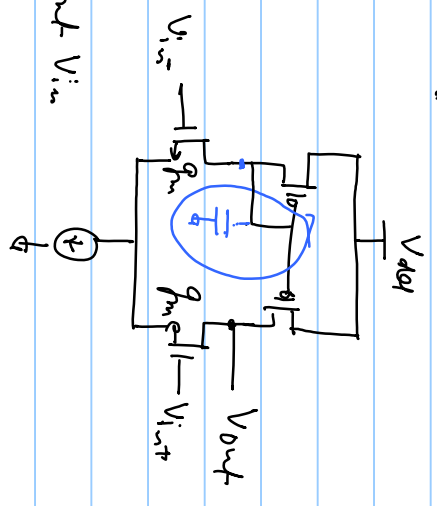


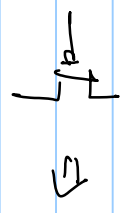$V_{out} = A V_{in} = g_m R_{out} V_{in}$




\Rightarrow

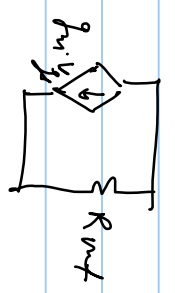

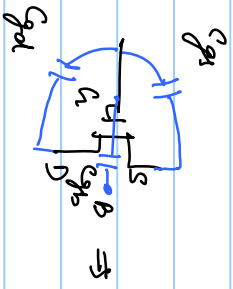

$$C = \frac{\epsilon A}{t}$$

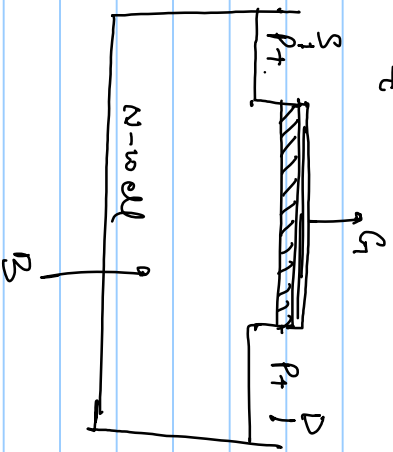

C_{gs} is the dominant capacitor.

Since gate is the common terminal to all the three capacitors, we get maximum capacitance at gate.