 


## Assignment-2: EE5325 - Power Management Integrated Circuits

### Excercise-1

For a sub-1V bandgap voltage reference shown in Figure-1:



**Figure-1**

- a) Assume  $m=10$ ,  $I_{E\_Q1}=I_{E\_Q2}=5\mu A$  at room temperature and identical PMOS transistors, calculate the values of  $R_1$ ,  $R_{2a}$ ,  $R_{2b}$  and  $R_3$  for  $V_{BG}=600mV$ .
- b) Analyze the effect of mismatch between  $M_{P1}$ ,  $M_{P2}$  and  $M_{P3}$ .
- c) Analyze the effect of mismatch between  $R_{2a}$  and  $R_{2b}$ .
- d) Analyze the effect of op-amp offset voltage and compare for  $m=5$  and  $m=10$ .

### Excercise-2

Consider the transfer function a standard 2<sup>nd</sup> order system:

$$H(s) = \frac{\omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

Considering  $\omega_n = 100 \text{ krad/sec}$ , fill the values of poles,  $w_{p1}$  and  $w_{p2}$  in following table for the corresponding values of  $\zeta$ .

$\zeta$	$Q=1/2\zeta$	$w_{p1}$ (rad/s)	$w_{p2}$ (rad/s)
10			
1			
0.7			
0.5			
0.2			
0.1			

## Assignment-2: EE5325 - Power Management Integrated Circuits

### Exercise-3

For the non-inverting amplifier shown in Figure-A and considering the op-amp model shown in Figure-B where  $A(s)=V_o(s)/V_i(s)$

 


Figure-A

 


Figure-B

- Find the loop gain transfer function,  $LG(s)$ , DC gain  $A_o$ , poles  $p_{1\_lg}$ ,  $p_{2\_lg}$  (roots of  $s$ ) and their respective frequencies,  $w_{p1\_lg}$  and  $w_{p2\_lg}$  in terms of  $g_{m1}$ ,  $R_{O1}$ ,  $C_{O1}$ ,  $g_{m2}$ ,  $R_{O2}$  and  $C_{O2}$ .
- Find the closed loop transfer function,  $H(s)=V_{out}(s)/V_{in}(s)$ , poles  $p_{1\_cl}$ ,  $p_{2\_cl}$  (roots of  $s$ ) and their respective frequencies,  $w_{p1\_cl}$  and  $w_{p2\_cl}$  in terms of  $g_{m1}$ ,  $R_{O1}$ ,  $C_{O1}$ ,  $g_{m2}$ ,  $R_{O2}$  and  $C_{O2}$ .
- Prove that, the circuit in Figure-A behaves same as the 2<sup>nd</sup> order transfer function in exercise-2 for feedback factor,  $\beta=1$  (i.e.  $R_1=0$  or  $R_2=\infty$ ) and find the expressions for damping factor ( $\zeta$ ), quality factor ( $Q$ ), natural frequency ( $w_n$ ) in terms of loop gain pole frequencies,  $w_{p1\_lg}$  and  $w_{p2\_lg}$  and DC gain,  $A_o$ .
- Considering  $g_{m1}=g_{m2}=0.1\text{mA/V}$  and  $R_{O1}=R_{O2}=1\text{M}\Omega$ , fill the values in following table for the corresponding values of  $C_{O1}$  and  $C_{O2}$

$C_{O1}$ (F)	$C_{O2}$ (F)	Loop Gain				Closed Loop			
		$w_{p1\_lg}$ (rad/s)	$w_{p2\_lg}$ (rad/s)	$w_{ugf}$ (rad/s)	PM (deg.)	$\zeta$	$Q=1/2 \zeta$	$w_{p1\_cl}$ (rad/s)	$w_{p2\_cl}$ (rad/s)
1e-9	1e-9								
10e-9	1e-10								
4e-8	2.5e-11								
1e-7	1e-11								
1.41e-7	7.07e-12								
2e-7	5e-12								
5e-7	2e-12								
1e-6	1e-12								
2e-6	5e-13								
1e-5	1e-13								

## Assignment-2: EE5325 - Power Management Integrated Circuits

- e) Analyze the effect of increasing the frequency spacing between loop gain poles,  $\omega_{p1\_lg}$  and  $\omega_{p2\_lg}$  on damping factor.
- f) Plot phase margin (PM) vs.  $\zeta$  and find the range of  $\zeta$  for which phase margin can be calculated as 90-100 times of  $\zeta$ .
- g) Enter the circuit in LTSpice and perform following simulations for all the values of  $\omega_{p1\_lg}$ ,  $\omega_{p2\_lg}$ :
  - i. Plot the bode magnitude phase and phase response of the loop gain transfer function for all values of  $\omega_{p1\_lg}$ ,  $\omega_{p2\_lg}$  and corresponding AC magnitude and phase response of the closed loop transfer function. Comment on effect of increasing and decreasing phase margin on the closed loop AC magnitude and phase response.
  - ii. Plot the step response of the closed loop circuit by applying a unit step (0 to 1V with initial delay of 10us and Trise = 1ns) for the time span of 10ms. Comment on the effect of increasing and decreasing phase margin as well as  $\zeta$ . Find the phase margin and corresponding value of  $\zeta$  for the fastest settling (when output settles within 95% of the final value).
- h) Change the value of feedback factor,  $\beta=1/10$  (i.e.  $R_1=10R_2$ ) and comment about the effect on phase margin, damping factor and unity gain frequency ( $\omega_{ugt}$ )