


Special Manpower Development Program in VLSI  
IEP : RF Integrated Circuits

Shanthi Pavan

Department of Electrical Engineering  
Indian Institute of Technology, Madras  
shanthi@ee.iitm.ac.in
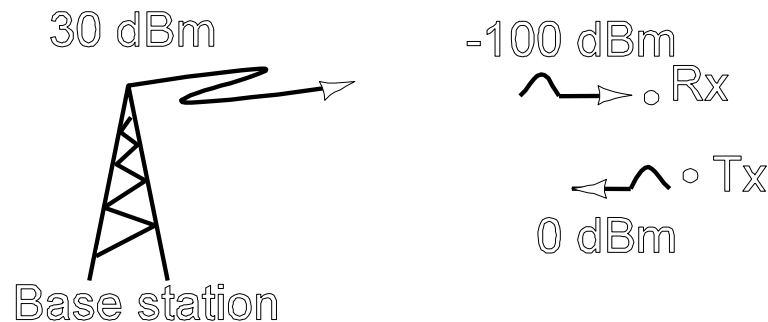
# Introduction to RFICs

- RF problem –
  - Received signal is *very small*, in presence of interferers



- Power measured in '**dBm**'


dB → log scale, since the range of power involved is huge.  
m → relative to 1 mW

$$\text{Power in dBm} = 10 \log_{10} \left( \frac{P}{1 \text{ mW}} \right)$$


0 dBm = 1 mW; -100 dBm = 0.1 pW !!!!

IEP : RF Integrated Circuits  
shanthi@ee.iitm.ac.in

# Simple RF receiver

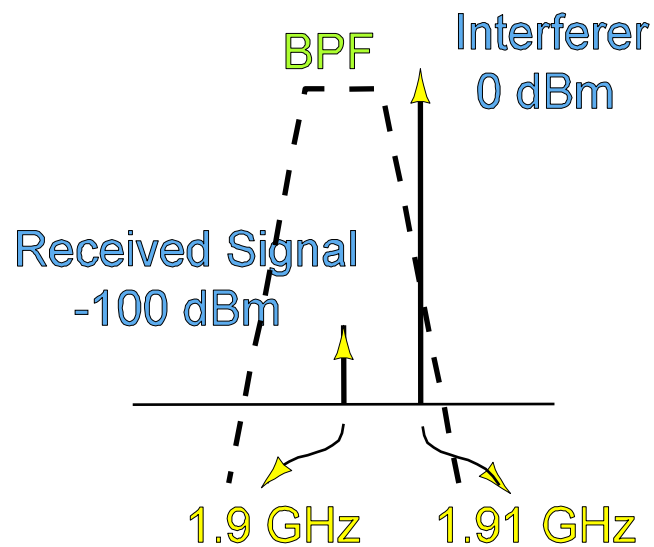

Use a filter to knock off the interferer

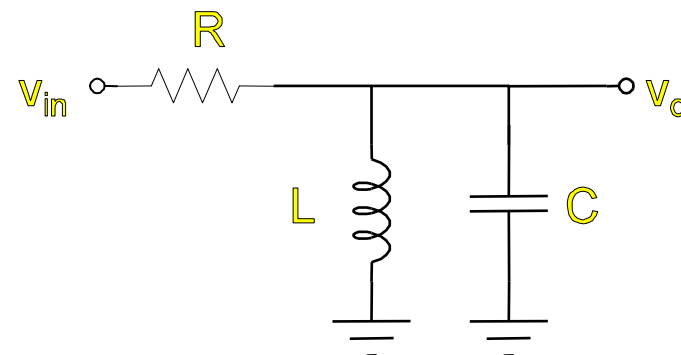


$$\omega_o = \frac{1}{\sqrt{LC}} ; \quad Q = \frac{R}{\sqrt{L/C}}$$

- What will be the Q required to reject the interferer ?

The Q required to get 3 dB rejection at 1.91 GHz  
(10 MHz from 1.9 GHz)


$$= f_0/BW = 1.9 \text{ GHz} / 20 \text{ MHz} = 85$$

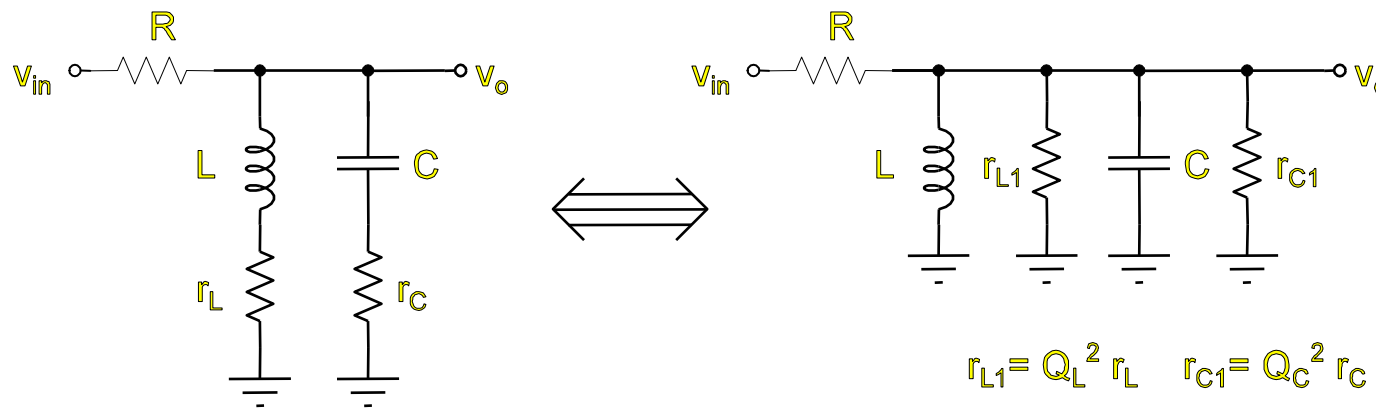- The Q of the filter is limited by the Q of passive components



$$\frac{1}{Q_{eq}} = \frac{1}{R} + \frac{1}{Q_L} + \frac{1}{Q_C}$$

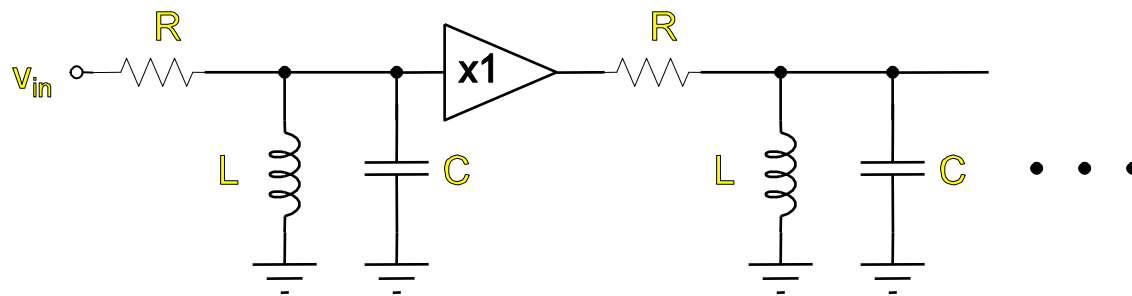- Very High Q passive components are impossible to realize !
- Cascading the filters, another way to realize sharp filters




### Limitations:

- Precise matching of L, C are required
  - Else, results in broad bandwidth
- Shift in all L's or C's  $\Rightarrow$  picking up interferer but not the desired signal
- High gain (of the order of  $10^5$ ) is impractical at RF.
  - Parasitic coupling between i/p and o/p of the amplifier leads to stability problem

- Therefore the gain is distributed at several frequencies.
  - breaks the loop due to parasitic coupling

Example :

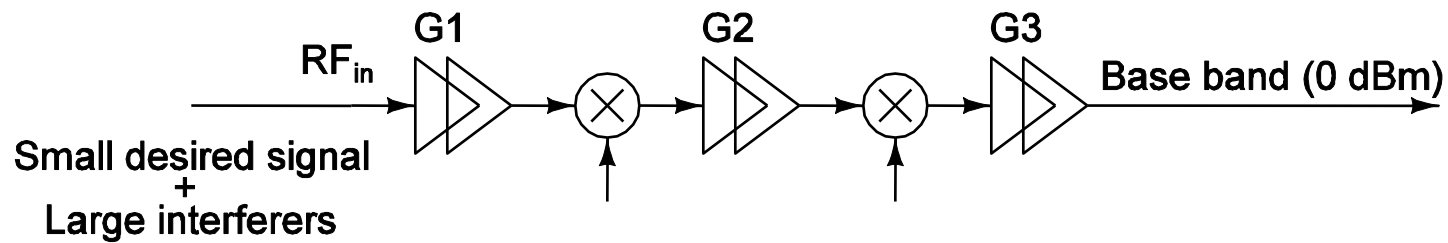


# Issues in RF Receivers

## 1. Noise

- Frequency translation and amplification needs devices (both active and passive)
- These devices add noise
- Even with zero input signal, output has noise (due to internal noise sources)

Consider the model of an antenna,

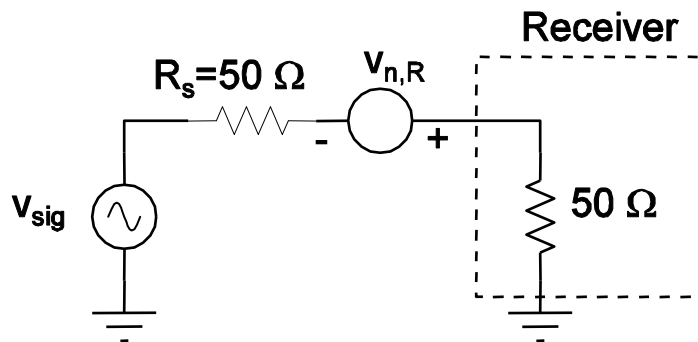

$V_{sig}$  : signal received by the antenna,

$R_s$  : Impedance of the antenna

$V_{n,R}$  : Equivalent voltage noise of the antenna

Signal power at the input of the receiver =  $\frac{\overline{V_{\text{sig}}^2}}{4 R_S}$  watts

Avg. noise power dissipated at the input of the receiver =  $\frac{\overline{V_{n,R}^2}}{4 R_S} = \frac{(4KTR_S)B}{4R_S}$  watts

$4KTR_S$  : Voltage noise power spectral density of  $R_S$

$B$  : Band width

Noise power at the input (in dBm) =  $10 \log (4KTR_S) + 10 \log (B)$   
=  $-174 \text{ dBm/Hz} + 10 \log (B)$

For a channel with bandwidth of 200 kHz, the noise power = -121 dBm

If the received signal power = -100 dBm, then

the SNR @ input = 21 dBm

=> Receiver output SNR cannot be greater than 21 dBm (for this case)



➤ ***Sensitivity*** :

Minimum i/p signal power required for a specified SNR @ o/p.

$$\text{Sensitivity} > \text{SNR}_{\text{out}} \text{ (in dB)} + 10 \log (B) - 174 \text{ dBm}$$

➤ ***Noise factor*** :


$$\text{Noise Factor} = \frac{\text{SNR @ i/p}}{\text{SNR @ o/p}}$$

$$\text{Noise Figure (NF)} = 10 \log (\text{Noise Factor})$$

- Noise factor is the measure of SNR degradation when the signal passes through the system.
- For a noise less receiver, SNR @ i/p = SNR @ o/p  
i.e. Noise factor = 1
- For a noisy receiver Noise factor > 1

## 2. Large signal issues

- Amplifiers are non-linear in reality.

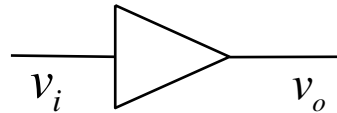


$$v_o = a_0 + a_1 v_i + a_2 v_i^2 + a_3 v_i^3 + \dots$$

$$(A \cos \omega_1 t + A \cos \omega_2 t)$$

$$\begin{aligned} v_o = & (a_0 + a_2 A^2) + (a_1 A + \frac{9}{4} a_3 A^3)(\cos \omega_1 t + \cos \omega_2 t) \\ & + \frac{a_2 A^2}{2} (\cos 2\omega_1 t + \cos 2\omega_2 t) + \frac{a_3 A^3}{4} (\cos 3\omega_1 t + \cos 3\omega_2 t) \\ & + a_2 A^2 [\cos(\omega_1 - \omega_2)t + \cos(\omega_1 + \omega_2)t] \\ & + \frac{3}{4} a_3 A^3 [\cos(2\omega_1 - \omega_2)t + \cos(2\omega_2 - \omega_1)t] \\ & + \frac{3}{4} a_3 A^3 [\cos(2\omega_1 + \omega_2)t + \cos(2\omega_2 + \omega_1)t] \end{aligned}$$

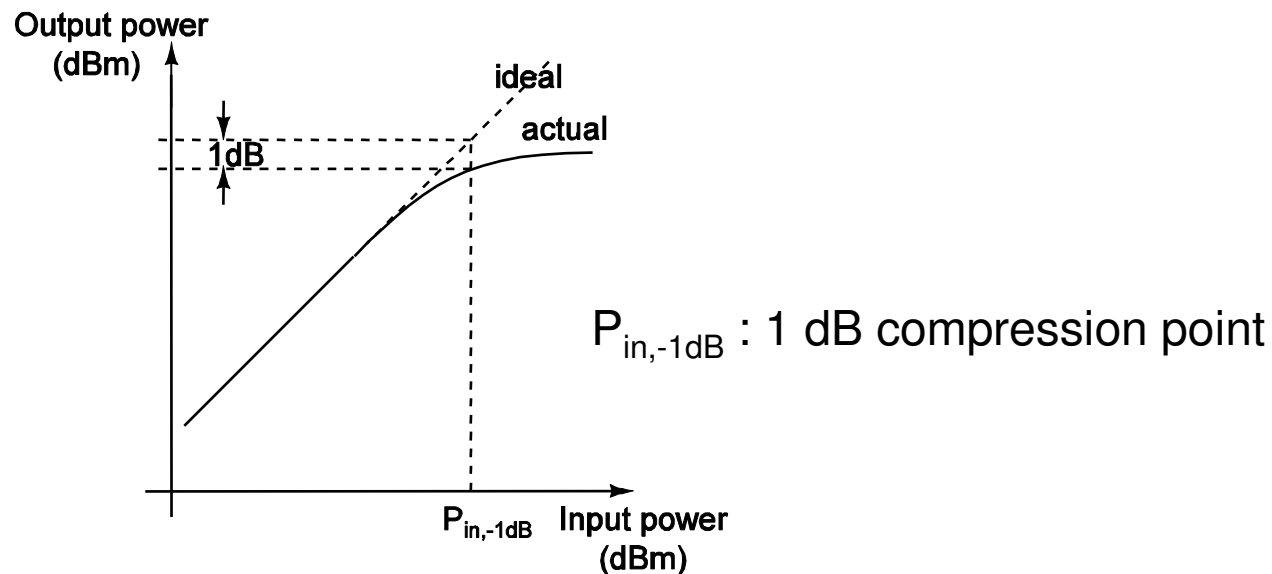
- Amplitude of the fundamental component at the output of the amplifier is,  $(a_1A + \frac{9}{4}a_3A^3)$
- Typically  $a_3$  is negative
- Therefore, amplitude of the fundamental at the output decreases with the increasing input signal strength


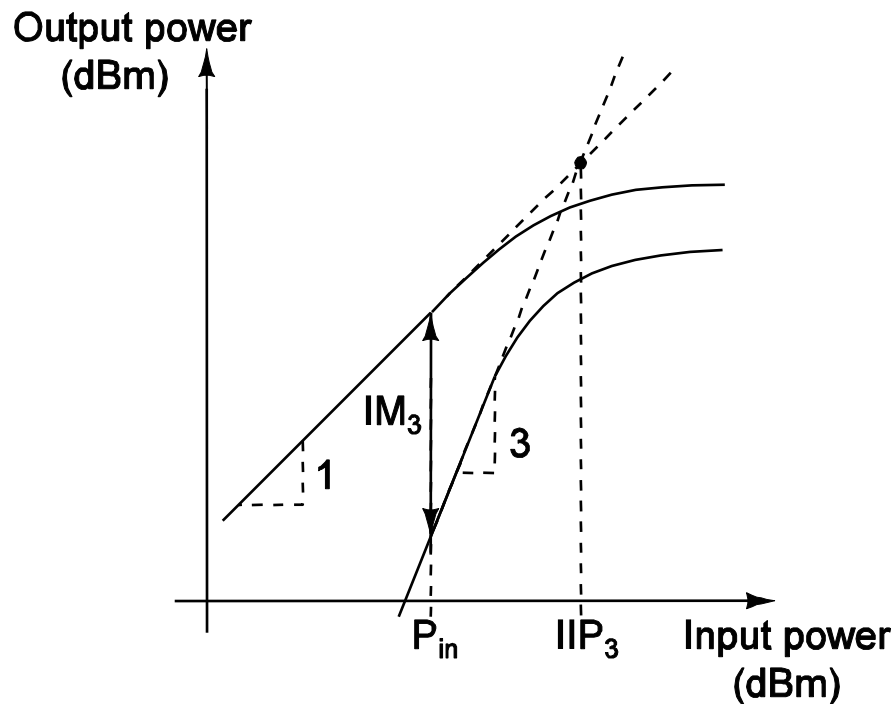
## Intermodulation

- Output components of frequency  $(2\omega_1 - \omega_2)$  and  $(2\omega_2 - \omega_1)$  are third order intermodulation terms.

- Third order intermodulation = 
$$IM_3 = \frac{\frac{3}{4} a_3 A^3}{a_1 A} = \frac{3 a_3 A^2}{4 a_1}$$



$IIP_3$  : Third order Input Intercept Point

$$(IIP_3 - P_{in}) \cdot 3 = IM_3 + (IIP_3 - P_{in})$$


$$IIP_3 = P_{in} + IM_3/2$$

(all quantities in dB)
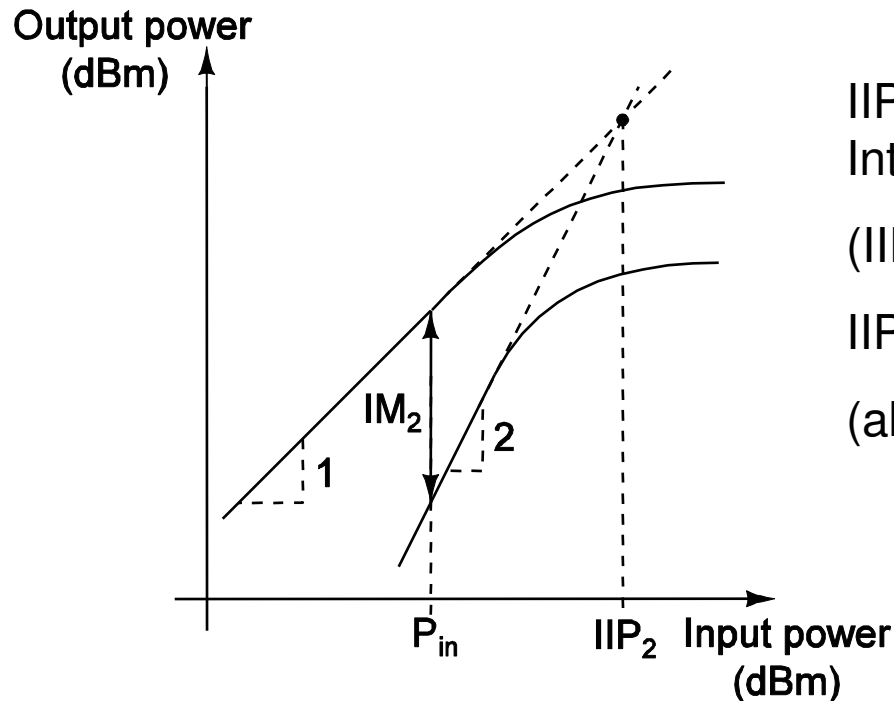
## Intermodulation

- Output components of frequency  $(\omega_1 - \omega_2)$  and  $(\omega_1 + \omega_2)$  are second order intermodulation terms.

- Second order intermodulation =  $IM_2 = \frac{a_2 A^2}{a_1 A} = \frac{a_2 A}{a_1}$



$IIP_2$  : Second order Input Intercept Point


$$(IIP_3 - P_{in}) \cdot 3 = IM_3 + (IIP_3 - P_{in})$$

$$IIP_3 = P_{in} + IM_3/2$$

(all quantities in dB)

# Problems with large signals:

## *Intermodulation-*

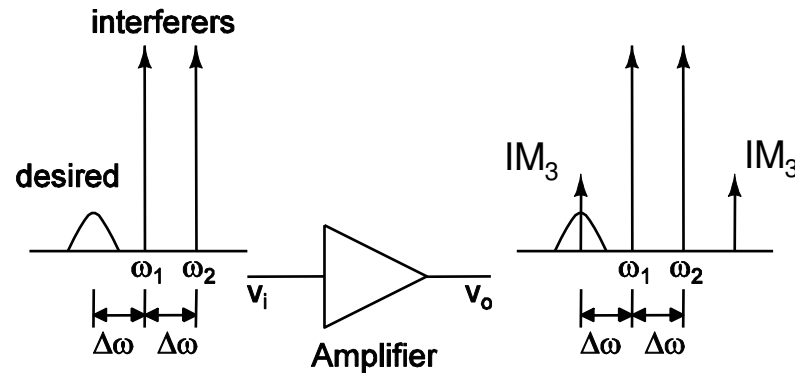


## *Blocking-*

Amplitude of o/p fundamental

$$= (a_1 A + \frac{3}{2} a_3 A B^2)$$

Gain for the fundamental

$$= (a_1 + \frac{3}{2} a_3 B^2)$$

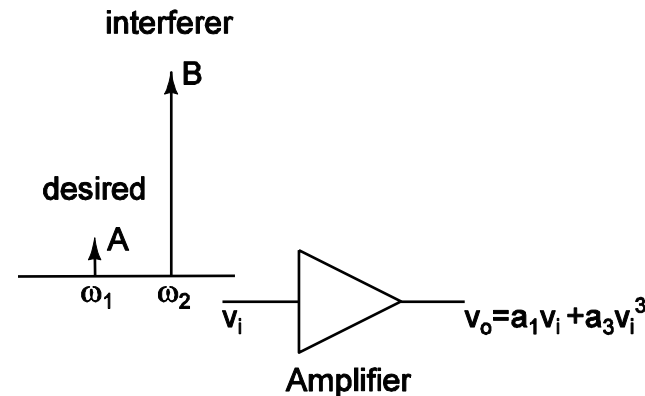

- Gain of desired channel reduced in the presence of large interferer ( $a_3$  is typically negative)
- If the interferer is modulated, 'B' changes with time => *Cross Modulation*

# Distortion in cascaded amplifiers

Let the non-linearity of the amplifiers  $A_1$  and  $A_2$  be given as

$$v_{o1} = a_1 v_i + a_3 v_i^3 ; v_o = b_1 v_{o1} + b_3 v_{o1}^3$$

$$\Rightarrow v_o \approx (a_1 b_1) v_i + (b_1 a_3 + b_3 a_1^3) v_i^3$$

For the amplifier  $A_1$ ,

$$A_{IIP3,1} = \sqrt{\frac{4 a_1}{3 a_3}}$$

For the amplifier  $A_2$ ,



$$A_{IIP3,2} = \sqrt{\frac{4 b_1}{3 b_3}}$$

Then for the equivalent amplifier  $A_{cas}$ ,


$$A_{IIP3,cas} = \sqrt{\frac{4 b_1 a_1}{3 b_1 a_3 + b_3 a_1^3}}$$

Re-arranging the above equation, it can be shown that,
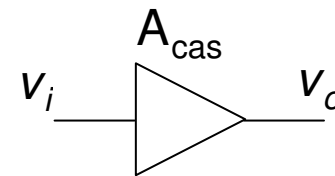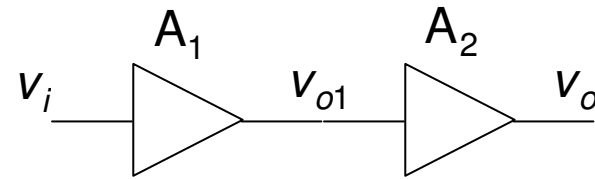
$$\frac{1}{A_{IIP3,cas}^2} = \frac{1}{A_{IIP3,1}^2} + \frac{a_1^2}{A_{IIP3,2}^2}$$




# Dynamic Range (DR)-

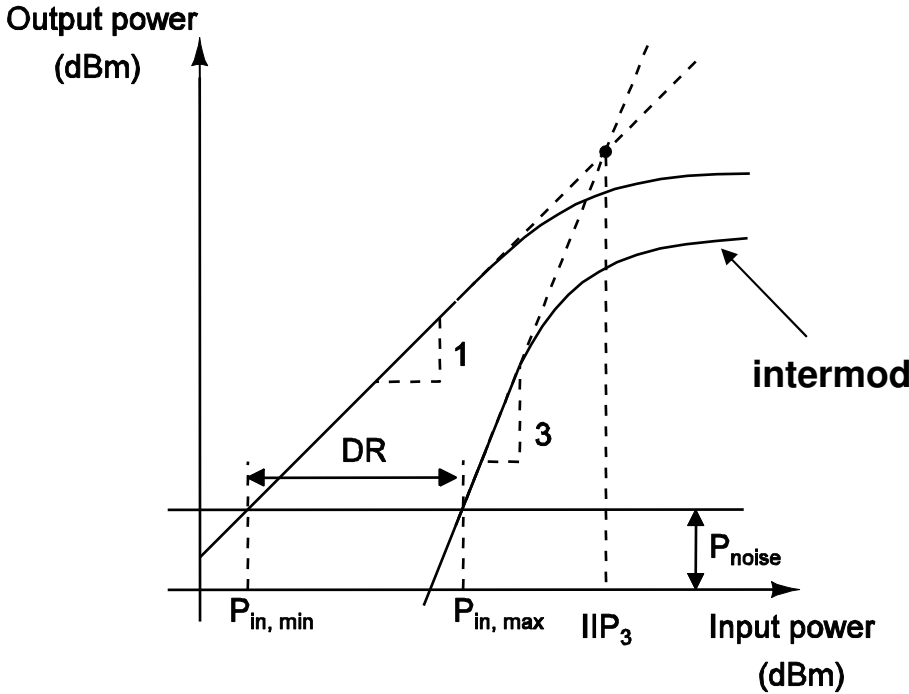



# Noise in Electronic Circuits

## 1. Resistor

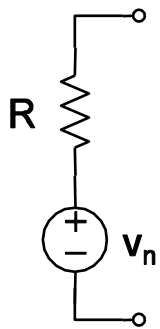



$v_n$  : Equivalent noise voltage of resistor R. It is assumed to be Gaussian white.

$\overline{v_n} = 0$  ;  $\overline{v_n^2} = 4KTR\Delta f$  assuming the resistor is in equilibrium with the surrounding

Noise power spectral density =  $S_v(f) = 4KTR \text{ V}^2/\text{Hz}$


## 2. L & C : No noise

## 3. MOSFET

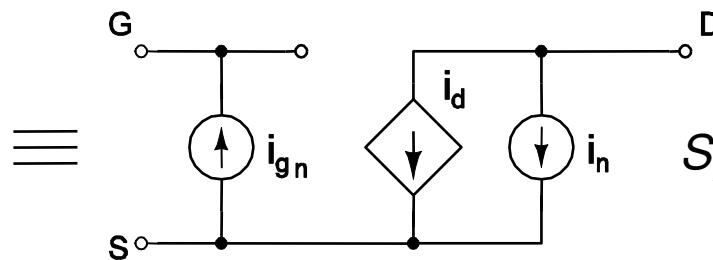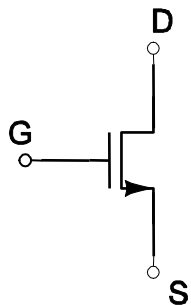


$$S_{i,n}(f) = \frac{8}{3}KT\eta g_m \text{ V}^2/\text{Hz}$$

## 4. Noise through a linear filter

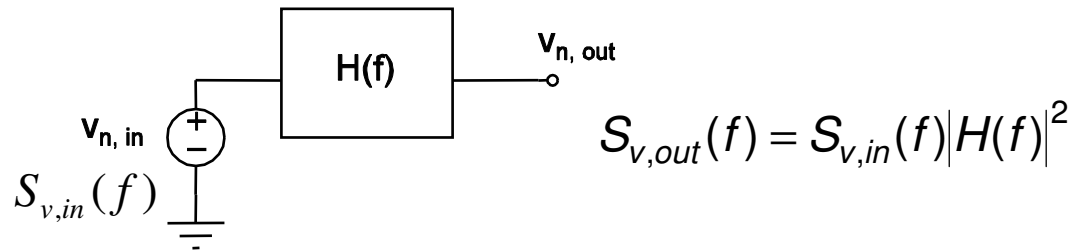

## 5. Noise in networks

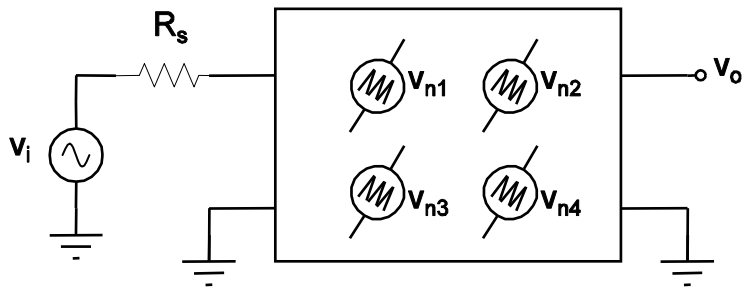

Output noise voltage =

$$v_{n,o} = v_{n1}H_1(f) + v_{n2}H_2(f) + v_{n3}H_3(f) + \dots$$

where,  $H_i(f)$  is the transfer function from  $i^{th}$  noise source to the output

Output noise power spectral density =

$$S_{v,o}(f) = S_{v,n1}(f) |H_1(f)|^2 + S_{v,n2}(f) |H_2(f)|^2 + S_{v,n3}(f) |H_3(f)|^2 + \dots$$

The transfer function  $H_i(f)$  can be written in terms of  $R_s$  as  $H_i(f) = \frac{A_i R_s + B_i}{C R_s + D}$

$$\therefore v_{n,o} = \sum_{k=1}^N v_{nk} \frac{A_k R_s + B_i}{C R_s + D}$$

If  $v_{n,in-eq}$  is the equivalent input referred noise, then  $v_{n,o} = v_{n,in-eq} \frac{A_{eq} R_s + B_{eq}}{C R_s + D}$


As  $R_s \rightarrow \infty, v_{n,o} \rightarrow 0$  and also  $v_{n,o} = v_{n,in-eq} \frac{A_{eq}}{C} \Rightarrow A_{eq} = 0$

$$\therefore v_{n,o} = v_{n,in-eq} \frac{B_{eq}}{C R_s + D} = \sum_{k=1}^N v_{nk} \frac{A_k R_s + B_i}{C R_s + D}$$

$$\Rightarrow v_{n,in-eq} = R_s \left( \sum_{k=1}^N v_{nk} \frac{A_k}{B_{eq}} \right) + \left( \sum_{k=1}^N v_{nk} \frac{B_k}{B_{eq}} \right)$$

$$v_{n,in-eq} = R_s I_n + V_n$$

# Noise factor of amplifier

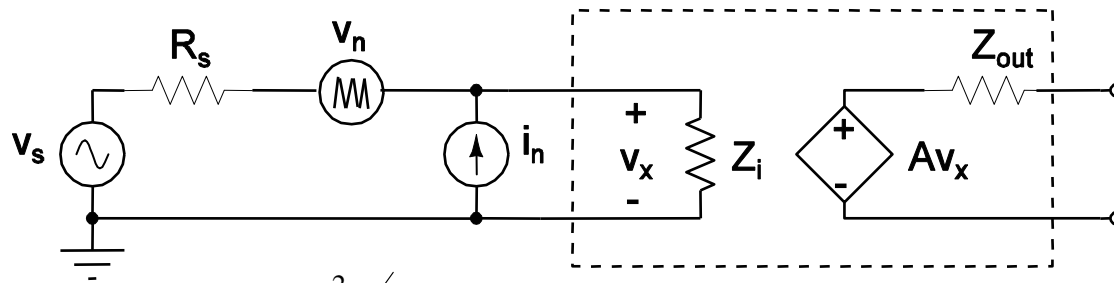

$$\text{Available SNR @ i/p} = \frac{\frac{v_s^2}{4R_s}}{4KTR_s} = \frac{v_s^2}{4KTR_s} \quad \text{taking 1 Hz bandwidth}$$

$$\text{Available signal power at the output} = v_s^2 \left| \frac{Z_i A}{Z_i + R_s} \right|^2 \frac{1}{4\Re[Z_{out}]}$$

$$\text{Available noise power at the output} = \left[ 4KTR_s + \overline{(v_n + i_n R_s)^2} \right] \left| \frac{Z_i A}{Z_i + R_s} \right|^2 \frac{1}{4\Re[Z_{out}]}$$


$$\text{Available SNR @ o/p} = \frac{v_s^2}{4KTR_s + \overline{(v_n + i_n R_s)^2}}$$

$$\text{Noise Factor} = \frac{\text{Available SNR @ i/p}}{\text{Available SNR @ o/p}} = 1 + \frac{\overline{(v_n + i_n R_s)^2}}{4KTR_s}$$

$$\overline{(v_n + i_n R_s)^2} = \overline{v_n^2} + R_s^2 \overline{i_n^2} + 2R_s \overline{v_n i_n}$$
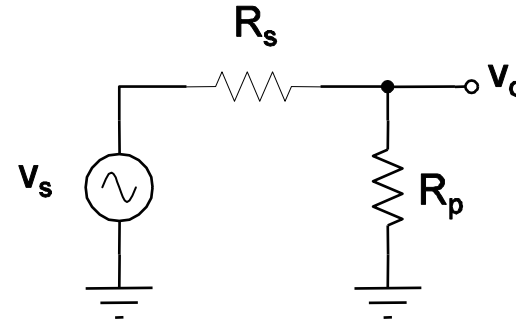
## Noise factor of a simple potential divider

Taking 1 Hz bandwidth,  
 Available SNR @ i/p =  $\frac{v_s^2 / 4R_s}{4KTR_s / 4R_s} = \frac{v_s^2}{4KTR_s}$




Available SNR @ o/p =  $\frac{v_s^2 \left( \frac{R_p}{R_p + R_s} \right)^2}{4KT \frac{R_s R_p}{R_p + R_s}} = \frac{v_s^2}{4KT} \frac{R_p}{R_p + R_s}$

Noise Factor =  $\frac{\text{Available SNR @ i/p}}{\text{Available SNR @ o/p}} = 1 + \frac{R_s}{R_p}$

For best noise figure,  $R_p = 0$  ; for Maximum power transfer,  $R_p = R_s$

# Noise factor of a CS amplifier

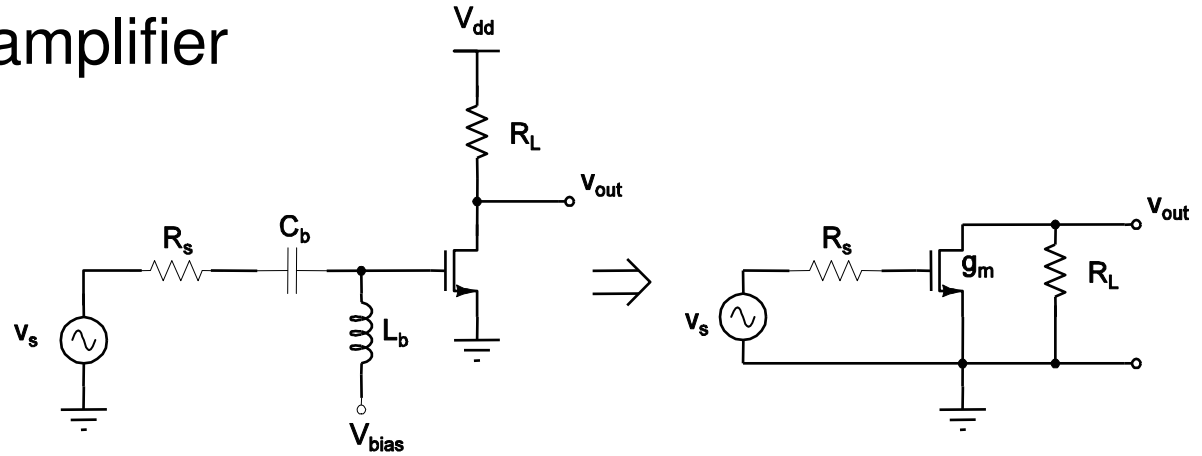

$$\text{Available SNR @ i/p} = \frac{V_s^2}{4KTR_s}$$


$$\text{Available signal power at the output} = \frac{v_s^2 (g_m R_L)^2}{4R_L}$$

$$\text{Available noise power at the output} = \left[ 4KTR_s (g_m R_L)^2 + \frac{8}{3} KT g_m R_L^2 + 4KTR_L \right] \frac{1}{4R_L}$$

$$\text{Available SNR @ o/p} = \frac{V_s^2}{4KTR_s + \frac{8}{3} \frac{KT}{g_m} + 4KT \frac{1}{g_m^2 R_L^2}}$$

$$\text{Noise Factor} = \frac{\text{Available SNR @ i/p}}{\text{Available SNR @ o/p}} = 1 + \frac{2}{3} \frac{1}{g_m R_s} + \frac{1}{g_m^2 R_s R_L}$$

# Noise factor of filters

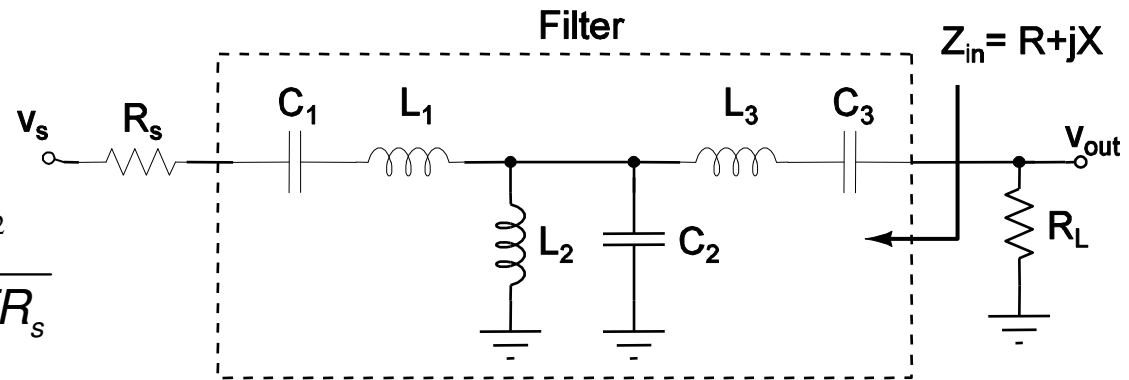

$$\text{Available SNR @ i/p} = \frac{v_s^2}{4KTR_s}$$

$$\text{Available SNR @ o/p} = \frac{v_{out,th}^2}{4KT\Re[Z_{in}]}$$

For a loss less filter, at  $f = f_c$ ,  $v_{out,th} = v_s$  and  $\Re[Z_{in}] = R_s$

$$\Rightarrow \text{Available SNR @ o/p} = \frac{v_s^2}{4KTR_s}$$

$\Rightarrow$  Noise factor = 1


For a lossy filter,

$$\text{Available SNR @ o/p} = \frac{v_s^2 G}{4KTR_s} \quad G: \text{the power gain of the filter}$$

Therefore, Noise factor =  $1/G = L$     L: Loss
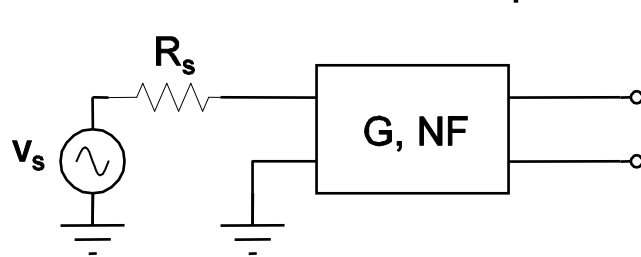
## Noise factor of cascaded amplifiers

- Consider an amplifier having power gain 'G' and noise factor 'NF'



$$NF = \frac{\frac{v_s^2}{4KTR_s}}{\frac{v_s^2 G}{4R_s}}$$


Available noise power @ o/p

∴ Available noise power @ o/p =  $NF KTG$

But,  $KTG$  = Available noise power @ o/p due to  $R_s$  alone

∴  $KTG (NF - 1)$  = Available noise power @ o/p due to the amplifier alone

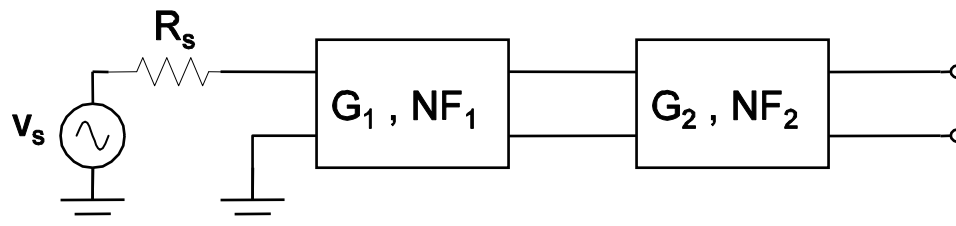- Now, consider two amplifiers connected in cascade





$$\text{Available signal power @ o/p} = \frac{\overline{v_s^2} G_1 G_2}{4R_s}$$

$$\text{Available noise power @ o/p} = KT(G_1 G_2) + [KTG_1(NF_1 - 1)] G_2 + KTG_2(NF_2 - 1)$$


$$\text{Available SNR @ i/p} = \frac{\overline{v_s^2}}{4KTR_s}$$

$$\text{Available SNR @ o/p} = \frac{\frac{\overline{v_s^2} G_1 G_2}{4KTR_s}}{KT(G_1 G_2) + [KTG_1(NF_1 - 1)] G_2 + KTG_2(NF_2 - 1)}$$

Therefore, the total Noise factor (NF) can be written as,

$$NF_{total} = NF_1 + \frac{(NF_2 - 1)}{G_1}$$

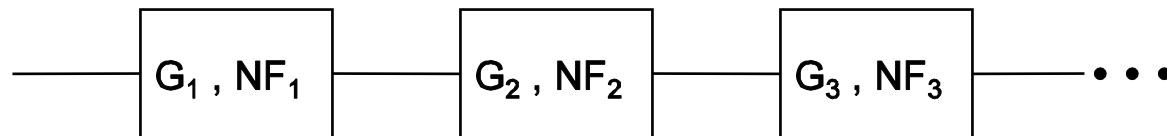
Generalizing the above result for any number of cascade,



$$NF_{total} = NF_1 + \frac{(NF_2 - 1)}{G_1} + \frac{(NF_3 - 1)}{G_1 G_2} + \dots$$

**Friis Formula**


## Example

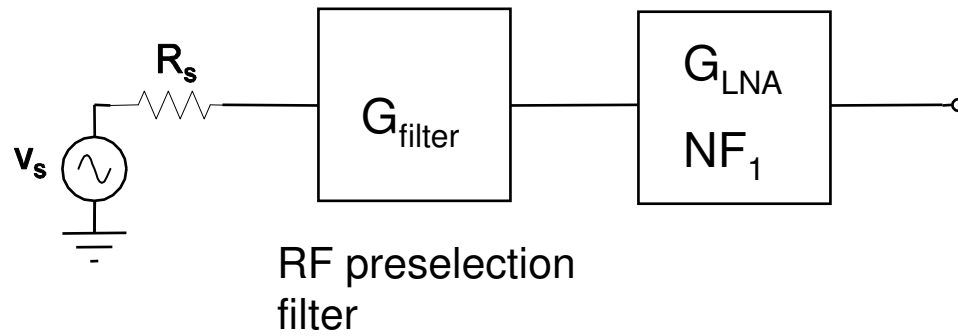

$$\begin{aligned} NF_{\text{total}} &= NF_{\text{filter}} + \frac{(NF_1 - 1)}{G_{\text{filter}}} \\ &= \frac{1}{G_{\text{filter}}} + \frac{(NF_1 - 1)}{G_{\text{filter}}} \\ &= \frac{NF_1}{G_{\text{filter}}} = NF_1 L_{\text{filter}} \end{aligned}$$

In 'dB' the Noise figure can be written as  $NF_{\text{total}}|_{\text{dB}} = NF_1|_{\text{dB}} + L_{\text{filter}}|_{\text{dB}}$

# Mixer and Mixer Noise

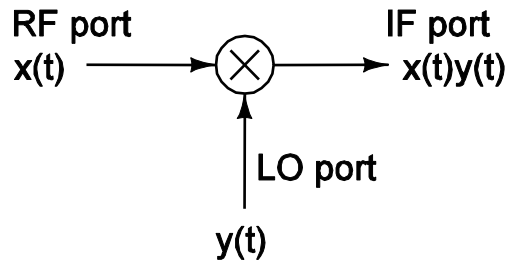

$$x(t) = A_{RF} \cos \omega_{RF} t,$$

$$y(t) = A_{LO} \cos \omega_{LO} t$$

$$x(t)y(t) = \frac{A_{RF}A_{LO}}{2} [\underbrace{\cos(\omega_{RF} - \omega_{LO}) t}_{\text{o/p of down conversion mixer}} - \underbrace{\cos(\omega_{RF} + \omega_{LO}) t}_{\text{Rejected by filter}}]$$

o/p of down  
conversion mixer

Rejected  
by filter

- In general,  $v_{IF}(t) = f(x(t)) g(y(t))$   
The functions 'f' and 'g' are non-linear


- Voltage gain of the mixer

$$= \frac{\text{signal amplitude @ IF port}}{\text{signal amplitude @ RF port}} = \text{Conversion gain}$$

- Available power gain

- Noise factor  $= \frac{\text{available power @ IF port}}{\text{available power @ RF port}} = \frac{\text{available SNR @ RF port}}{\text{available SNR @ IF port}}$

## Example 1

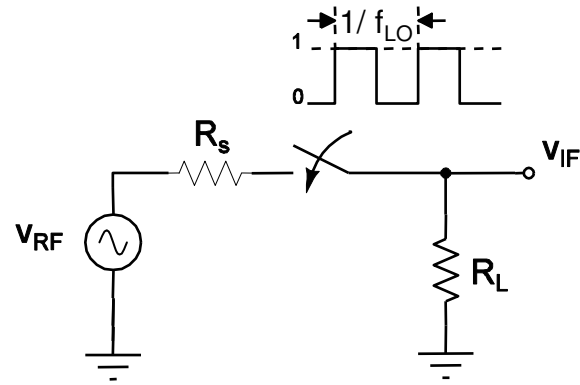


$$v_{RF}(t) = A_{RF} \cos \omega_{RF} t$$

$$v_{IF} = A_{RF} \cos(\omega_{RF} t) \frac{R_L}{R_L + R_s} \left[ \frac{1}{2} + \frac{1}{2} \frac{4}{\pi} \cos(\omega_{LO} t) + \frac{1}{2} \frac{4}{3\pi} \cos(3\omega_{LO} t) + \dots \right]$$

$$= \frac{A_{RF}}{2} \frac{R_L}{R_L + R_s} \frac{2}{\pi} \cos(\omega_{IF} t) + \dots$$

$$\text{Conversion gain} = \frac{R_L}{R_L + R_s} \frac{1}{\pi}$$

## Example 2

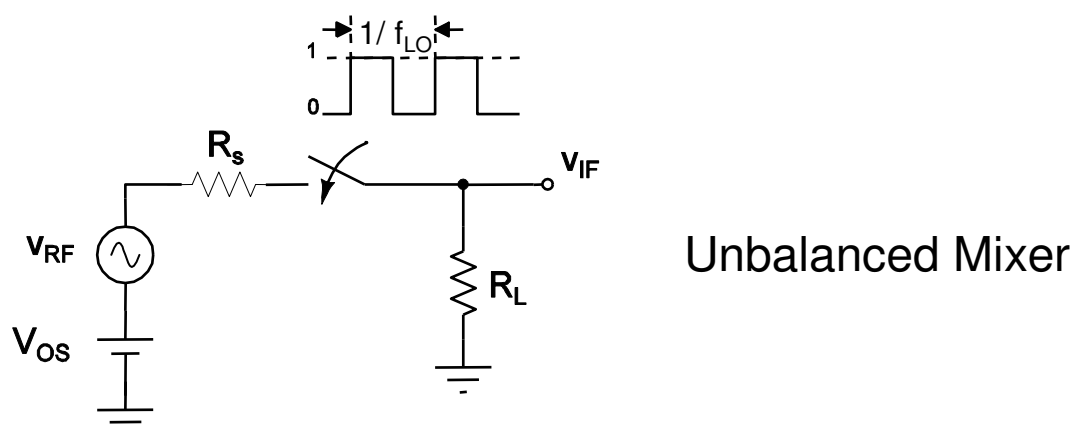

$$V_{IF} = \frac{R_L}{R_L + R_s} [V_{OS} + A_{RF} \cos(\omega_{RF} t)] \left[ \frac{1}{2} + \frac{1}{2} \frac{4}{\pi} \cos(\omega_{LO} t) + \dots \right]$$


$$= \underbrace{\frac{A_{RF}}{2} \frac{R_L}{R_L + R_s} \cos(\omega_{RF} t)}_{\text{RF feed through}} + \frac{V_{OS}}{2} + \underbrace{\frac{V_{OS}}{2} \frac{2}{\pi} \cos(\omega_{LO} t)}_{\text{LO feed through}} + \frac{A_{RF}}{2} \frac{R_L}{R_L + R_s} \frac{2}{\pi} \cos(\omega_{IF} t) + \dots$$

RF feed through => Noise, low frequency components

LO feed through => Desensitizes subsequent amplifiers ( $A_{LO} \gg A_{RF}$ )

## Improvement



### 1. Single balanced mixer

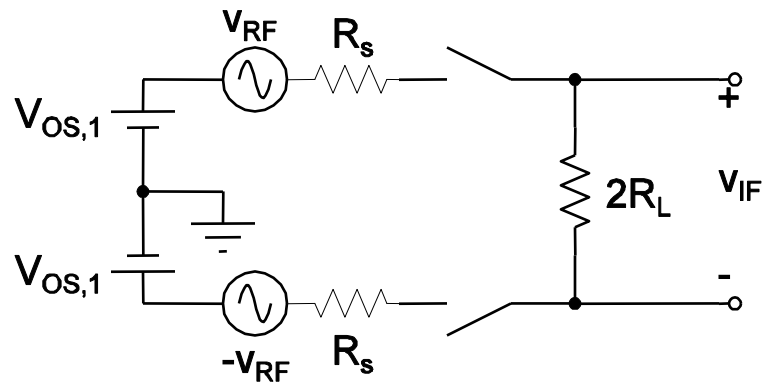

$$V_{IF} = 2A_{RF} \frac{R_L}{R_L + R_s} \cos(\omega_{RF}t) \left[ \frac{V_{OS}}{2} + \frac{1}{2} + \frac{2}{\pi} \cos(\omega_{LO}t) + \dots \right]$$

- No LO feed through

## 2. Double balanced mixer

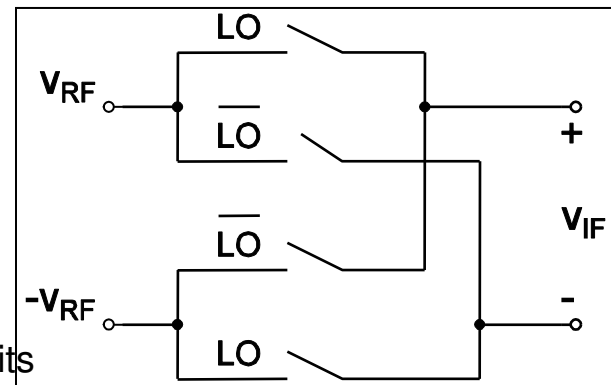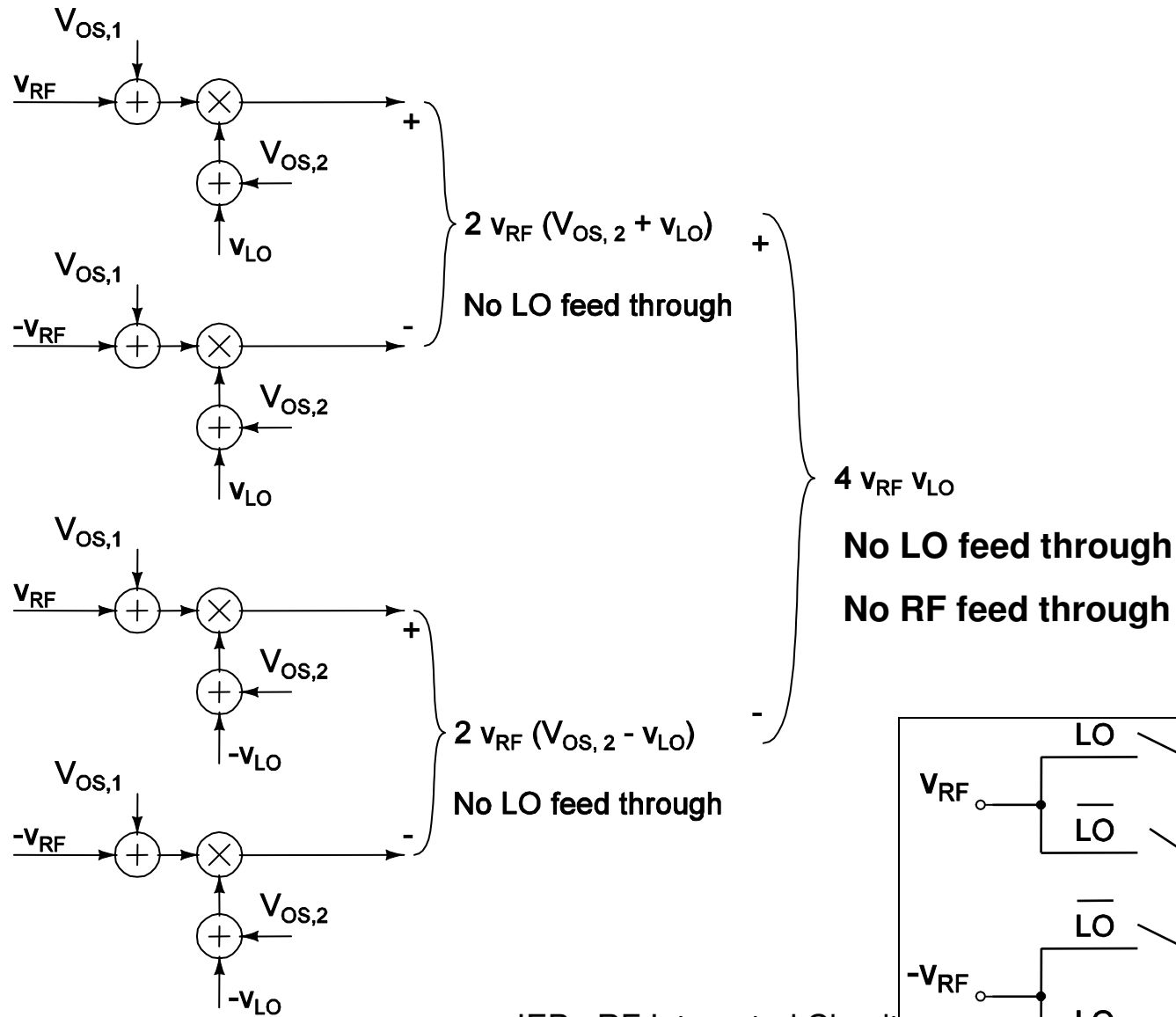


# Noise in Mixers

Consider an ideal mixer-

$$\text{SNR @ input of mixer} = \frac{\overline{V_s^2}}{4KTR_s}$$

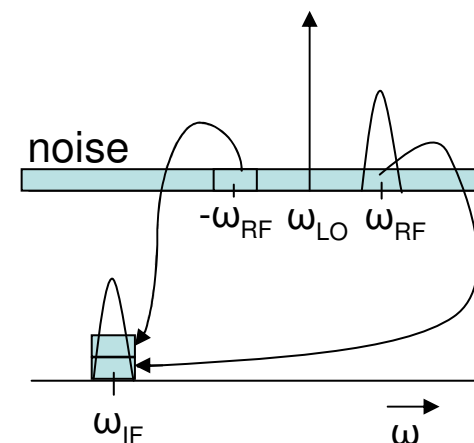
## 1. Single side band signal -

- Thermal noise of both the signal band and the image band are translated to IF.
- SNR @ output is half the SNR @ input  
=> Noise figure = 3 dB



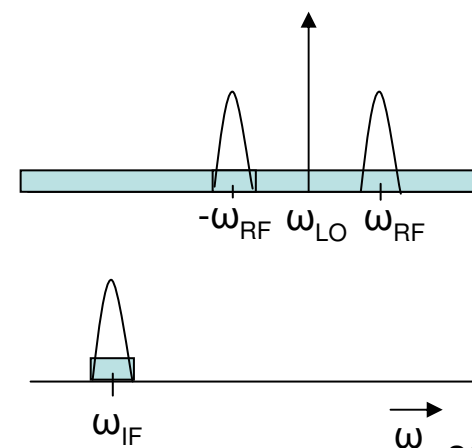
## 2. Double side band signal -

- SNR @ output is equal to the SNR @ input  
=> Noise figure = 0 dB
- DSB Noise figure is 3 dB smaller than SSB Noise figure





# Spurious responses in Mixers

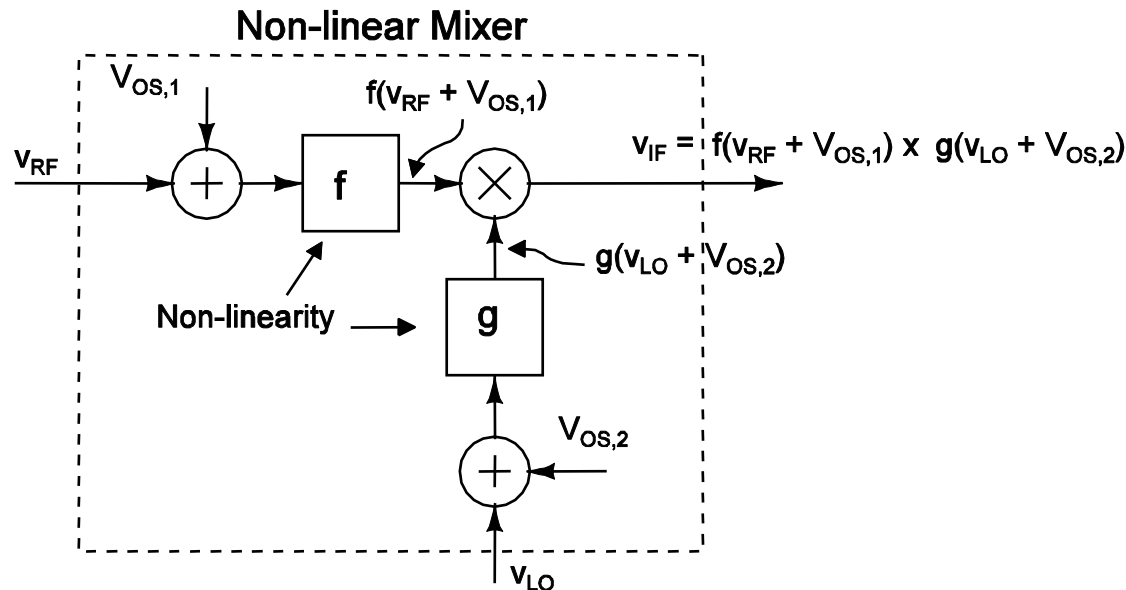

- $f(v_{RF} + V_{OS,1})$  will have the frequency  $mf_{RF}$ ,  $m=0, 1, 2, \dots$
- $g(v_{LO} + V_{OS,2})$  will have the frequency  $nf_{LO}$ ,  $n=0, 1, 2, \dots$
- $f_{LO} - f_D = f_{IF} \Rightarrow$  High side LO ;  $f_{RF} - f_D = f_{IF} \Rightarrow$  Low side LO ;  
 $f_D$  : *desired signal*
- For every combination of  $m$  and  $n$ , there is some frequency  $f_{RF} = f_S$  that satisfies,  $|mf_S \pm nf_{LO}| = f_{IF}$ . Then  $f_S$  is the ‘*Spurious Signal*’
- $m=0 \Rightarrow$  LO feed through ;  $n=0 \Rightarrow$  RF feed through

- Possible combinations –

$$mf_s + nf_{LO} = f_{IF}$$

$$mf_s - nf_{LO} = f_{IF}$$

$$mf_s - nf_{LO} = -f_{IF}$$

- Consider High side LO,

$$f_{LO} - f_D = f_{IF} \Rightarrow f_{LO} = f_D + f_{IF}$$

$$|mf_s \pm nf_{LO}| = f_{IF}$$

$$|mf_s + n(f_D + f_{IF})| = f_{IF}$$

Rearranging,

$$mf_s = -n(f_D + f_{IF}) + f_{IF}$$

$$\text{and } mf_s = n(f_D + f_{IF}) \pm f_{IF}$$

Normalizing w.r.t.  $f_{IF}$ ,

$$S = \frac{-n+1}{m} + \frac{n}{m} D$$

$$\text{and } S = \frac{n \pm 1}{m} \pm \frac{n}{m} D$$

$$S = \frac{f_s}{f_{IF}} \quad \& \quad D = \frac{f_D}{f_{IF}}$$

- $m=1$  and  $n=1$  is the desired mode
- Plot of  $S$  vs  $D$  for given  $m$  and  $n$  is called 'Spur chart'

Example-


$$1. \quad m=2, n=1 \Rightarrow S = \frac{n \pm 1}{m} \pm \frac{n}{m} D \Rightarrow S = \frac{D}{2} + \frac{1 \pm 1}{2}$$

$$2. \quad m=2, n=2 \Rightarrow S = \frac{n \pm 1}{m} \pm \frac{n}{m} D$$

$$\Rightarrow S = \frac{D}{2} + \frac{1}{2} \text{ or } S = \frac{D}{2} + \frac{3}{2}$$

Second harmonic of RF beating with  
second harmonic of LO demodulating to IF

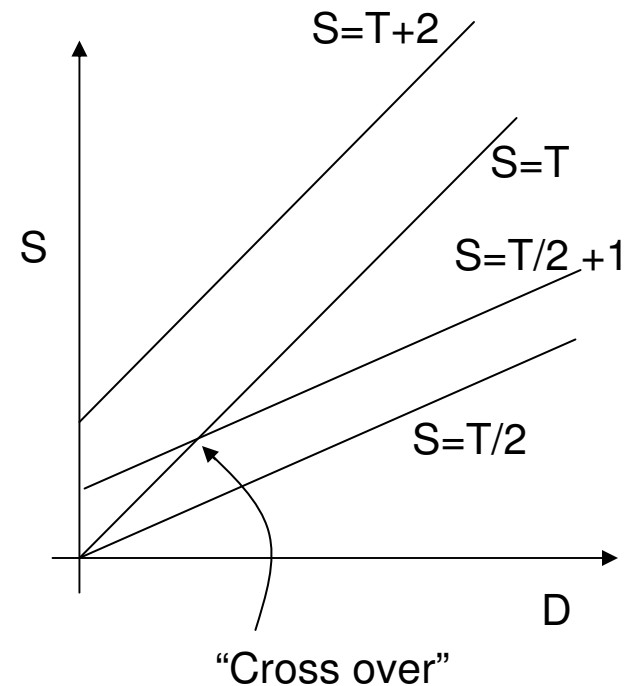
$$S = \frac{D}{2} + \frac{1}{2} \Rightarrow \text{Half IF problem}$$




# Filters

- Need a Linear filter (to avoid inter-modulation)
- Therefore passive filters are used in general
  - LC filters
  - Crystal filters
  - Ceramic filters

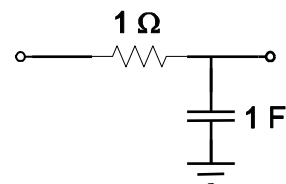
## Frequency transformation (from Low pass to band-pass)




Low-pass

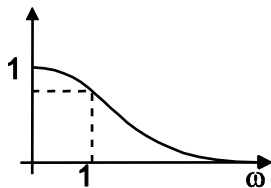

$$H(s) = \frac{1}{1 + s}$$

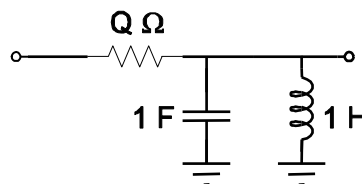

Band-pass

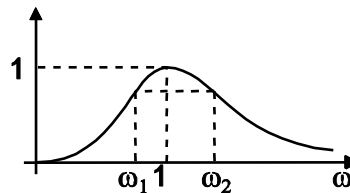

$$H(s) = \frac{1}{1 + Q \left( s + \frac{1}{s} \right)}$$

Transformation from low pass to band pass  $\Rightarrow \mathbf{s} \rightarrow \mathbf{Q}\left(\mathbf{s} + \frac{\mathbf{1}}{\mathbf{s}}\right)$

Let  $\omega_{LP}$  be the cut-off frequency of the low pass filter. Then, for band pass filter,



$$j\omega_{LP} = \mathbf{Q}\left(j\omega + \frac{\mathbf{1}}{j\omega}\right)$$

$$\Rightarrow \omega = \frac{\omega_{LP}}{2Q} \pm \sqrt{\frac{\omega_{LP}^2}{4Q^2} + 1}$$

$$\Rightarrow \omega_1 = \frac{\omega_{LP}}{2Q} - \sqrt{\frac{\omega_{LP}^2}{4Q^2} + 1} \quad \& \quad \omega_2 = \frac{\omega_{LP}}{2Q} + \sqrt{\frac{\omega_{LP}^2}{4Q^2} + 1}$$

$$\text{Center frequency} = \omega_o = \frac{1}{\sqrt{\omega_1\omega_2}}$$
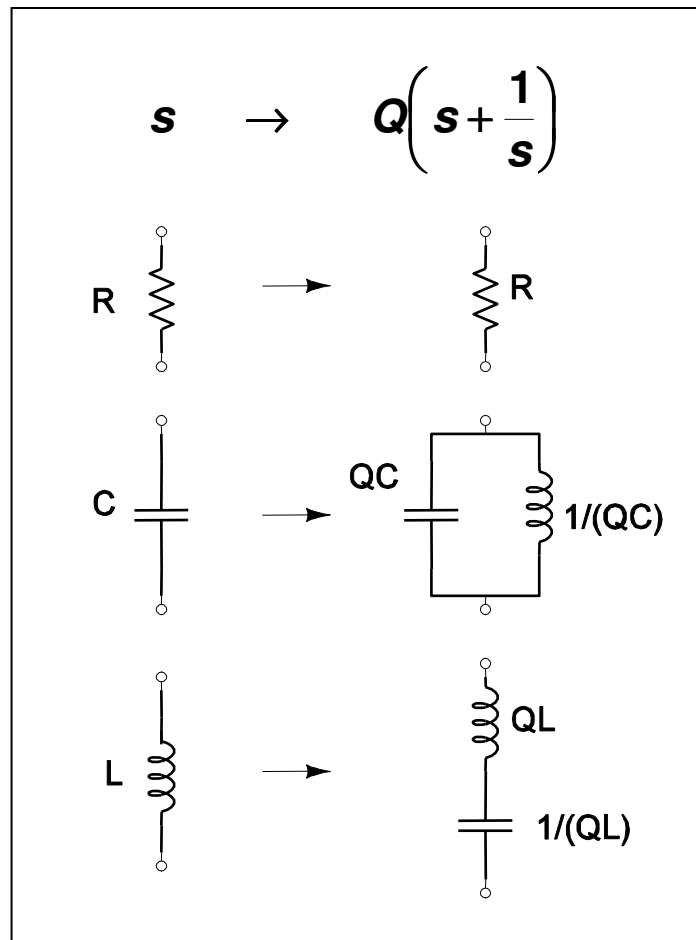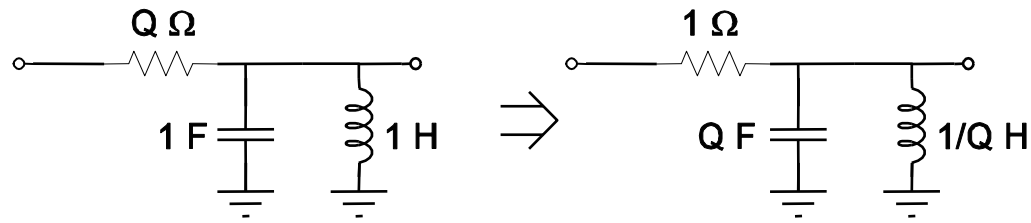
$$\text{Quality factor} = Q = \frac{\omega_o}{\omega_2 - \omega_1}$$



Example:

A 4<sup>th</sup> order low-pass Butterworth band-pass has 3 dB frequencies 100 MHz and 121 MHz. Find the equivalent frequency of the low-pass prototype corresponding to 121 MHz. -

$$f_o = \frac{1}{\sqrt{100 \times 121}} = 110 \text{ MHz} ; \quad Q = \frac{\omega_o}{\omega_2 - \omega_1} = \frac{110}{21} = 5.25$$

$$\text{Equivalent frequency of the low pass prototype} = Q \left( \frac{f}{f_o} - \frac{f_o}{f} \right) = 5.25 \left( \frac{121}{110} - \frac{110}{121} \right) \\ = 1 \text{ Hz}$$

# Local Oscillators

- Ideally Local oscillator should give a sinusoidal signal of constant amplitude and phase


$$\text{i.e. } v_{LO} = A \cos(\omega_{LO}t + \phi)$$

- In reality both the amplitude and phase will be function of time

$$\text{i.e. } v_{LO} = A(t) \cos(\omega_{LO}t + \phi(t))$$


- $A(t)$  : Amplitude noise &  $\phi(t)$  : Phase noise

- The spectrum LO will be like-

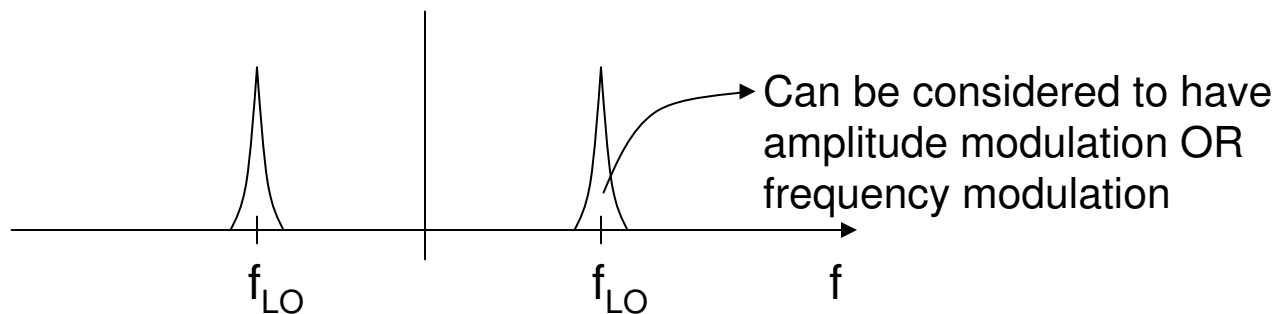



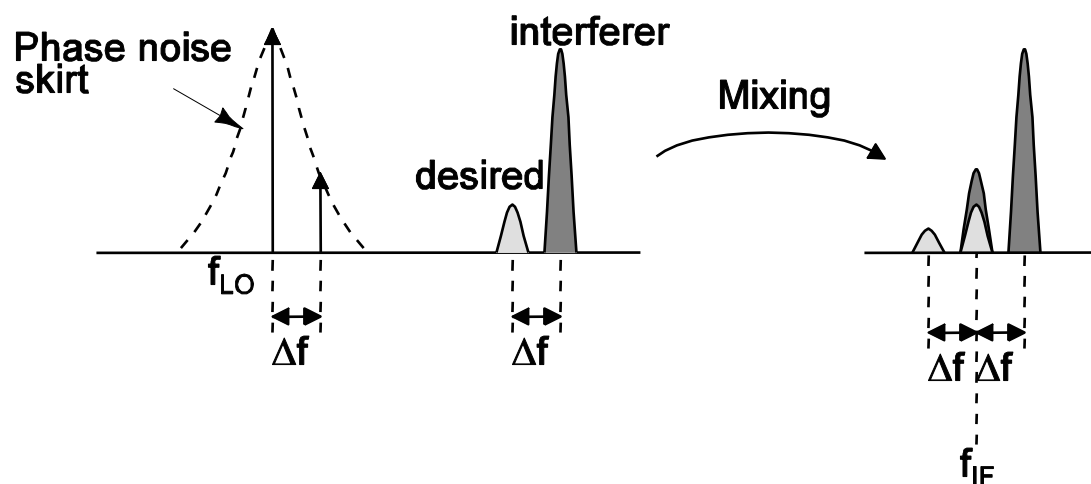
- Amplitude noise is not of concern. A Zero-Cross Detector can be used to switch the switch in the mixer.
- Phase noise is of concern because, zero crossing is the function of time, resulting in 'timing jitter'.
- The timing jitter may cause the interferer to leak into the IF after mixing.



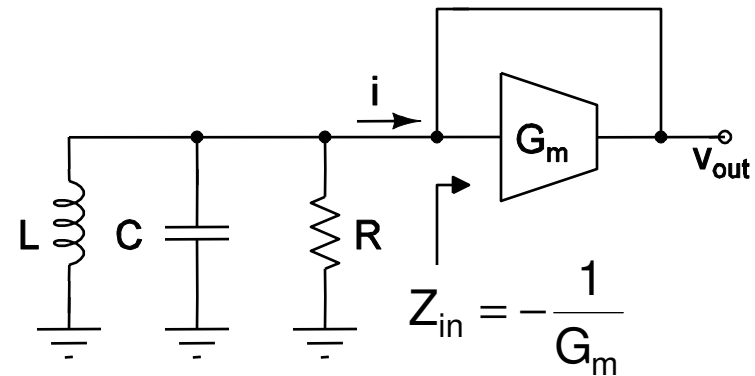
Example: Let the desired channel and interferer strengths be -98 dBm and -23 dBm respectively, separated by  $\Delta f = 200$  kHz. Calculate the reduction in LO skirt at  $\Delta f = 200$  kHz so as to have an SNR of 6 dB (Ans:  $98-23+6 = 81$  dB)

An oscillator schematic is shown below.

- R is the equivalent resistance of the tank circuit formed by L & C
- The transconductor  $G_m$  connected in unity feed back has an input impedance  $Z_{in} = -\frac{1}{G_m}$



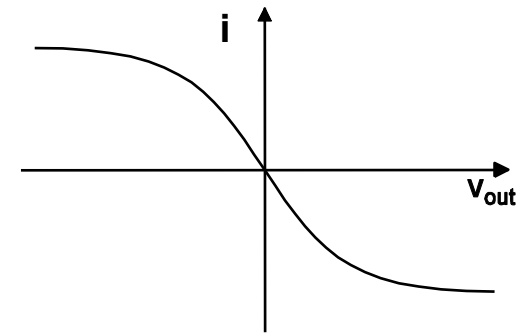- For oscillation,  $G_m \geq \frac{1}{R}$
- The amplitude of oscillation is limited by the non-linearity of the transconductor



Let us assume the transconductor has a non-linearity of the form,

$$i = -(G_0 v_{out} - G_1 v_{out}^3)$$

Let  $v_{out} = A \sin(\omega t)$

$$\begin{aligned} \Rightarrow i &= -(G_o A \sin(\omega t) - G_1 A^3 \sin^3(\omega t)) \\ &= -\left( G_o A \sin(\omega t) - G_1 A^3 \frac{3 \sin(\omega t) - \sin(3\omega t)}{4} \right) \\ &= -A \sin(\omega t) \left[ G_o - \frac{3}{4} G_1 A^2 \right] - \frac{G_1 A^3}{4} \sin(3\omega t) \end{aligned}$$

- 3<sup>rd</sup> harmonic current  $\Rightarrow$  3<sup>rd</sup> harmonic in  $v_{out}$ , but will have less amplitude compared to fundamental due to the tank selectivity
- The amplitude will be stable when  $\left| \frac{i}{v} \right| = \frac{1}{R}$


*i.e.*  $\frac{i}{A \sin(\omega t)} = \left[ G_o - \frac{3}{4} G_1 A^2 \right] = \frac{1}{R}$

$$\Rightarrow A = \sqrt{\frac{G_o - 1/R}{\frac{3}{4} G_1}}$$


- The differential equation governing the KCL at the output node is

$$\frac{1}{L} v_{out} + \frac{1}{R} \frac{dv_{out}}{dt} + C \frac{d^2 v_{out}}{dt^2} - \left( G_O \frac{dv_{out}}{dt} - 3G_1 v_{out}^2 \right) = 0 \rightarrow \text{Vander Pol equation}$$

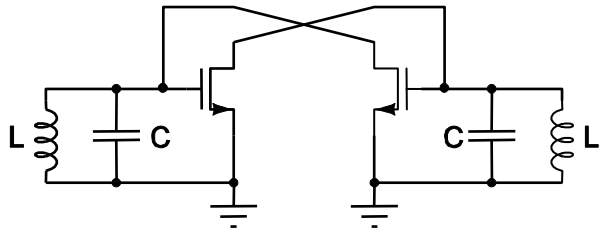
- Fully differential circuit implementation-



Differential signal picture

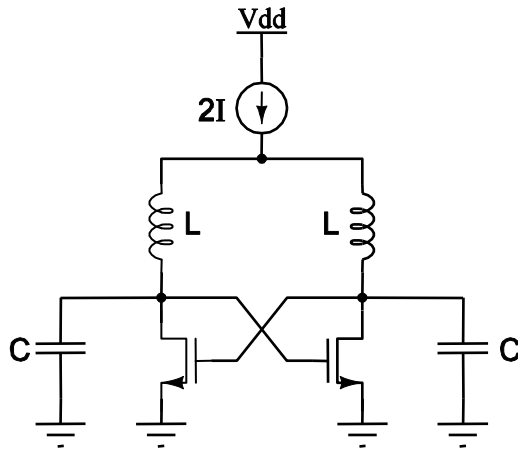

Fully differential schematic

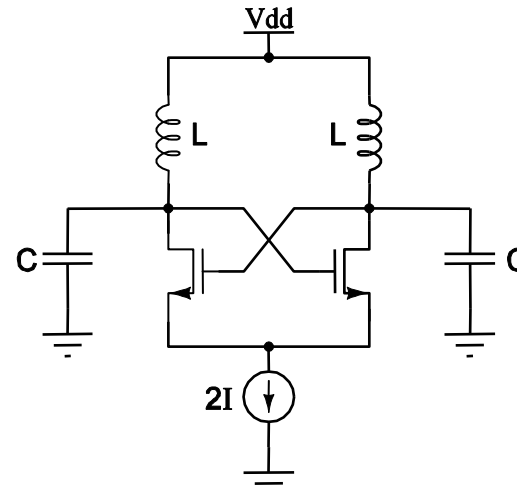


Alternative schematic

# Phase noise models
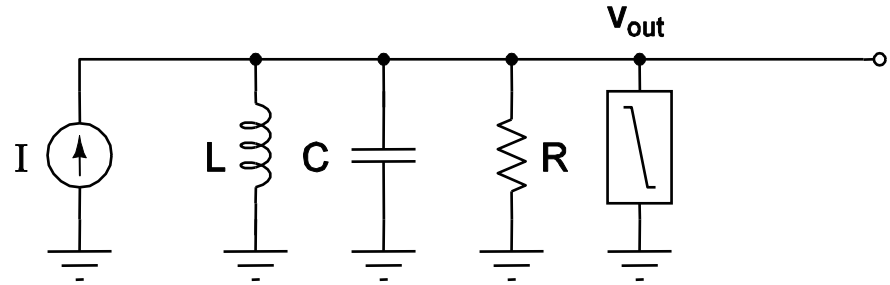
## 1. Leeson's model


If  $v_{out} = Af(t)$ , where  $f(t)$  is a solution, then  $f(t+t_0)$  is also a solution (but depends on the initial condition).



- A charge dumped on tank circuit, causes an amplitude shift and phase shift in the voltage across it.
- If the dumping of charge is due to the noise, the phase shift in the oscillator will be noise dependent
- i.e. noise in the phase => 'Phase Noise'

Assuming linear circuit and the active device is noise less,

$$S_{i_n}(f) = \frac{4KT}{R}$$

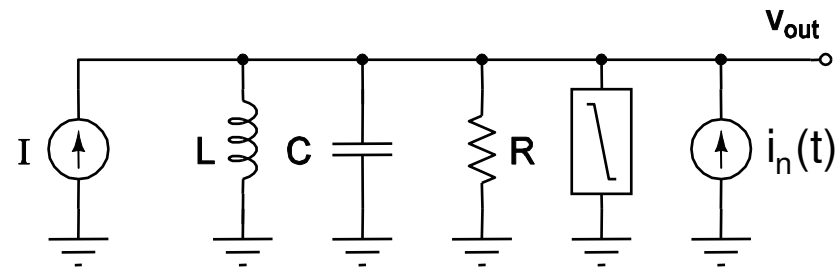

In steady state, the impedance at  $v_{out}$  near oscillation frequency  $\omega_o$  is

$$Z(j\omega) = \frac{j\omega L}{1 - \omega^2 LC} = \frac{j\omega L}{1 - \left(\frac{\omega}{\omega_o}\right)^2}$$

Therefore, the voltage noise spectral density at frequency  $(\omega_o + \Delta\omega)$  is

$$S_{V_{n,o}}(f) = \frac{4KT}{R} |Z(j\omega_o + j\Delta\omega)|^2$$


$$\approx \frac{4KT}{R} \frac{L}{C} \left(\frac{\omega_o}{2\Delta\omega}\right)^2$$

This contains both the Amplitude and Phase noise.

Assuming Phase noise is half of the total noise,


$$\begin{aligned} \text{Phase noise} &\approx \frac{2KT}{R} \frac{L}{C} \left( \frac{\omega_o}{2\Delta\omega} \right)^2 \\ &\approx \frac{KTR}{2} \left( \frac{\omega_o}{Q\Delta\omega} \right)^2 \end{aligned}$$
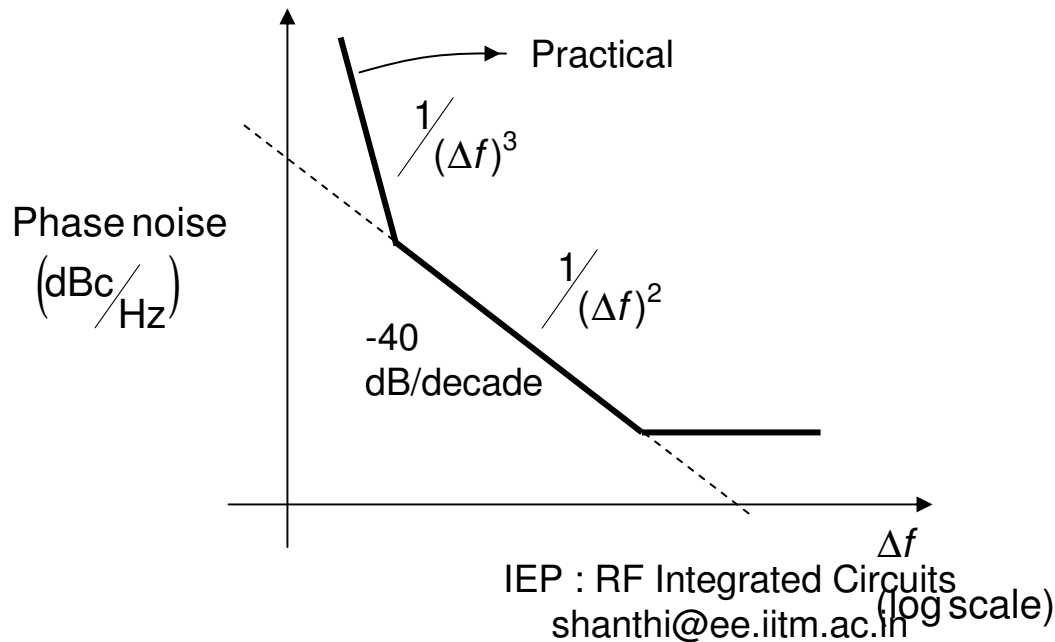
$$\frac{\text{Phase noise @ } (\omega_o + \Delta\omega)}{\text{Carrier power @ } \omega_o} \approx \frac{1}{A_{rms}^2} \frac{4KTR}{2} \left( \frac{\omega_o}{Q\Delta\omega} \right)^2 \quad \text{dBc/Hz}$$


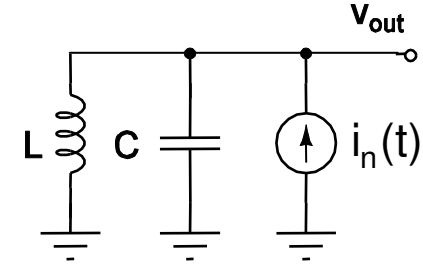
# 1. Hajimiri's phase noise model

- For an LC oscillator, if a charge is dumped, the oscillation will settle to a new amplitude and phase. The change is dependent on the time at which the charge is dumped.



- The plot of time instance of charge dumping verses the phase change will be a sinusoid of a amplitude =  $\frac{\Delta q}{CV_o}$  where,  $\Delta q$  is the charge and  $V_o$  is the amplitude of oscillation prior to charge dump.

$$i.e. \Delta\phi(t) = -\frac{\Delta q}{CV_o} \sin(\omega_o\tau)u(t-\tau)$$

$$\frac{\Delta\phi(t)}{\Delta q} CV_o = -\sin(\omega_o\tau)u(t-\tau)$$

$$\left(\frac{\Delta\phi(t)}{\Delta q}\right) Q_{max} = -\Gamma(\tau)u(t-\tau)$$

$$\left(\frac{\Delta\phi(t)}{\Delta q}\right) : \text{unit impulse response} \quad \& \quad \Gamma(\tau) : \text{Impulse Sensitivity Function (ISF)}$$




- The total phase noise due the charge dumped by the noise source  $i_n(t)$  on the LC tank is,

$$\begin{aligned} \text{Total phase noise} &= \int_0^{\infty} i_n(\tau) \left( \frac{1}{Q_{\max}} \right) \Gamma(\tau) u(t-\tau) d\tau \\ &= \int_0^t i_n(\tau) \left( \frac{1}{Q_{\max}} \right) \Gamma(\tau) d\tau \end{aligned}$$

- $\Gamma(\tau)$  is periodic with period  $\frac{2\pi}{\omega_o}$

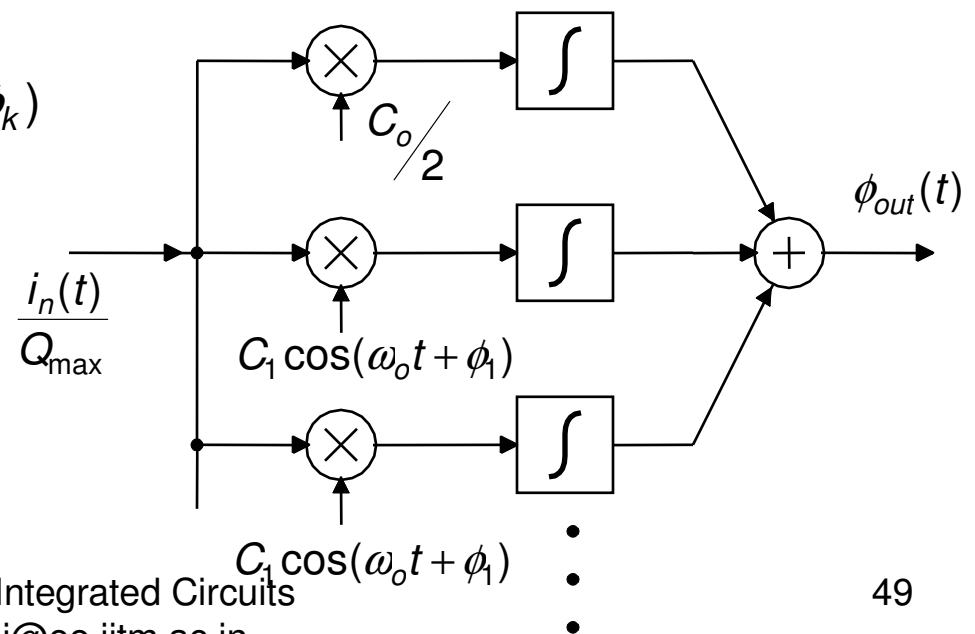
$$\Rightarrow \Gamma(\tau) = \frac{C_o}{2} + \sum_{k=1}^{\infty} C_k \cos(k\omega_o\tau + \phi_k)$$



- The oscillator o/p is of the form  $v_o(t) = \cos(\omega_o t + \phi(t))$
- For very small  $\phi(t)$ ,  $v_o(t) = \cos(\omega_o t) - \phi(t) \sin(\omega_o t)$
- Therefore, low frequency component of  $\phi(t)$  is of interest, as it beats with  $\sin(\omega_o t)$  and the resulting frequency will be very close to  $\omega_o$

$$\text{If, } \frac{i_n(t)}{Q_{\max}} = \frac{I_o \sin(\Delta\omega t)}{Q_{\max}}$$
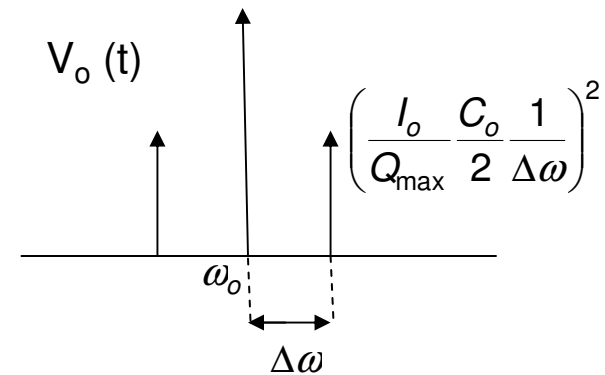
$$\text{Then, } \phi(t) \approx \frac{I_o}{Q_{\max}} \frac{C_o}{2} \frac{1}{\Delta\omega} \cos(\Delta\omega t) \longrightarrow$$



- Generalizing,

$$\text{If, } i_n(t) = I_o \sin((k\omega_o + \Delta\omega)t)$$

$$\text{Then, } \phi(t) \approx \frac{I_o}{Q_{\max}} \frac{C_k}{2} \frac{1}{\Delta\omega} \cos((k\omega_o + \Delta\omega)t)$$

- Assuming  $i_n(t)$ , is white noise with noise spectral density  $= \frac{\overline{i_n^2(t)}}{\Delta f}$

- Noise power at the oscillator output, at a frequency offset of  $\Delta\omega$  is

$$= 10 \log_{10} \left[ \frac{\overline{i_n^2} / \Delta f}{(4Q_{\max})^2} \times \frac{1}{(\Delta\omega)^2} \times \sum_{k=2}^{\infty} C_k^2 \right] \text{ dBc/Hz}$$

- Considering 1/f noise, NSD of  $i_n(t)$  is  $= \frac{\overline{i_n^2(t)} (\omega_{1/f})}{\Delta f} \left( \frac{\omega_{1/f}}{\Delta\omega} \right)$

The noise power at the oscillator output, at a frequency offset of  $\Delta\omega$  is

$$= 10 \log_{10} \left[ \frac{\left( \frac{\overline{i_n^2}}{\Delta f} \right) \omega_{1/f}}{(4Q_{\max})^2} \times \frac{1}{(\Delta\omega)^3} \times C_o^2 \right] \text{ dBc/Hz}$$

$\therefore$  for very low frequency  $\Delta\omega$ ,  $C_o$  is only dominant

# Image Rejection

- Two ways to reject the filter
  1. Using Image reject filter
    - High Q filters are required – difficult to achieve
  2. Cancelling the image
- Latter of the two is preferred
- Image rejection techniques
  1. Hartley image reject mixer
  2. Weaver image reject mixer
  3. Direct conversion


## Hilbert transform

$X_+(f)$  can be obtained from  $X(f)$  as,

$$X_+(f) = X(f) \frac{1}{2} [1 + \text{sgn}(f)] \quad ; \quad \text{sgn}(f) \text{ is complex}$$

$$X_+(f) = X(f) \frac{1}{2} [1 + j(-j \text{sgn}(f))]$$

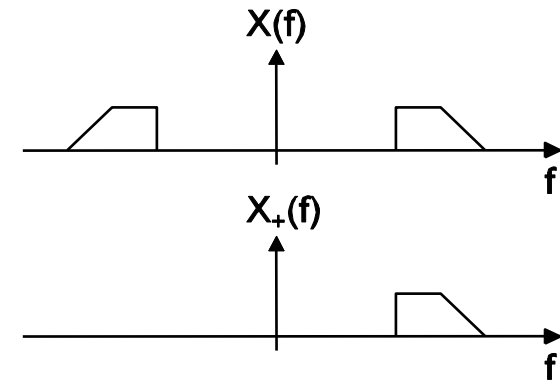$-j \text{sgn}(f)$  is real and known as Hilbert filter



$$X_+(f) = \frac{1}{2} X(f) + j \frac{1}{2} X(f) (-j \text{sgn}(f))$$

$$= \frac{1}{2} X(f) + j \frac{1}{2} \hat{X}(f) \quad \hat{X}(f) \text{ is the Hilbert transform of } X(f)$$


$$\Rightarrow x_+(t) = \frac{1}{2} [x(t) + j\hat{x}(t)] \rightarrow \text{Analytic signal}$$


To get back  $x(t)$  from  $x_+(t)$ ,

$$\Rightarrow x(t) = 2 \Re[x_+(t)]$$
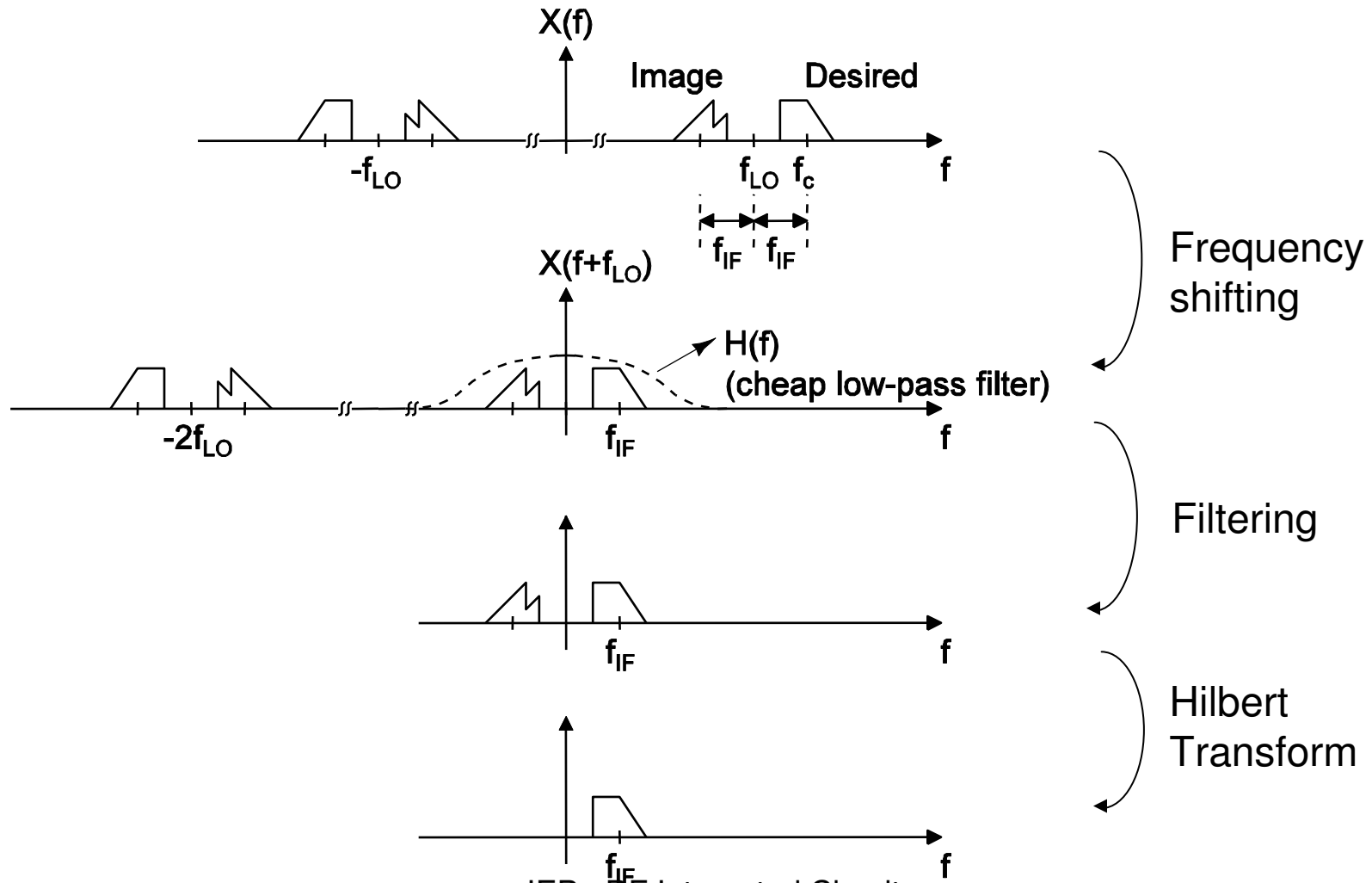
# 1. Hartley Image Reject Mixer


- The steps followed in rejecting the image is shown in the figure below



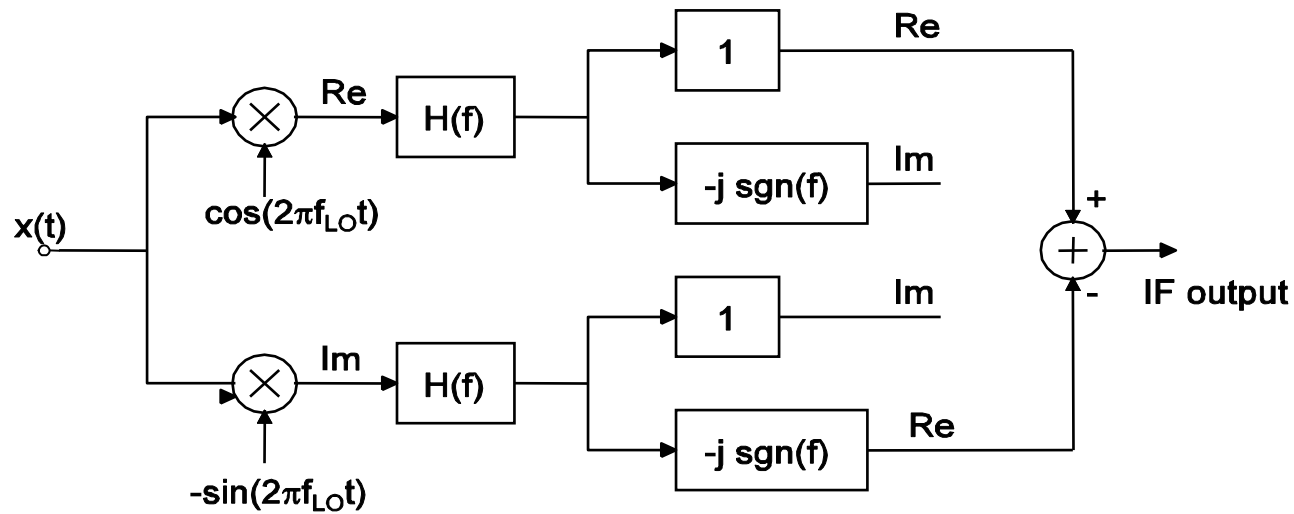

Hartley image reject mixer

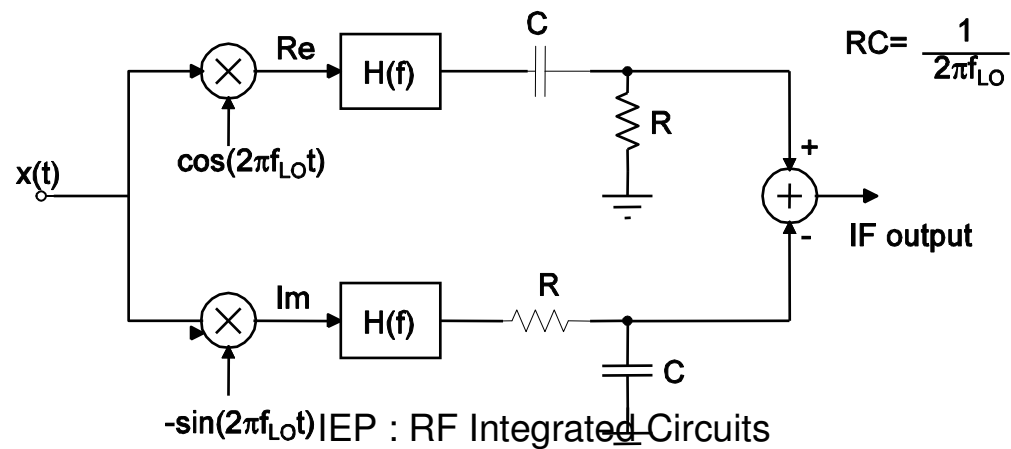
- If the RF signal is very narrow band,  $(-sgn(f))$  block need to provide  $90^\circ$  phase-lag only at  $f_{IF}$ . The Hartley image reject mixer can be simplified as-




IEP : RF Integrated Circuits  
shanthi@ee.iitm.ac.in
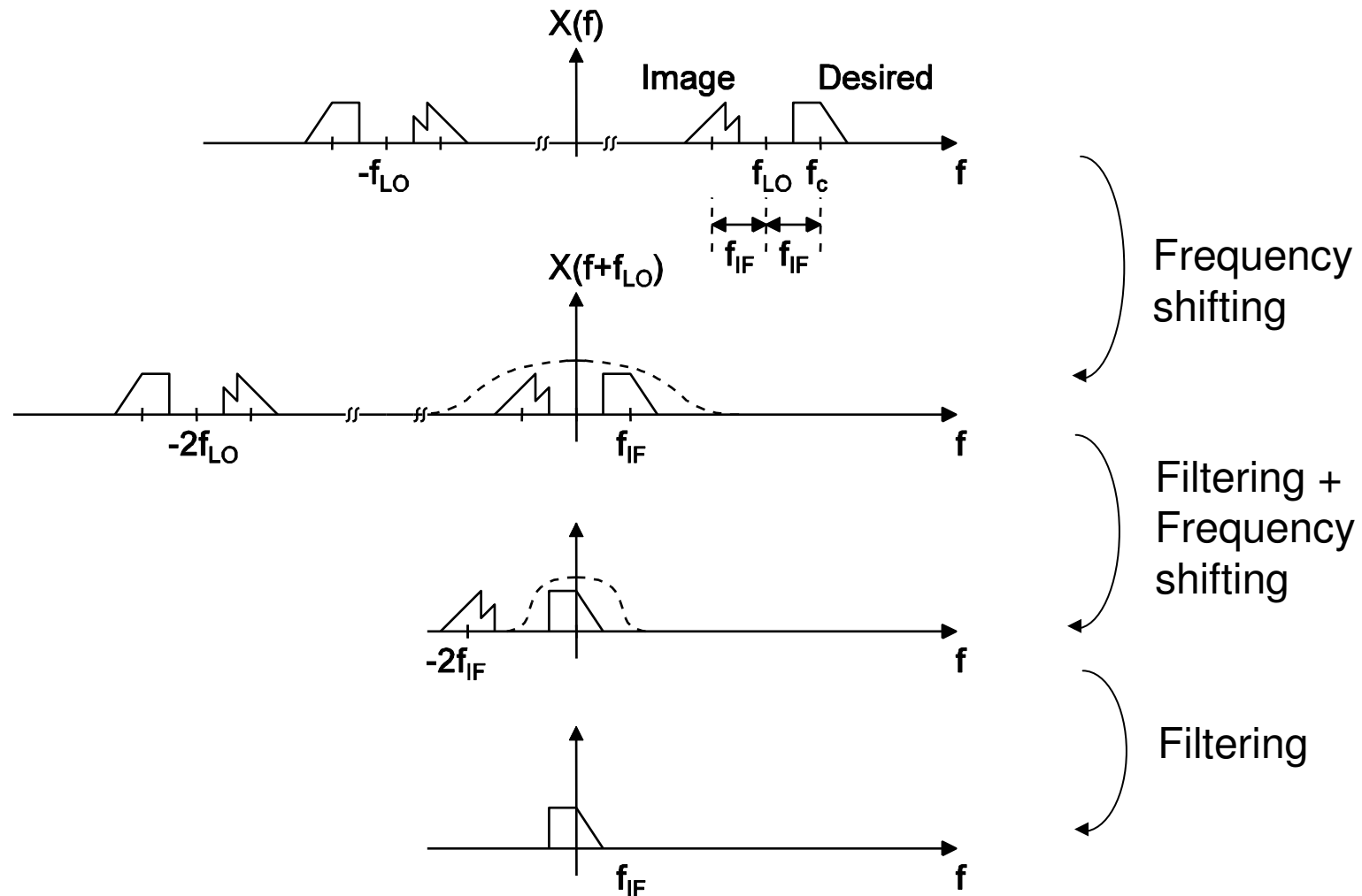
## 2. Weaver Image Reject Mixer

- The steps followed in rejecting the image is shown below






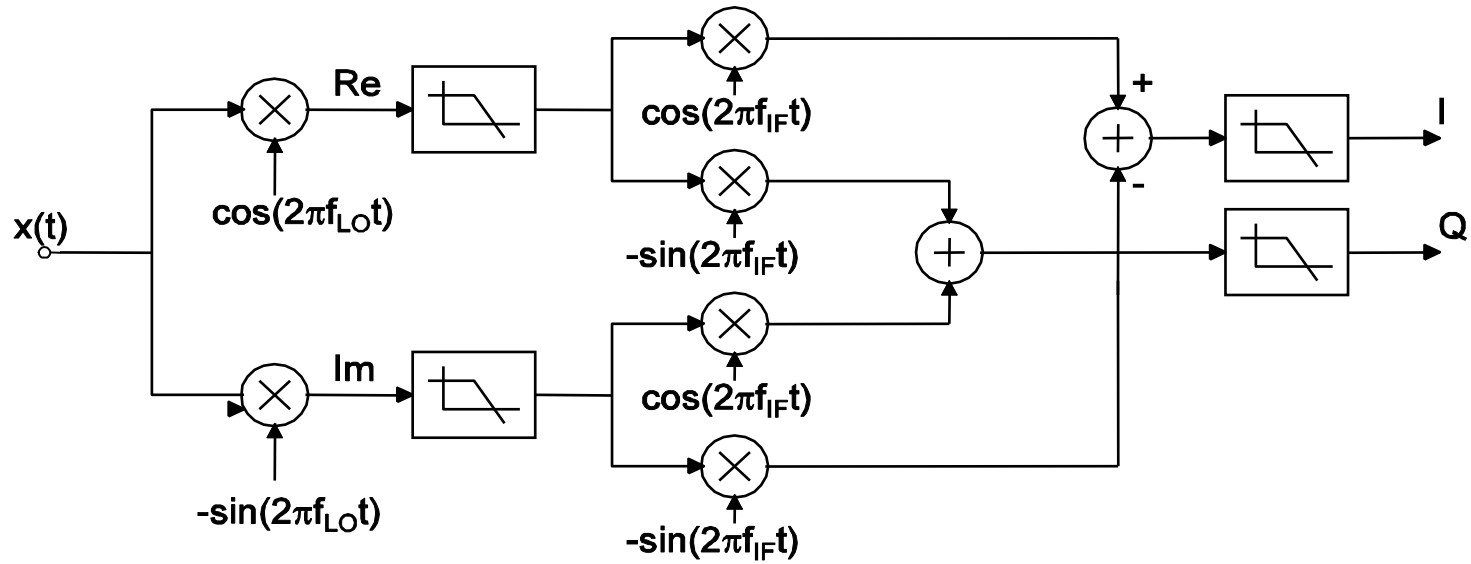

Weaver image reject filter
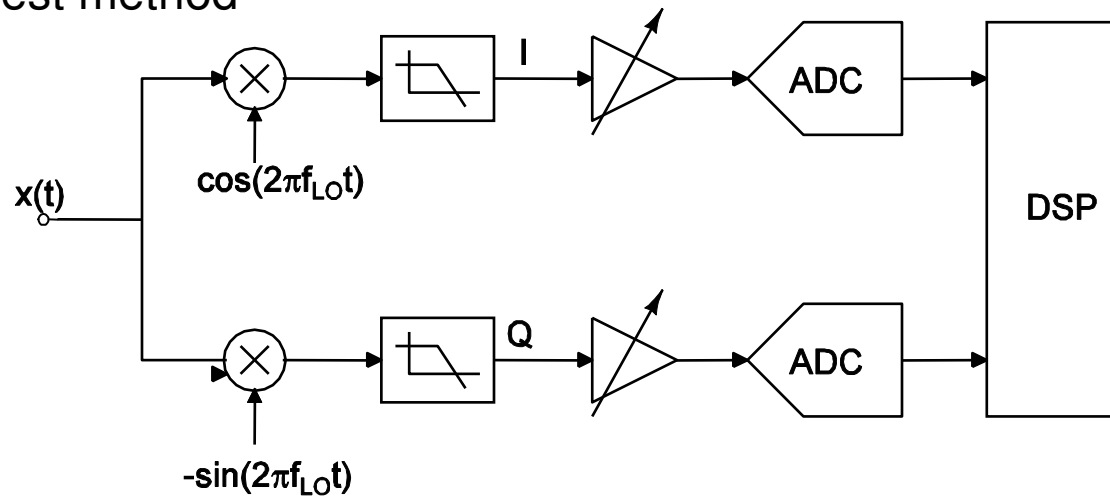
### 3. Direct conversion (Zero IF) mixer

- One step conversion from RF band to base band
- Simplest method




#### Limitations

- a) Predominant component of I & Q are 'DC'
- Filter DC off-sets will contaminate the information
  - $1/f$  noise  $\Rightarrow$  slow varying DC
  - 2<sup>nd</sup> order intermodulation (out-of band  $IIP_2$ )
  - 3<sup>rd</sup> order intermodulation
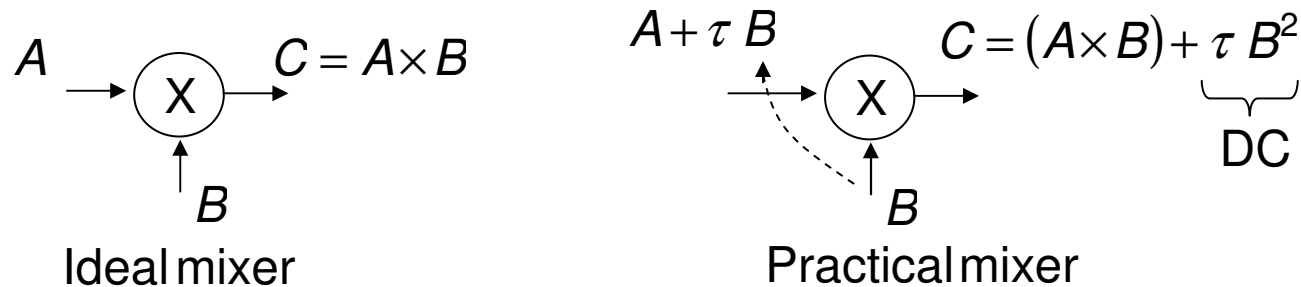
## b) Mixer

- Finite isolation between the RF port and LO port, causes a 'DC' component to appear at the mixer output



## c) LNA

- Finite reverse isolation of LNA makes the LNA non-unilateral.
- The LO component leaked to the input of LNA will reflect back, causing a 'DC' component at mixer output