

Figure 1: Figure for Problems 1 and 2

Figure 1 pertains to Questions 1 and 2. The two linear networks (labelled N) are identical, and excited by DC voltage sources  $V_1$  and  $V_2$ , as shown in the figure. When  $V_1 = 1V$  and  $V_2 = 3V$ ,  $V_{out}$  is found to be  $6V$ .

Q. 1: Determine  $V_{out}$  when  $V_1 = 4V$  and  $V_2 = -4V$ .

Q. 2: Determine  $V_{out}$  when  $V_1 = 7V$  and  $V_2 = -5V$ .

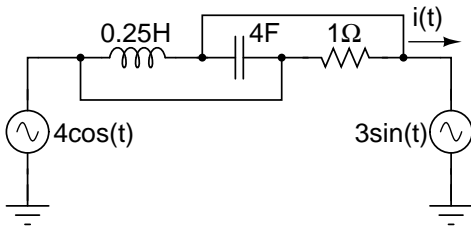


Figure 2: Figure for Question 3

Q. 3: Determine the amplitude of the sinusoidal current  $i(t)$ .

Q. 4: In Figure 3, the capacitors have initial conditions as shown.  $u(t)$  is the unit step function. Determine  $V_x$  as a function of time.

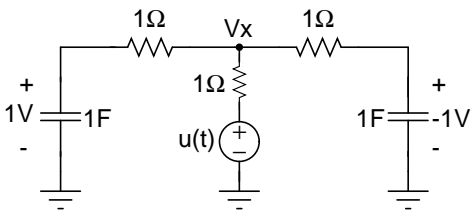


Figure 3: Figure for Question 4

Q. 5: Let  $H(s)$  denote the transfer function of the RLC network shown in Figure 4. Determine  $H(j1)$ .

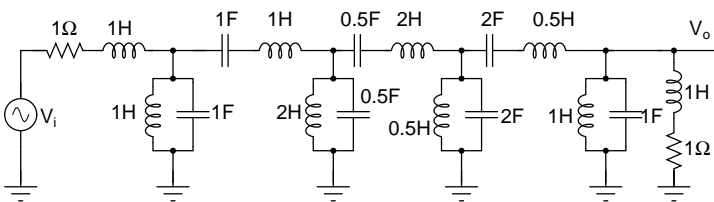


Figure 4: Figure for Question 5

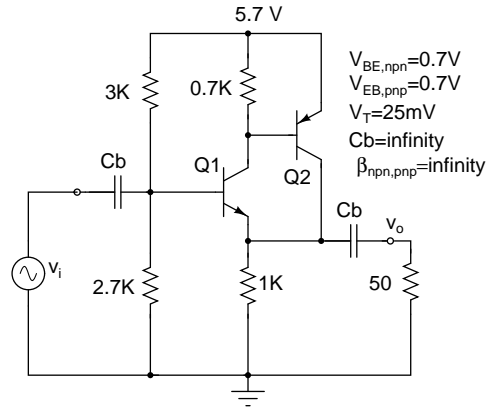


Figure 5: Figure for Questions 6 and 7

Figure 5 pertains to this problem and the next.

Q. 6: Determine the quiescent collector current of the pnp transistor Q2.

Q. 7: Determine the small signal gain  $v_o/v_i$ .

Q. 8: In Figure 6, determine the output voltage of the opamp. The diodes have a cut-in voltage of  $0.7V$ .

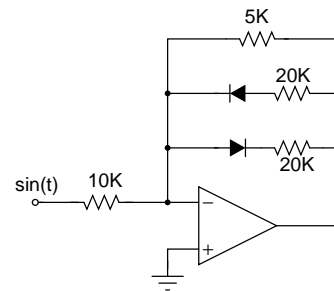


Figure 6: Figure for Question 8

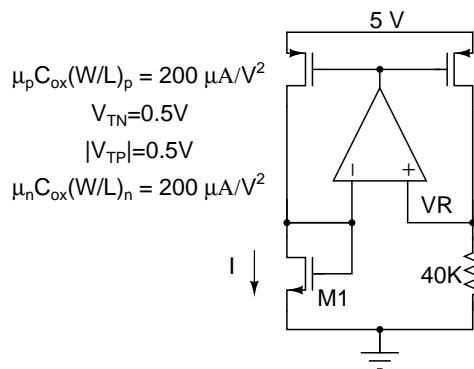


Figure 7: Figure for Questions 9 and 10

Figure 7 pertains to this problem and the next. It is known that a non-zero current flows through the transistors. The opamp is ideal.

Q. 9: Determine the current through M1.

Q. 10: Determine the voltage across the resistor (VR).