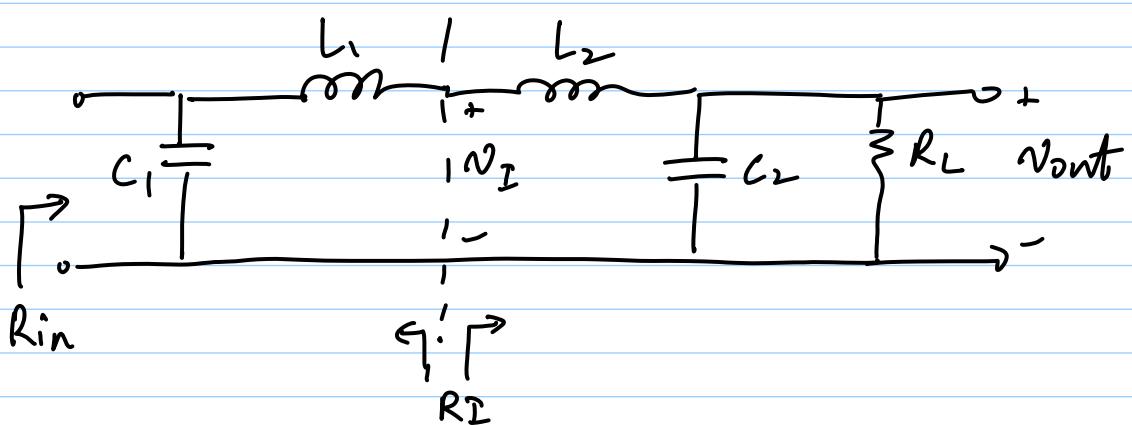


Q-relation in T₀ & T matches

8/16/2011



$$Q = \omega_0 \cdot \frac{\text{Energy stored}}{\text{Avg. power loss}}$$

We want to prove the relation:

$$Q = Q_L + Q_R$$

R_I is the equivalent input impedance of the right-side L-match ($L_2 - C_2$)

Power is dissipated only in R_L

$$\therefore \frac{V_{out}^2}{R_L} = \frac{V_I^2}{R_I} \quad \text{--- } ①$$

$$\text{current through } L_1 \text{ & } L_2 = \frac{V_I}{R_I} \quad \text{--- } ②$$

from ① & ②

$$Q = \omega_0 \cdot \frac{\cancel{\frac{1}{2}}(L_1 + L_2) \left(\frac{V_I}{R_I}\right)^2}{\cancel{\frac{1}{2}} \frac{V_{out}^2}{R_L}}$$

$$= \omega_0 \cdot (L_1 + L_2) \cdot \frac{\frac{V_I^2}{R_I^2}}{\frac{V_I^2}{R_I}}$$

$$= \omega_0 \frac{(L_1 + L_2)}{R_I} = Q_L + \underline{Q_R}$$