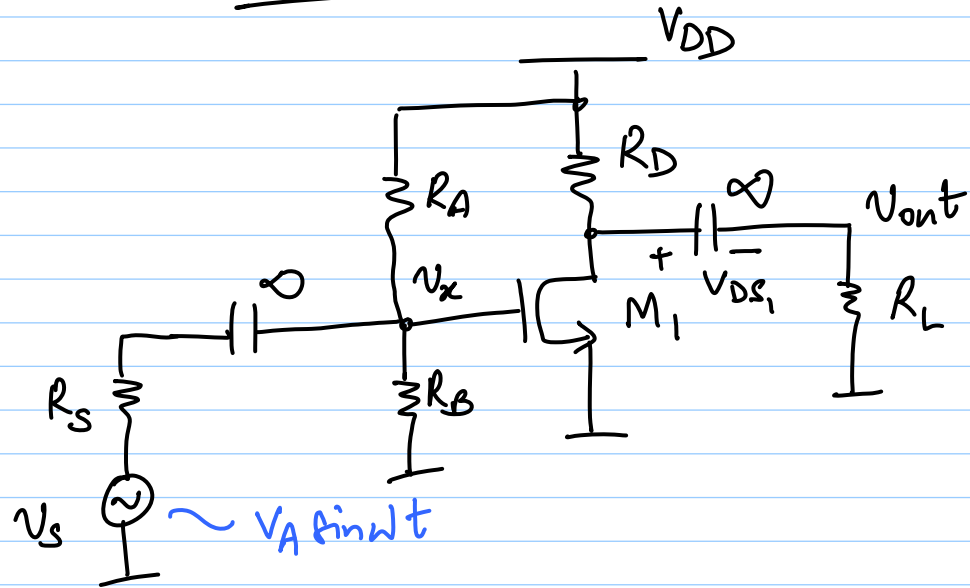



17-8-12

Lec 10



- * M_1 - sat region
- * $R_A || R_B \gg R_s \Rightarrow v_x \approx v_s$
- * Gain $|A| = g_m (R_D || R_L) \gg 1$

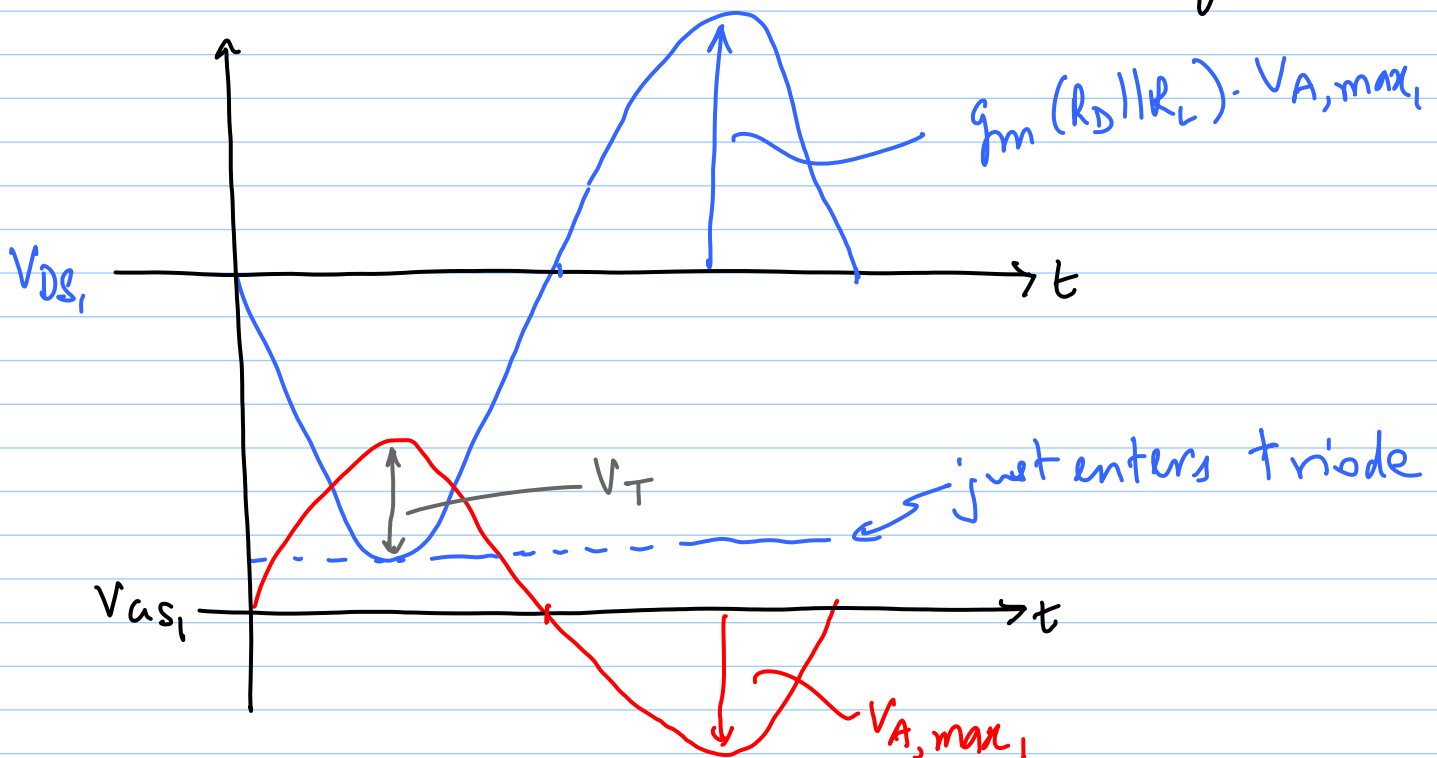* As $V_a \uparrow$, $V_D \downarrow \Rightarrow$ as V_A increases, M_1 moves towards triode region



$V_{A,max}$ = maximum value of V_A that keeps M_1 from going into triode region at any time (positive half cycle)

* $V_{A,max}$ depends on O.P. (e.g. V_{DS1})

in general,

$$V_A = V_{AS} + V_S$$

$$V_D = V_{DS1} - g_m(R_D || R_L) \cdot V_S$$

@ $V_{A,max}$, $V_D = V_A - V_T$

$$\Rightarrow V_{DS1} - g_m(R_D || R_L)V_{A,max} = V_{AS1} + V_{A,max} - V_T$$

$$V_{A,max} = \frac{V_{DS1} - V_{AS1} + V_T}{1 + g_m(R_D || R_L)}$$

Negative half cycle



MOSFET drain current


$$I_D = I_{D1} + g_m V_S$$

quiescent current

incremental current

in-phase with V_S

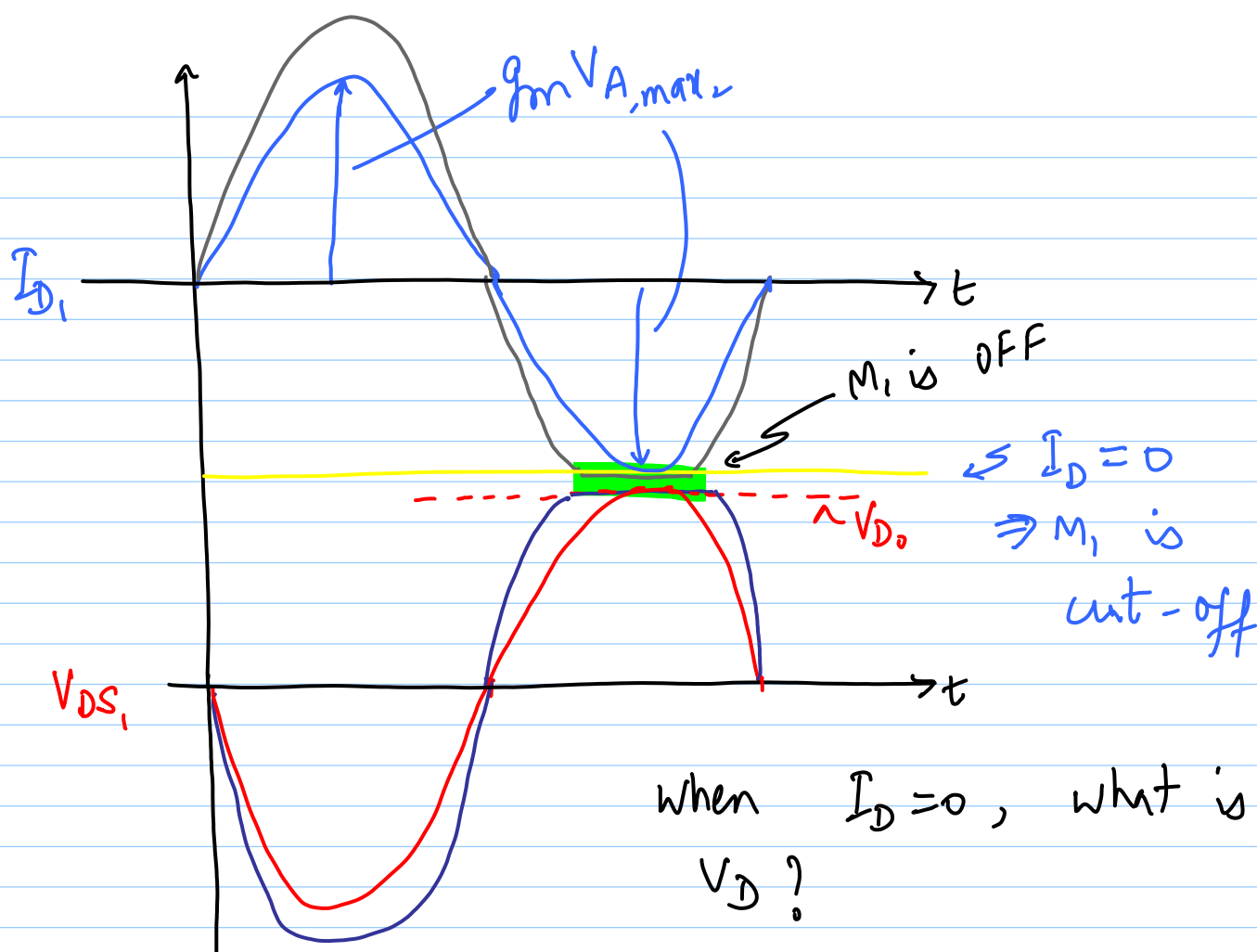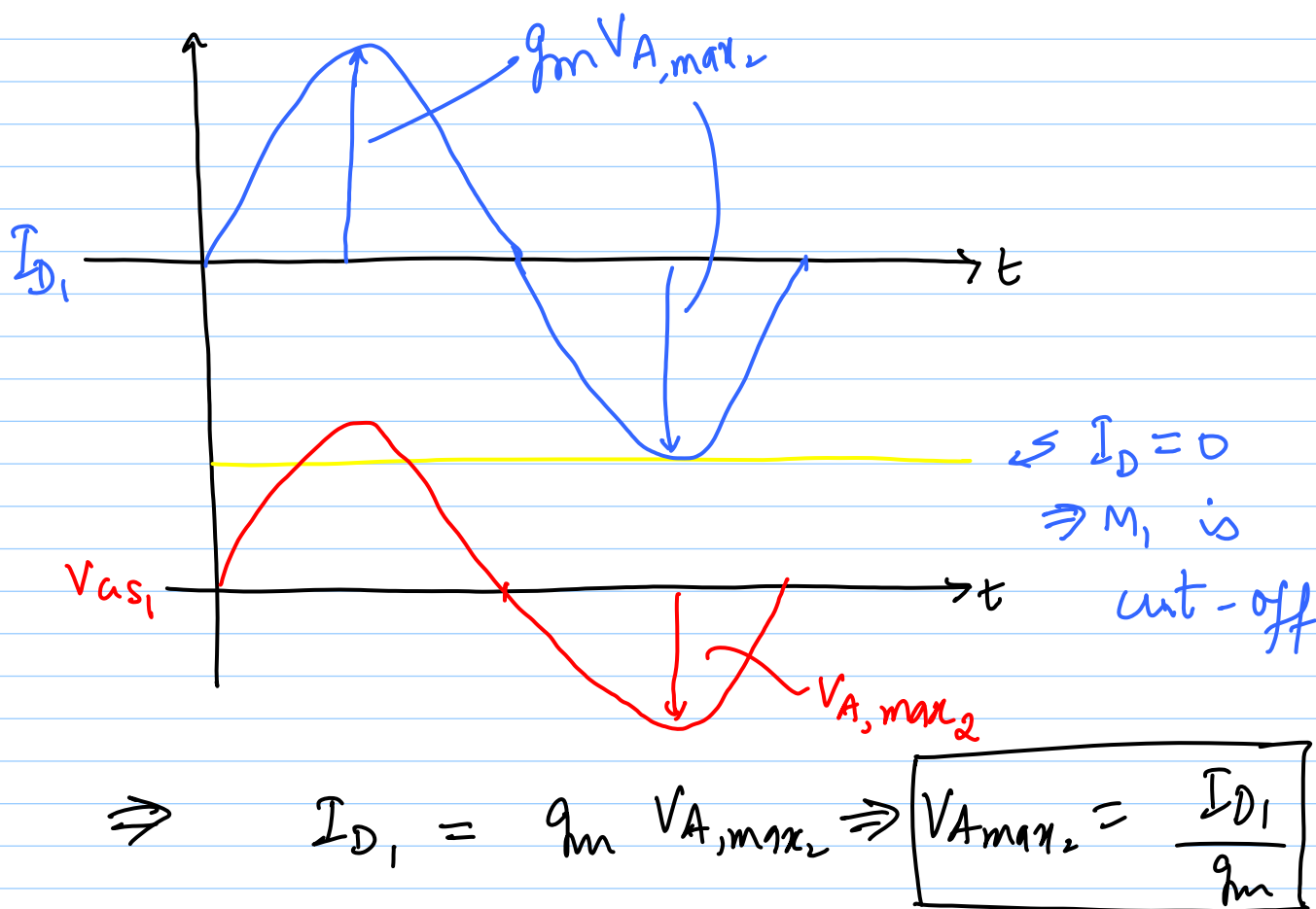

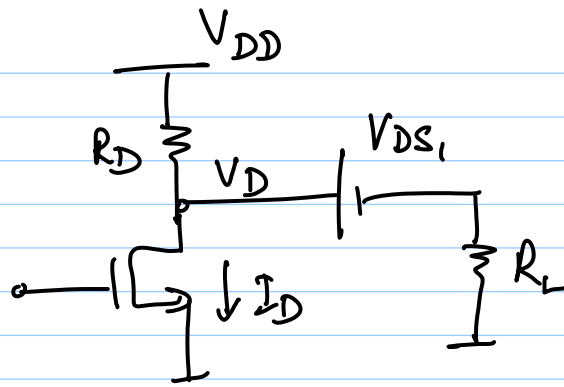


If $I_D = 0$, KCL @ drain gives:

$$\frac{V_{DD} - V_{D0}}{R_D} = \frac{V_{D0} - V_{DS1}}{R_L}$$

$$\Rightarrow V_{D0} = \frac{R_L V_{DD} + R_D V_{DS1}}{R_D + R_L}$$

* Max limit on V_A (no clipping):
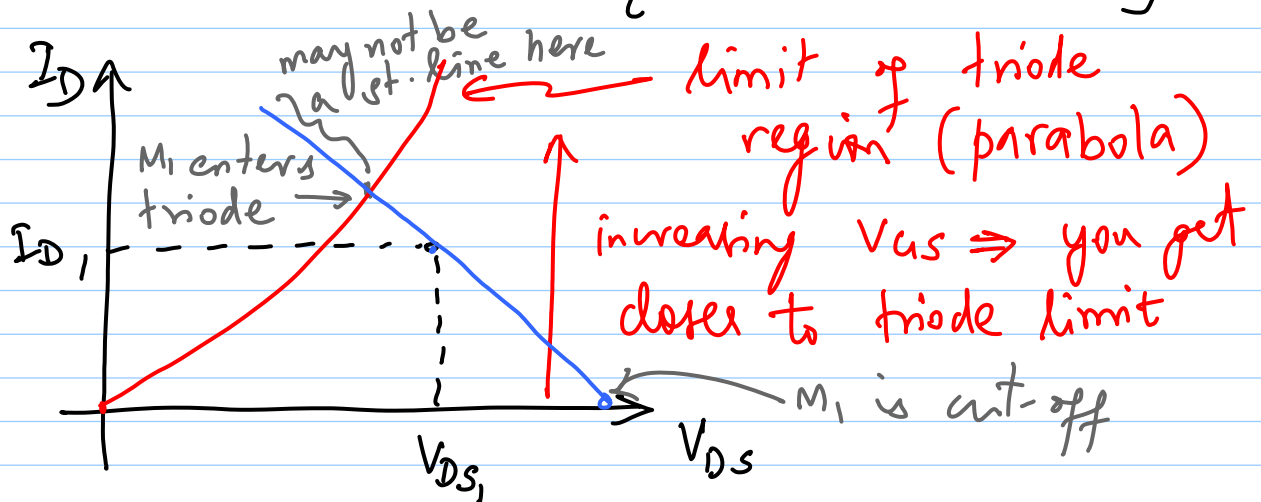
$$V_{A,max} = \min. \{ V_{A,max1}, V_{A,max2} \}$$



to use of $I_D - V_{DS}$ points as V_{GS} is applied = straight line (linear approx.) in small signal

→ As $v_s \uparrow$, $I_D \uparrow$ & $V_{DS} \downarrow$ (the half cycle)
and vice versa

$$\text{slope of line} = \frac{\partial I}{\partial V_{DS}} = \frac{-1}{\text{inc. res. @ drain}}$$


$$= \frac{-1}{R_D \parallel R_L}$$

$$\left. \begin{aligned} v_d &= -g_m (R_D \parallel R_L) \cdot v_s \\ i_d &= g_m v_s \end{aligned} \right\}$$

* To maximise swing, choose (I_D, V_{DS})
equidistant between triode & cut-off
i.e. +ve H.C. $\Rightarrow M_1$ just enters triode
-ve H.C. $\Rightarrow M_1$ just cuts off

$\Rightarrow$ choose $V_{A, \max_1} = V_{A, \max_2}$

E.g.

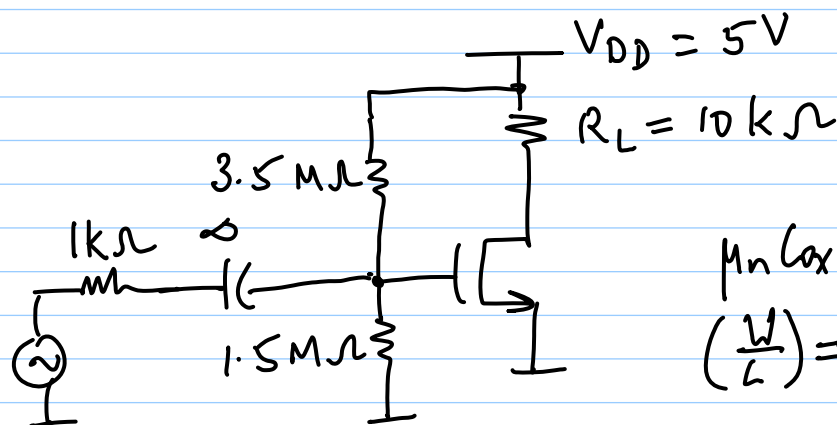

$$\mu_n C_{ox} = 100 \mu A/V^2$$

$$\left(\frac{W}{L}\right) = 10 ; V_T = 1V$$

$$V_{GS} = 1.5V$$

$$I_D = \frac{1}{2} \left(100 \frac{\mu A}{V^2} \right) \cdot 10 \cdot (0.5V)^2$$

$$= 125 \mu A$$

$$\Rightarrow V_{DS} = V_{DD} - I_D R_L = 5 - (0.125)(10k) = 3.75V$$

$$g_m = \frac{2I_D}{V_{GS} - V_T} = \frac{0.25mA}{0.5} = 0.5mS$$

$$\Rightarrow \text{inc. gain} = -g_m R_L = -5$$

Swing limits :

triode (+ve Hc)

$$V_G = 1.5V + V_A \sin \omega t$$

$$V_D = 3.75V - 5 V_A \sin \omega t$$

for triode limit, $V_D = V_G - V_T$

$$3.75 - 5 V_A = 1.5 + V_A - 1$$

$$\Rightarrow V_A = \frac{3.25}{6} \approx 541.67 mV (= V_{Amax})$$

cut-off (-ve HC)

$I_D = 0$ at -ve peak

$$I_D = 125 \mu A + g_m V_A \sin \omega t$$

$$\Rightarrow V_A = \frac{125 \mu A}{0.5 \text{ ms}} = 250 \text{ mV} \\ (= V_{A, \max})$$

$\therefore$ max V_A for no dipping = 250 mV

normally, cut off is specified by

$$I_D = 0 \Rightarrow V_{GS} \leq V_T$$

$\therefore$ limit of cut-off region is

$$V_{GS} = V_T$$

$$V_{GS1} - V_{A, \max 2} = V_T$$

$$\Rightarrow V_{A, \max 2} = V_{GS1} - V_T = 1.5 \text{ V} - 1 \text{ V} \\ = 0.5 \text{ V}$$

whereas we calculated $V_{A, \max 2} = 0.25 \text{ V}$

Where is the discrepancy?