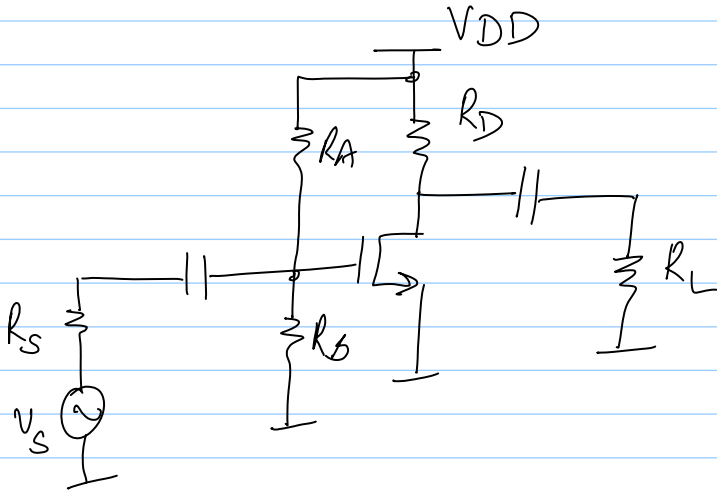


28.8.12

Lec 14



We know

- * How this ckt came about
- * Gain
- * Swing limits

Issues

- * Non-linearity $\rightarrow$ swing limits
- * ∞ caps $\rightarrow$ large caps would do
- * Tolerances : e.g. $R_A = 1.5M\Omega \pm 5\%$

M_1 :

M_n , C_{ox} , $\frac{W}{L}$, V_T

$\rightarrow$ Vary with
* ambient conditions (temp. etc.)
* time

$\rightarrow$ Cannot guarantee $V_{T1} = V_{T2}$
for M_1 & M_2 , for example
i.e. random variations in device
properties

If V_T changes $\Rightarrow I_D$ will change,
 V_{DSAT} etc. will also change

On an IC $\Rightarrow$ multiple copies of same devices have same properties
 $\rightarrow$ but change over different IC fabrications


$\rightarrow$ Ratios of like components vary similarly

e.g. $R_A = 1.5 M\Omega$, $R_B = 3.5 M\Omega$

If $R_A \rightarrow +10\%$, $R_B \rightarrow +10\%$.

$\Rightarrow \frac{R_B}{R_A}$ varies much lesser

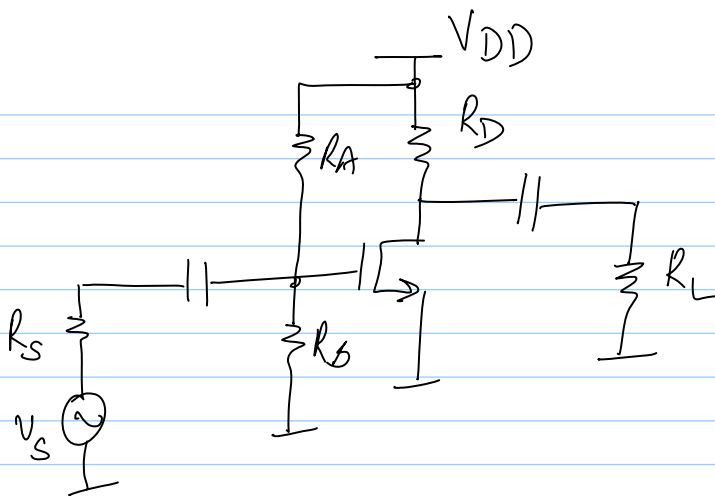Ratios of similar components well controlled than 10%.



Problems

- 1) Bias current varies with V_T
 $\Rightarrow$ Swings & inc. gain dependent on V_T

$\rightarrow$ V_{AS} is fixed, but V_T varies



Solutions:

- 1) If we know V_T , make V_{AS} track V_T change i.e. make $(V_{AS} - V_T)$ constant based on current we want

So far: apply V_{as} , create I_D based on V_T etc.

Now: figure out what V_{as} is to be applied for a certain I_D

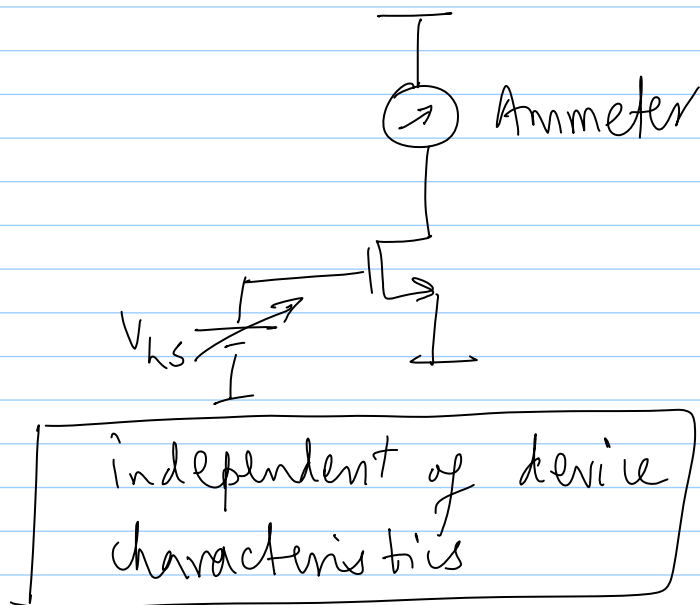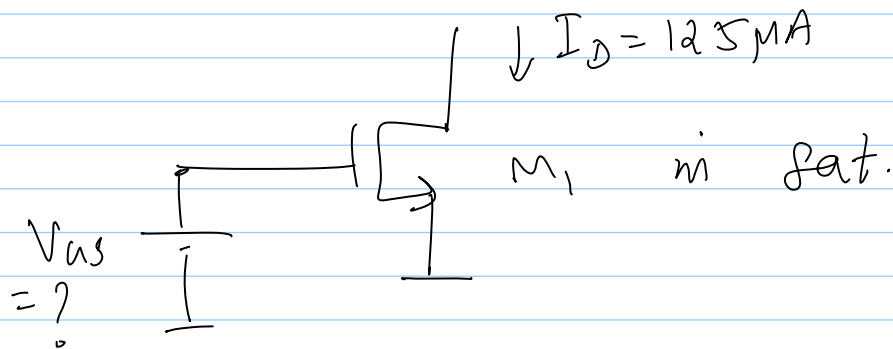e.g. $I_D = 100 \mu A$, $V_{as} - V_T = 0.5 V$



* Apply V_{as}

* measure I_D

* If $I_D > 100 \mu A$,

$V_{as} > V_{as1}$,

$\Rightarrow$ reduce V_{as}

* If $I_D < 100 \mu A$,

$V_{as} < V_{as1}$,

$\Rightarrow$ increase V_{as}

$\Rightarrow$ Negative Feedback

open loop method :


$V_{as1} \rightarrow I_{D1}$
 $V_{as2} \rightarrow I_{D2}$) solve device equations to get I_{nloz} & V_T

$100\mu A \Rightarrow$ reference quantity

actual $I_D \Rightarrow$ output quantity

use the error $(I_D - 100\mu A)$ - difference between output & reference to tweak input (V_{as})

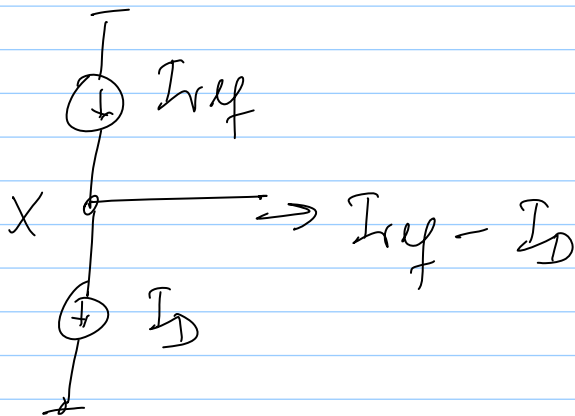$(I_{ref} - I_D) =$ comparing I_{ref} & I_D



$I_{ref} = I_D$, V_x can be anything, but since no charge is added/removed, V_x does not change!

* I_f $I_{ref} > I_D$, $V_x \uparrow$ with time

* $I_{ref} < I_D$, $V_x \downarrow$ with time