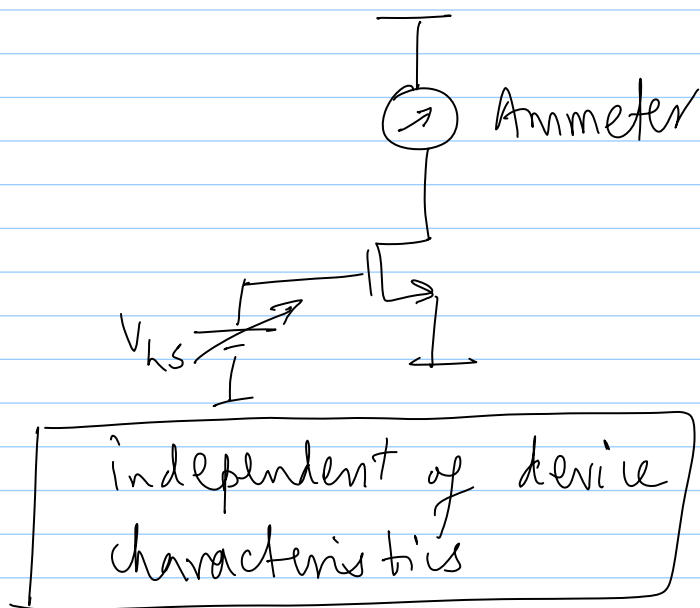


30-8-12

Lec 15



* Apply V_{ds}

* measure I_D

* If $I_D > 100\mu A$,

$V_{ds} > V_{ds}$,

$\Rightarrow$ reduce V_{ds}

* If $I_D < 100\mu A$,

$V_{ds} < V_{ds}$,

$\Rightarrow$ increase V_{ds}

$\Rightarrow$ Negative Feedback

open loop method:


$V_{ds1} \rightarrow I_{D1}$
 $V_{ds2} \rightarrow I_{D2}$) Solve device equations to get I_{nlo} & V_T

$100\mu A \Rightarrow$ reference quantity (I_{ref})

actual $I_D \Rightarrow$ output quantity

use the error $(I_{ref} - I_D) =$ difference between reference & output to tweak input (V_{ds})

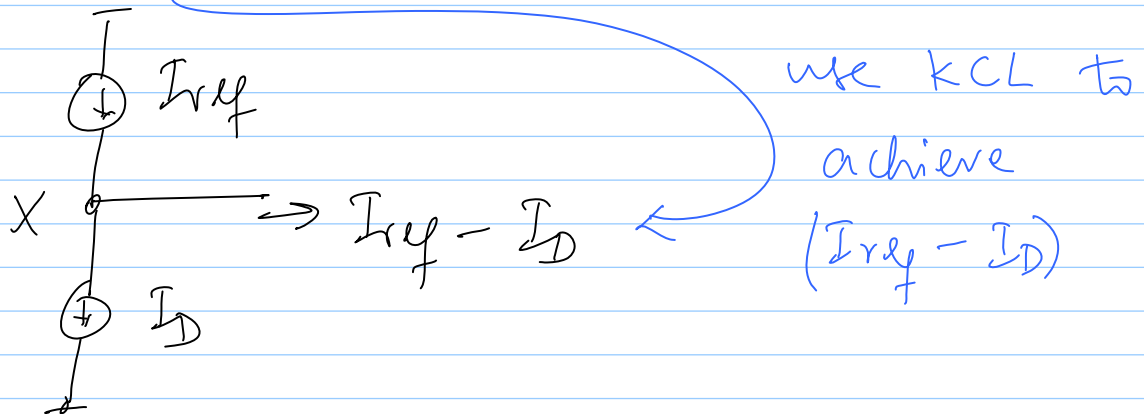
$(I_{ref} - I_D)$ = comparing I_{ref} & I_D



If $I_{ref} = I_D$, V_x can be anything,
but since no charge is added/removed,
 V_x does not change!

* If $I_{ref} > I_D$, $V_x \uparrow$ with time

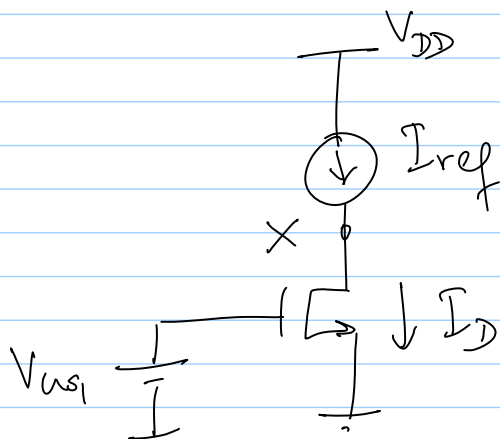* If $I_{ref} < I_D$, $V_x \downarrow$ with time




* $I_D > I_{ref} \Rightarrow V_x \downarrow$
 $\Rightarrow$ reduce V_{as1}

* $I_D < I_{ref} \Rightarrow V_x \uparrow$
 $\Rightarrow$ increase V_{as1}

$\Rightarrow V_x$ & V_{as} move in same direction

⇒ connect G to X!

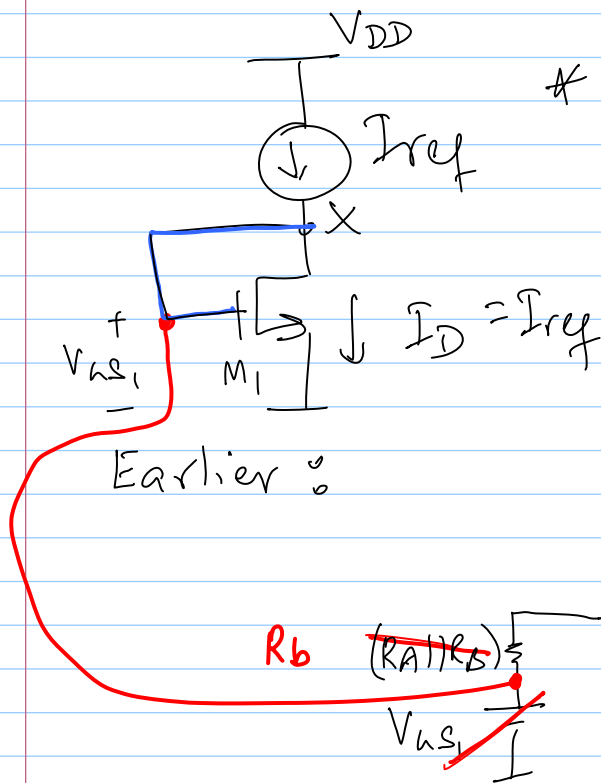


* Verify that device is still in saturation

$$V_D = V_a \Rightarrow \underline{\underline{V_D > V_a - V_T}}$$

M_1 & M_2 have same $\mu_n C_{ox}$ & V_T on an IC

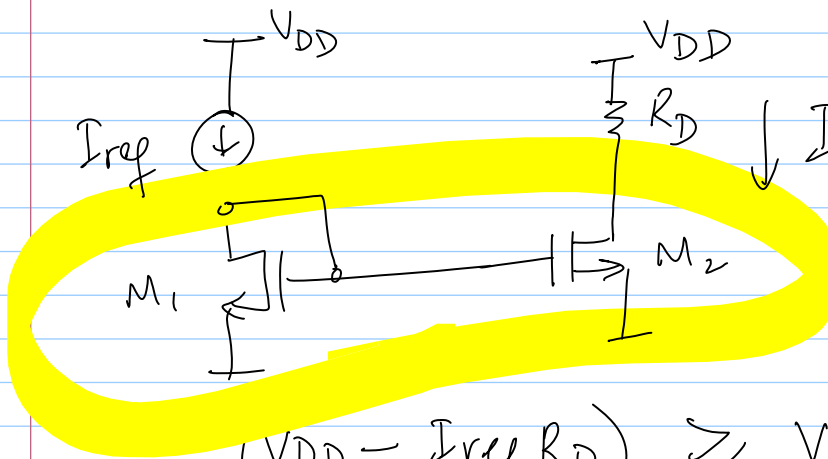* No current through new connection
 ⇒ no dc drop across R_b
 → V_x remains @ V_{gs1}




$I_{D2} = I_{ref}$ provided R_D is such that M_2 is still in sat.

$$(V_{DD} - I_{ref} R_D) \geq V_{gs1} - V_T \text{ for } M_2 \text{ to be in sat.}$$

→ CURRENT MIRROR

e.g.

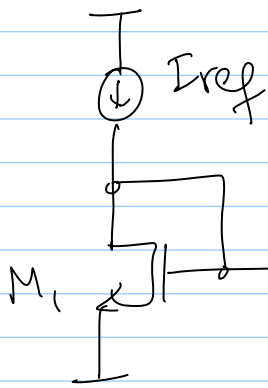

Assume V_{D2} , V_{D3} , V_{D4} are large enough to keep M_2, M_3, M_4 in sat.

identical MOSFETs