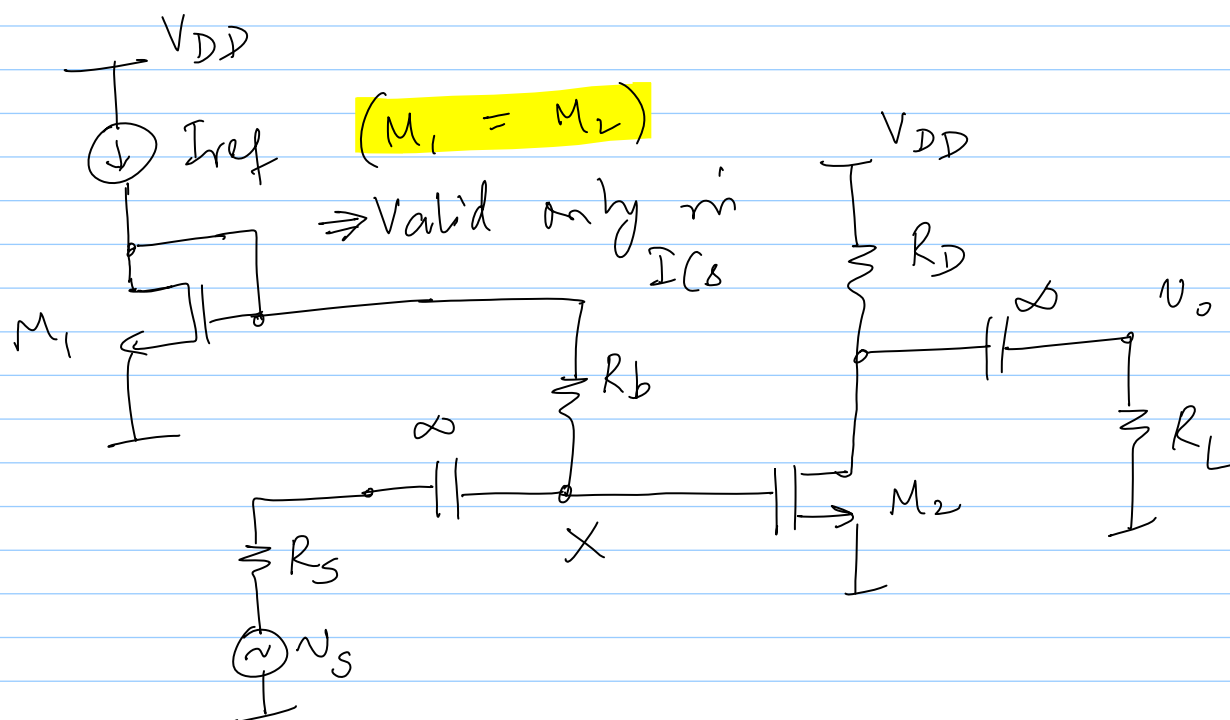



4-9-12


Lec 16



$$\frac{v_x}{v_s} = ? ; \quad \frac{v_o}{v_s} = ?$$

Incremental eq.ckt :

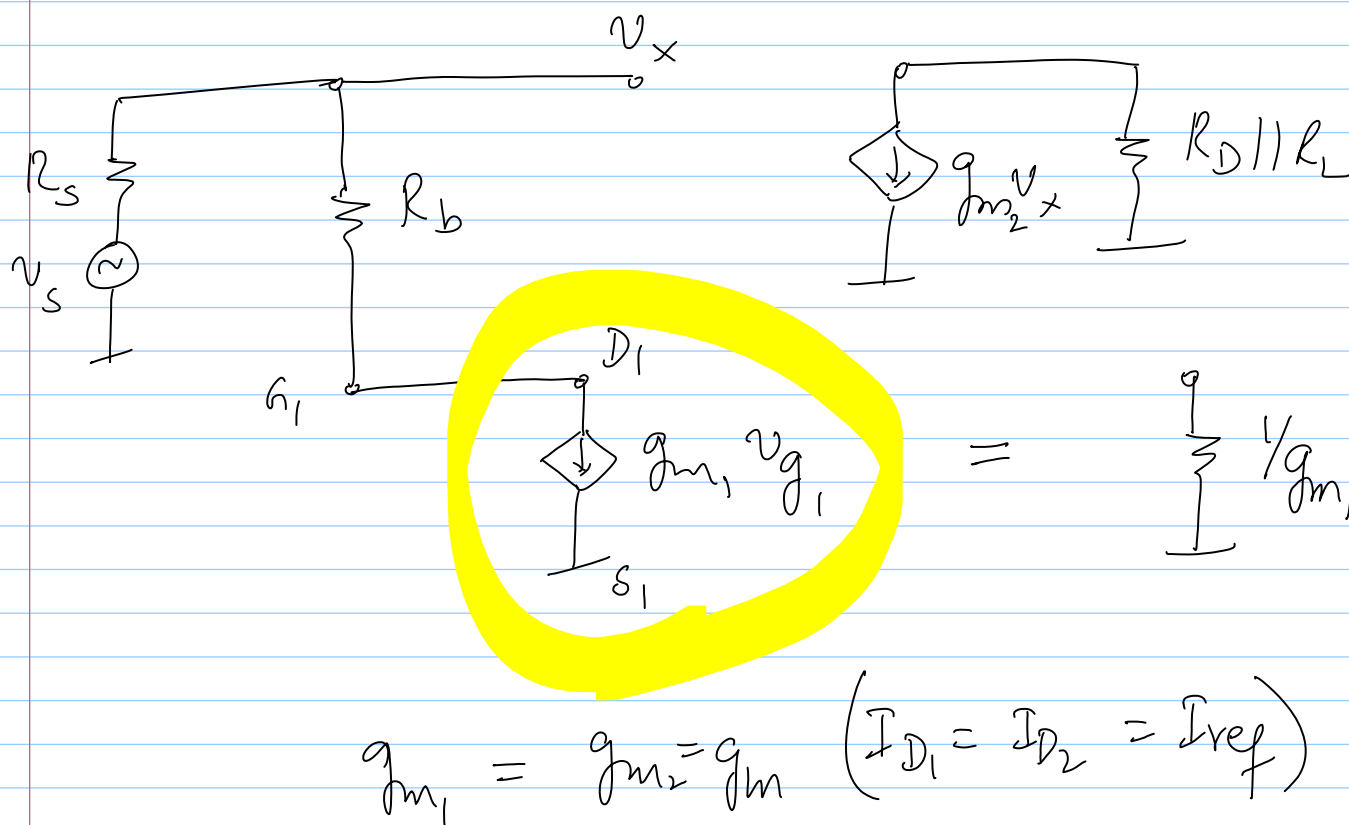

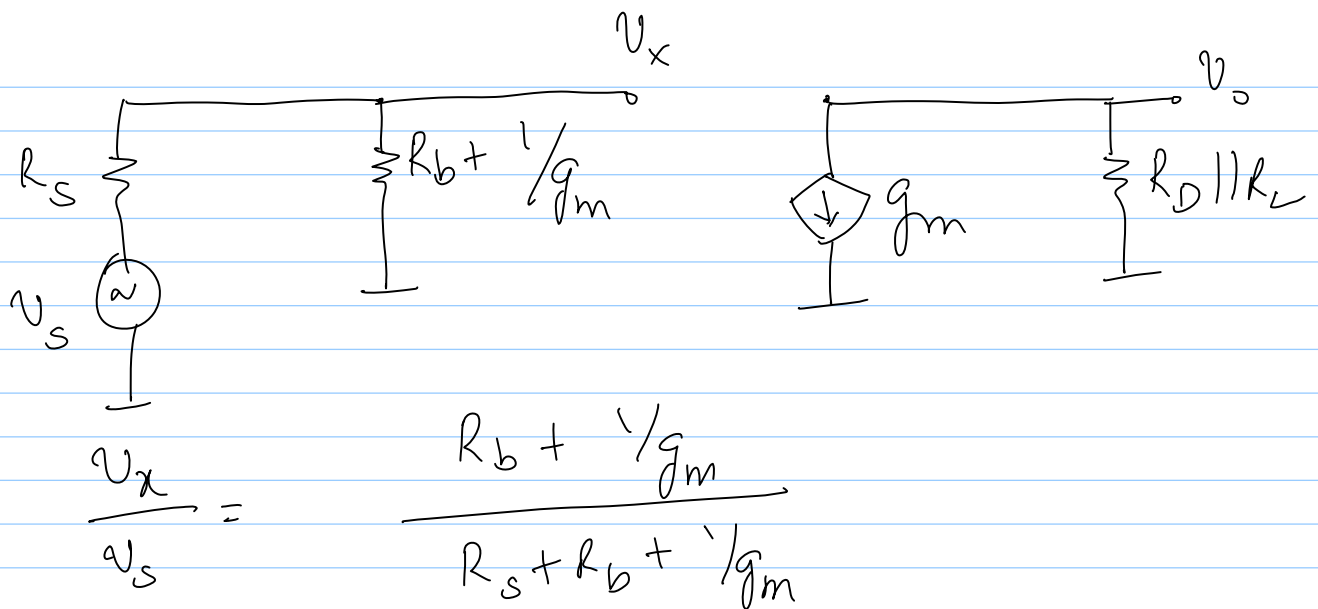

$$\frac{v_o}{v_s} = - \left(\frac{R_b + 1/g_m}{R_s + R_b + 1/g_m} \right) \cdot g_m \cdot (R_D \parallel R_L)$$

* We usually choose $R_b \gg R_s$
(as before)



$$\Rightarrow R_b + 1/g_m \gg R_s$$

$$\Rightarrow \frac{v_o}{v_s} \approx -g_m (R_D \parallel R_L)$$

* Swing limits = same as before
because $\begin{cases} I_D = \text{same as before} \\ V_D = \text{"} \end{cases}$

* If $V_{T1,2}$ changes $\Rightarrow$ gain is constant

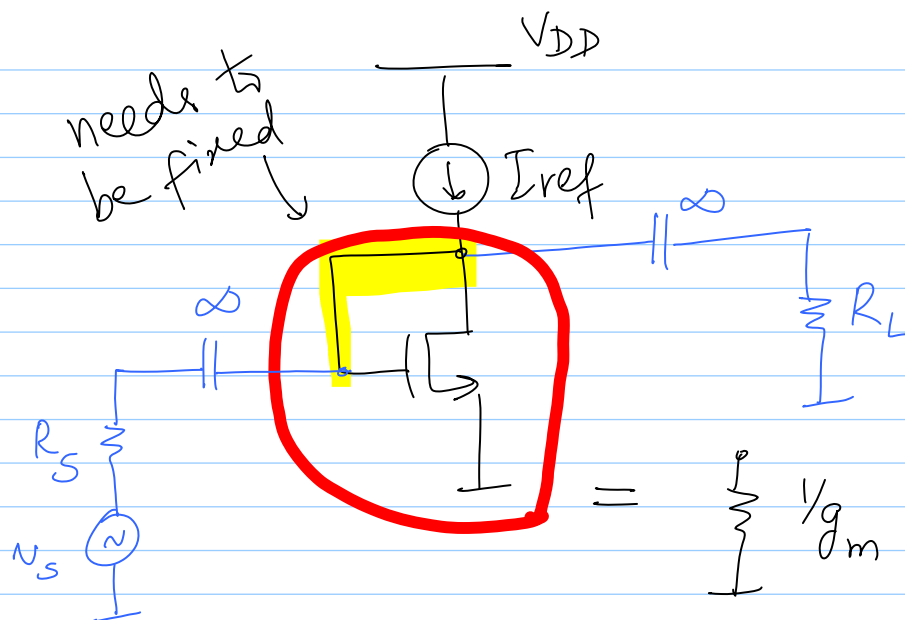
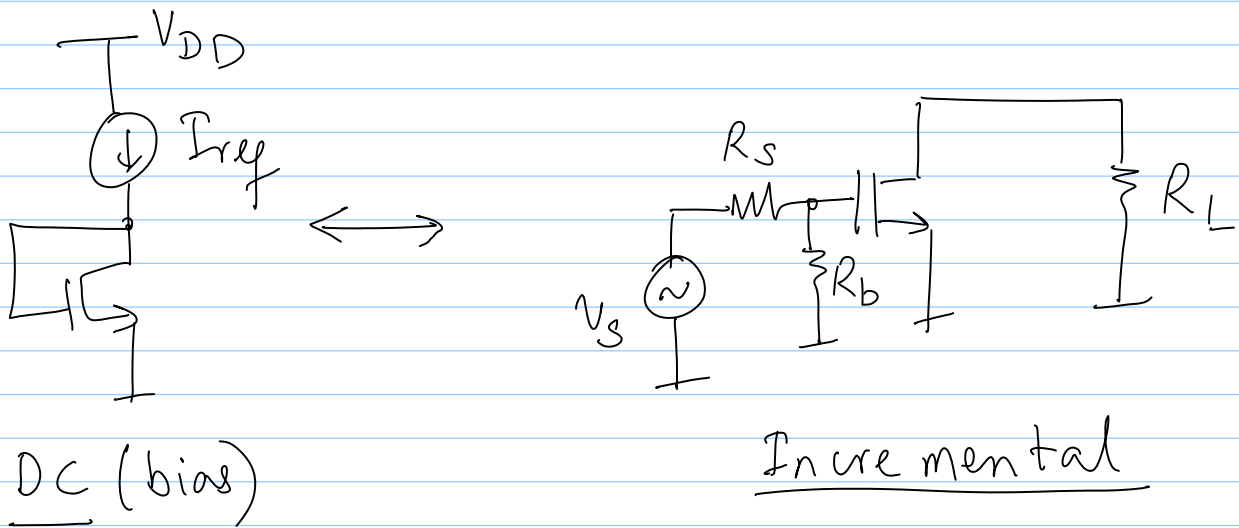
* Can this be done without using an extra transistor?



$$\text{gain} = \frac{R_L \parallel \frac{1}{g_m}}{R_L \parallel \frac{1}{g_m} + R_s} \quad \text{not what we want!}$$


* We want to decouple D&G for incr. picture

1)

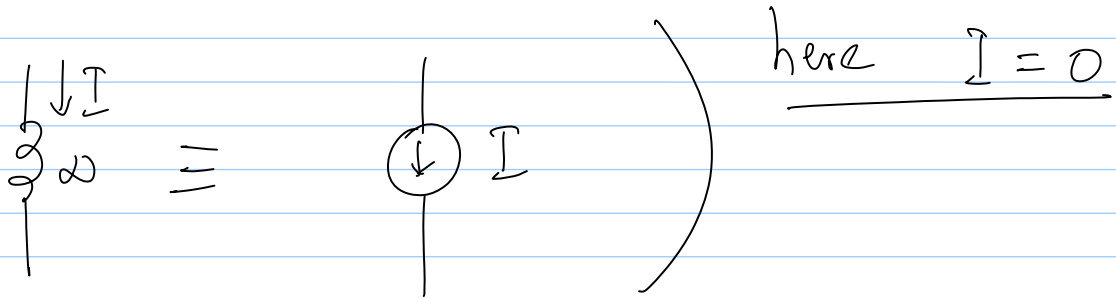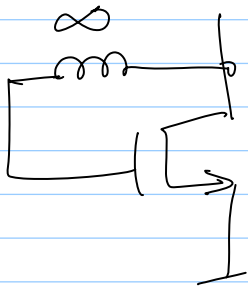



$\Rightarrow$ Impractical (L in ICs are very large)

2)

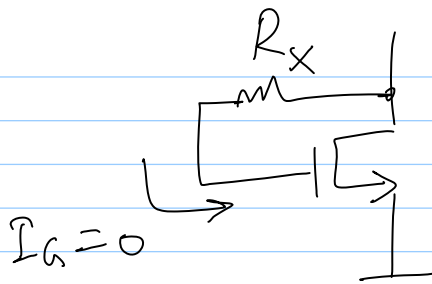

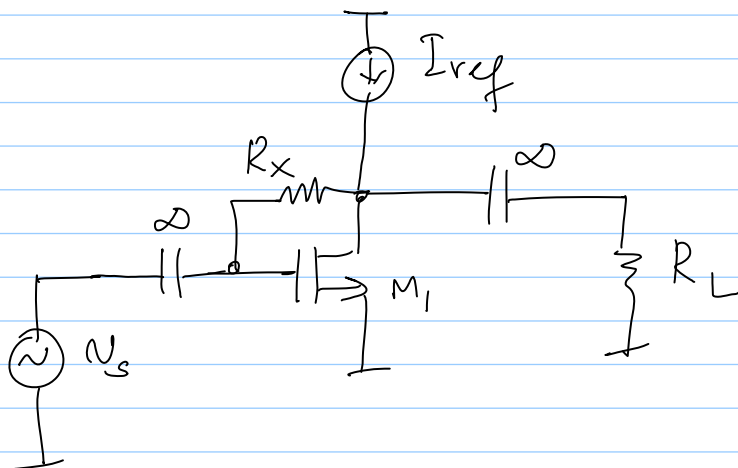* R_x is very large
* voltage drop across R_x is zero



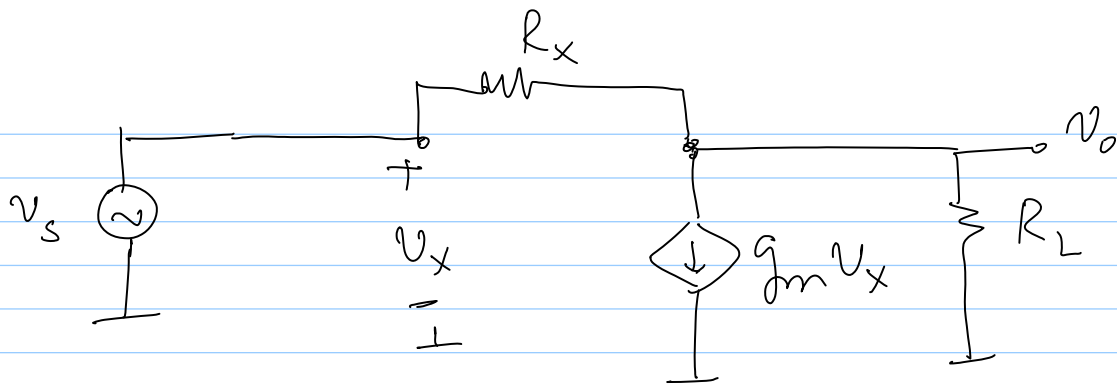

$$v_x = v_s$$

$$\frac{v_s - v_o}{R_x} = g_m v_s + \frac{v_o}{R_L}$$

$$v_s (G_x - g_m) = v_o (G_x + G_L)$$

$$\Rightarrow \frac{v_o}{v_s} = \frac{G_x - g_m}{G_x + G_L}$$

$$\frac{v_o}{v_s} = -\frac{g_m}{G_L} \left[\frac{1 - G_x/g_m}{1 + G_x/G_L} \right]$$

* $g_m > G_L$ for large gain

* $G_x \ll G_L \Rightarrow G_x \ll g_m$

$\therefore R_x = \text{large} \Rightarrow R_x \gg R_L \Rightarrow \text{gain} \approx -g_m R_L$

* Swing limits = lower

$\rightarrow I_D = \text{same as before} \Rightarrow \text{cut off limit is the same}$

$\rightarrow \text{voltage across } R_x = 0; V_D = V_G$