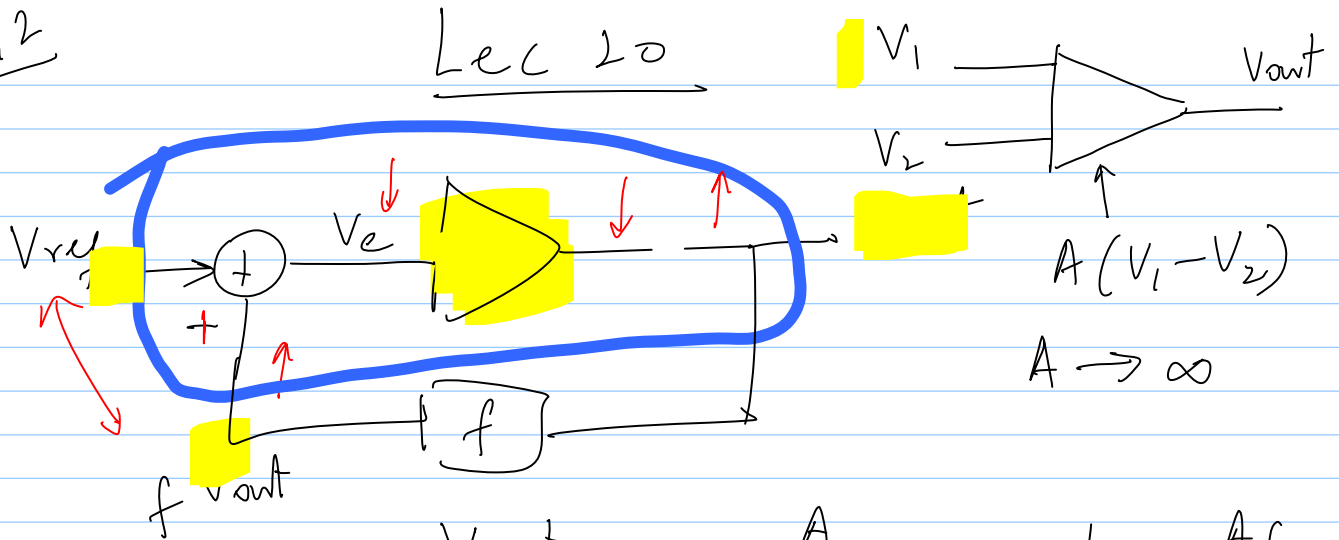


14-9-12

Lec 20



$$\frac{V_{out}}{V_{ref}} = \frac{A}{1 + Af} = \frac{1}{f} \cdot \frac{Af}{1 + Af}$$


$A_f \equiv \text{Loop Gain}$



$\frac{A}{1 + Af} \equiv \text{CLOSED LOOP GAIN}$

$$V_e = 0$$

$$A_f \rightarrow \infty \quad (LH \rightarrow \infty)$$

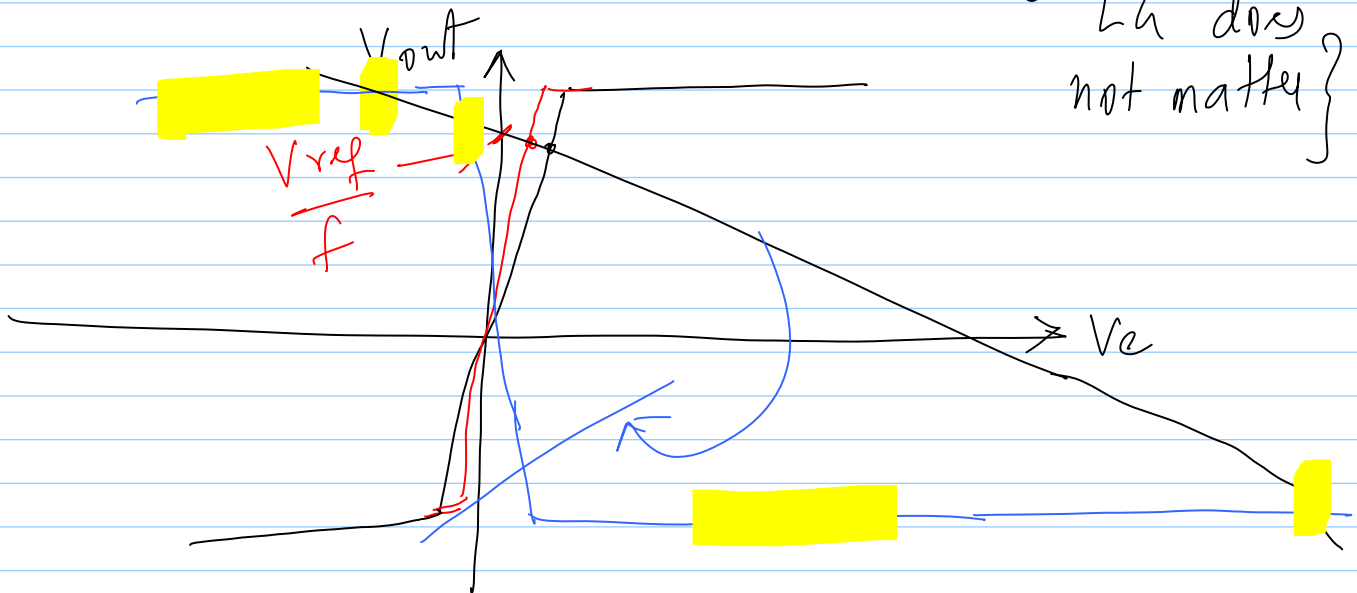$I_f \quad LH \rightarrow \infty, \quad CLG = \frac{1}{f}$ { actual value of LH does not matter }





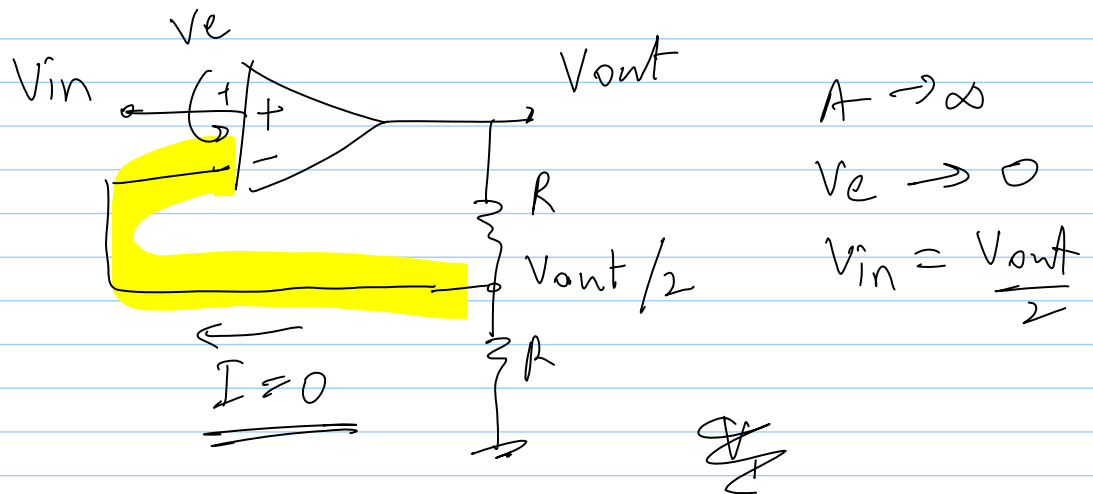
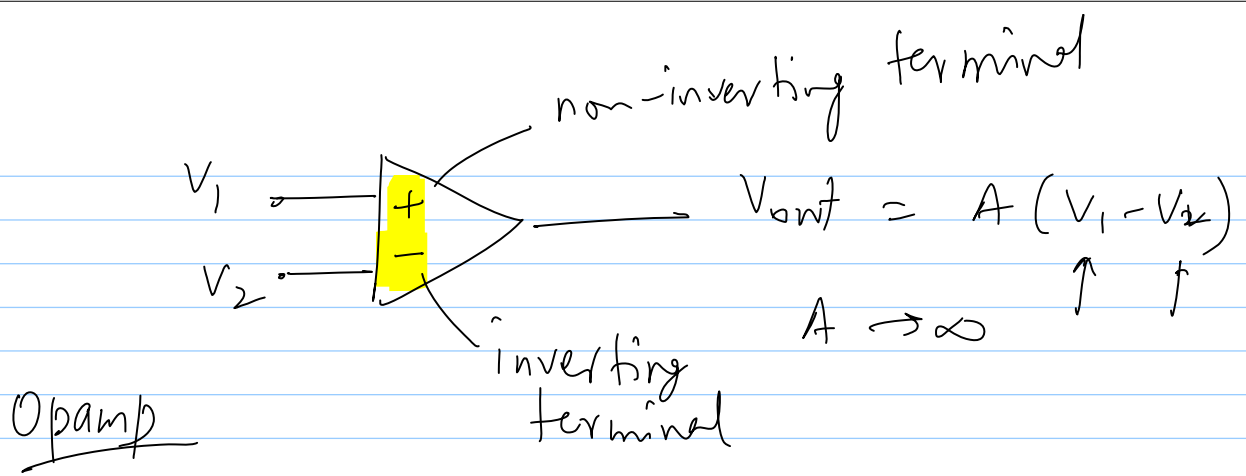


1) gain = -2

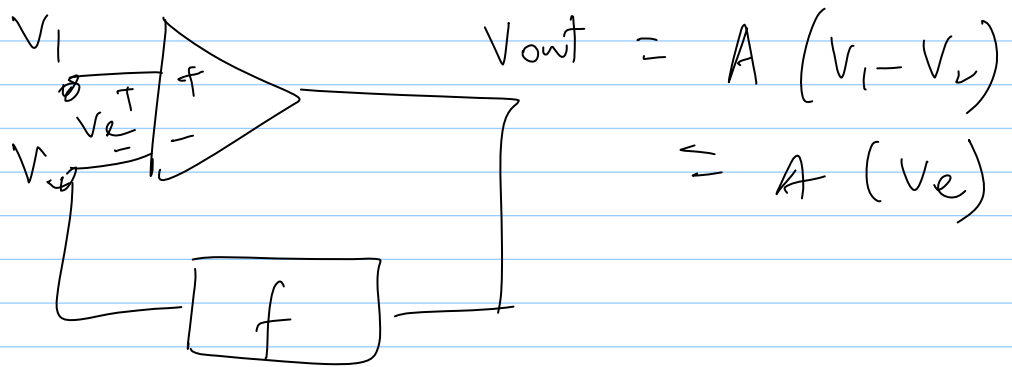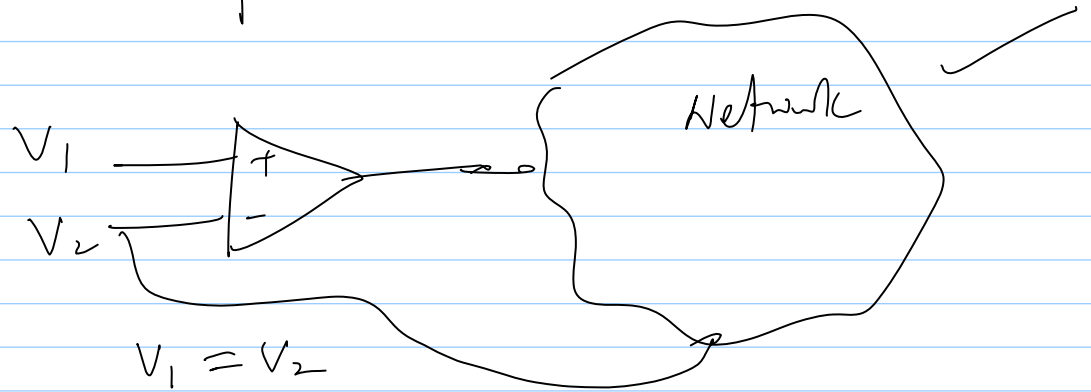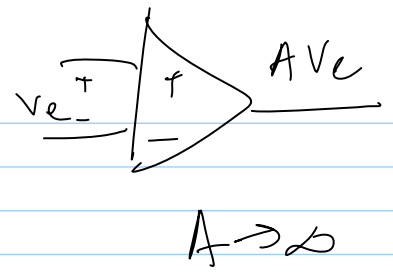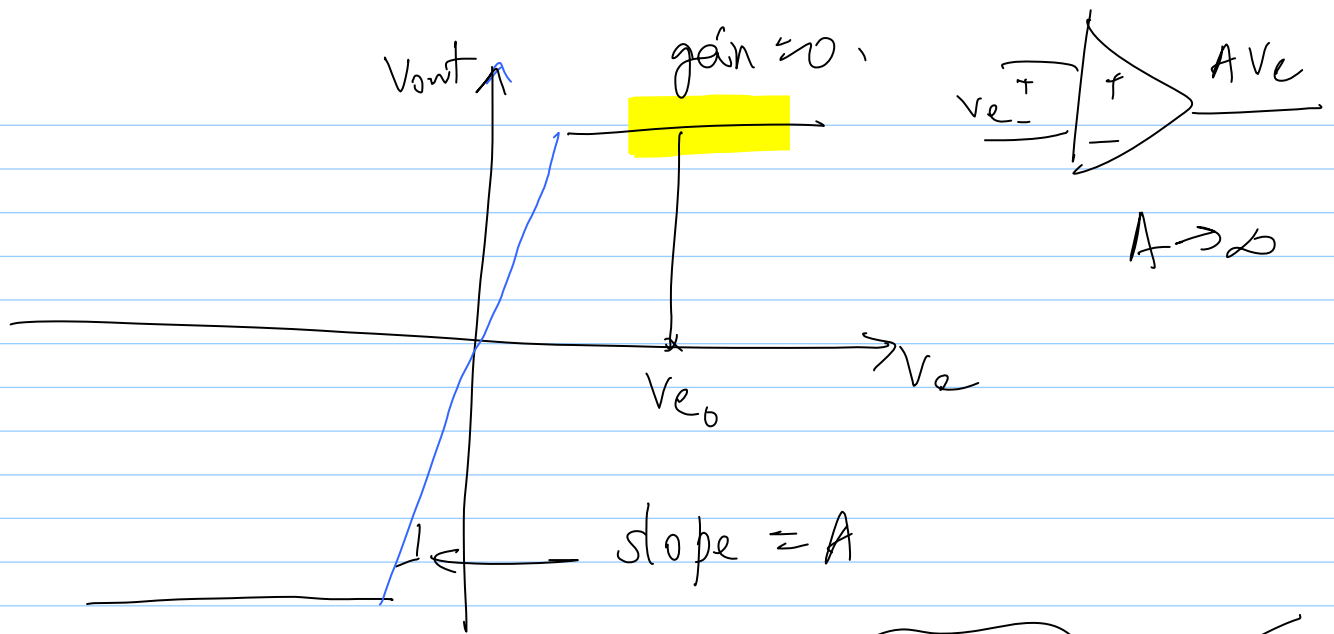2) $V_{out} = \text{man. voltage possible}$



ideal

$$V_{out} = \left(-V_{in} + \frac{V_{out}}{2} \right) \cdot A$$





$$V_{out} = A (V_1 - V_2)$$


$$= A (V_e)$$

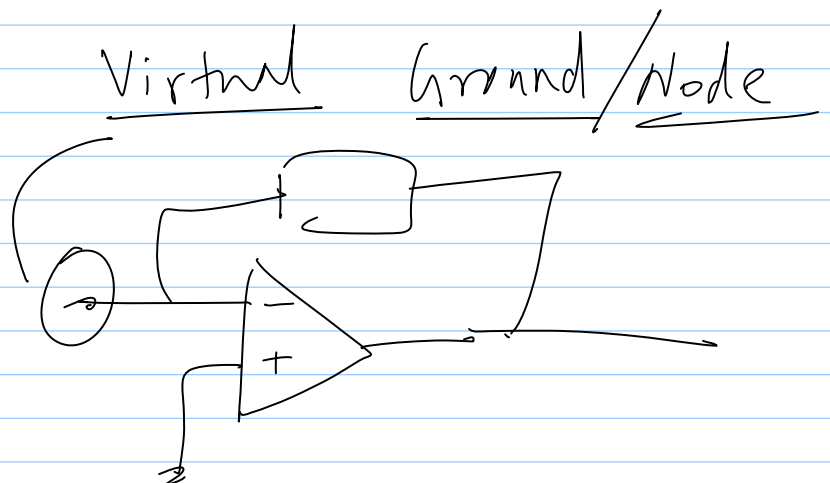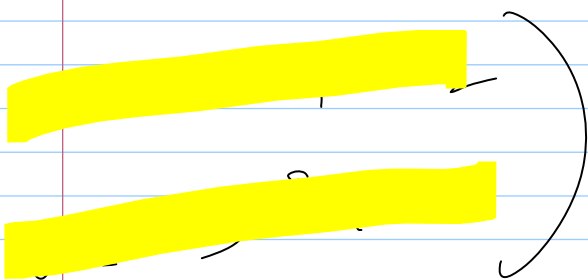

Ideal VCVS

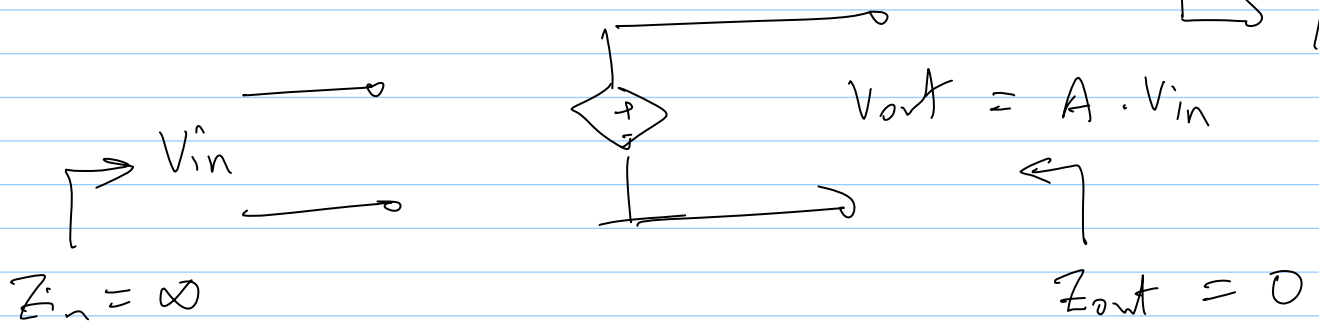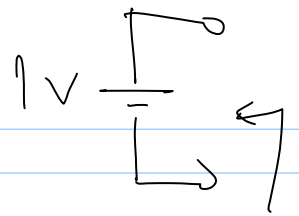

	Z_{in}	Z_{out}
VCVS	∞	0
VCCS	∞	∞
CCVS	0	0
CCCS	0	∞

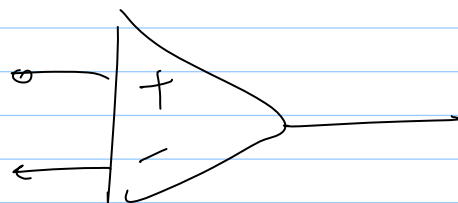

V_1

V_2

