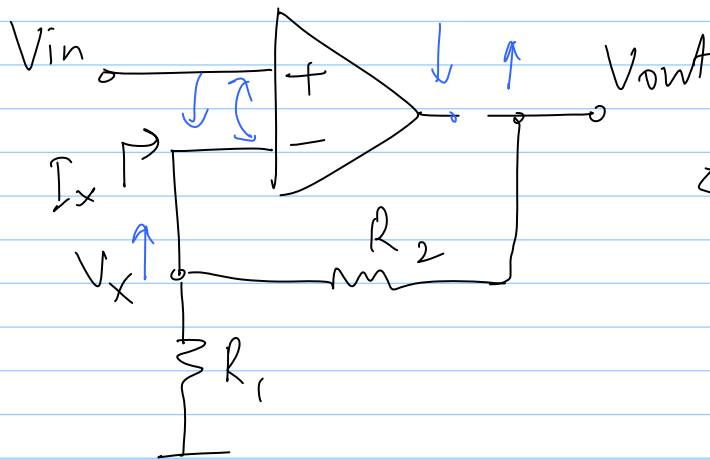


18-9-12

Lec 21

VCVS

$$V_{in}, V_{out} = A V_{in}$$



← Negative f.b.

1) $V_x = V_{in}$

2) $I_x = 0 \Rightarrow V_x = \frac{R_1}{R_1 + R_2} V_{out}$


$$V_{out} = \left(1 + \frac{R_2}{R_1}\right) V_{in}$$

Gain of 1

* $R_2 = 0$

* $R_1 = \infty$

* both $R_2 = 0$ & $R_1 = \infty$




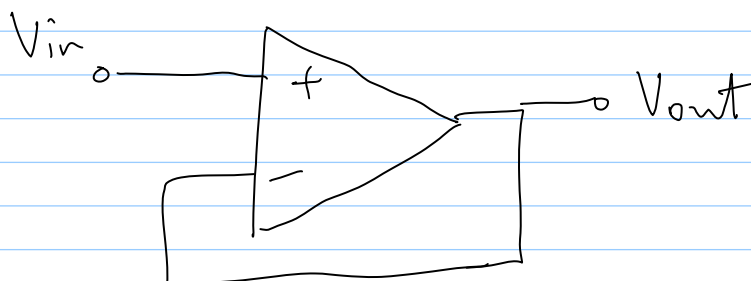




Voltage follower

$$V_{out} = V_{in}$$

CCVS $\Rightarrow Z_{in} = 0 ; Z_{out} = 0$

I_{in} ; $V_{out} = R I_{in}$

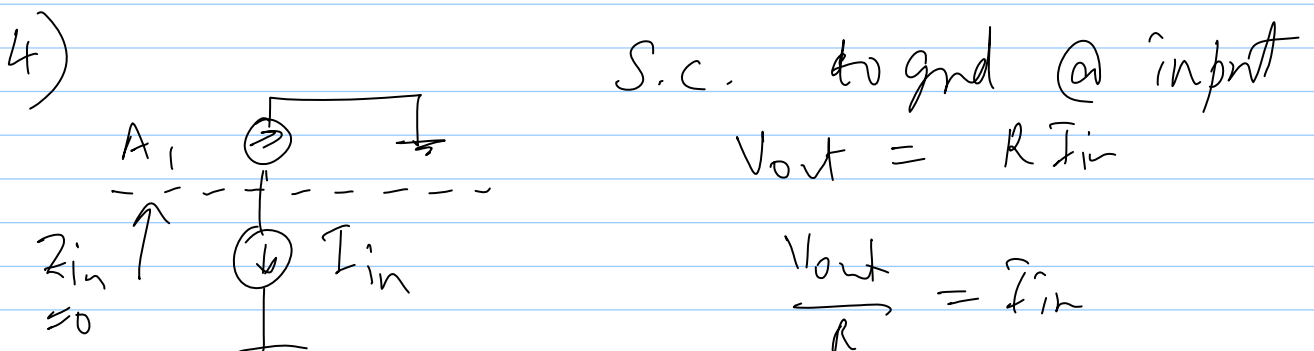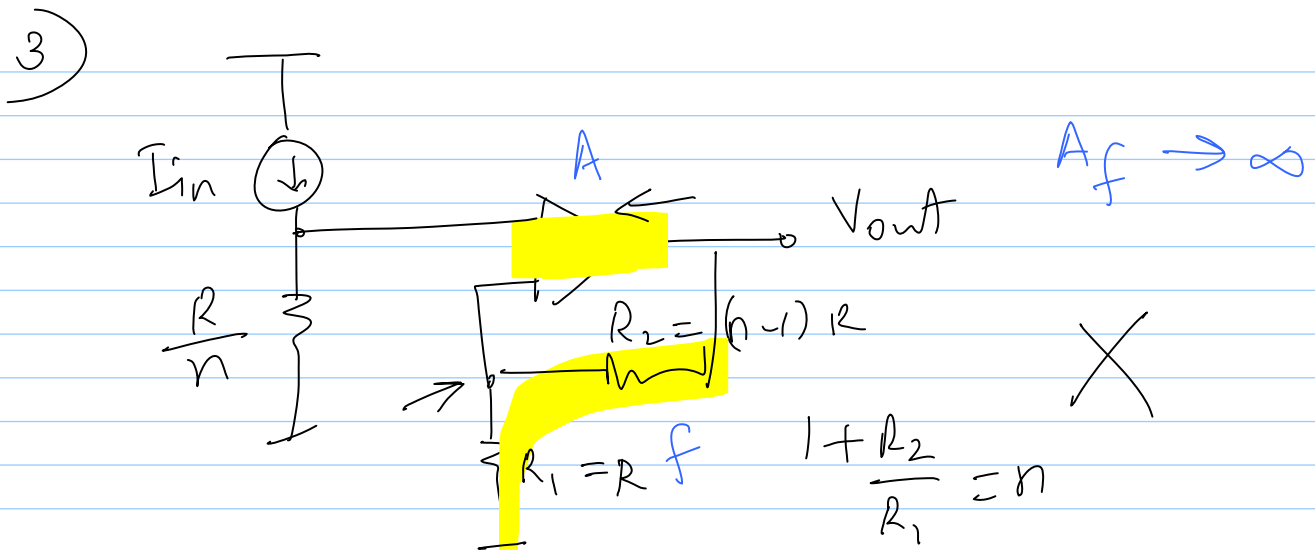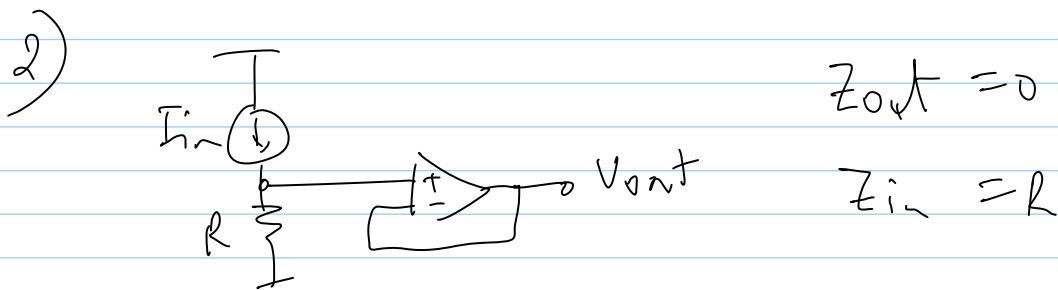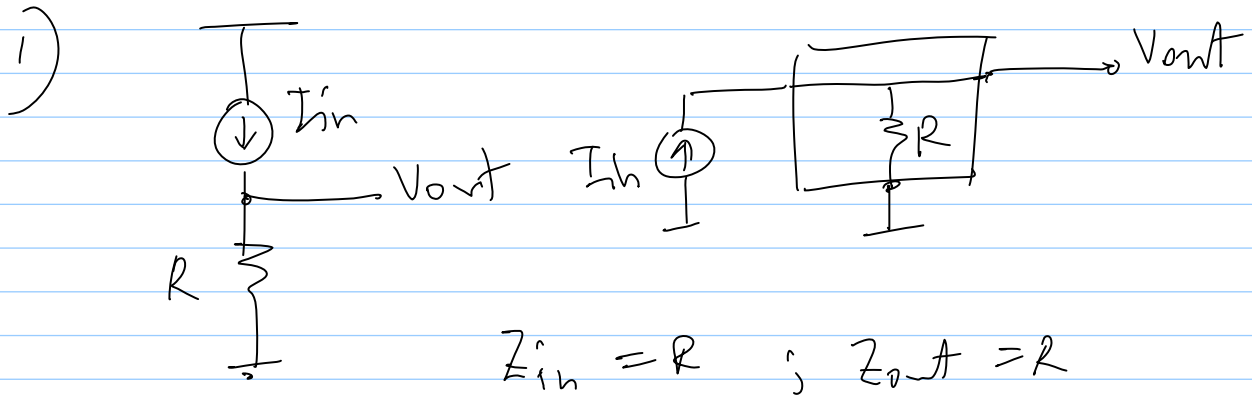

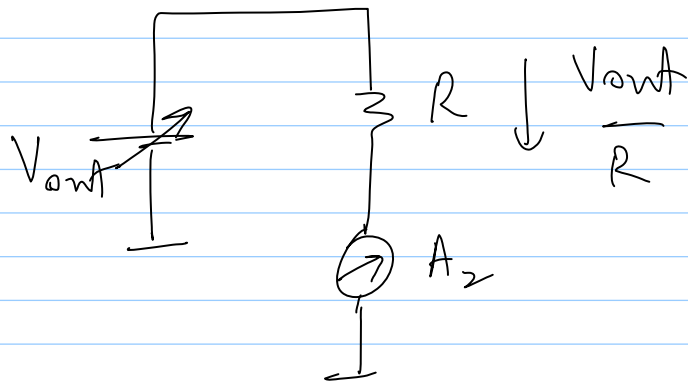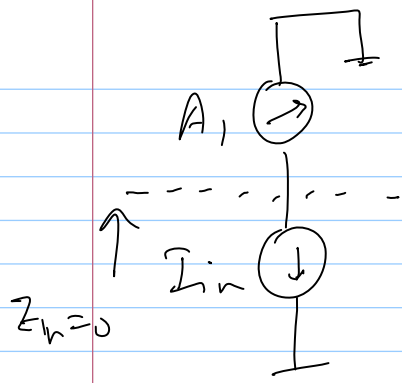


* Measure A_1, A_2

* $A_1 > A_2 \Rightarrow I_{in} > \frac{V_{out}}{R} \Rightarrow \uparrow V_{out}$

$A_1 < A_2 \Rightarrow I_{in} < \frac{V_{out}}{R} \Rightarrow \downarrow V_{out}$


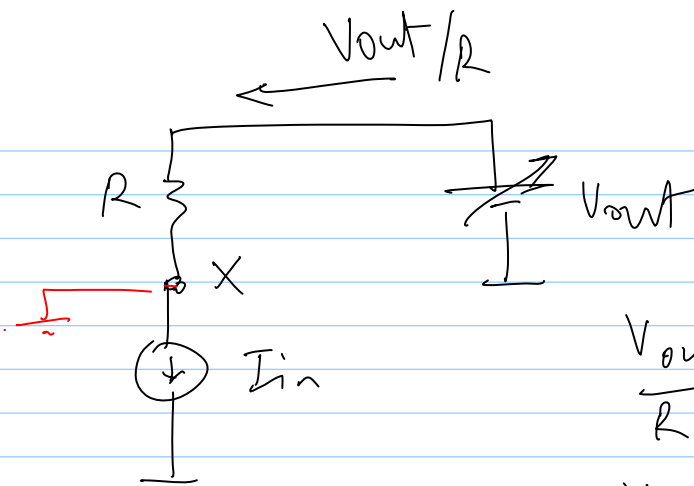
comparing $A_1 - A_2 \Rightarrow$ correct in series




$$\frac{V_{out}}{R} = I_{in}$$

$\frac{V_{out}}{R} > I_{in} \Rightarrow V_x \uparrow (\downarrow V_{out})$

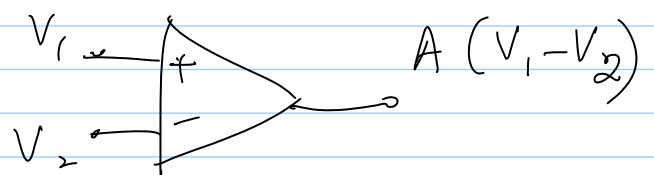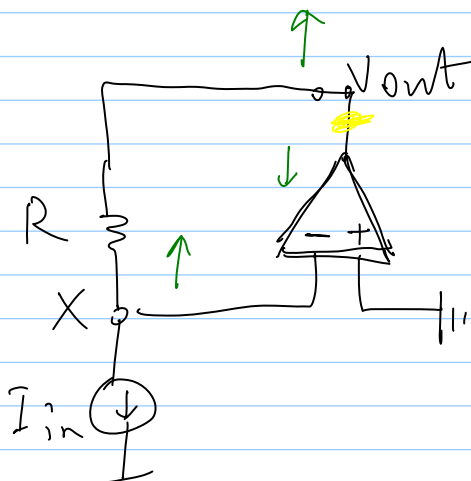$\frac{V_{out}}{R} < I_{in} \Rightarrow V_x \downarrow (\uparrow V_{out})$



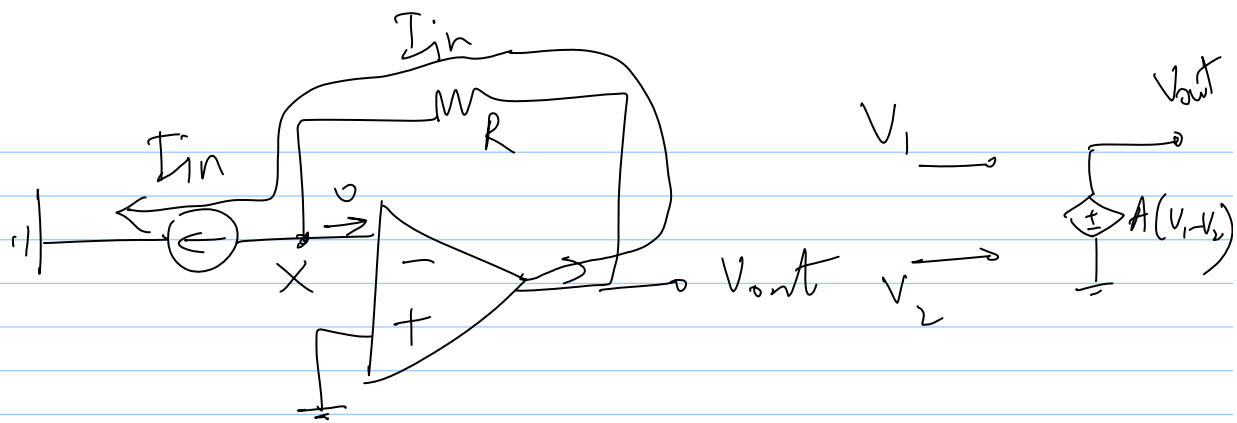



* $V_X = 0 \Rightarrow Z_{in} = 0$

* $\frac{V_{out} - V_X}{R} = I_{in} \Rightarrow \boxed{V_{out} = R I_{in}}$

* $Z_{out} = 0$


* $X = \text{Virtual ground}$

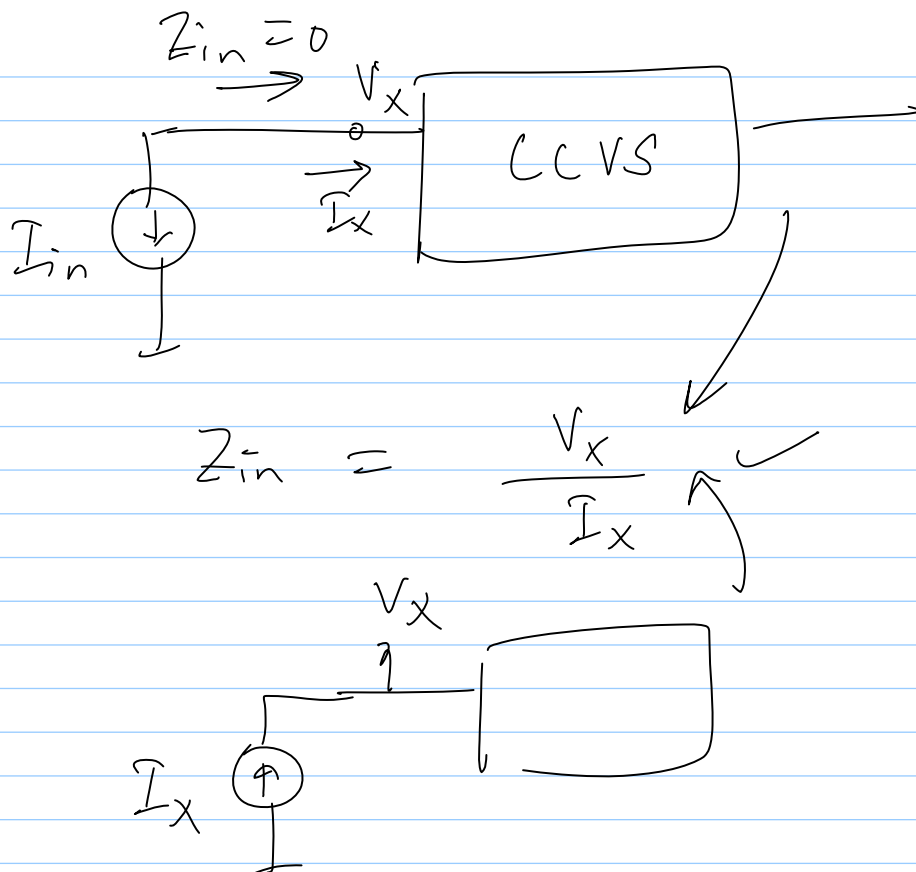

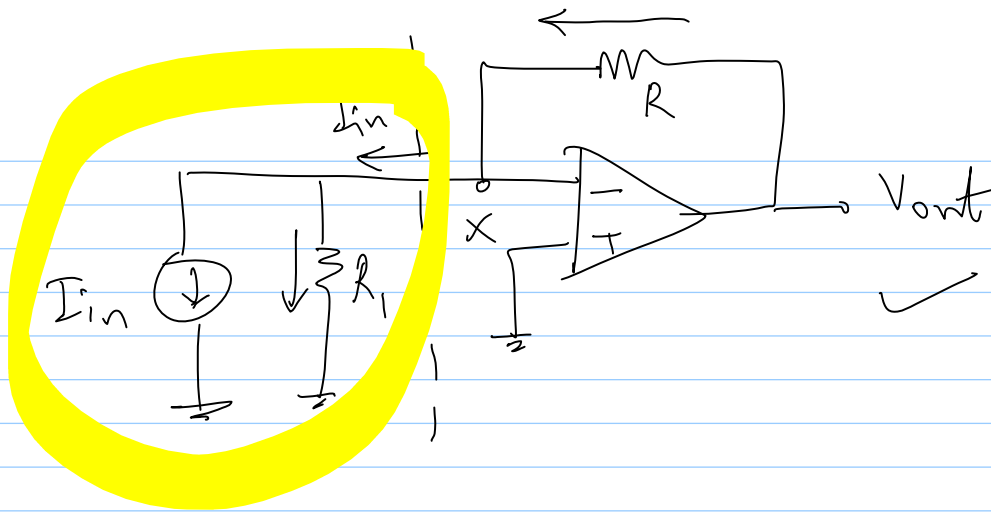

* $V_x = 0 \Rightarrow I_{R_1} = 0$) R_1 does not matter

$V_{out} = R I_{in}$

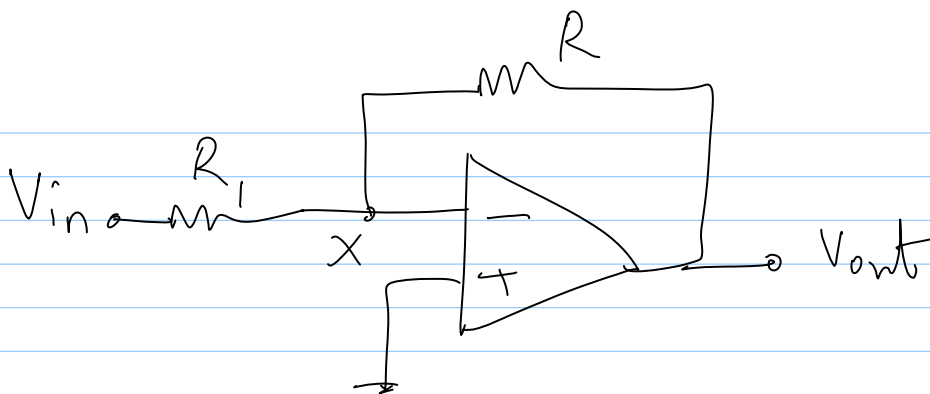

* $V_x = 0$, $I_{opamp} = 0$

$$\frac{V_{in}}{R_1} = -\frac{V_{out}}{R}$$

$$\frac{V_{out}}{V_{in}} = -\frac{R}{R_1}$$

Inverting
Amplifier