

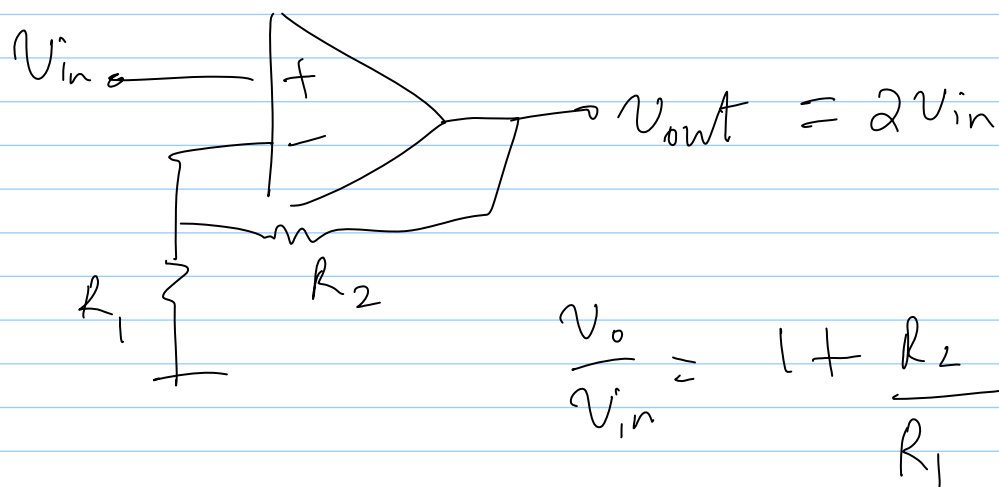


20-9-12

Lec 22

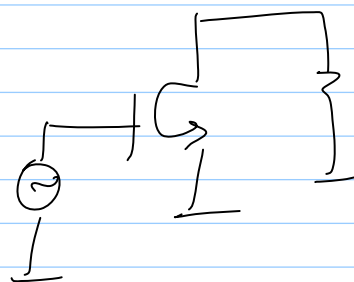



$$\frac{v_o}{v_{in}} = 1 + \frac{R_2}{R_1}$$

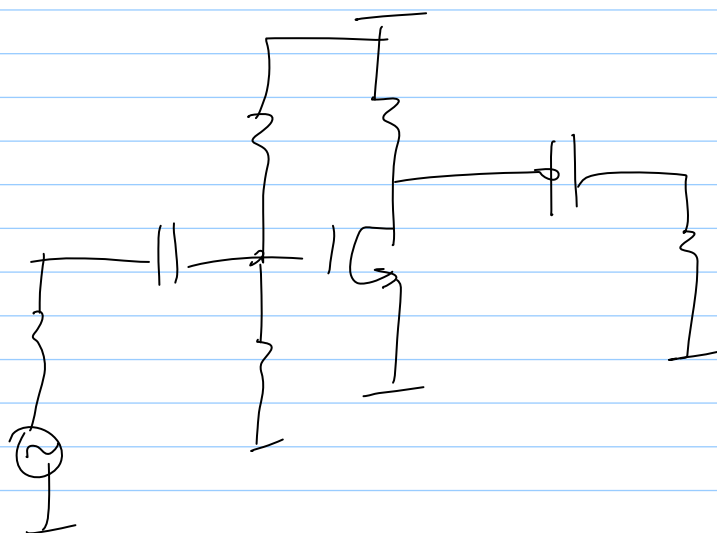

Case 1 : measure I_D
f.b. V_a

Case 2 : measure I_S
f.b. V_S

Case 3 : measure I_D
f.b. V_S

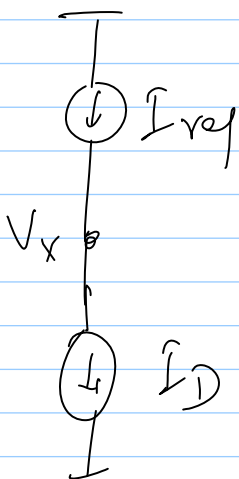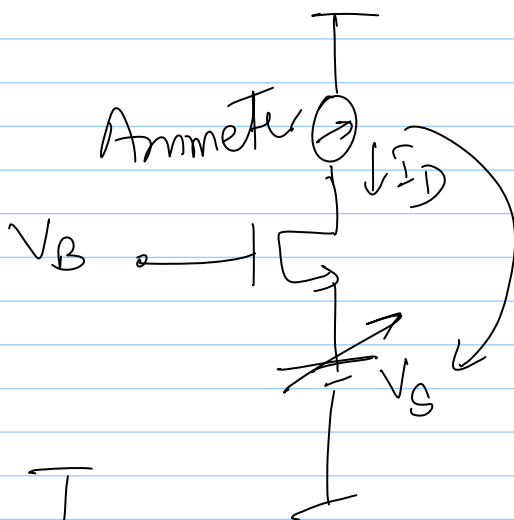

* measure I_D



* $I_D < I_{ref} \Rightarrow \begin{matrix} \uparrow V_{as} \\ \downarrow V_S \end{matrix}$

$I_D > I_{ref} \Rightarrow \begin{matrix} \downarrow V_{as} \\ \uparrow V_S \end{matrix}$


$I_D < I_{ref} \Rightarrow V_x \uparrow$

$I_D > I_{ref} \Rightarrow V_x \downarrow$

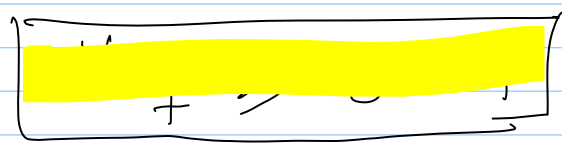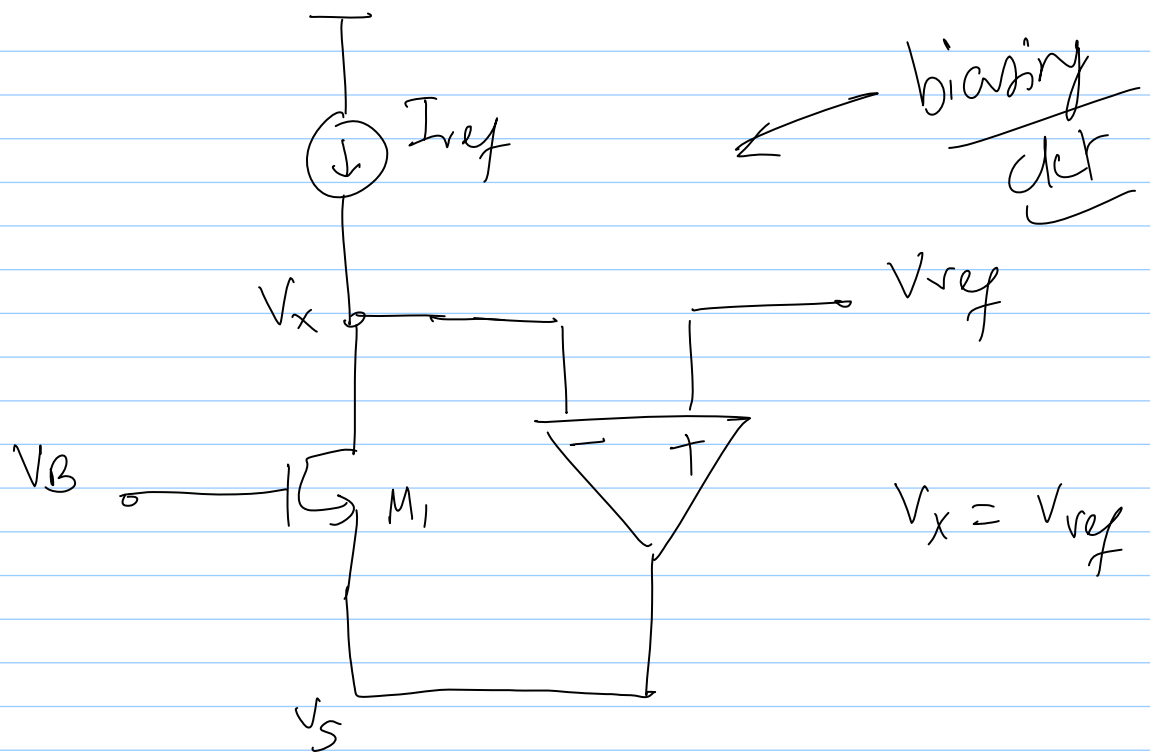$I_D = I_{ref} \Rightarrow V_x \text{ constant}$



s.t. M_1 is in sat.

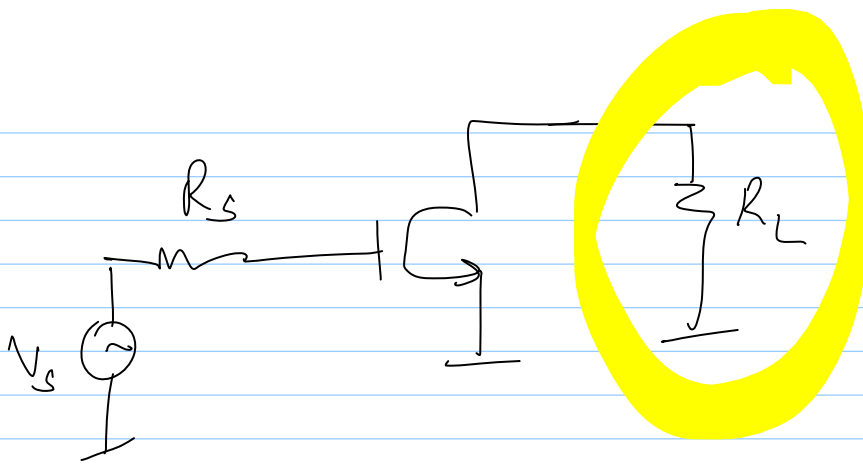

inc. eq. ckt.

