
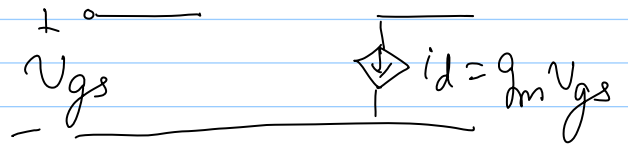


25-9-12



Lec 24

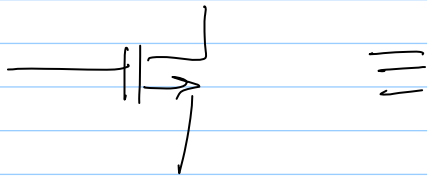


$$g_m \rightarrow \infty$$


VCVS $Z_{in} = \infty$, $Z_{out} = 0$

$$v_{in} = v_{out}$$

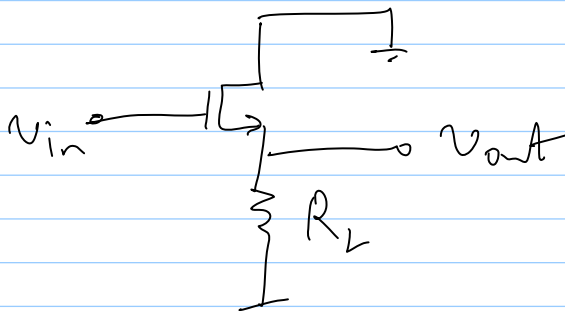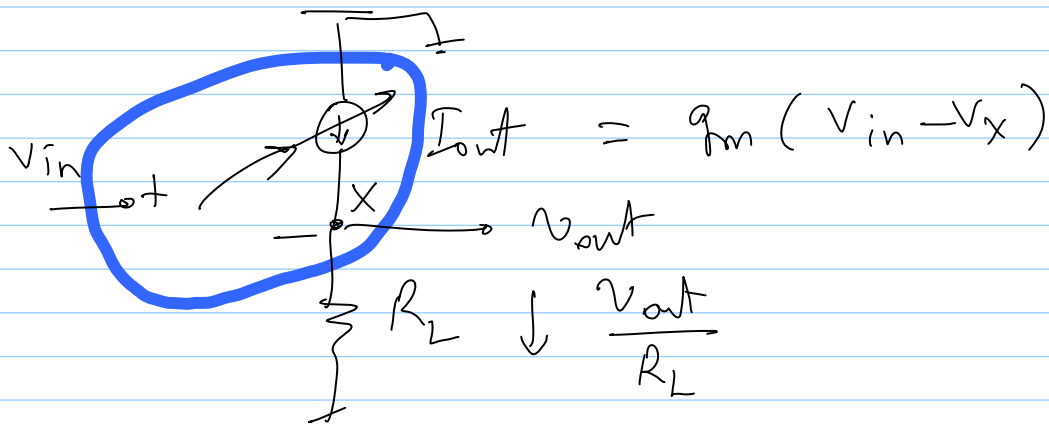


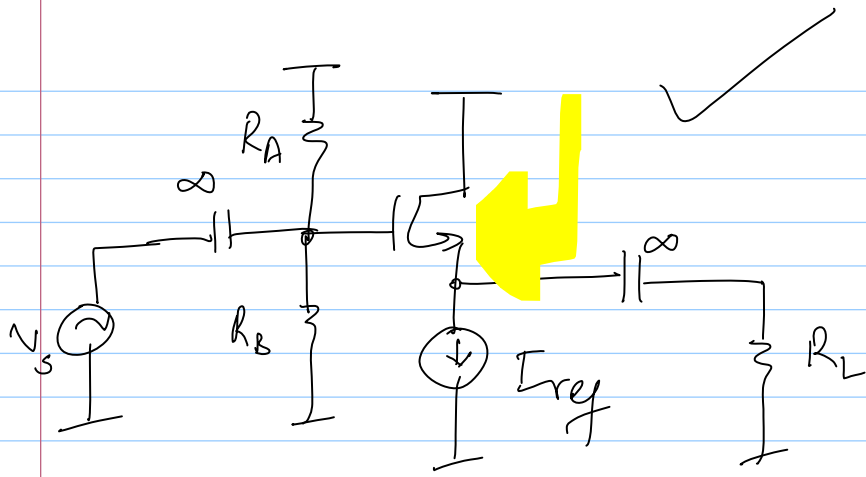


Common
Drain
Amplifier

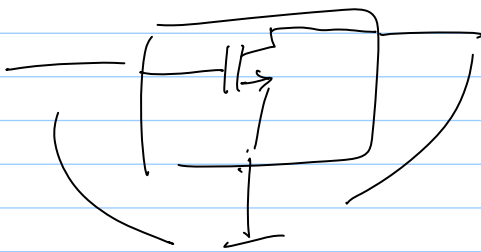

C.S.A.

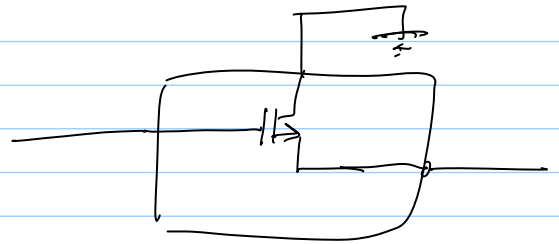



C.D.A.

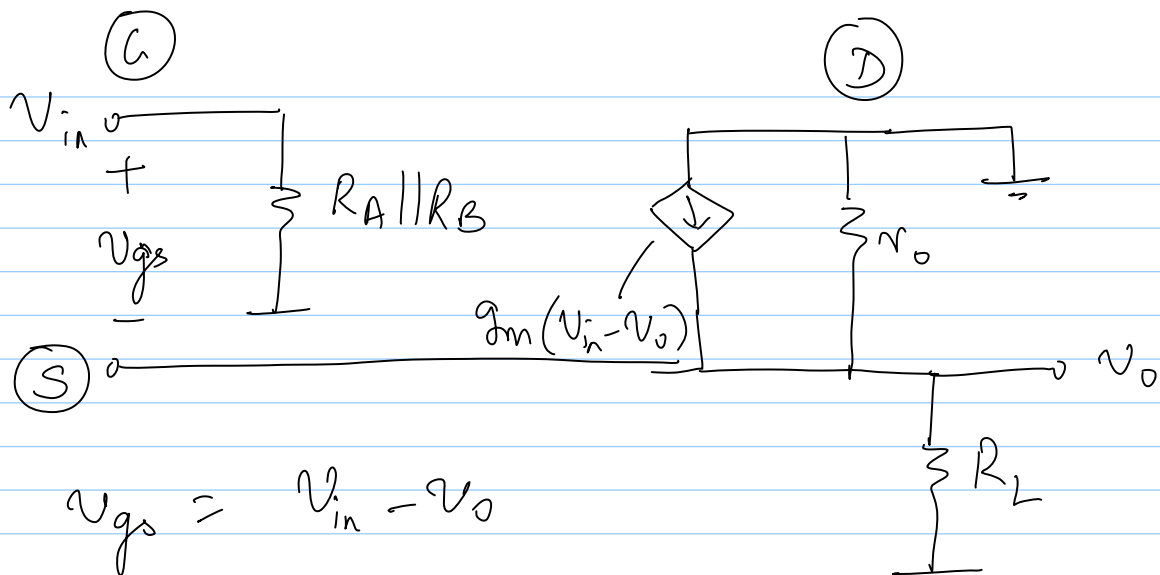

$$v_{gs} = v_{in} - v_o$$

$$Z_{in} = R_A || R_B \quad (\text{can be very large})$$

$$Z_{out} = ?$$

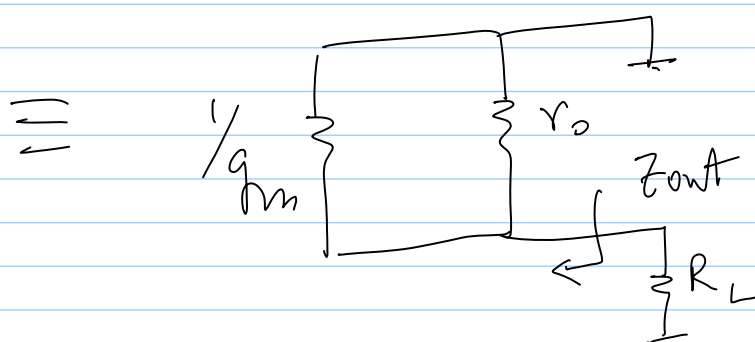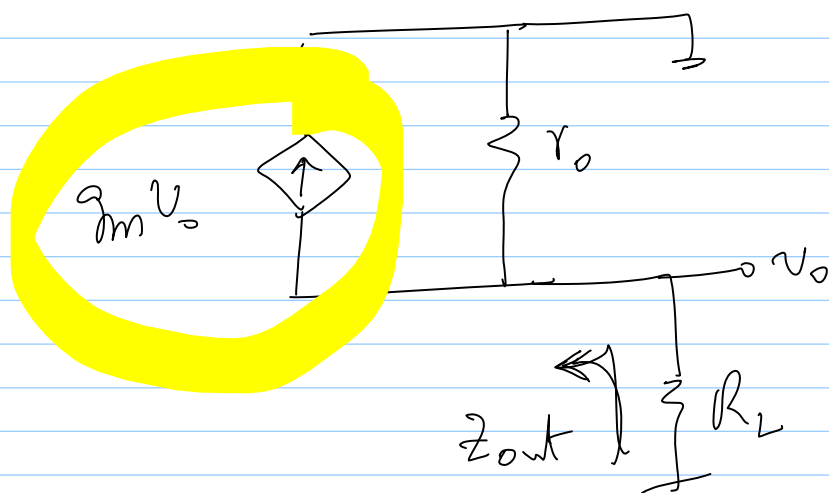


$$z_{out} = r_o \parallel \frac{1}{g_m}$$

$$= \frac{r_o}{1 + g_m r_o}$$

$$= \frac{1}{g_m} \cdot \frac{g_m r_o}{1 + g_m r_o}$$

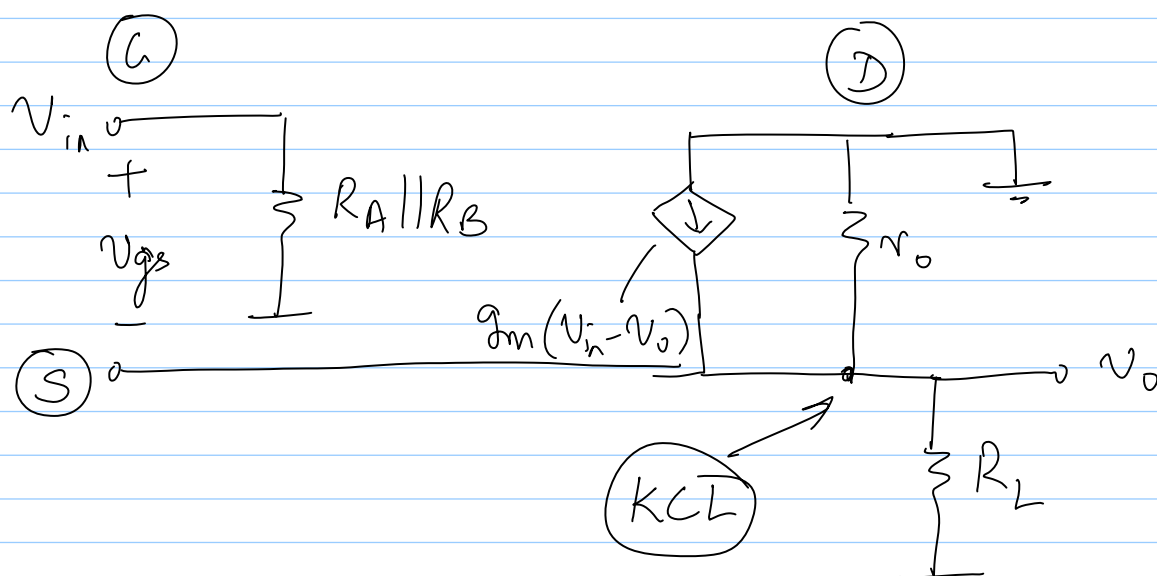If $g_m r_o \gg 1 \Rightarrow z_{out} = 1/g_m$




$$v_{out} (G_L + g_o) = g_m v_{in} - g_m v_{out}$$

$$v_{out} (G_L + g_o + g_m) = g_m v_{in}$$

$$\frac{v_{out}}{v_{in}} = \frac{g_m}{g_m + G_L + g_o}$$

* $\frac{v_{out}}{v_{in}} < 1$ SOURCE FOLLOWER

$= 1 \quad g_m \rightarrow \infty$

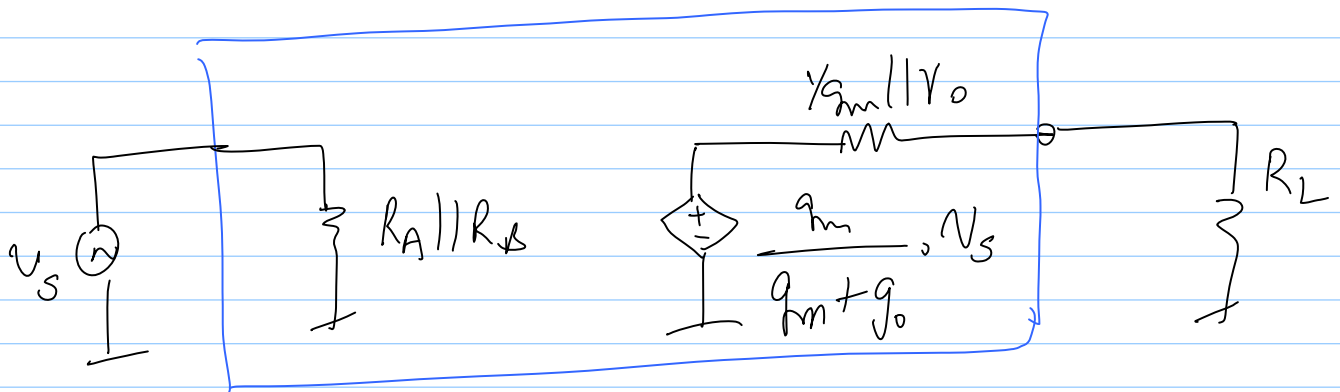

* Choose large $R_A || R_B$

* as $g_m \rightarrow \infty$, $gain \rightarrow 1$
 $Z_{out} \rightarrow 0$

* If $r_o = \infty$, $\frac{v_{out}}{v_s} = \frac{g_m}{g_m + G_L}$

$$\frac{v_{out}}{v_s} = \frac{g_m R_L}{1 + g_m R_L} \rightarrow 1 \text{ when } g_m R_L \gg 1$$

$$R_L \gg \frac{1}{g_m}$$

Swing limits of Common Drain Amp

$$v_s = V_A \sin \omega t$$

as $V_A \uparrow \Rightarrow$ * $g_m \rightarrow \infty$ may not be valid

* Clipping $\begin{cases} \text{cutoff} \\ \text{triode} \end{cases}$

Cutoff (V_{A1})

$$I_D = \underbrace{I_Q}_{I_{ref}} + \underbrace{i_d}$$

i_d

neglect g_o

$$i_d = \frac{v_{out}}{R_L} = \frac{1}{R_L} \cdot \frac{g_m R_L}{1 + g_m R_L} \cdot v_s$$

$$I_D = I_{ref} + \frac{g_m R_L}{1 + g_m R_L} \cdot \frac{V_{A1} \sin \omega t}{R_L}$$

$$I_D = 0 \Rightarrow V_{A1} = I_{ref} R_L \left(1 + \frac{1}{g_m R_L} \right)$$

triode limit (V_{A2})

$$V_D = V_G - V_T$$

$$V_{DD} = \frac{V_{DD} \cdot R_B}{R_A + R_B} + V_{A2} \sin \omega t - V_T$$

$$V_{A2} = \frac{V_{DD} \cdot R_A}{R_A + R_B} + V_T$$





$$V_{A_{max}} = \min \cdot \{ V_{A1}, V_{A2} \}$$

$$g_m R_L = 10$$

$$1) R_L = 1k\Omega \Rightarrow g_m = 10mS$$



$$2) R_L = 10k\Omega \Rightarrow g_m = 1mS$$
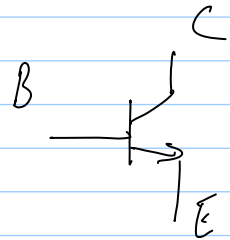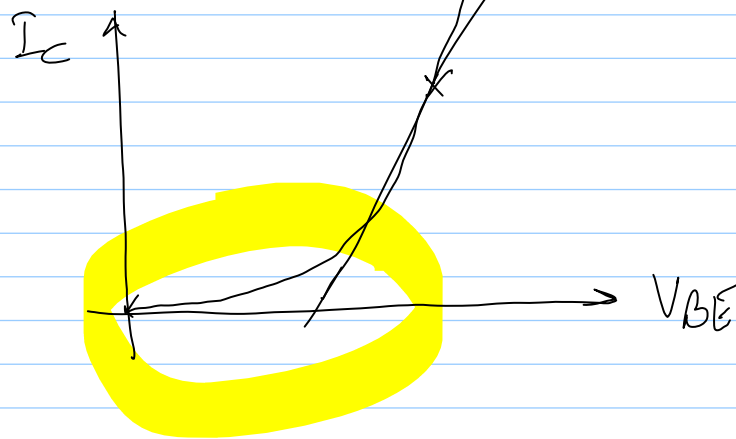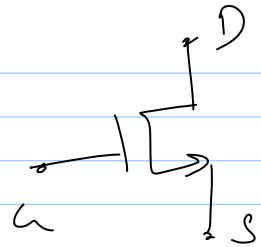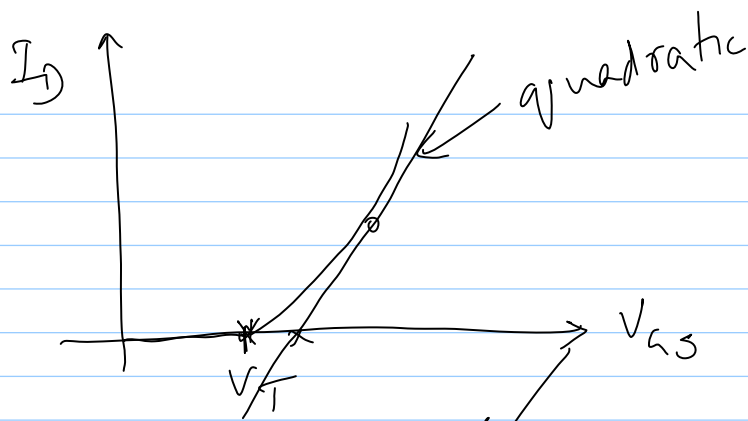
$$3) R_L = 100\Omega \Rightarrow g_m = 100mS$$



VCLS using a MOSFET
(incremental)

$$i_{out} = \frac{v_{in}}{R}$$

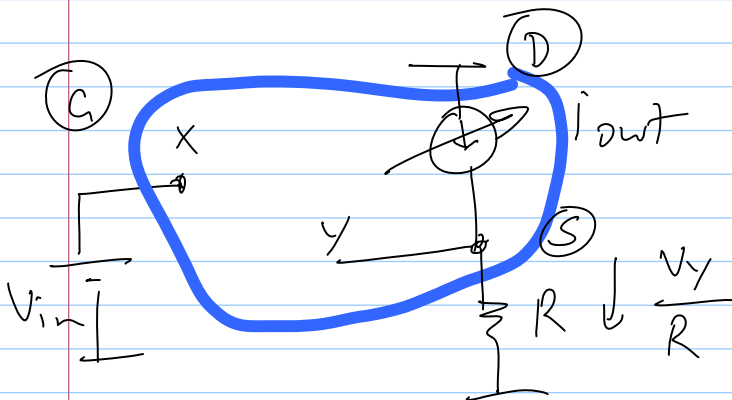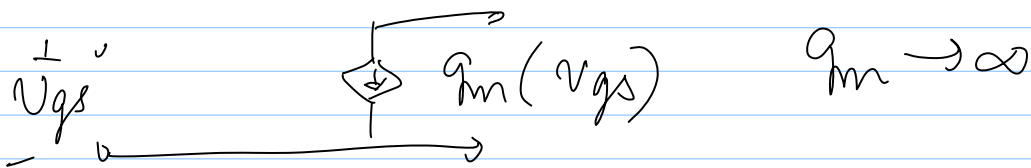

$v_x > v_y \Rightarrow i_{out}$ is too low
 $\Rightarrow \uparrow i_{out}$

$v_x < v_y \Rightarrow i_{out}$ is too large
 $\Rightarrow \downarrow i_{out}$

$$i_{out} \propto (v_x - v_y) \Rightarrow i_{out} = g_m(v_x - v_y)$$

as $g_m \rightarrow \infty$, $V_x = V_y$

$$\text{or } i_{out} = \frac{V_{in}}{R}$$

