

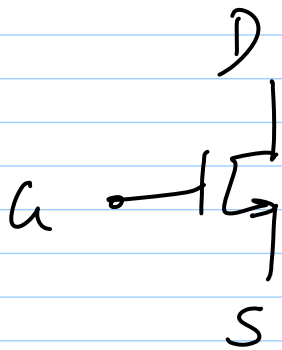
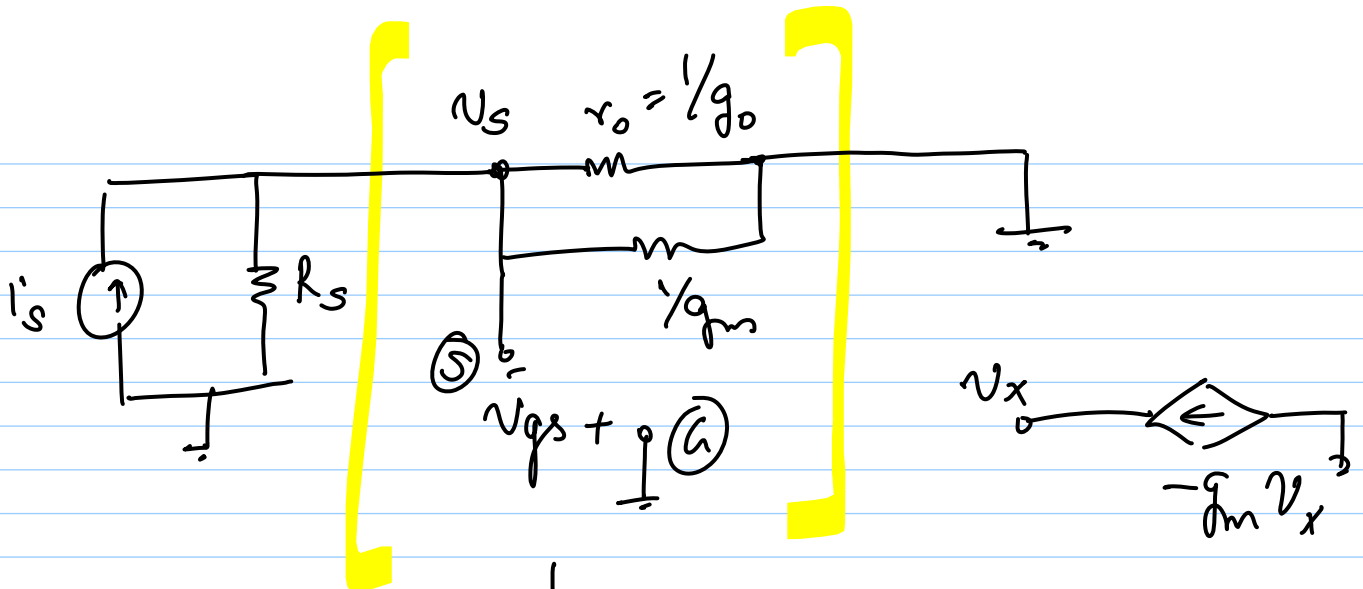


28-9-12


Lec 27

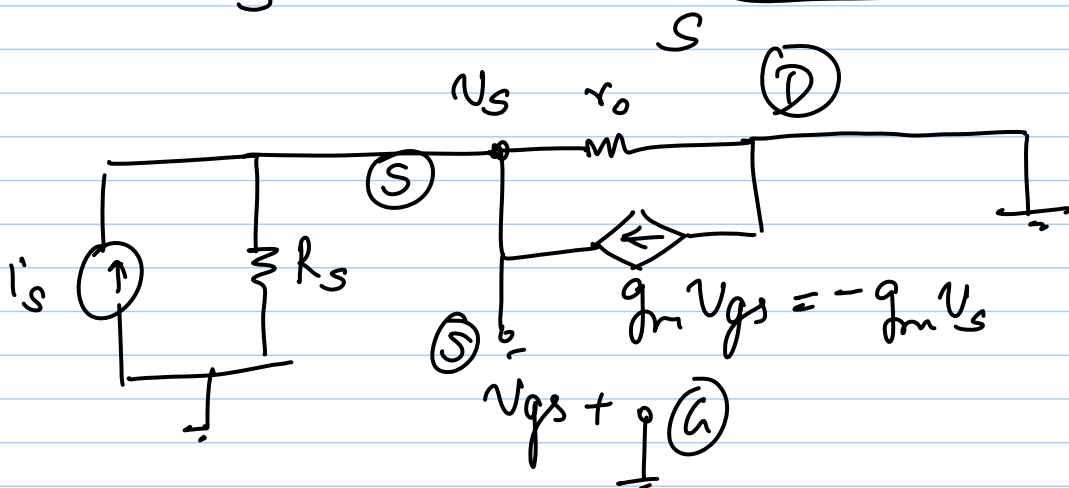


G o —

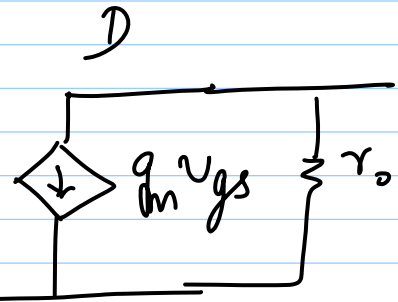

$$Z_{in} = \frac{1}{g_m + g_o}$$

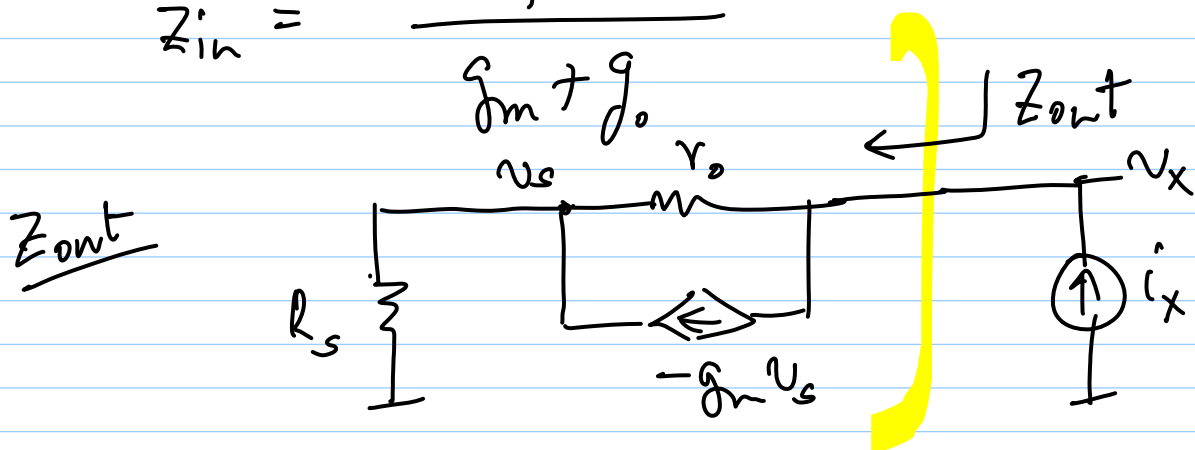

Z_{out}

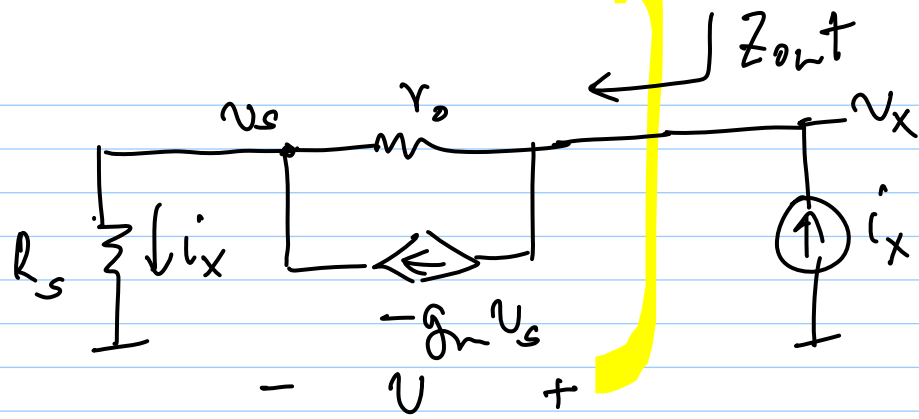


$$v_s = R_s i_x$$

$$v = (i_x + g_m v_s) \cdot r_o$$

$$= i_x (1 + g_m R_s) r_o$$

$$v_x = v + v_s = i_x [(1 + g_m R_s) r_o + R_s]$$
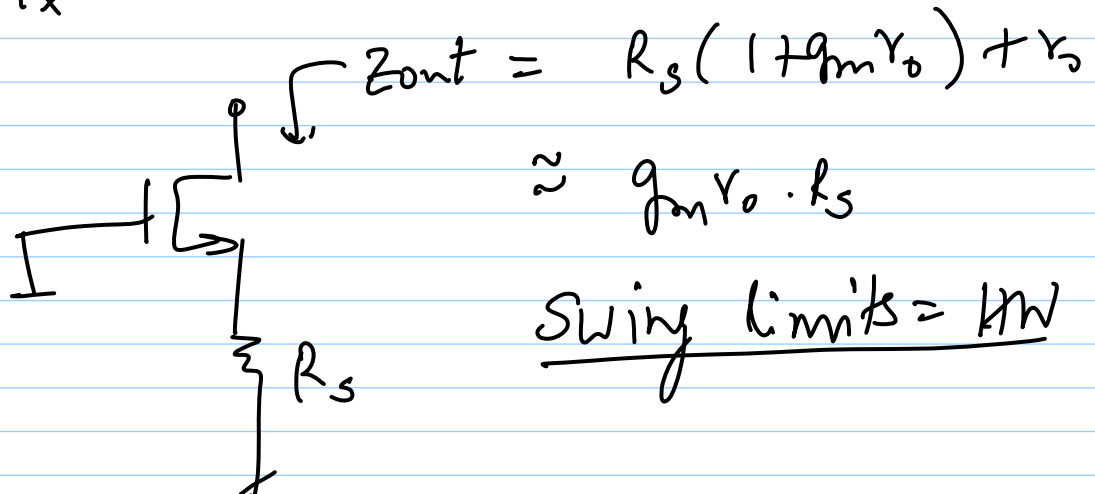
$$Z_{out} = \frac{v_x}{i_x} = R_s (1 + g_m r_o) + r_o$$



$$Z_{out} = R_s (1 + g_m r_o) + r_o$$

$$\approx g_m r_o \cdot R_s$$

Swing limits = HW


VCVS — Common drain amp.

VCCS — Trans-admittance amp.

CCCS — Common-gate ampl.


CCVS — Transimpedance amp:

$$V_{out} = R i_s$$

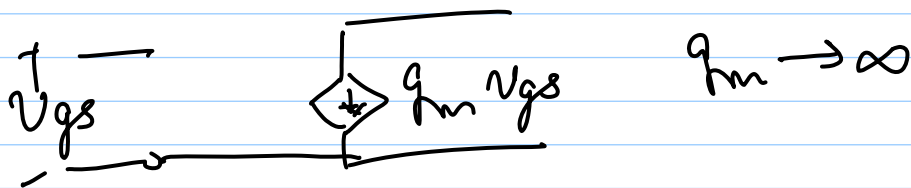




$$V_{out} = R i_s$$

$$V_{out} - R i_s = 0 \quad \checkmark$$

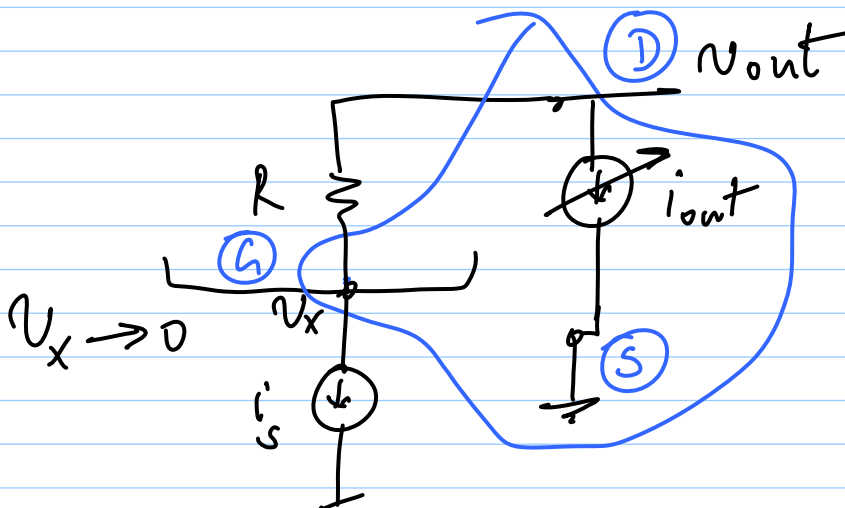

* $v_x > 0 \Rightarrow \downarrow V_{out}$
 $\Rightarrow \uparrow i_{out}$

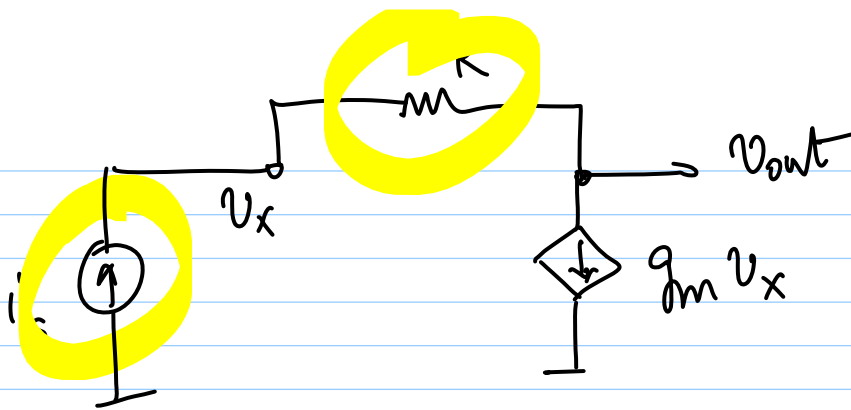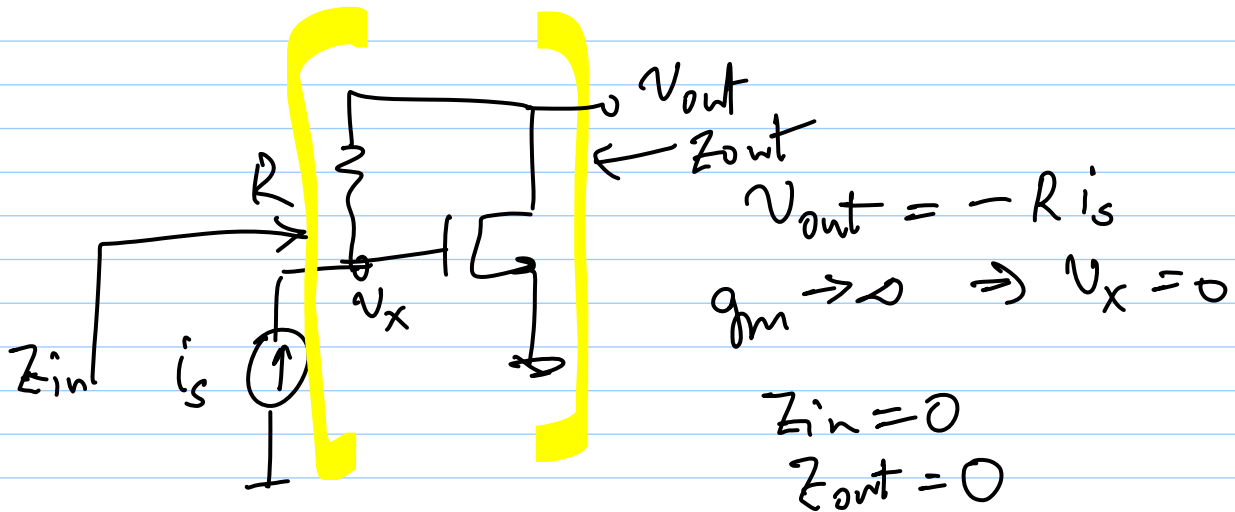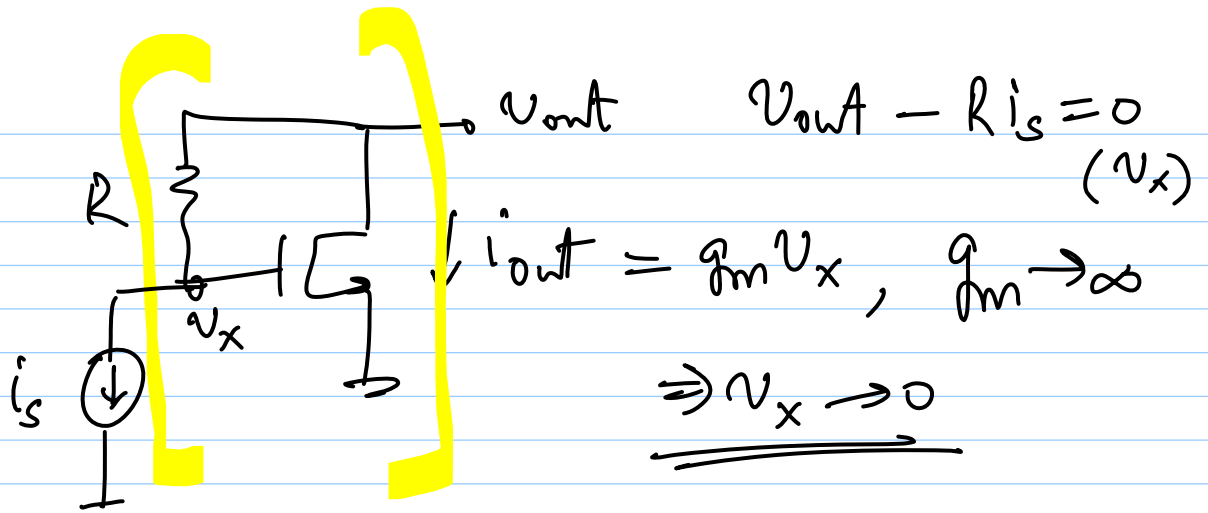
* $v_x < 0 \Rightarrow \uparrow V_{out}$
 $\Rightarrow \downarrow i_{out}$




$$i_s = g_m v_x$$

$$Z_{in} = 1/g_m$$

$$Z_{out} = 1/g_m$$

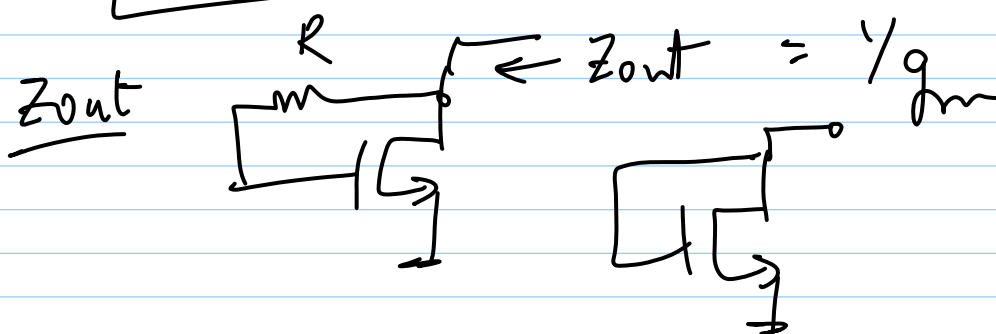

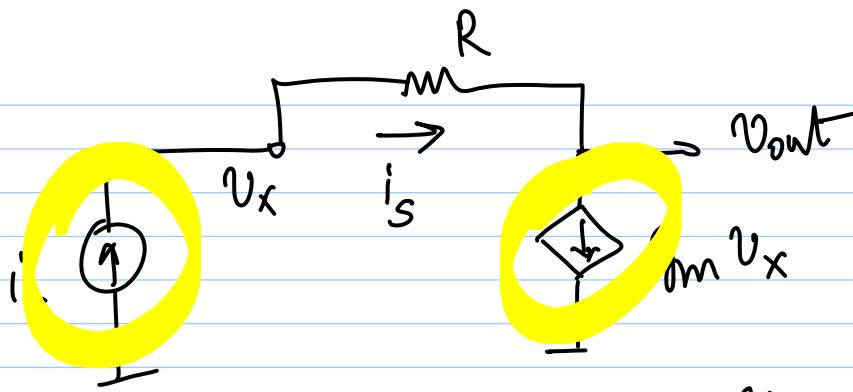

$$\left. \begin{aligned} v_{out} &= v_x - i_s \cdot R \\ i_s &= g_m v_x \end{aligned} \right\} \begin{aligned} v_{out} &= i_s \left[\frac{1}{g_m} - R \right] \\ \frac{v_{out}}{i_s} &= \frac{1}{g_m} - R \end{aligned}$$

$$\frac{v_{out}}{i_s} = -R \left(1 - \frac{1}{g_m R} \right) \quad g_m R \rightarrow \infty \Rightarrow \frac{v_{out}}{i_s} \rightarrow -R$$

$$g_m R \gg 1 \Rightarrow \boxed{g_m \gg \frac{1}{R}}$$

