

2-8-12

Lec 3

$$\Delta V_S = \Delta I_D \cdot R_S + \Delta V_D$$

$$\Delta I_D = \frac{I_S}{V_t} \exp\left(\frac{V_{D_0}}{V_t}\right) \cdot \Delta V_D$$

$$\approx \frac{I_{D_0}}{V_t} \cdot \Delta V_D$$

$$\Rightarrow \Delta V_D = \frac{V_t}{I_{D_0}} \cdot \Delta I_D$$

$$\Delta V_S = \Delta I_D \cdot R_S + \Delta I_D \cdot \frac{V_t}{I_{D_0}}$$

$\Rightarrow$ Incremental quantities related linearly

* $I = f(V)$ can be linearised around (V_0, I_0) - OP

$\rightarrow$ any nonlinearity can be handled this way


$\rightarrow V = g(I)$ can also be used

e.g. $V_D = V_t \ln\left(\frac{I_D}{I_S} + 1\right)$

$$I_D' = I_{D_0} + \Delta I_D$$

expand V_D' in a Taylor series

assumptions : ΔV_D is "small-signal"

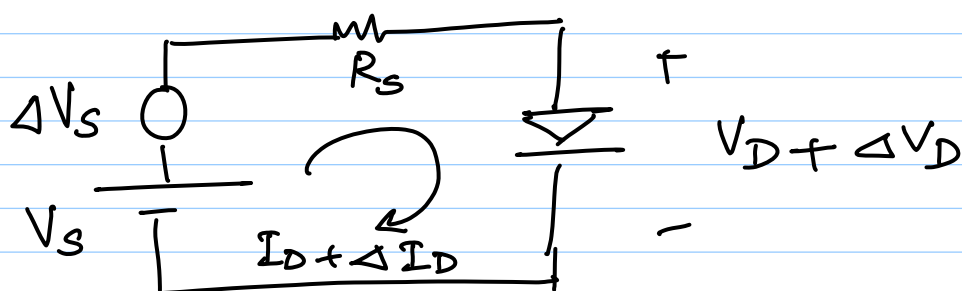

* If V_s is changed by a small amount - i.e. the "signal" is small - the loop currents and node voltages also change by a small amount
 $I_D \leftrightarrow V_D \leftrightarrow V_s \Rightarrow$ non-linear relation
 $I_D' \leftrightarrow V_D' \leftrightarrow V_s' \Rightarrow$ " "

$\Delta I_D \leftrightarrow \Delta V_D \leftrightarrow \Delta V_s \Rightarrow$ linear relation




i.e. absolute voltage - current are still related by a NL eqn.

BUT: incremental V & I are related linearly

Going back to diode network:

$$\Delta I_D = \frac{\Delta V_s}{R_s + \frac{V_t}{I_{D0}}}$$

what kind of network has this loop eqn?

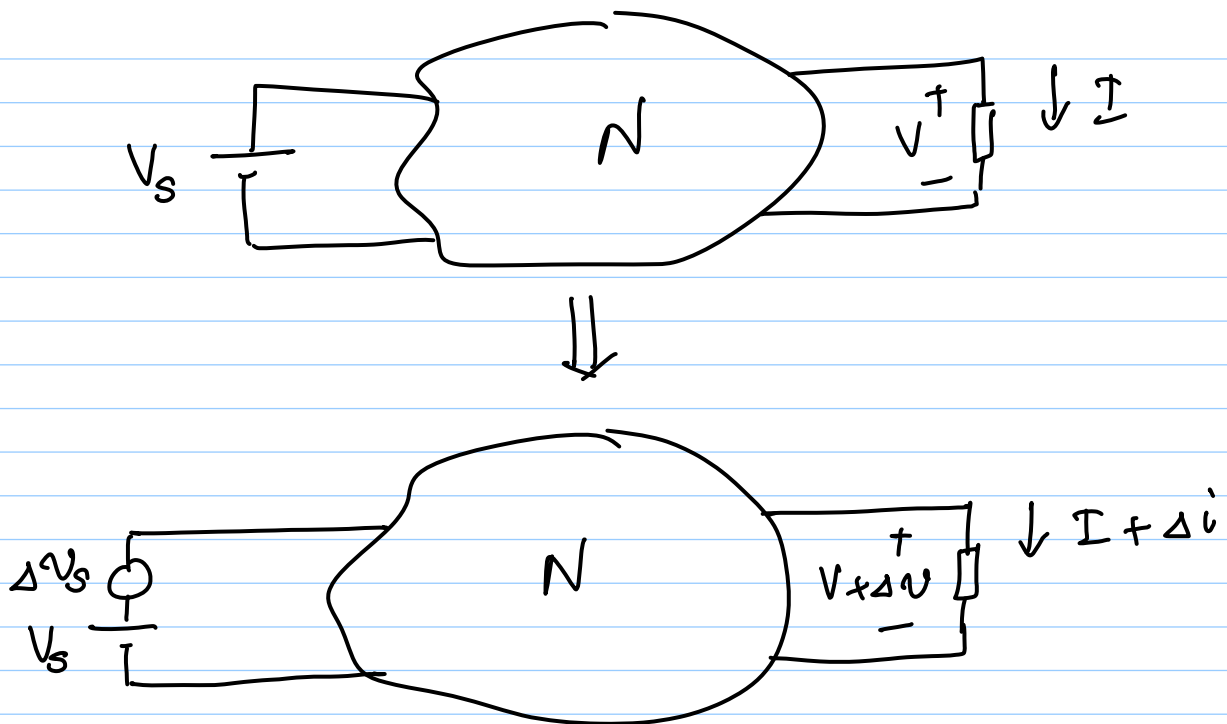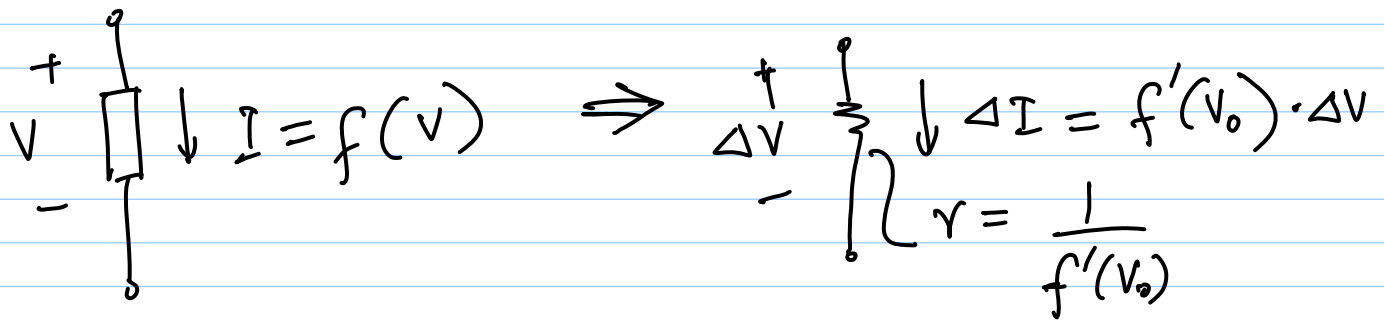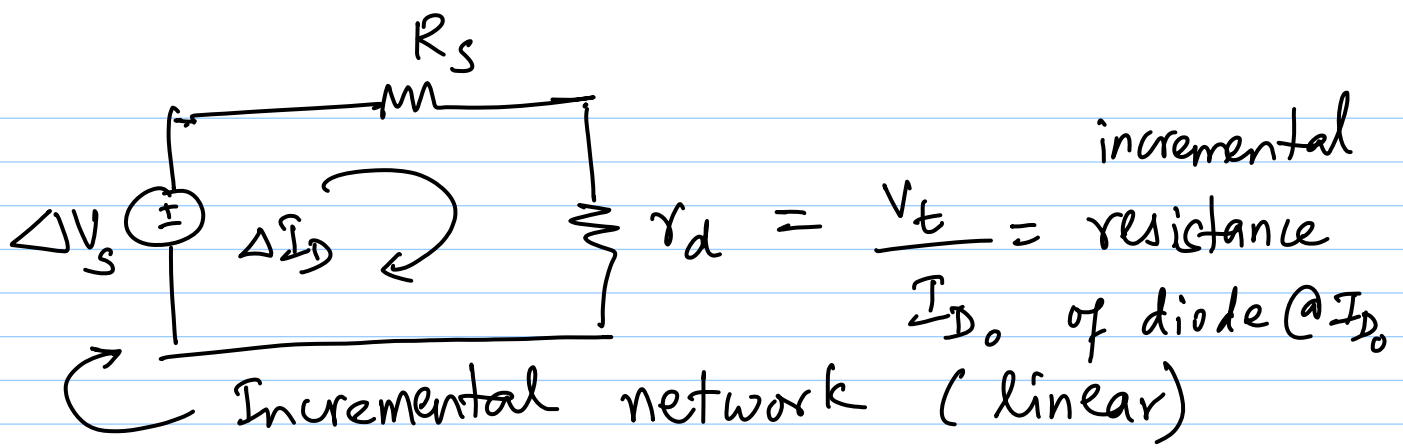

$$I = f(v)$$

$$I + \Delta i = f(v + \Delta v) \approx f(v) + f'(v) \cdot \Delta v$$

$$\therefore \Delta i = f'(v) \cdot \Delta v$$

$$\frac{\Delta v}{\Delta i} = \text{resistance} = \frac{1}{f'(v)}$$



* $\frac{\Delta v}{\Delta i}$ depends on v, i etc.

* $I \Rightarrow$ Quiescent Current

$\Delta i \Rightarrow$ incremental current

$V \Rightarrow$ Quiescent Voltage

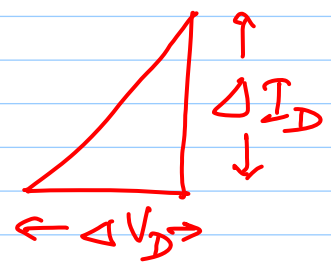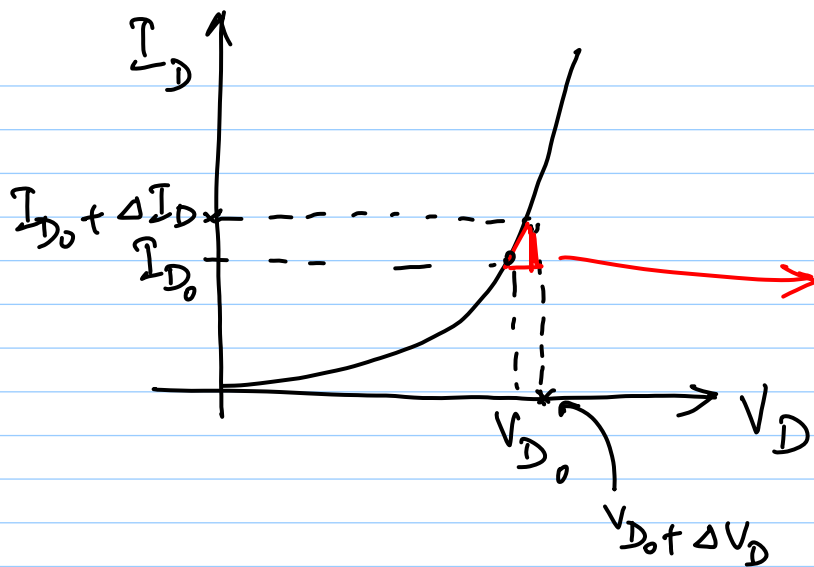$\Delta v \Rightarrow$ incremental voltage






$$\frac{\Delta I_D}{\Delta V_D} = \left. \frac{d I_D}{d V_D} \right|_{V_{D0}}$$


$\frac{\Delta V_D}{\Delta I_D} =$ incremental resistance (or dynamic)
 $\frac{\Delta I_D}{\Delta V_D} =$ " conductance
 both depend on V_{D0}, I_{D0}

$\therefore (V_{D_0}, I_{D_0})$ is called the operating point of the nonlinear device

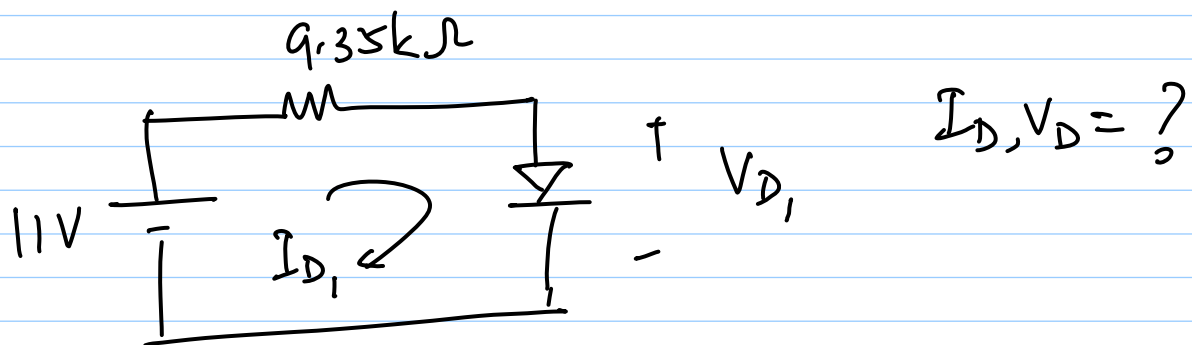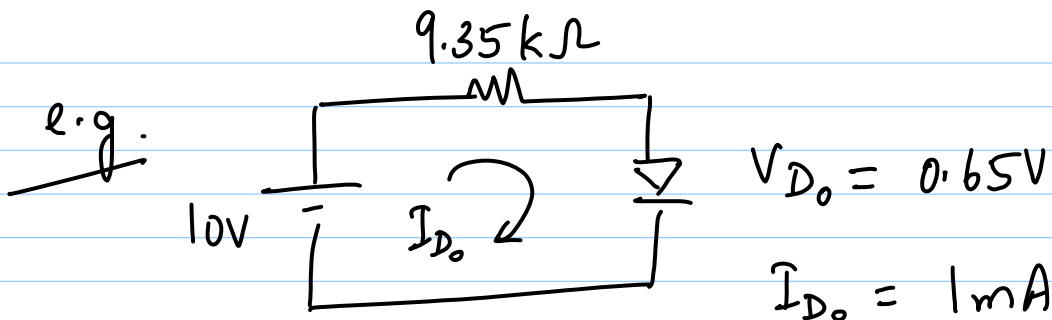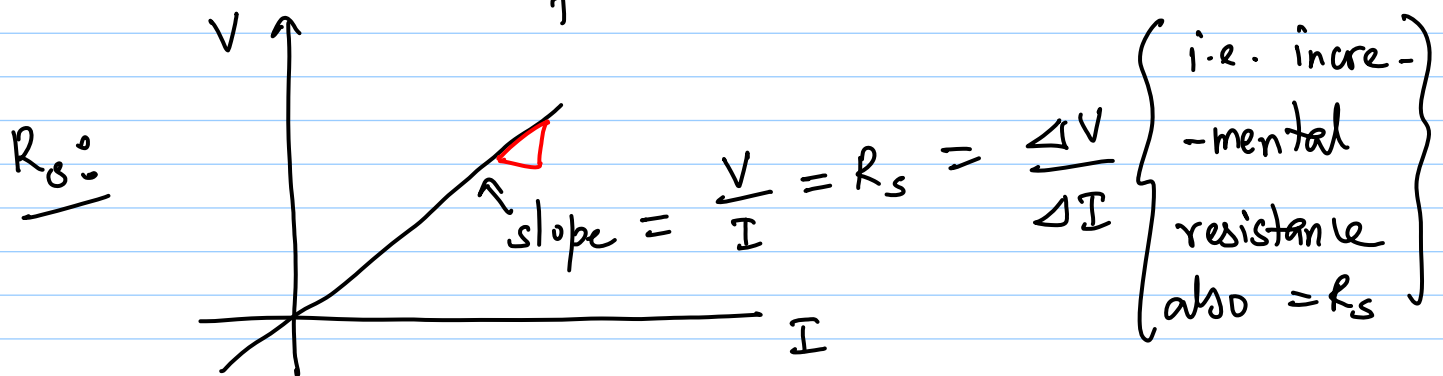alternatively, if you want to find incremental resistance/conductance of a NL device, you need to find the o.p. of the device



Incremental Equivalent Ckt

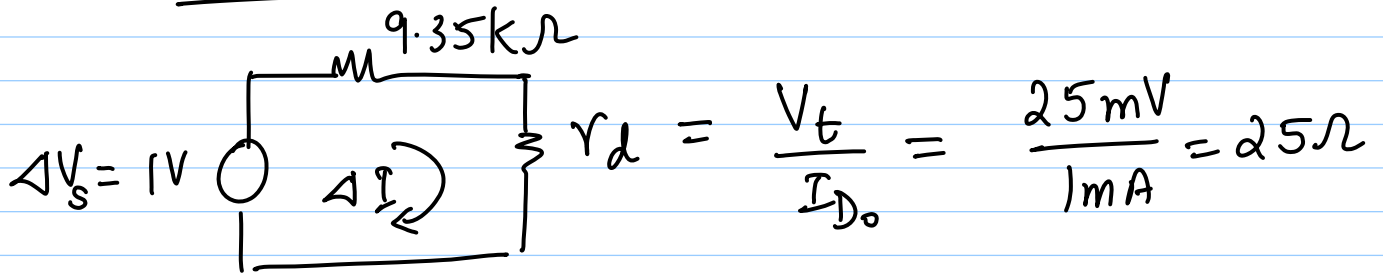

$$\Delta I = \frac{1}{9.35k\Omega + 25} \approx 107\mu A$$

$$I_{D1} = 1.107mA$$

$$I_f \quad V_s = 9V, \quad I_{D2} = ?$$

$$\Delta V_s = -1V \Rightarrow \Delta I_D = -107\mu A$$

$$\Rightarrow I_{D2} = 0.893mA$$

Next : is linear approx. valid?

$$\Delta V_D = \Delta I_D \cdot r_d = 107\mu A \times 25$$

$$\approx 2.7mV$$

$$f''(V_{D0}) = ?$$

$$I_D = I_s \exp\left(\frac{V_D}{V_t}\right)$$

$$f''(V_{D0}) = \frac{I_s}{V_t^2} \exp\left(\frac{V_{D0}}{V_t}\right) \approx \frac{I_{D0}}{V_t^2}$$


$$\text{second term} = \frac{f''(V_{D0}) \cdot (\Delta V_D)^2}{2}$$

$$= \frac{I_{D_0}}{2V_t^2} \cdot (\Delta V_D)^2$$

$$I_D = I_{D_0} + \frac{I_{D_0}}{V_t} \cdot (\Delta V_D) + \frac{I_{D_0}}{2V_t^2} (\Delta V_D)^2 + \dots$$

$\Rightarrow$ we need $\Delta V_D \ll 2V_t$ $\sim 50\text{mV}$ quite valid

$\nearrow 2.7\text{mV}$

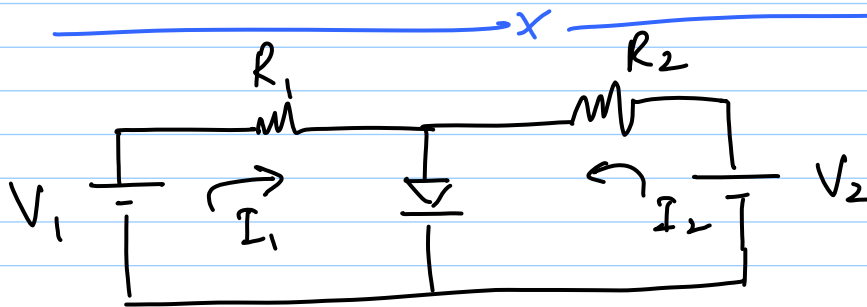


Use NL eqns to find out O.P.

e.g. $\frac{V_1 - 0.65}{R_1} = I_1$ & $\frac{V_2 - 0.65}{R_2} = I_2$


$$I_{D_0} = I_1 + I_2$$

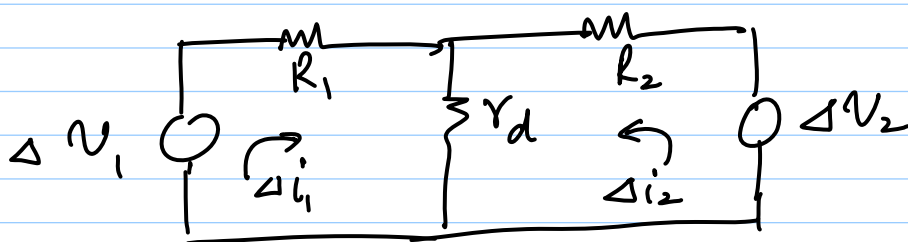If $V_1 \rightarrow V_1 + \Delta V_1$ & $V_2 \rightarrow V_2 + \Delta V_2$
Incremental picture:




$$r_d = \frac{V_t}{I_{D_0}}$$
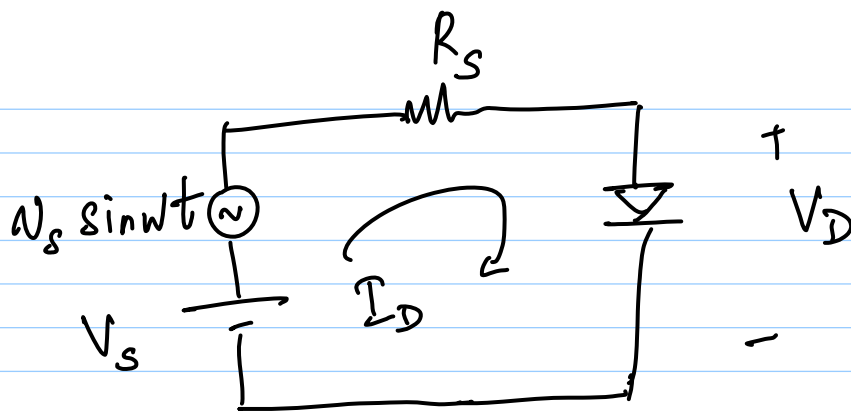
$$\Delta i_d = \Delta i_1 + \Delta i_2 \dots$$



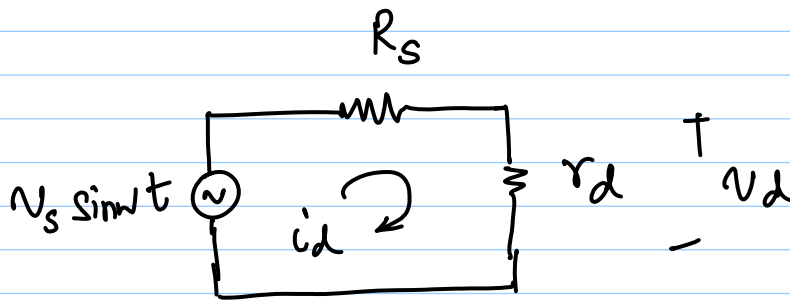If V_s is very small,
 $I_D = I_{D0} + i_d$
 $V_D = V_{D0} + v_d$



Incremental
 (or "small-signal")

picture

$\Rightarrow$ can determine i_d & v_d (also
 sinusoids)