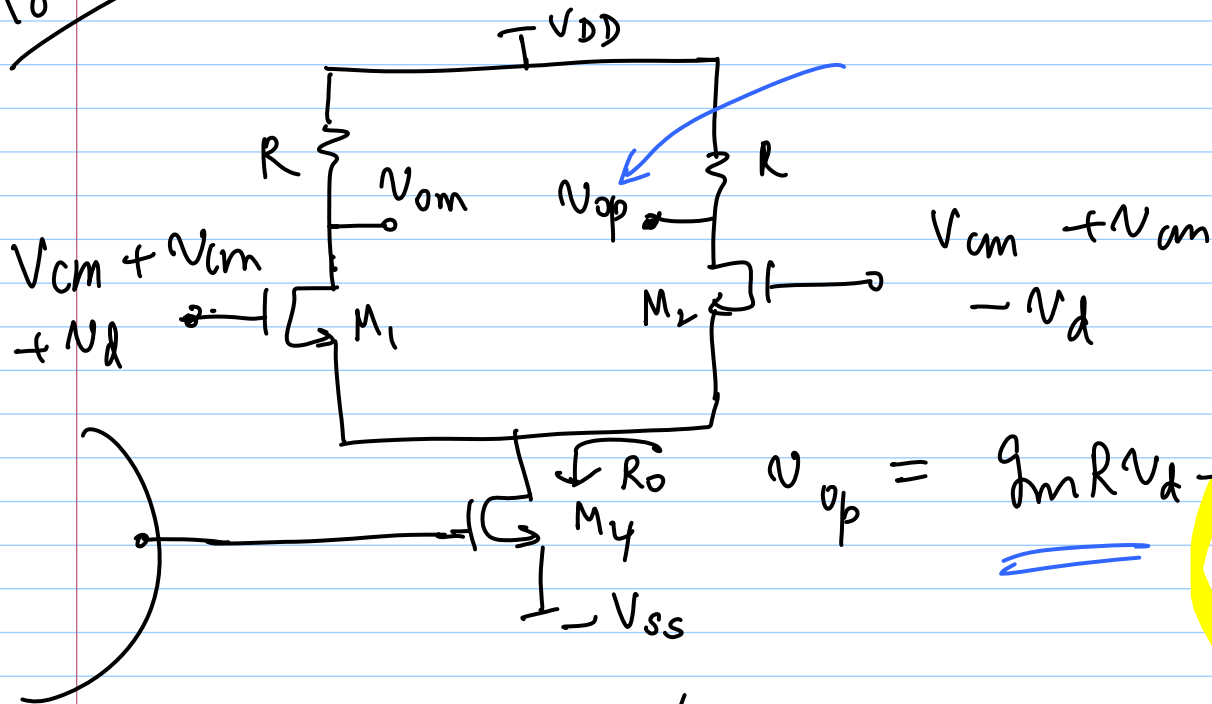


18/10/12

Lec 34



$$v_{op} = \underline{g_m R v_d} - \underline{\frac{g_m R}{1 + 2g_m R_o} v_{cm}}$$

$$g_m \gg \frac{1}{2R_o}$$

$$v_{op} = \underbrace{g_m R v_d}_{\text{diff. mode gain}} - \underbrace{\frac{R}{2R_o} v_{cm}}_{\text{common mode gain}}$$



$$v_{om} = -g_m R v_d - \frac{R}{2R_o} v_{cm}$$


DM gain $\gg$ CM gain

CMRR $\equiv$ common mode rejection ratio

$$= \left| \frac{A_{dm}}{A_{cm}} \right| = \frac{g_m R}{R/2R_o} = 2g_m R_o$$
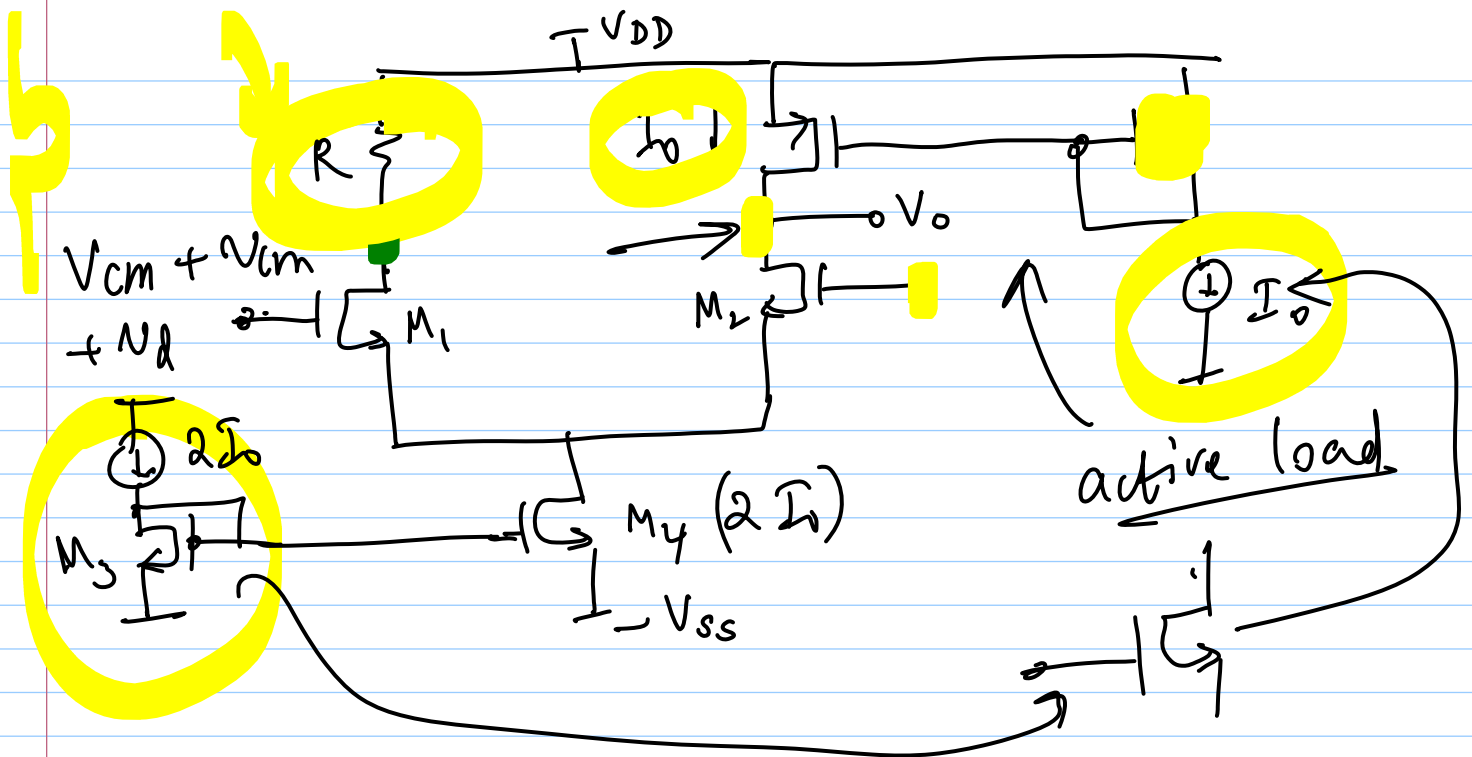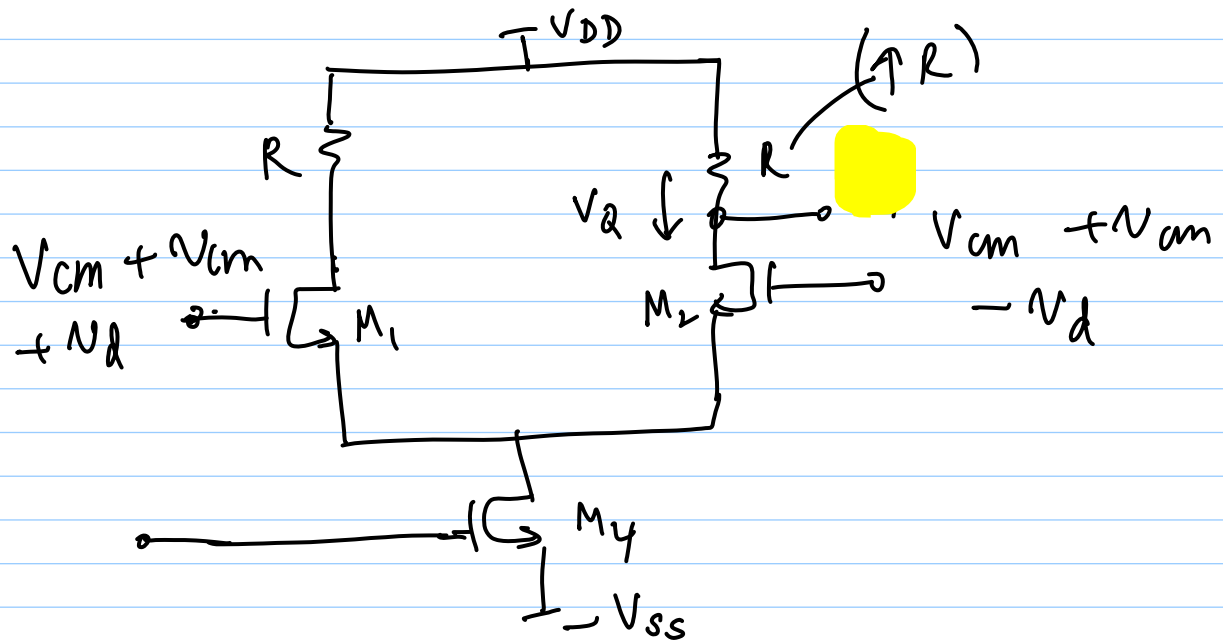
$$\begin{pmatrix} V_a = 1 \text{ mV} \\ V_b = 0 \text{ mV} \end{pmatrix} \rightsquigarrow \begin{pmatrix} 100 \text{ mV} \\ 1000 \text{ mV} \end{pmatrix}$$



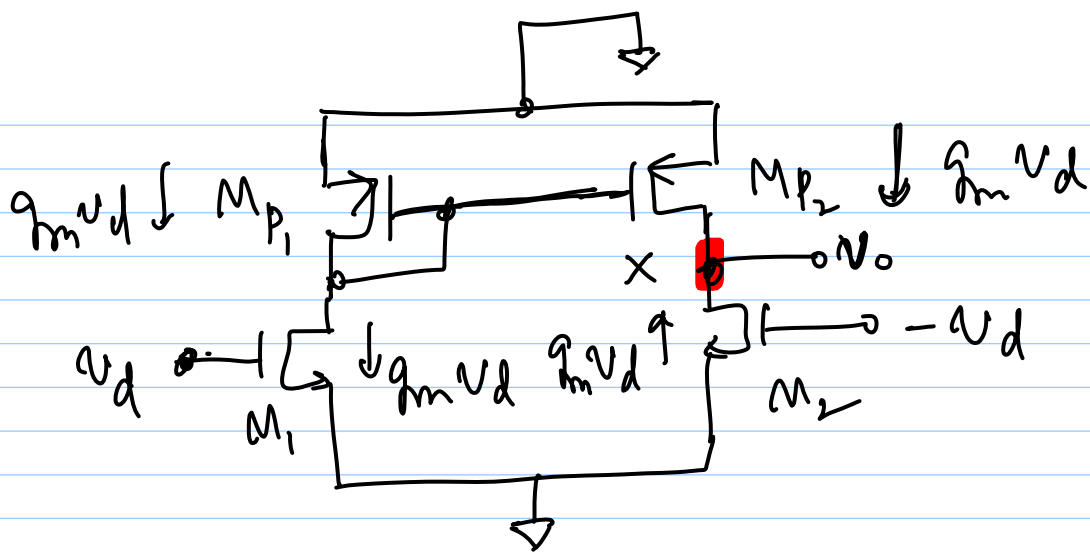

i_{out} = total current flowing into

(x)

$$\Rightarrow \frac{v_o}{v_d} = \infty$$