
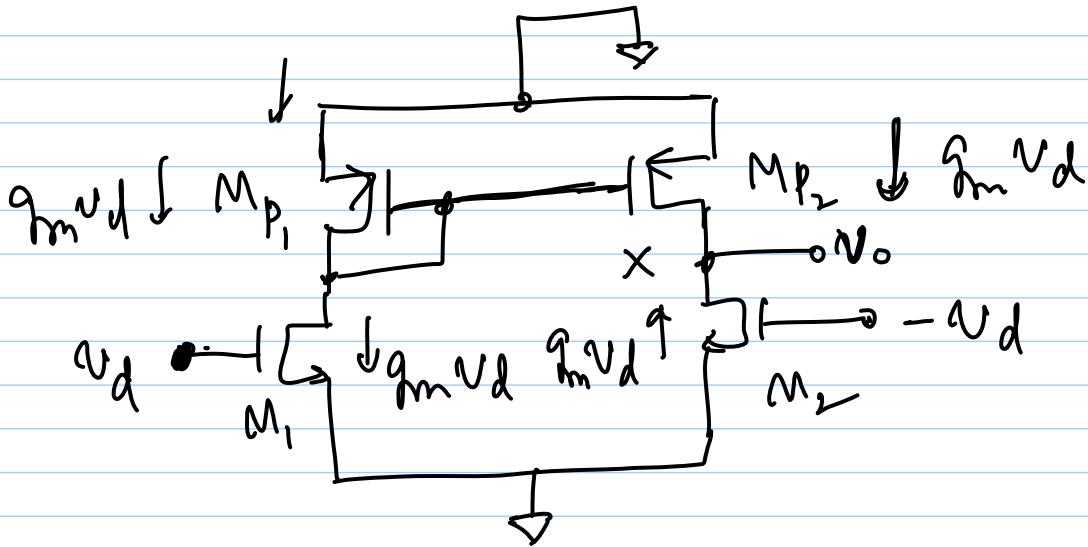


19-10-12

# Lec 35

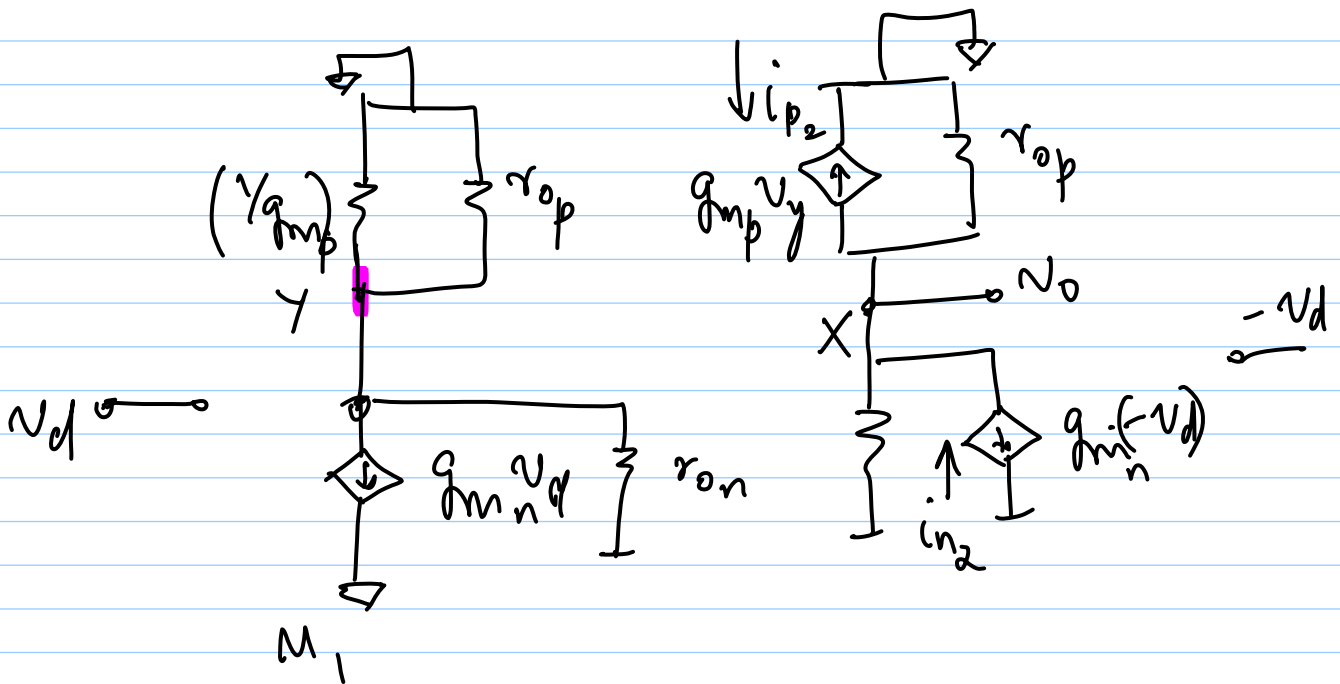

$i_x = \text{total current flowing into } \textcircled{x}$   
 $= 2 g_m v_d \checkmark$



$$v_y \approx - g_{mn} v_d \cdot \frac{1}{g_{mp}}$$


$$i_{p2} = (-1) \times \left( -g_{m_n} v_d \cdot \frac{1}{g_{m_p}} \right) \cdot g_{m_p}$$

$$= g_{m_n} \cdot v_d$$

$$i_{n2} = g_{m_n} \cdot v_d$$

$$v_o = (i_{p2} + i_{n2}) (r_{op} \parallel r_{on})$$
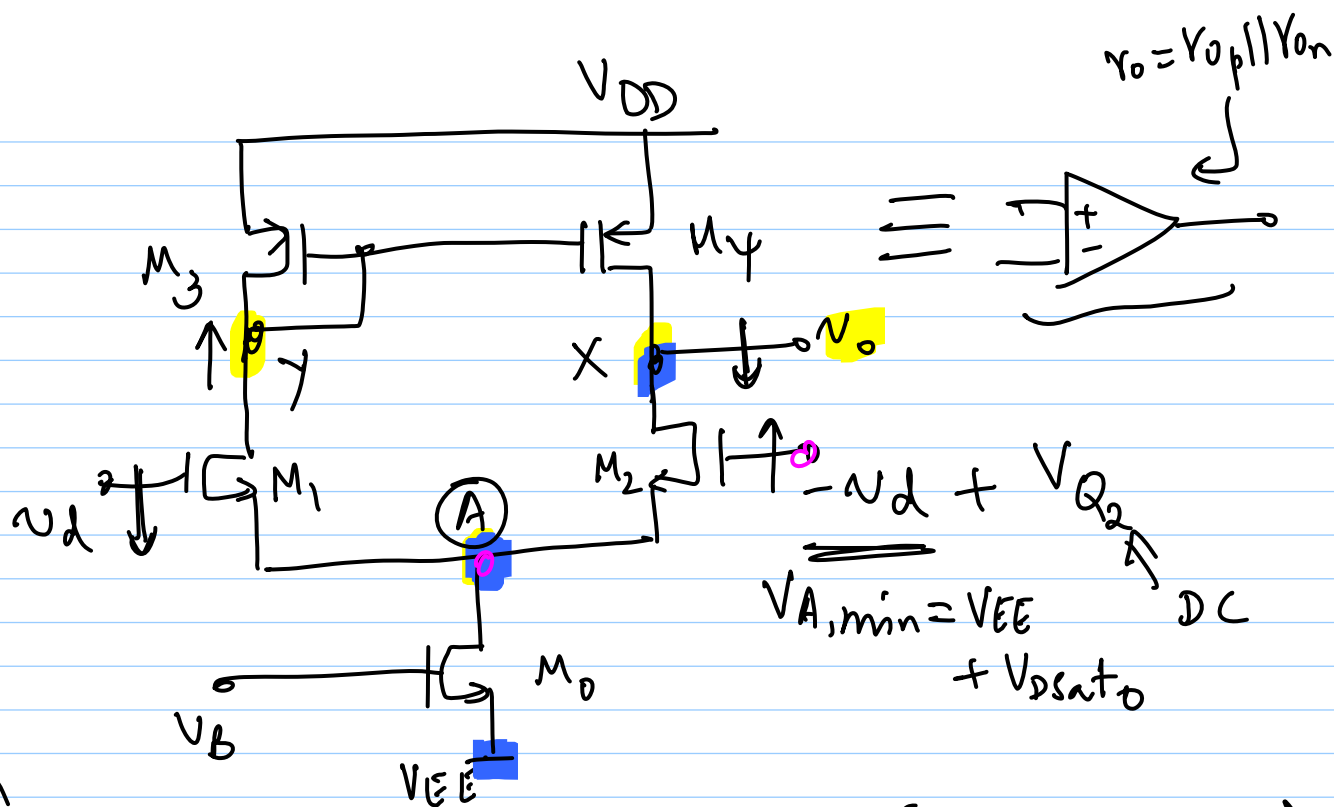
$$\frac{v_o}{v_d} = 2 g_{m_n} (r_{op} \parallel r_{on})$$




$v_d \uparrow$

$$v_{o, \max} = V_{DD} - V_{Dsat4} \quad (M_4 \text{ in triode})$$

$v_d \downarrow$


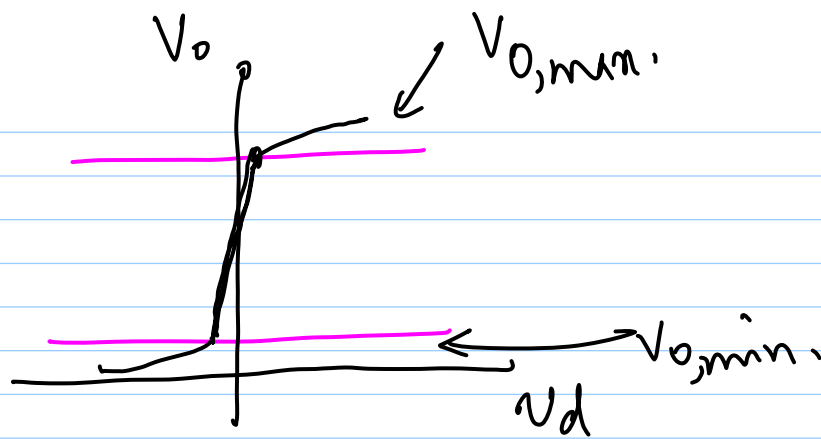
$$v_{o, \min} = V_{Q2} - V_T \quad (M_2 \text{ in triode})$$



$$V_{Q_2, \min} = V_{EE} + V_{DSAT_0} + V_{AS_2}$$

$$\rightarrow V_{O, \min} = V_{Q_2, \min} - V_T$$
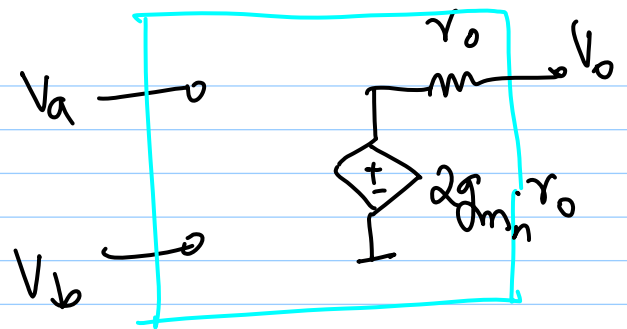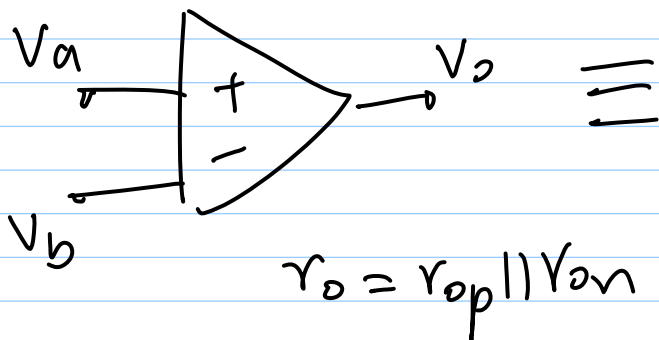
$$= V_{EE} + V_{DSAT_0} + \underbrace{V_{AS_2}}_{V_{DSAT_2}} - V_T$$



A Problem 1 : finite gain ( $\sim 100$ )

