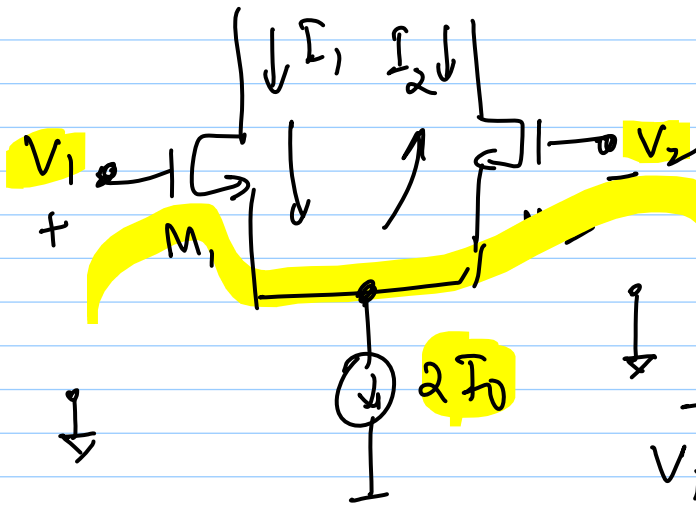


23-10-12

Lec 36



$$V_{id} = V_1 - V_2$$


$$I_{od} = I_1 - I_2$$

$$V_{id} = 0 \Rightarrow I_1 = I_2 = I_0$$

KVL

$$V_1 - V_{as1} + V_{as2} - V_2 = 0$$
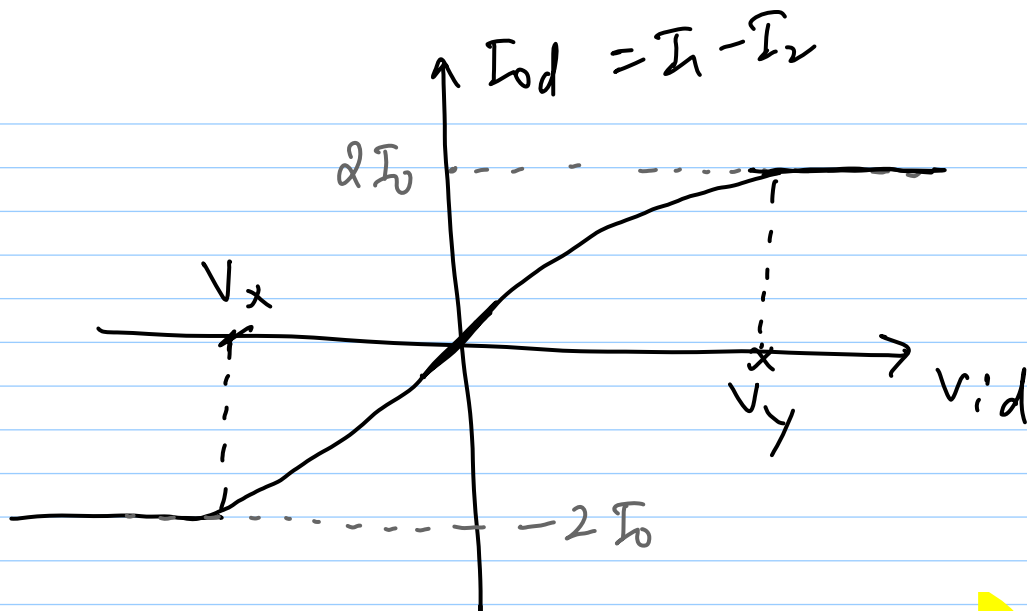
$$\begin{aligned} V_{id} = V_1 - V_2 &= V_{as1} - V_{as2} \\ &= \left[V_T + \sqrt{\frac{2I_1}{k'(W/L)}} \right] - \left[V_T + \sqrt{\frac{2I_2}{k'(W/L)}} \right] \end{aligned}$$



$$V_{id} = \frac{\sqrt{I_1} - \sqrt{I_2}}{\sqrt{\frac{1}{2}k'(W/L)}}$$

$$I_1 + I_2 = 2I_0$$

①

②

(HW)
Solve
for
 I_1, I_2

$$I_1 = I_0 + \frac{k'}{4} \left(\frac{W}{L} \right) V_{id} \sqrt{\frac{8 I_0}{k' \left(\frac{W}{L} \right)} - V_{id}^2}$$

$$I_2 = I_0 - \left\{ \begin{array}{c} \text{, ,} \end{array} \right\}$$


$$I_m = K' \left(\frac{W}{L} \right) \cdot V_{dsat}$$


$$V_{d_{sat}} = \sqrt{\frac{2 I_0}{k' \left(\frac{W}{L}\right)}}$$

$$I_1 = I_0 + \frac{1}{2} \mu_m V_{id} \sqrt{1 - \left(\frac{V_{id}}{2V_{dsat}} \right)^2} \quad \checkmark$$

$$I_1 = I_0 - (\quad)$$

Small - Signal
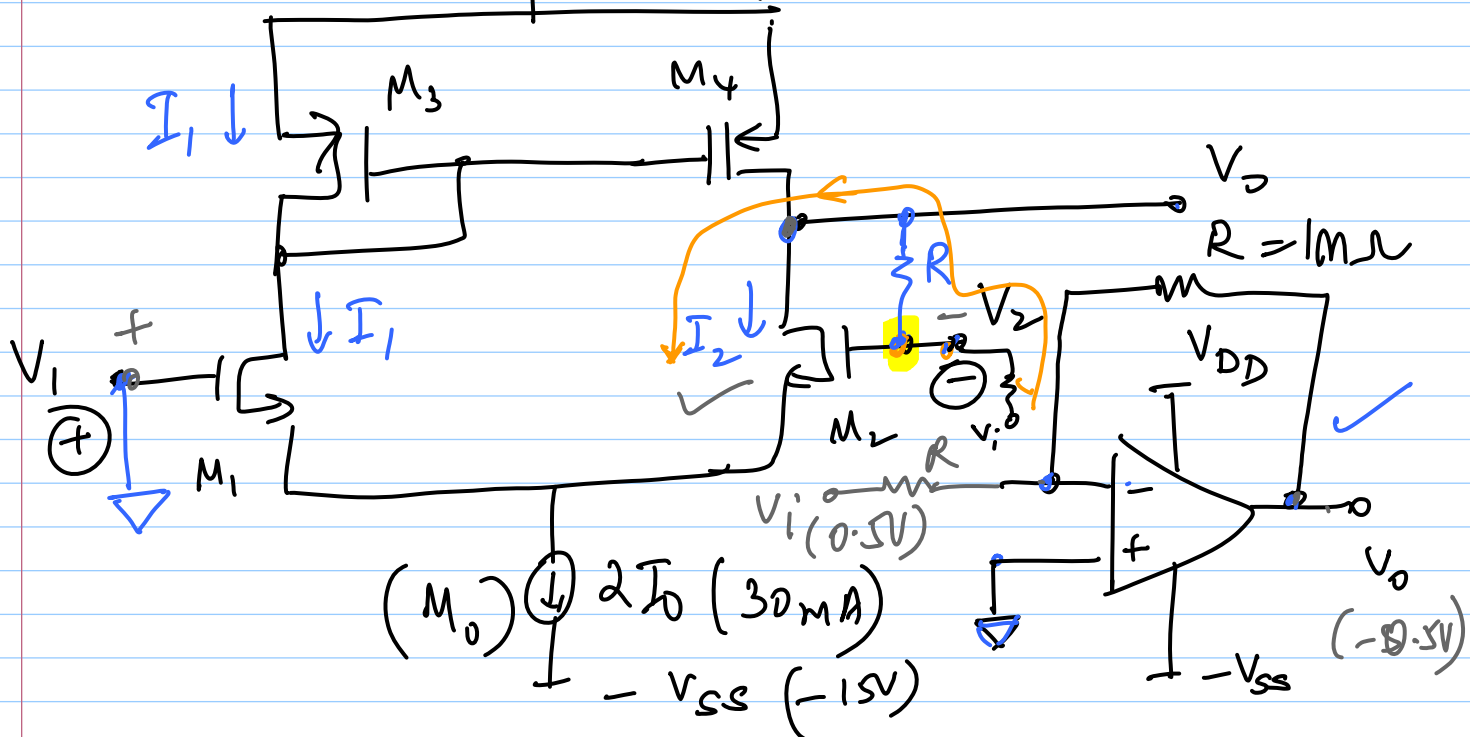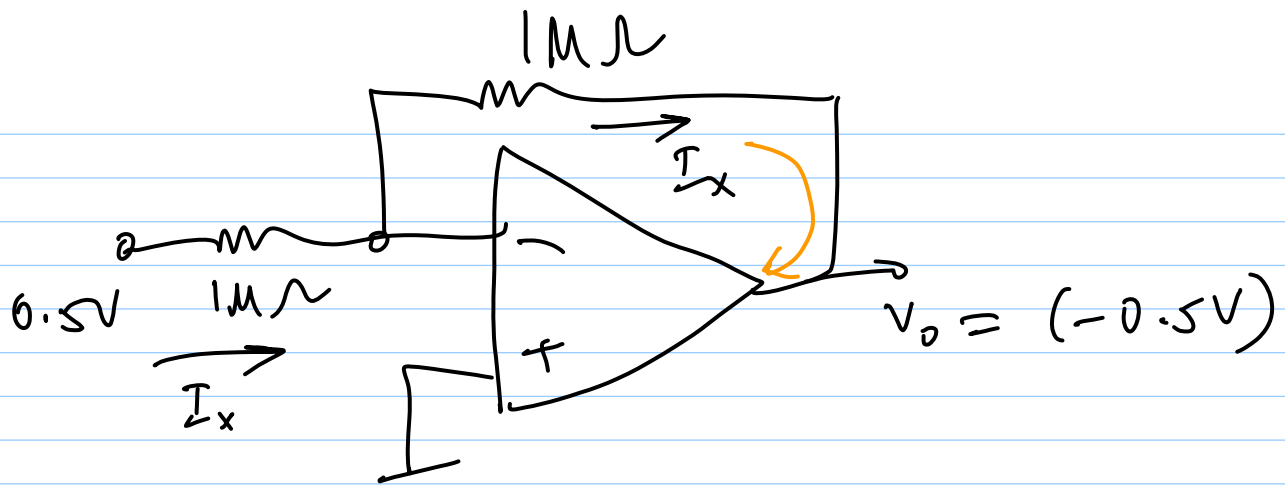
$$(x) \quad v_2 > 0$$
$$I_2 \supset I_1$$
$$V_{id} \ll 2 V_{data} \cdot \frac{1}{1 + V_{DD} (15V)}$$




$$I_x = \frac{0.5}{1M\Omega} = \underline{0.5\mu A}$$

