



31-10-12

Lec 39


Amplifier

* Every node of the amp. has a parasitic cap associated with it
 $\Rightarrow$ pole associated with the cap
@ each node

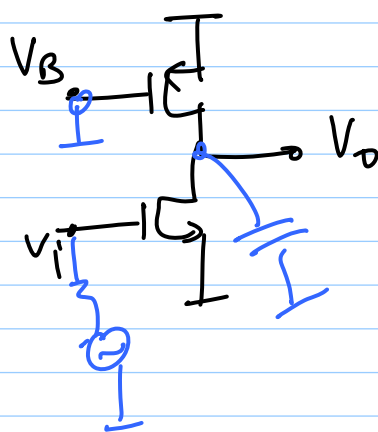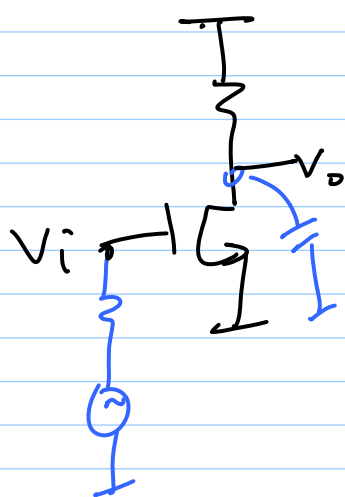
* More gain $\Rightarrow$ cascade of amplifiers
 $\Rightarrow$ more # nodes $\Rightarrow$ more # poles



2-pole system
 $\leftarrow$

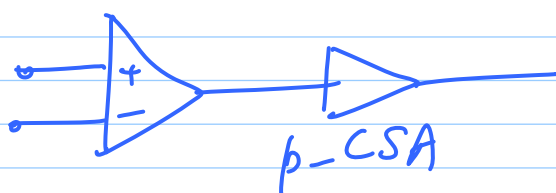

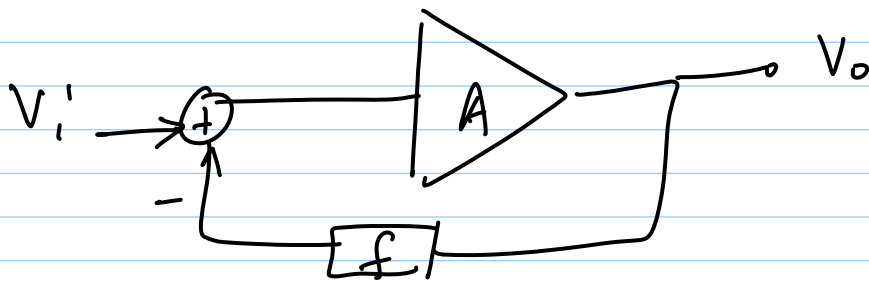$\leftarrow$ more nodes
 $\Rightarrow$ more poles



$$\frac{V_o}{V_i} = \frac{1}{f} \frac{A f}{1 + A f}$$

$$\sim \frac{1}{f} \text{ if } A f \underset{\substack{\text{large}}}{\gg} 1$$

$$A = A(s)$$

$$\Rightarrow CLG = \frac{1}{f} \cdot \frac{A(s) \cdot f}{1 + A(s) \cdot f} = CLG(s)$$


$$A(s) = \frac{A_o}{1 + s/\omega_p} \leftarrow \text{single pole amp.}$$

@ low freq. , $A(s) \approx A_o$

$$LG \approx A_o f$$

$$CLG \approx \frac{1}{f}$$

* $\omega \uparrow \Rightarrow |A(\omega)|$ starts reducing @ ω_p
 but CLG stays close to $1/f$
 till $|A(\omega) \cdot f| \sim 1$

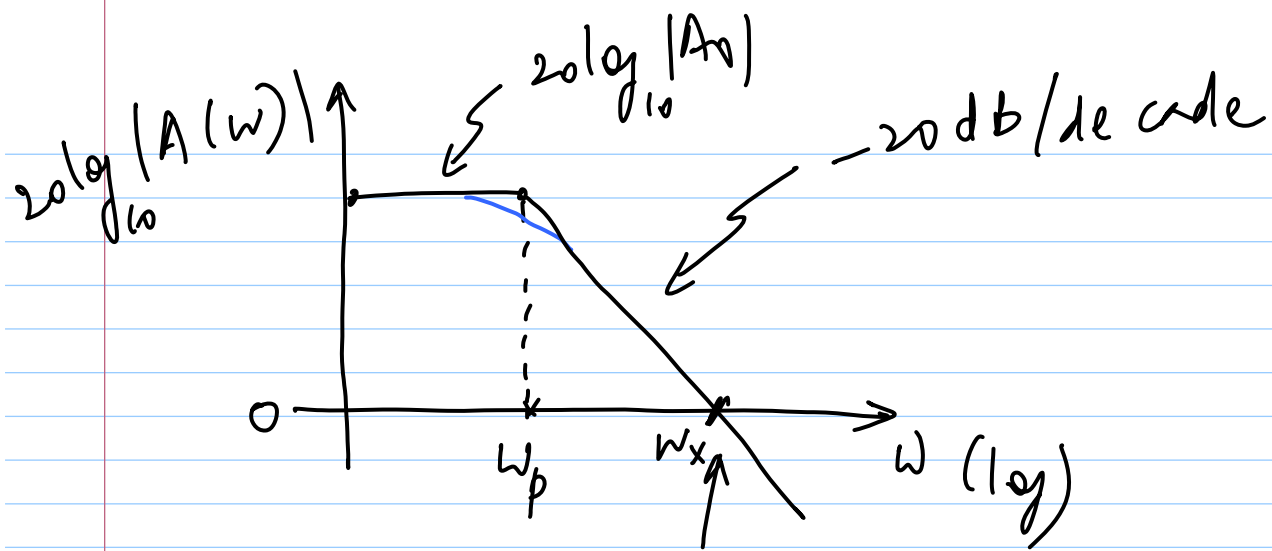

$$A_0 f = \underline{10000}$$

CLG

$$w_x = w_p \cdot A_0$$

$$CLG(s) = \frac{1}{f} \cdot \frac{A(s) \cdot f}{1 + A(s) \cdot f}$$

$$= \frac{1}{f} \cdot \frac{A_0 f}{1 + s/w_p} \cdot \cancel{f} \left[\frac{1}{1 + \left(\frac{A_0 f}{1 + s/w_p} \right)} \right]$$


$$= \frac{1}{f} \cdot \frac{A_0 f}{1 + \frac{s}{w_p} + A_0 f}$$

$$CLG(s) = \frac{1}{f} \cdot \frac{A_0 f}{1 + A_0 f} \cdot \frac{1}{1 + \frac{s}{w_p(1 + A_0 f)}}$$

$$CLG(\omega) = \frac{1}{f} \cdot \frac{A_0 f}{1 + A_0 f} \cdot \frac{1}{1 + \frac{s}{\omega_p(1 + A_0 f)}}$$

$$\text{fwd amp BW} = \omega_p$$
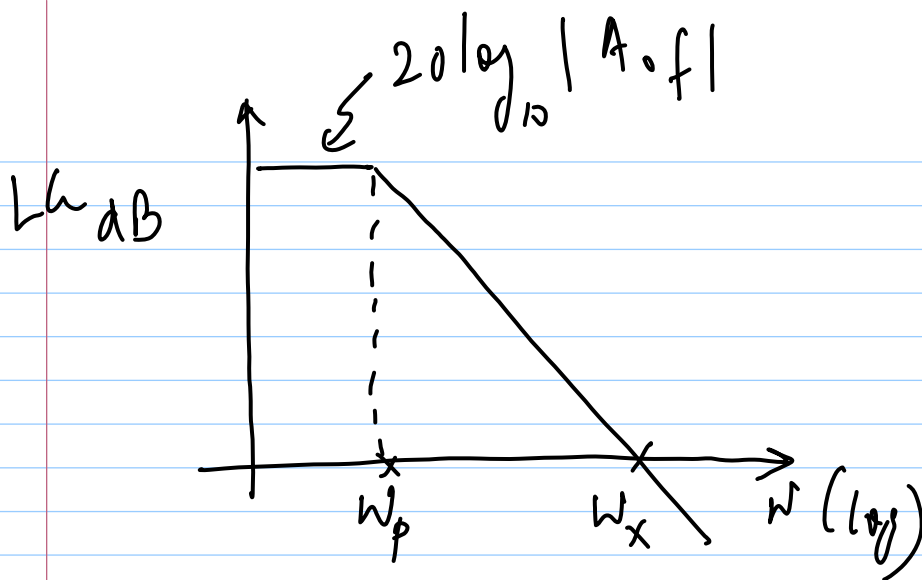
$$CLG \text{ BW} = \omega_p (1 + A_0 f) \approx \omega_p A_0 f$$



$$\omega_x = A_0 f \cdot \omega_p$$

* stability — 1) poles in LHP ✓

2) Unconditionally stable

2-pole system

$$A(s) =$$

$$\frac{A_0}{(1 + s/\omega_p)^2}$$

$$CL(s) = \frac{1}{f} \cdot \frac{A_{of}}{1 + A_{of}} \cdot \frac{1}{1 + \frac{2s}{A_{of} \cdot \omega_p} + \frac{s^2}{\omega_p^2 \cdot A_{of}}}$$

* stability — 1) LHP pole ✓


2) Unconditionally stable

general 2nd order

$$\left(1 + \frac{s}{\omega_0 \cdot Q} + \frac{s^2}{\omega_0^2}\right) \leftarrow \text{Dr.} \quad \checkmark$$

$$\nearrow s^2 + 2\zeta\omega_n s + \omega_n^2 \quad \text{Quality factor}$$
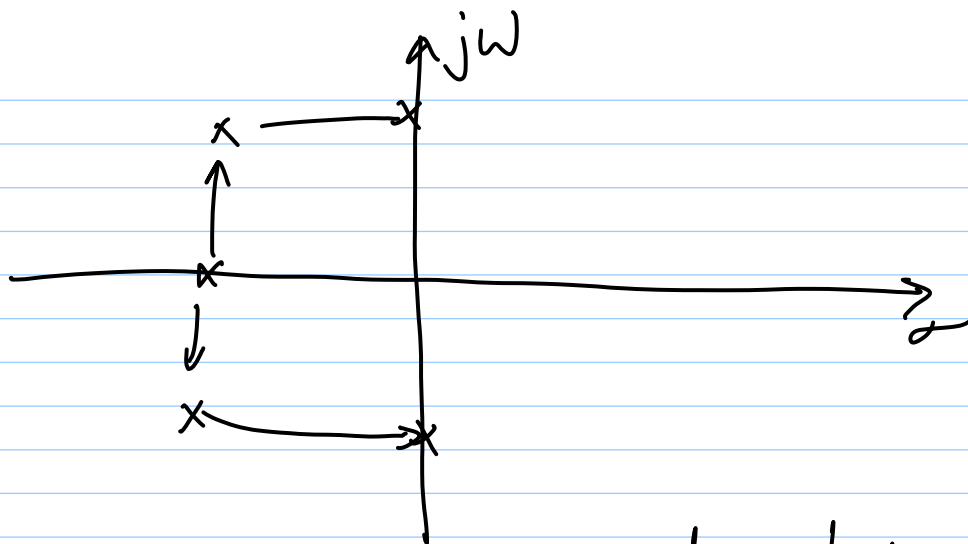
$$\frac{\zeta}{\omega_0} = -\frac{1}{2Q} \pm j\sqrt{1 - \frac{1}{4Q^2}} \quad \checkmark$$



Small $-Q \Rightarrow$ 2 real poles in LHP

$Q = \frac{1}{2} \Rightarrow$ 2 equal poles

$Q > \frac{1}{2} \Rightarrow$ complex conjugate poles

$Q = \infty \Rightarrow$ poles on jw axis