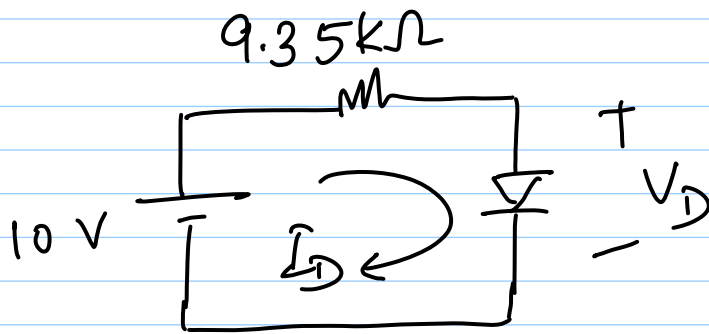


3-8-12

Lec 4




$$V_D \approx 0.65V$$


$$I_D \approx 1mA$$

$$r_d \approx 25\Omega$$

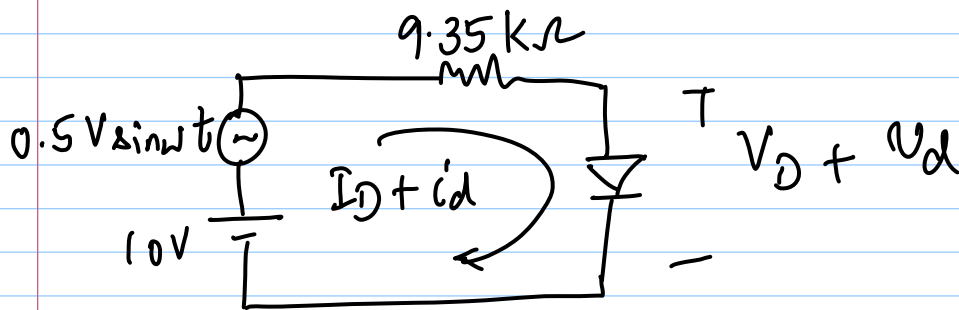Say, a sinusoid is added along with the 1V source.



Incremental network

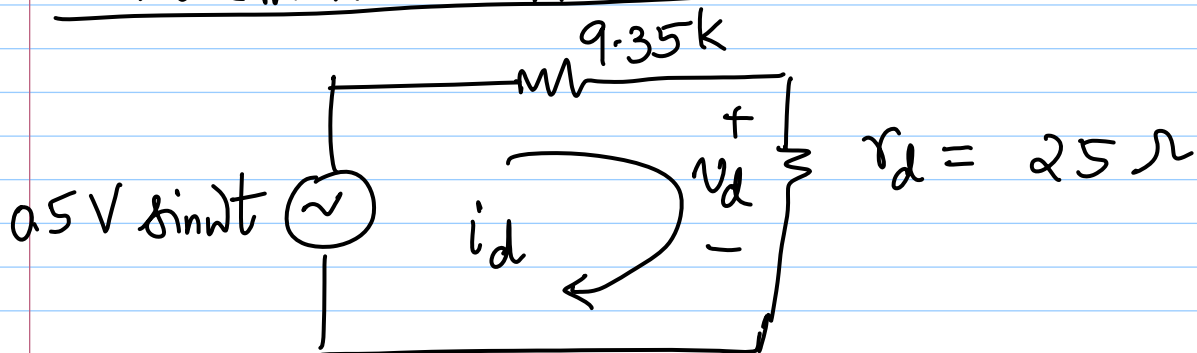

based on earlier calculation for 11V,
you can tell that

$$v_d = 1.35mV \sin \omega t$$

inc. network : $\rightarrow$ all elements are linear
 $\rightarrow$ no dc sources

* Inc. voltage across the diode

$$V_d = \frac{r_d}{r_d + 9.35k} \cdot 0.5V \sin \omega t$$

* Total voltage across the diode is Quiescent + Increment

$$\approx 0.65V + \frac{r_d}{r_d + 9.35k} \cdot 0.5V \sin \omega t$$

* Can be extended to network with several NL elements - replace each $r_i = \frac{1}{f_i(V_i)}$

1) Find operating point








$\rightarrow$ incremental v, i are dependent on the Q-point

$\rightarrow$ solve non-linear equations


2) Draw the incremental equivalent circuit



$\rightarrow$ Linear network

3) Total node voltage or branch current
 $=$ Quiescent voltage/current
 $+ \text{Incremental voltage/current}$

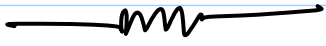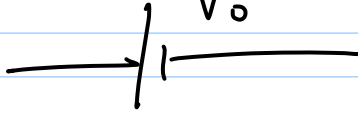 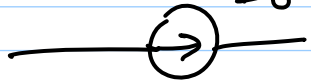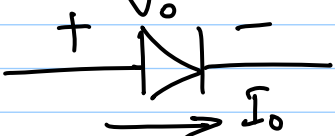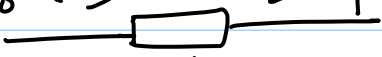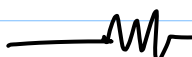
Element	Ther. eqv.
R 	R 
V_o 	 short ckt
I_o 	 open ckt
V_o 	V_t / I_o 
$I_o \Rightarrow$  $I = f(V)$ $+ V_o -$	$r = \frac{1}{f'(V_o)}$ 

Element	Ther. eqv.
V_o 	 open ckt

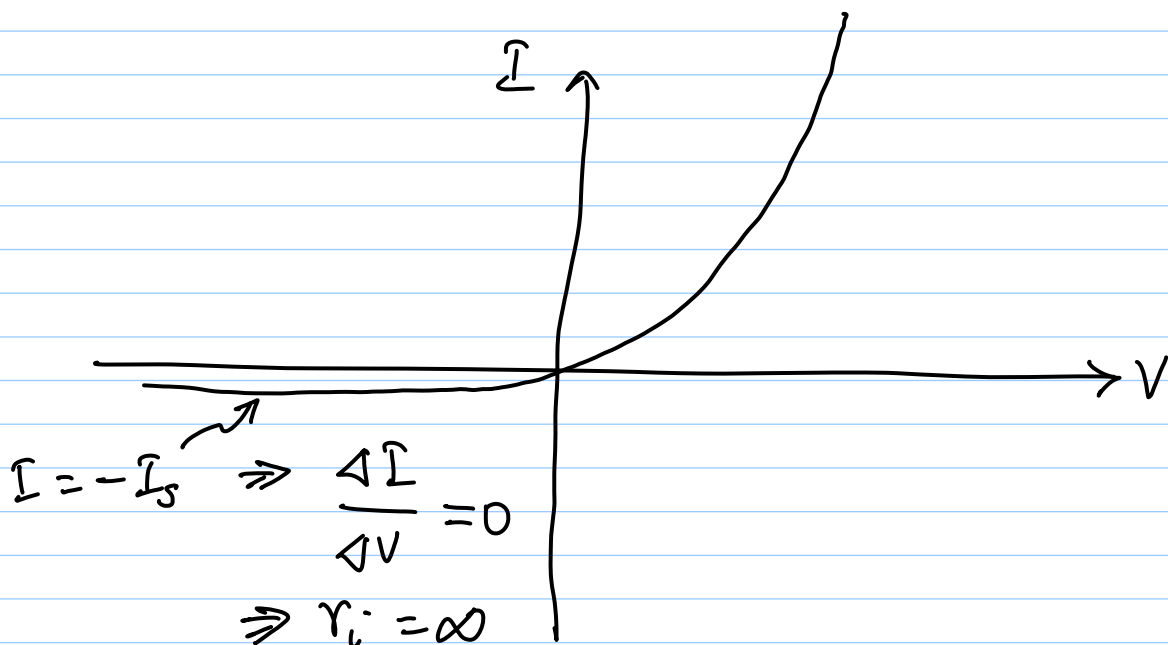

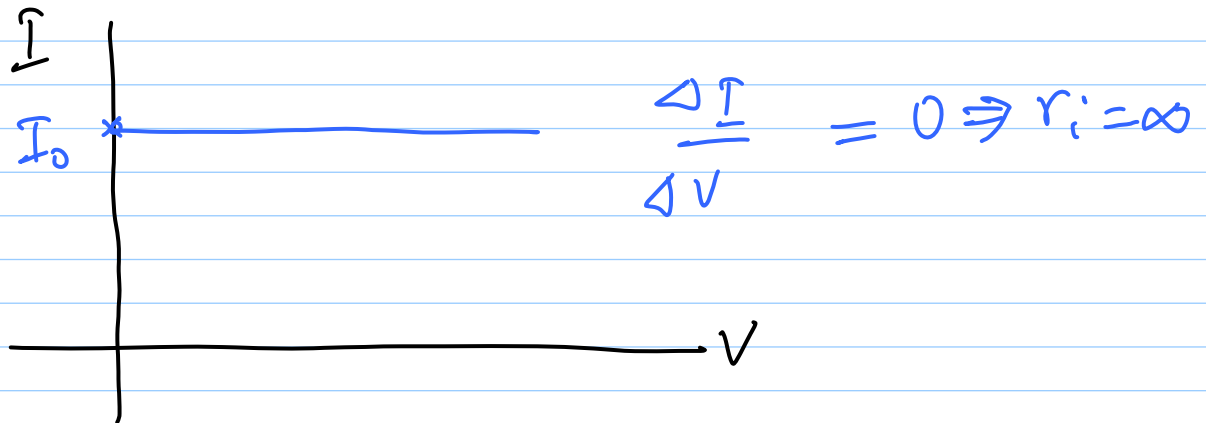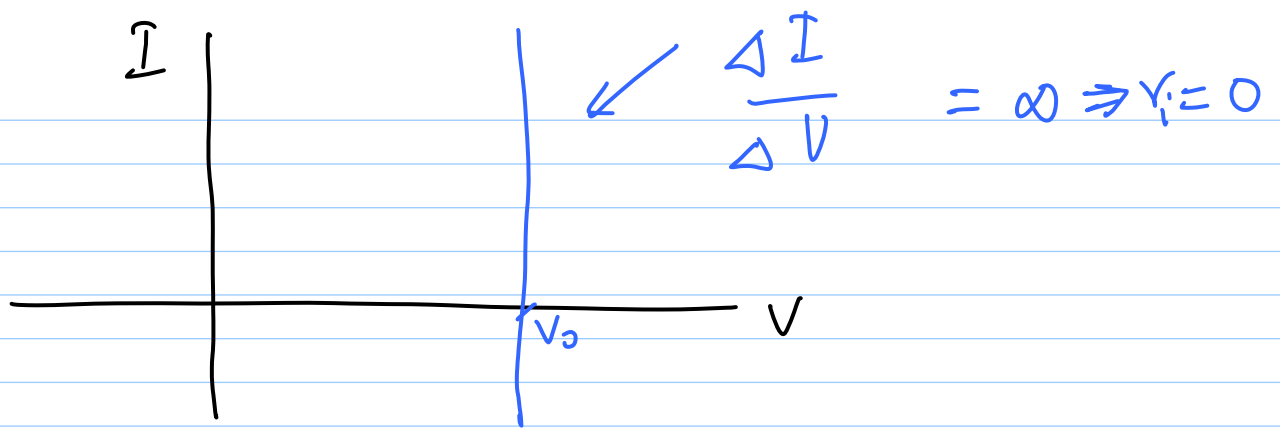


e.g.

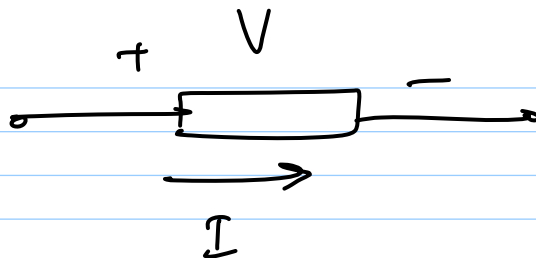


$$I = \alpha V^2, V \geq 0$$

$$= 0, V < 0$$




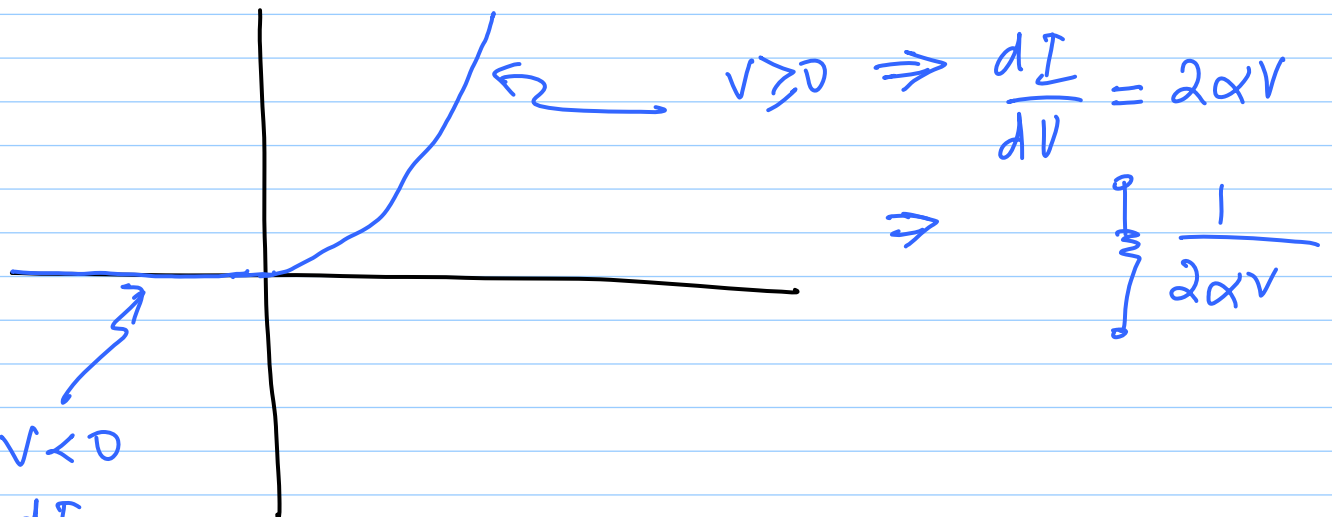


$$\Rightarrow \frac{dI}{dV} = 0$$

$\Rightarrow \rightarrow$ dan seterusnya

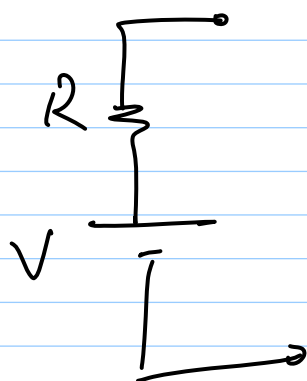

Thc. eav.

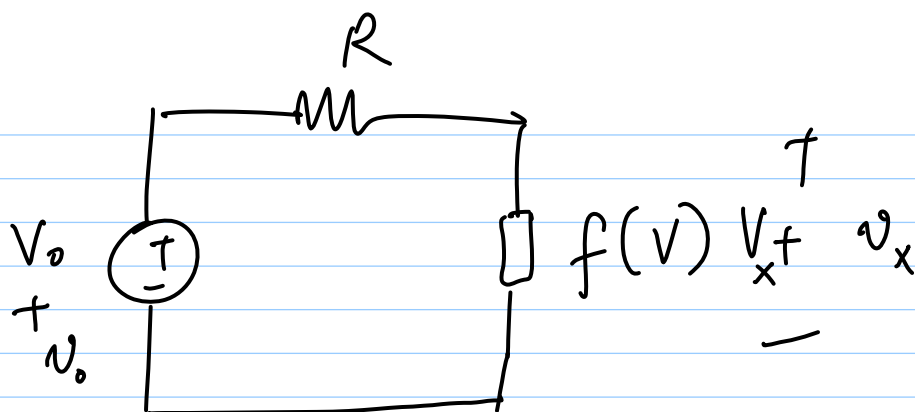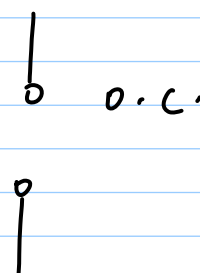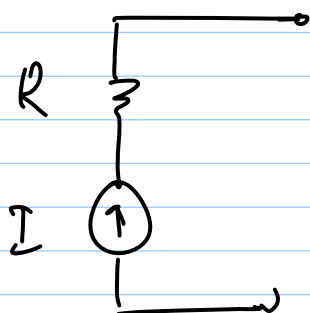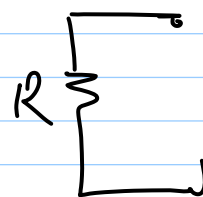

* Is $v_x > V_o$ possible?

$$v_x = \frac{r_i}{R + r_i} V_o$$

Tunnel
Diode

→ only if slope of $f(v)$ is negative in some region of characteristic (and o.p. is in that region)

* purely linear passive devices $\Rightarrow$ Is amplification possible?


$\rightarrow$ voltage gain - Yes (LC, transformer...)

$\rightarrow$ power gain - no

* non-linear devices


$\rightarrow$ incremental voltage & power gain is possible

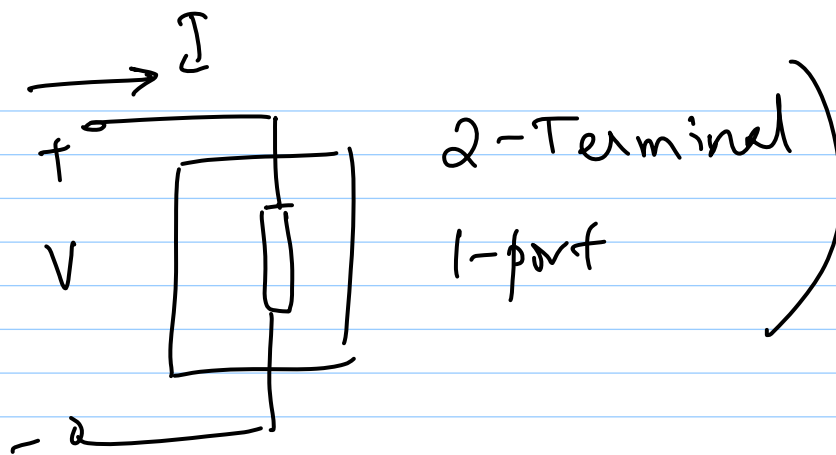$\rightarrow$ Battery power is still used up overall



1 parameter required to describe it
e.g. R

Two-port networks

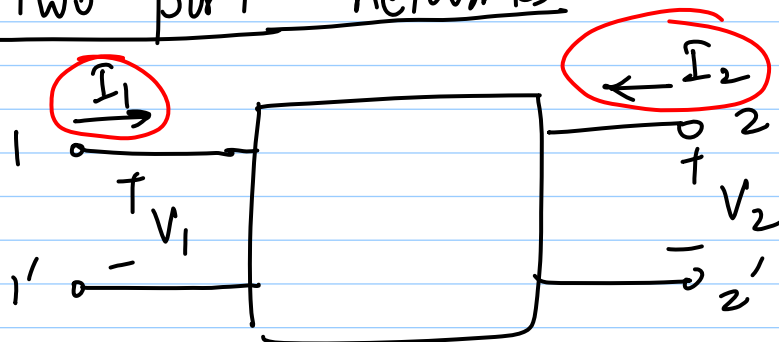

4 parameters required to describe 2-port

* note current directions


$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \underbrace{\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix}}_{\substack{\text{impedance} \\ \text{or } Z\text{-parameters}}} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \underbrace{\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix}}_{Y\text{-parameters}} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

- * Other combos possible
- * $I_1, I_2 = \text{Linear function of } V_1, V_2 \text{ \& vice versa}$

$$I_1 = Y_{11} V_1 + Y_{12} V_2$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2$$

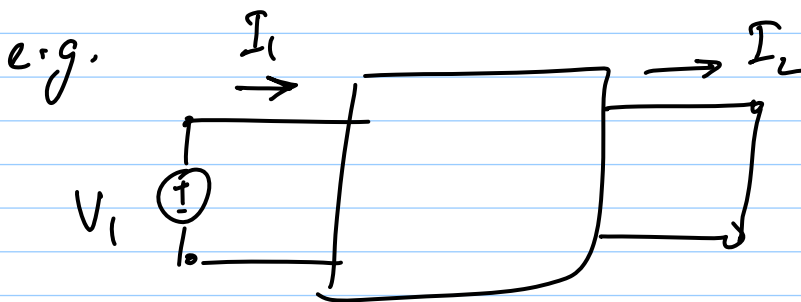

$$I_1 = Y_{11} V_1$$

$$I_2 = -Y_{21} V_1$$