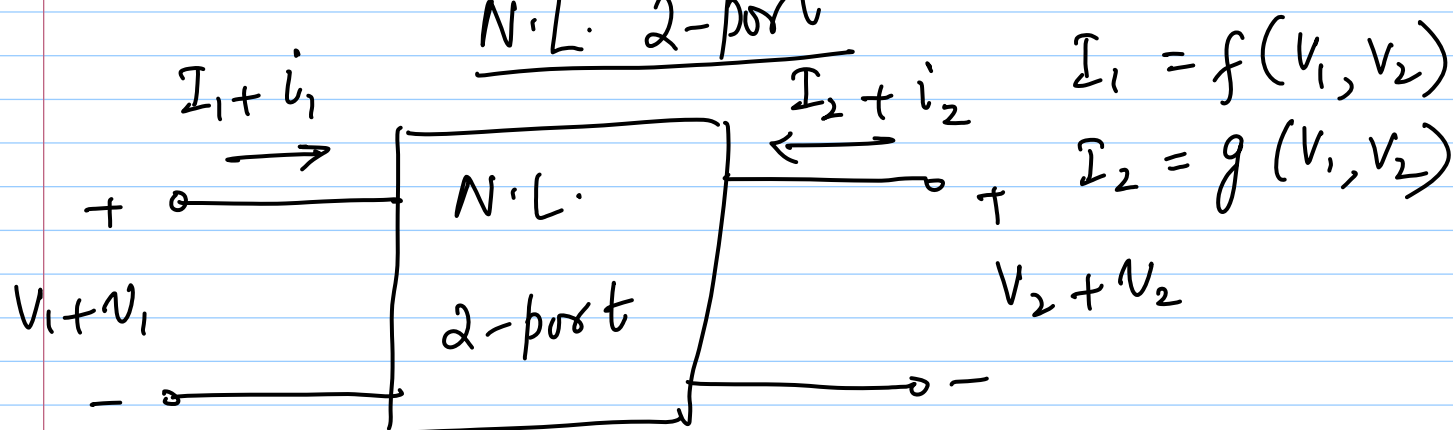


7-8-12

Lec - 5

N.L. 2-port



$$I_1 + i_1 = f(V_1 + v_1, V_2 + v_2)$$

$$I_1 = f(V_1, V_2)$$

* If v_1 & v_2 are very small, $f()$ & $g()$ can be expanded in a 2-D Taylor Series around O.P. $\begin{pmatrix} V_1, I_1 \\ V_2, I_2 \end{pmatrix}$

* Approximate surface by a plane

@ O.P.

$$I_1 + i_1 \approx I_1 + \frac{\partial f}{\partial V_1} \cdot v_1 + \frac{\partial f}{\partial V_2} \cdot v_2$$

$$\Rightarrow i_1 = \frac{\partial f}{\partial V_1} \cdot v_1 + \frac{\partial f}{\partial V_2} \cdot v_2$$

$$iii) \quad i'_2 = \frac{\partial g}{\partial v_1} \cdot v_1 + \frac{\partial g}{\partial v_2} \cdot v_2$$

$\Rightarrow$ incremental 2-port quantities are linearly related

$$\begin{bmatrix} i'_1 \\ i'_2 \end{bmatrix} = \begin{bmatrix} \partial f / \partial v_1 & \partial f / \partial v_2 \\ \partial g / \partial v_1 & \partial g / \partial v_2 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$



incremental y -matrix

$$[i] = [y][v] \text{ for "small signals"}$$

* You could similarly conceive of incremental $[z]$, $[h]$ & $[g]$ parameters


Graphical Representation

$\Downarrow$ 1) Linear 1-port

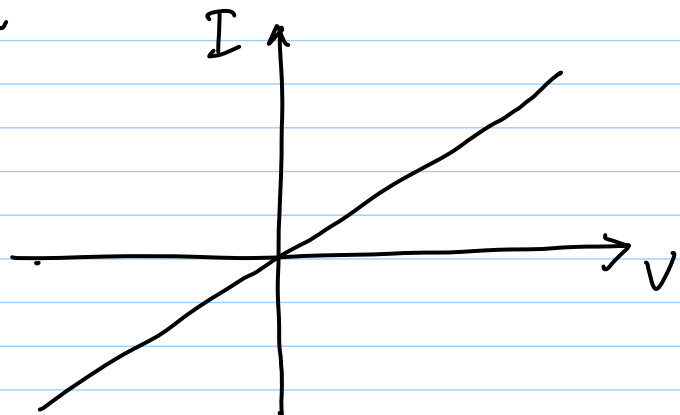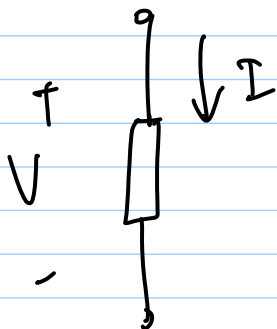


* passive 1-port : $v \cdot i \geq 0 \Rightarrow$ 1st & 3rd quadrants

2) Non-linear 1-port

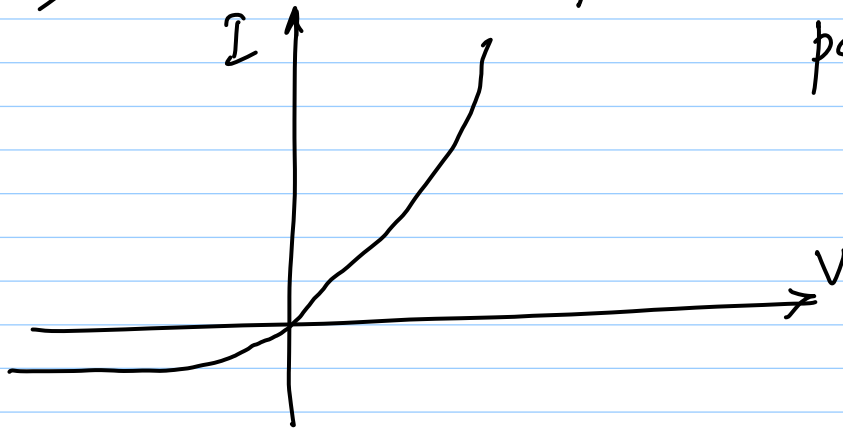

passive $\Rightarrow$ 1st & 3rd Q


II Linear 2-port

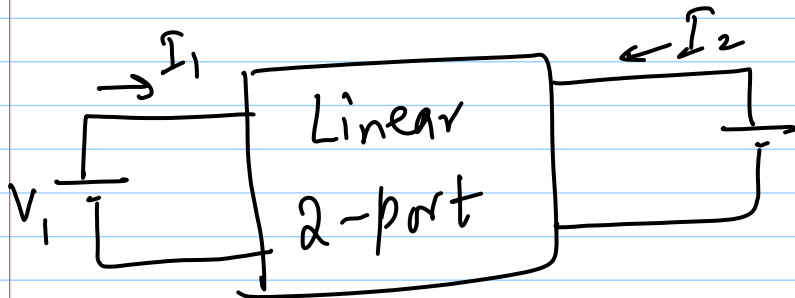

$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$


Output Characteristics

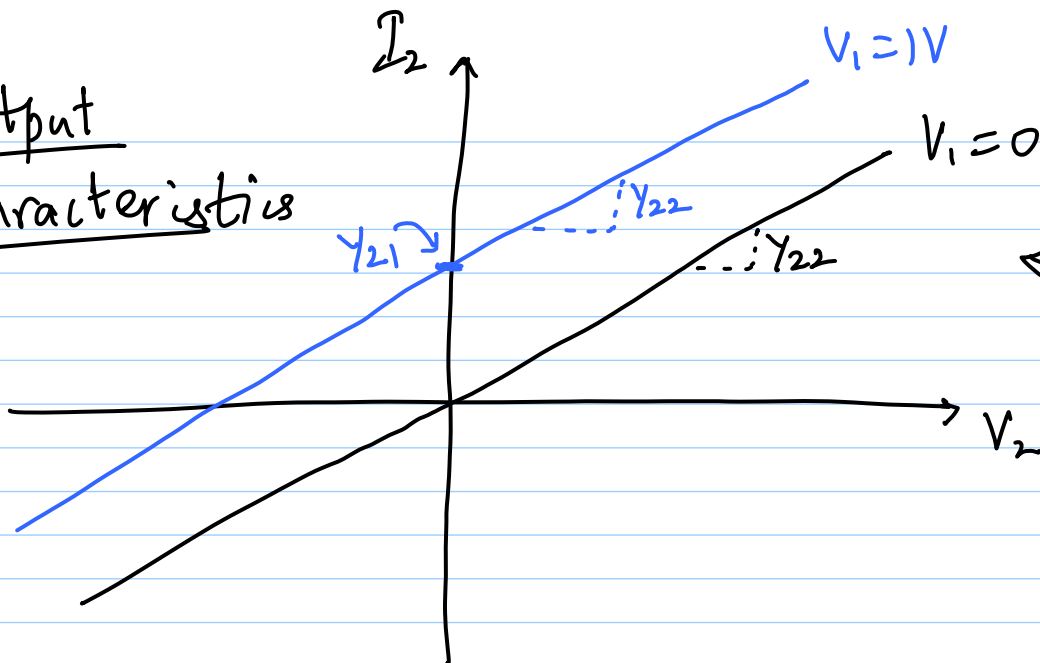

$\leftarrow$ instead of plotting a surface

I_1 vs V_1 plot $\Rightarrow$ Input characteristics
passive linear 2-port $\Rightarrow V_1 I_1 + V_2 I_2 \geq 0$
or
NL


Amplifiers:

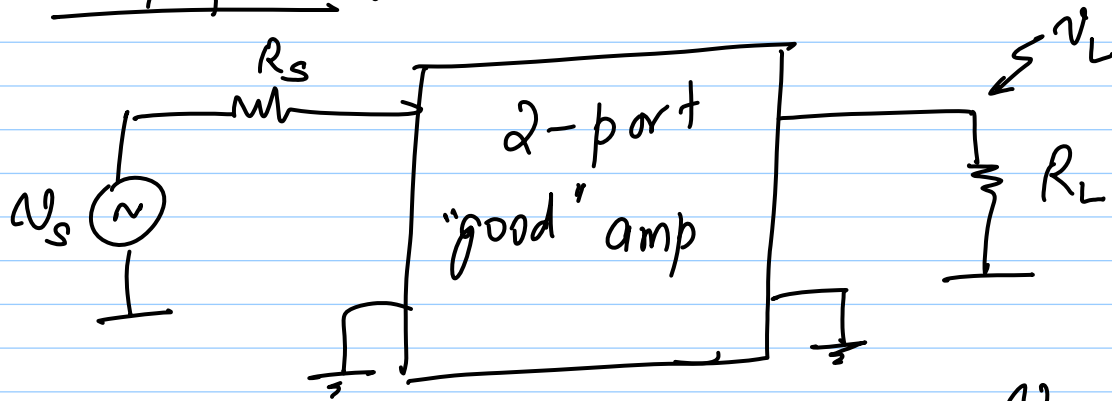

* we want large gain $= \frac{v_L}{v_s}$




* we want v_L to be independent of R_s (i.e. independent of source quality) — i.e. gain should not change if source is changed

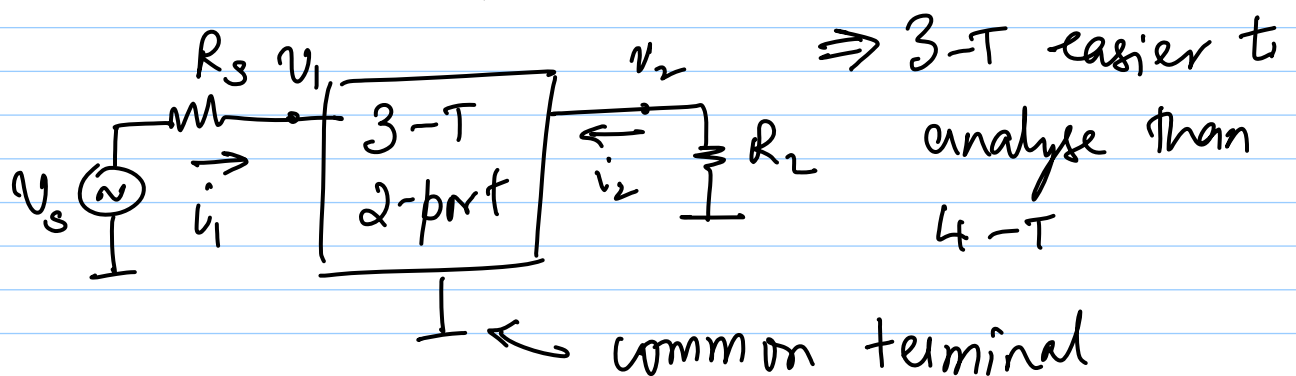* We would also like gain to be independent of R_L too.



What are the constraints on $[y]$ so that we can achieve a "good" amplifier?
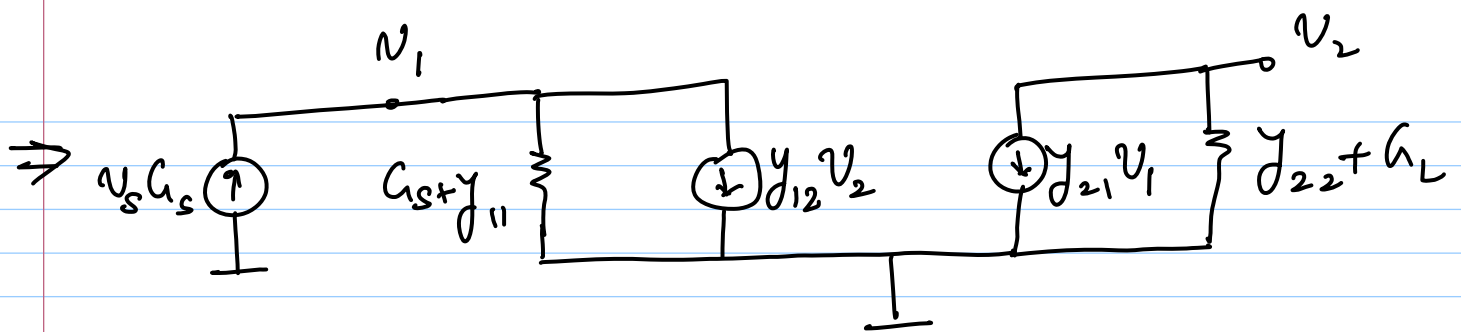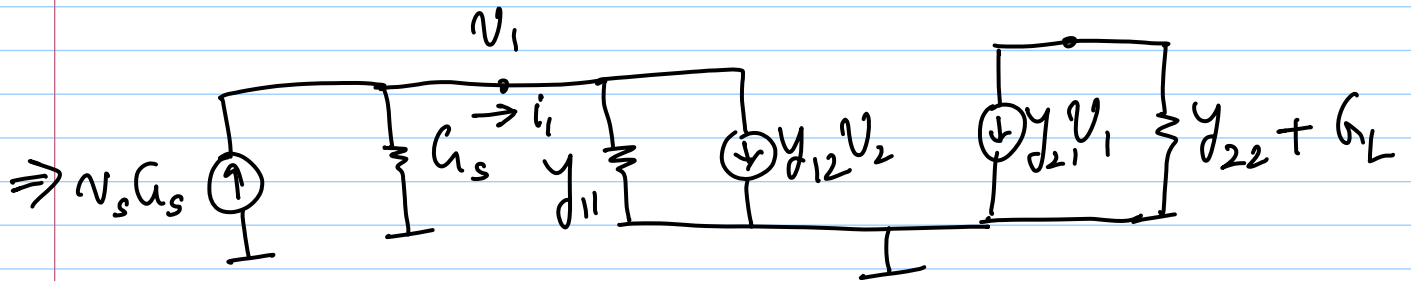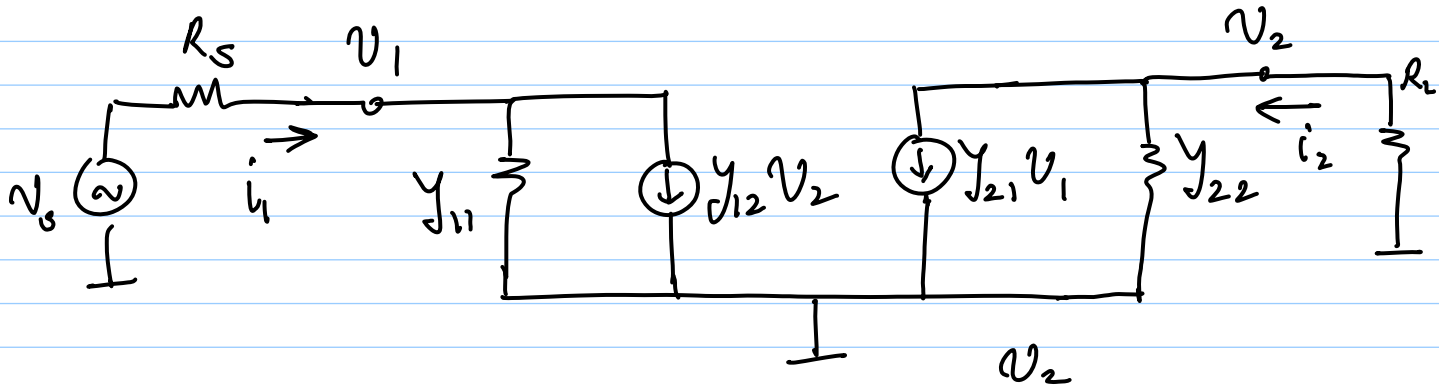
$$\left. \begin{aligned} \hat{i}_1 &= y_{11} v_1 + y_{12} v_2 \\ \hat{i}_2 &= y_{21} v_1 + y_{22} v_2 \end{aligned} \right\} \text{replace by a network}$$



KCL @ input & output :

$$v_s G_s = v_1 (G_s + y_{11}) + y_{12} v_2 \quad \text{--- (1)}$$

$$y_{21} v_1 + v_2 (y_{22} + G_L) = 0 \quad \text{--- (2)}$$

gives

$$v_1 = \frac{v_s G_s - y_{12} v_2}{G_s + y_{11}}$$

plug into (2)

$$y_{21} \left[\frac{v_s G_s - y_{12} v_2}{y_{11} + G_s} \right] + (y_{22} + G_L) \cdot v_2 = 0$$

$$v_s \left[\frac{y_{21} G_s}{y_{11} + G_s} \right] = v_2 \left[\frac{-(y_{22} + G_L) + y_{12} y_{21}}{y_{11} + G_s} \right]$$

$$\Rightarrow v_s \left[\frac{y_{21} G_s}{y_{11} + G_s} \right] = v_2 \left[\frac{y_{12} y_{21} - (y_{22} + G_L)(y_{11} + G_s)}{y_{11} + G_s} \right]$$

$$\Rightarrow \frac{v_2}{v_s} = \frac{y_{21} G_s}{\underbrace{y_{12} y_{21}}_A - \underbrace{(y_{22} + G_L)(y_{11} + G_s)}_B}$$

1) * If $y_{12} y_{21} = (y_{22} + G_L)(y_{11} + G_s)$,

Gain = ∞ ! { instability }

* y_{21} = quantifies effect of i/p port on output port (desired)

* y_{12} = effect of o/p port on i/p port (undesired)

$\Rightarrow$ design for $y_{12} = 0$

$$\Rightarrow \frac{v_2}{v_s} = \frac{y_{21} G_s}{-(y_{22} + G_L)(y_{11} + G_s)}$$