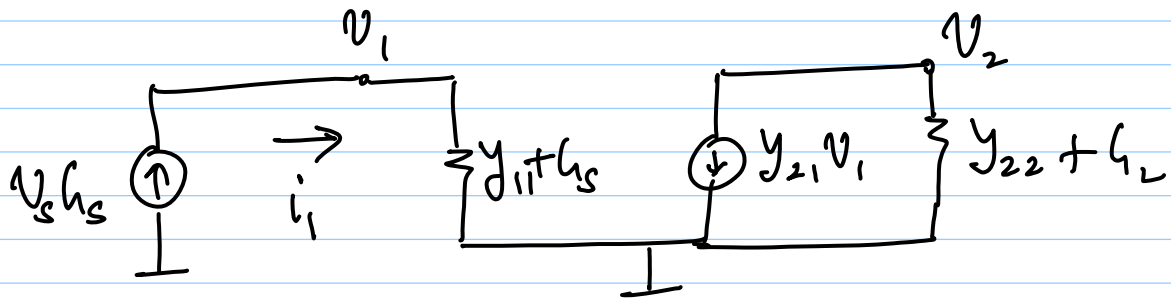


8-8-12

Lec 6

1)



2) Gain independent of G_s

$$\text{Gain} = \frac{-Y_{21}}{(Y_{22} + G_L)} \cdot \frac{G_s}{Y_{11} + G_s}$$

$$\Rightarrow \boxed{\text{set } Y_{11} = 0} \quad \text{i.e. make } i_1 = 0$$

$$\frac{V_2}{V_s} = \frac{-Y_{21}}{Y_{22} + G_L}$$

3) Gain as large as possible

$\Rightarrow Y_{21}$ as large as possible
and

$Y_{22} + G_L$ as small as possible

* We have no control over G_L

$\rightarrow$ make $Y_{22} = 0$

$$\Rightarrow \boxed{\frac{v_2}{v_s} = -\frac{y_{21}}{G_L}} \quad \text{still dependent on } G_L$$

* We need a 2-port network with the following incremental y-matrix

$$\begin{bmatrix} 0 & 0 \\ \text{as large as possible} & 0 \end{bmatrix}$$

$$\text{If } I_1 = f(v_1, v_2) \text{ \& } I_2 = g(v_1, v_2)$$

$$y_{11} = \partial f / \partial v_1 \quad ; \quad y_{12} = \partial f / \partial v_2$$

$$y_{21} = \partial g / \partial v_1 \quad ; \quad y_{22} = \partial g / \partial v_2$$

$$y_{11} = \frac{\partial f}{\partial v_1} = 0 \quad ; \quad y_{12} = \frac{\partial f}{\partial v_2} = 0$$


$$\Rightarrow I_1 = I_0 \text{ (constant)}$$

$$y_{22} = \frac{\partial g}{\partial v_2} = 0 \quad ; \quad y_{21} = \frac{\partial g}{\partial v_1} = \text{large}$$

$\Rightarrow$ we want $I_2 = g(V_1)$ only

$\left. \begin{array}{l} I_1 = I_0 \\ I_2 = g(V_1) \end{array} \right\}$ graphical representation

Output Characteristics

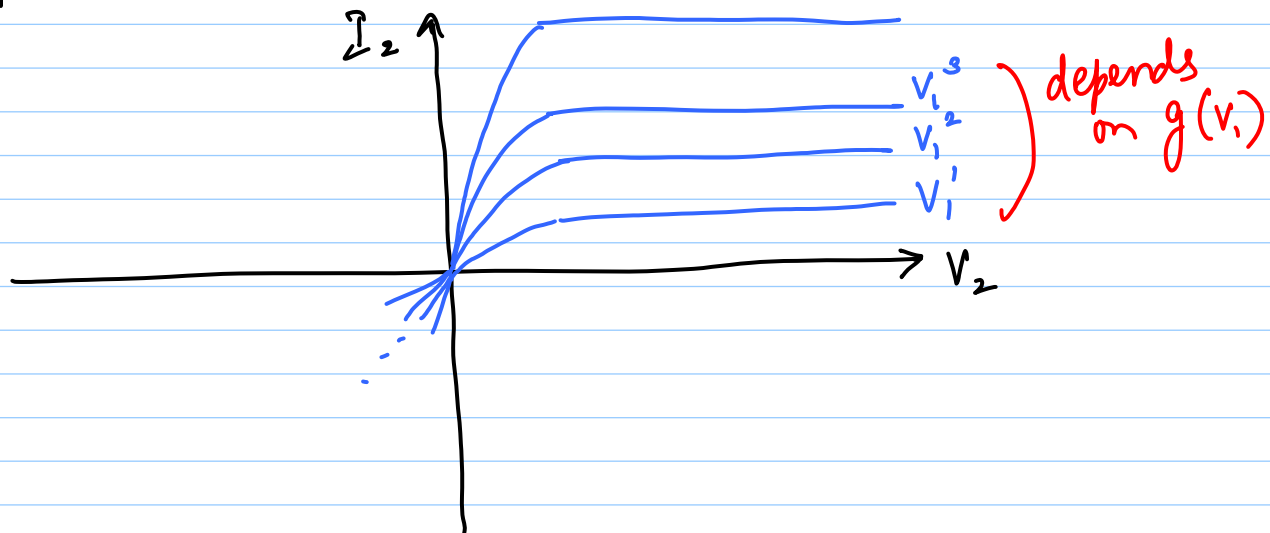

* Special case of $I_1 = 0$

passivity $\Rightarrow \underbrace{V_1 I_1}_0 + V_2 I_2 \geq 0$


$$\Rightarrow V_2 I_2 \geq 0 \quad \left\{ \begin{array}{l} \text{1st \& 3rd Q} \\ \text{only} \end{array} \right\}$$

* All devices that exhibit high incremental gain have characteristics similar to these!

* MOSFET $\Rightarrow I_1 = 0$

JFET, BJT $\Rightarrow I_1$ very small

MOSFET

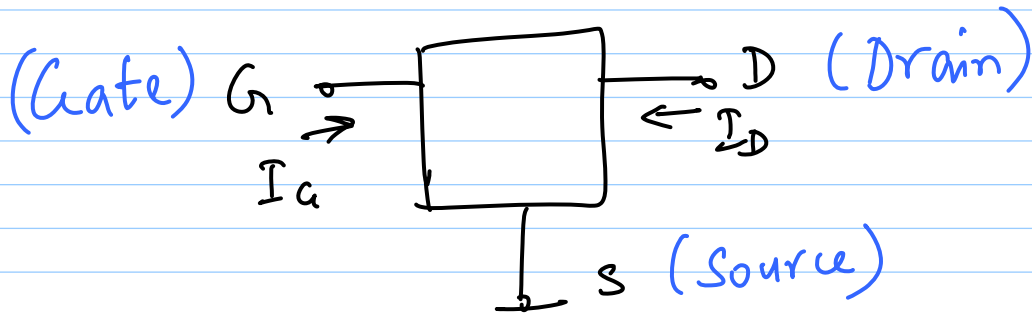

$$I_G = 0$$

I_f $V_{as} > V_T$


$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{as} - V_T)^2 \text{ for } V_{Ds} \geq V_{as} - V_T \quad \text{saturation region}$$

$$= \mu_n C_{ox} \left(\frac{W}{L} \right) \left[(V_{as} - V_T) V_{Ds} - \frac{V_{Ds}^2}{2} \right] \text{ for } V_{Ds} < (V_{as} - V_T)$$


$$I_D = 0 \text{ if } V_{as} < V_T$$

μ_n = mobility of electrons
 C_{ox} = oxide capacitance
 W, L = Geometric parameters
 V_T = Threshold voltage

learn more
in devices
course

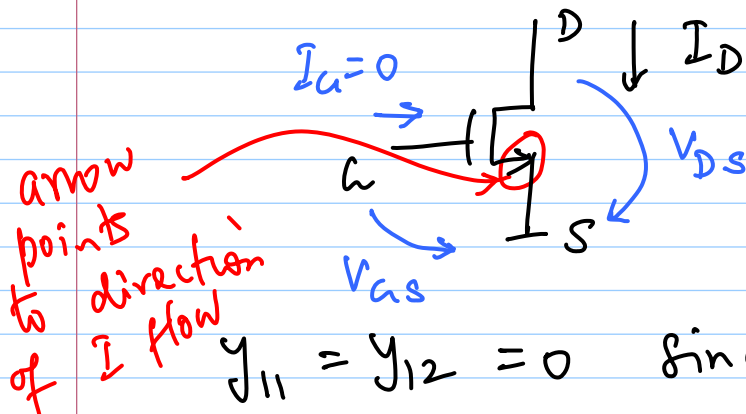


In this course:

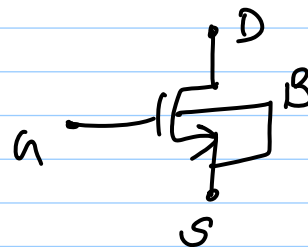

$$y_{11} = y_{12} = 0 \text{ since } I_G = 0$$

$$y_{21} = \partial I_D / \partial V_{as} = \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{as} - V_T) \text{ for } V_{as} > V_T \text{ \& } V_{Ds} \geq V_{as} - V_T$$

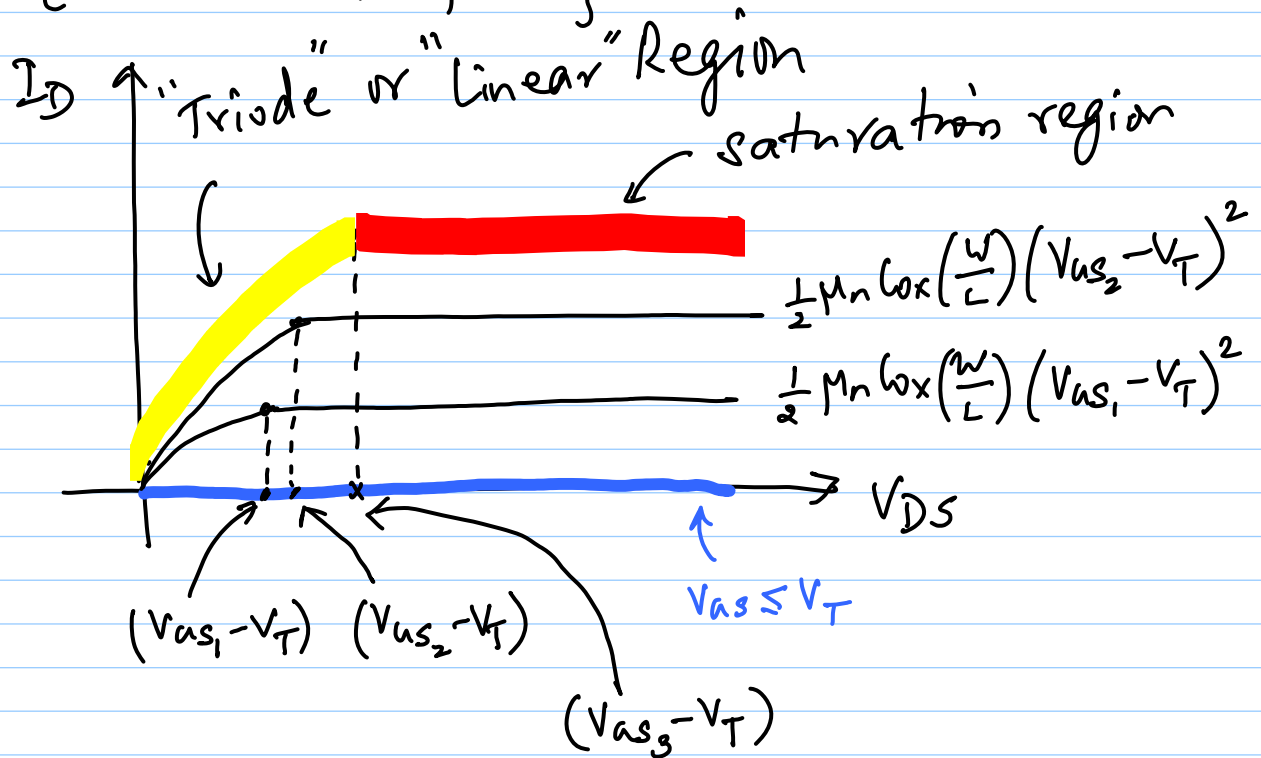* In saturation : I_D is independent of V_{DS}
 $\{ I_2 \text{ indep. of } V_2 \}$



* "Enhancement mode" MOSFET
 or "normally OFF" device :

$$V_T > 0 \Rightarrow @ V_{GS} = 0$$


$$I_D = 0$$

e.g. If $V_T = 0.3V$, $I_D = 0$ for $V_{GS} \leq 0.3V$
 $I_D > 0$ for $V_{GS} > 0.3V$


* "Depletion mode" MOSFET

or "normally ON" device

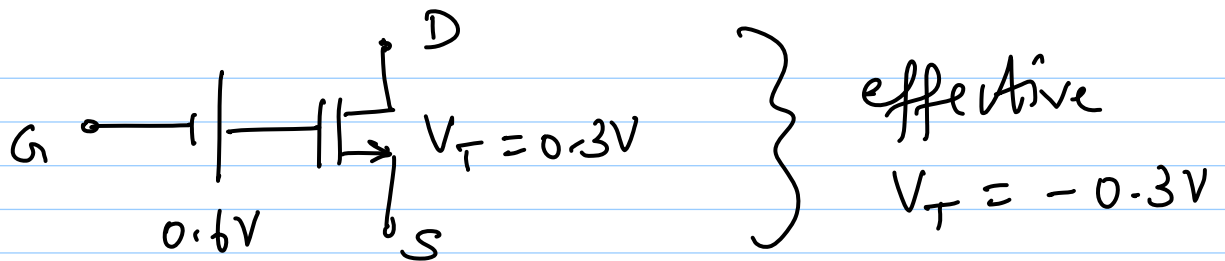
$$V_T < 0 \Rightarrow @ V_{GS} = 0, I_D > 0$$



→ everything else is the same

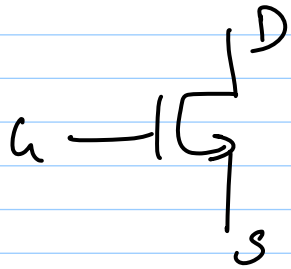

⇒ nMOS transistor
→ e^- carriers

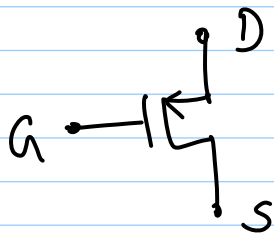

⇒ pMOS transistor
→ hole carriers

later in the course

enhancement mode nMOS transistor equations:

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_T)^2 \begin{cases} V_{GS} \geq V_T \\ V_{DS} \geq V_{GS} - V_T \end{cases}$$

$$= \mu_n C_{ox} \left(\frac{W}{L} \right) \left[(V_{GS} - V_T) V_{DS} - \frac{1}{2} V_{DS}^2 \right] \begin{cases} V_{GS} \geq V_T \\ V_{DS} < V_{GS} - V_T \end{cases}$$