
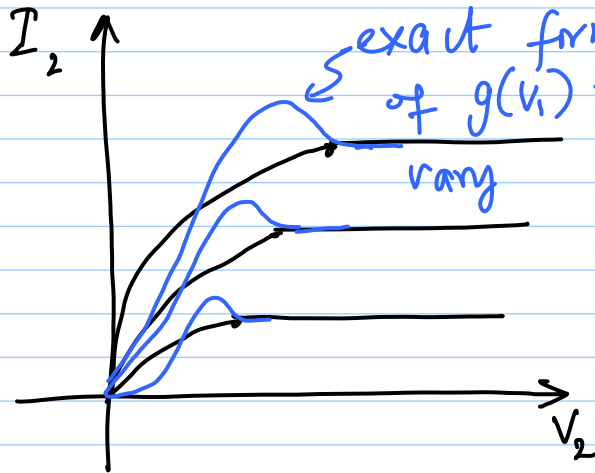


9-8-12

Lec 7

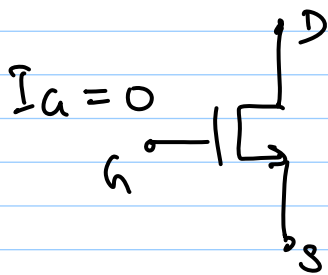


$I_1 = 0$ and
passive 2-port
 $\Rightarrow$ 1st & 3rd - Q
only



$I_D = 0$ for $V_{GS} < V_T$

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_T)^2 \begin{cases} V_{GS} \geq V_T \\ V_{DS} \geq V_{GS} - V_T \end{cases}$$
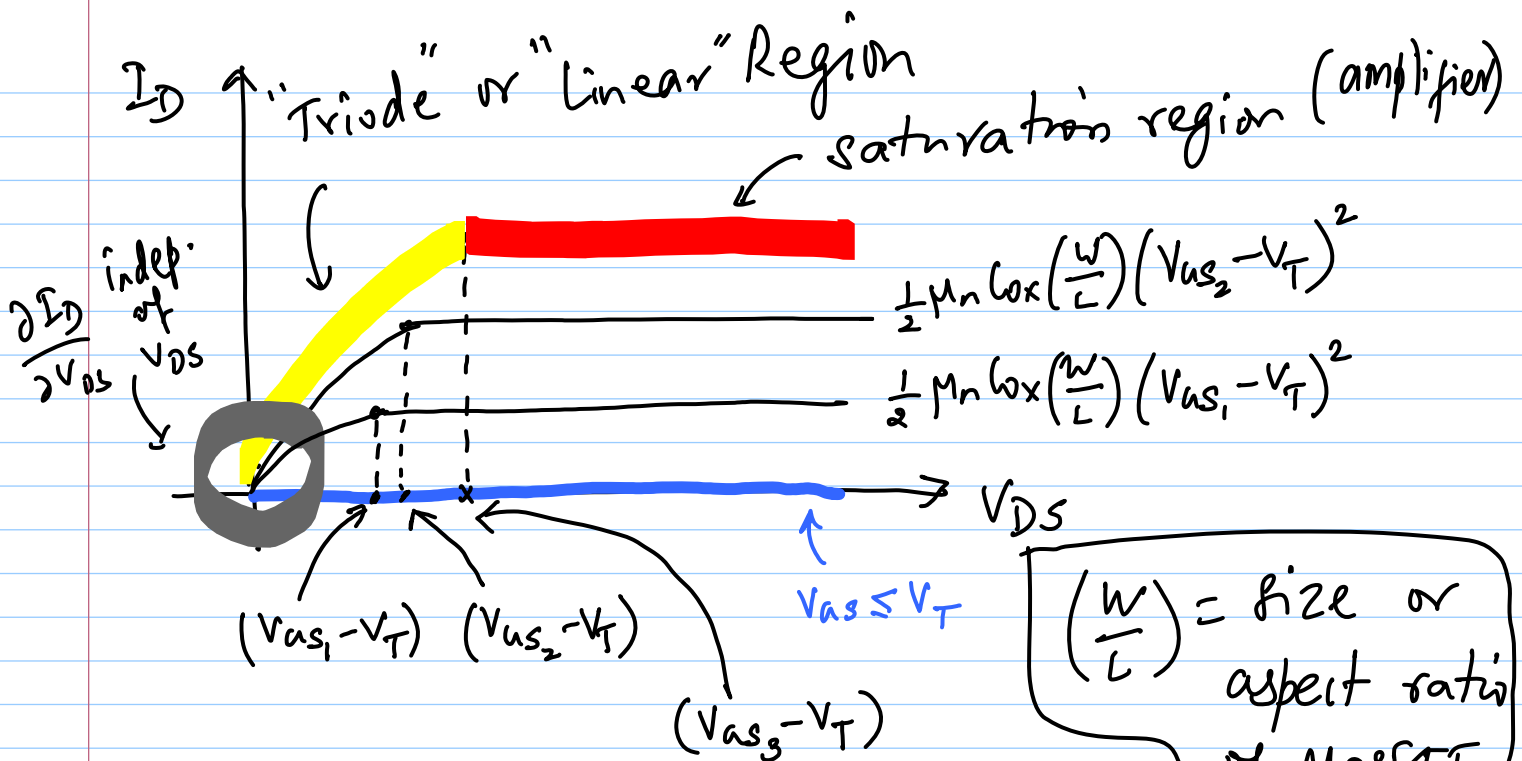
$$I_D = \mu_n C_{ox} \left(\frac{W}{L} \right) \left[(V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right] \begin{cases} V_{GS} \geq V_T \\ V_{DS} < V_{GS} - V_T \end{cases}$$



$V_{DS} < V_{GS} - V_T \Rightarrow$ Linear region

$$I_D = \mu_n C_{ox} \left(\frac{W}{L} \right) \left[(V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right]$$

$$\frac{\partial I_D}{\partial V_{DS}} = \mu_n C_{ox} \left(\frac{W}{L} \right) [V_{GS} - V_T - V_{DS}] \quad \left\{ = y_{22} \right\}$$

$$\approx \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_T) \quad \text{if } V_{DS} \ll V_{GS} - V_T$$

$\Rightarrow$ Voltage-controlled resistor

$$r_{ds} = f(V_{GS} - V_T)$$

$$(V_{GS} - V_T) = V_{DSat} \quad \text{If } V_{DS} < V_{DSat}, y_{22} \neq 0$$

Sometimes also $= V_{OV}$ or Gate overdrive voltage

$$V_{DS} = V_{GS} - V_T = \text{limit of sat. region}$$

$$V_D - V_S = V_G - V_S - V_T$$

$$\Rightarrow V_D = V_G - V_T \quad (\text{decoupled from source voltage})$$

In saturation:

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_T)^2$$

$$y_{11} = 0, \quad y_{12} = 0, \quad y_{22} = 0$$

$$y_{21} = \frac{\partial I_D}{\partial V_{GS}} = \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_T)$$

$g_m \Rightarrow$ units of conductance, but
i/p and o/p ports are involved

"transconductance" $g_m = \frac{\partial I_D}{\partial V_{GS}}$
 $= \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)$

Different expressions:

1) $g_m = \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_T)$

2) $g_m = 2 \times \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_T)^2 \div (V_{GS} - V_T) = \frac{2 I_D}{V_{GS} - V_T}$


3) $g_m^2 = \frac{2}{2} \mu_n^2 C_{ox}^2 \left(\frac{W}{L} \right)^2 (V_{GS} - V_T)^2$

$= 2 \mu_n C_{ox} \left(\frac{W}{L} \right) I_D$

$\Rightarrow g_m = \sqrt{2 \mu_n C_{ox} \left(\frac{W}{L} \right) I_D}$

All 3 forms
of g_m show
dependence on
operating point



MOSFET Amplifier

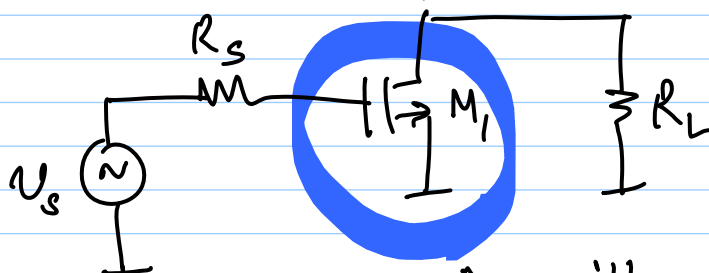

small-signal
picture

$\swarrow$ will work as amplifier if
 M_1 is in saturation region

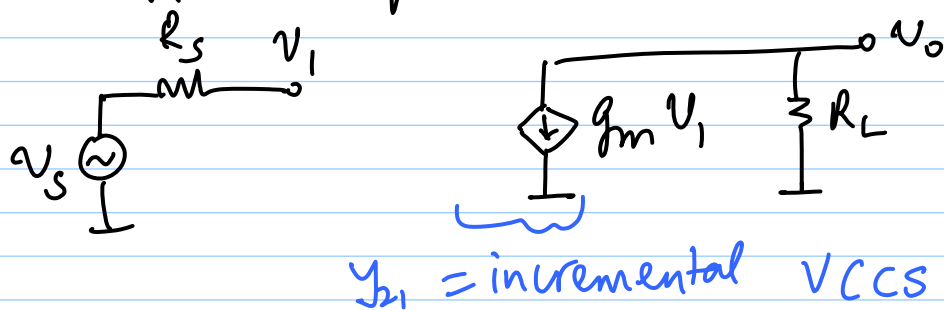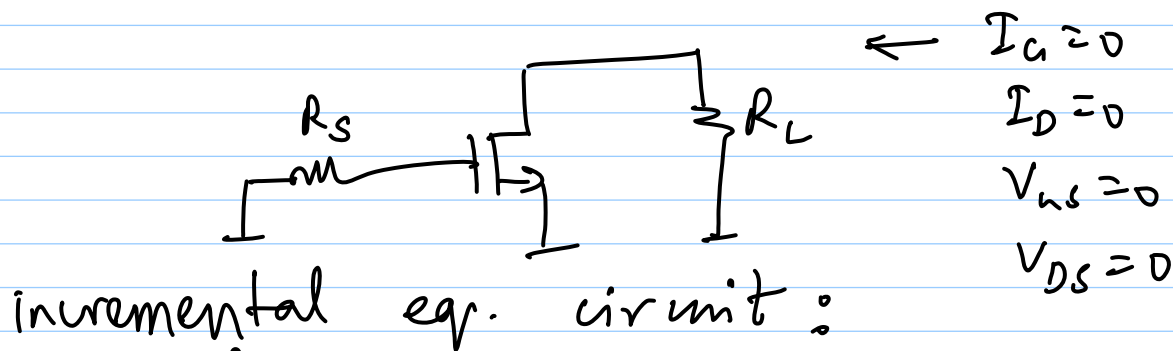i.e. operating point should be in saturation region





$$\frac{v_o}{v_i} = -g_m R_L$$

Incremental gain depends on op. pt. -
through g_m
Transistor "biasing"

Op. point:


* $V_{DS} \geq V_{GS} - V_T$

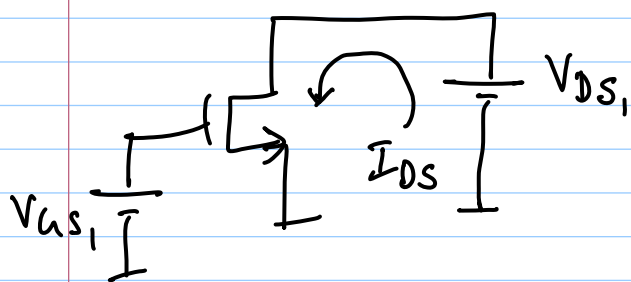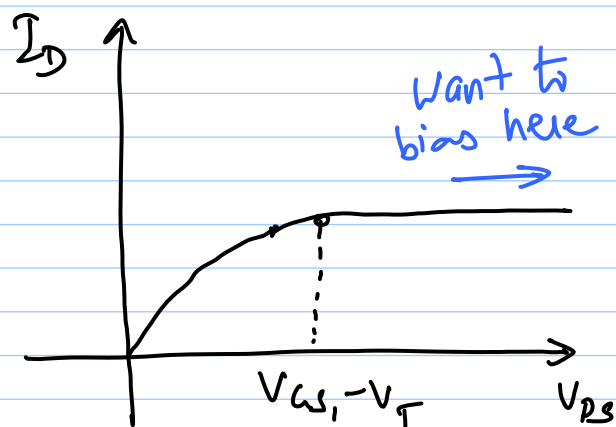

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS1} - V_T)^2$$

* $V_{DS1} \gg V_{GS1} - V_T$ is desirable


adding signal source:

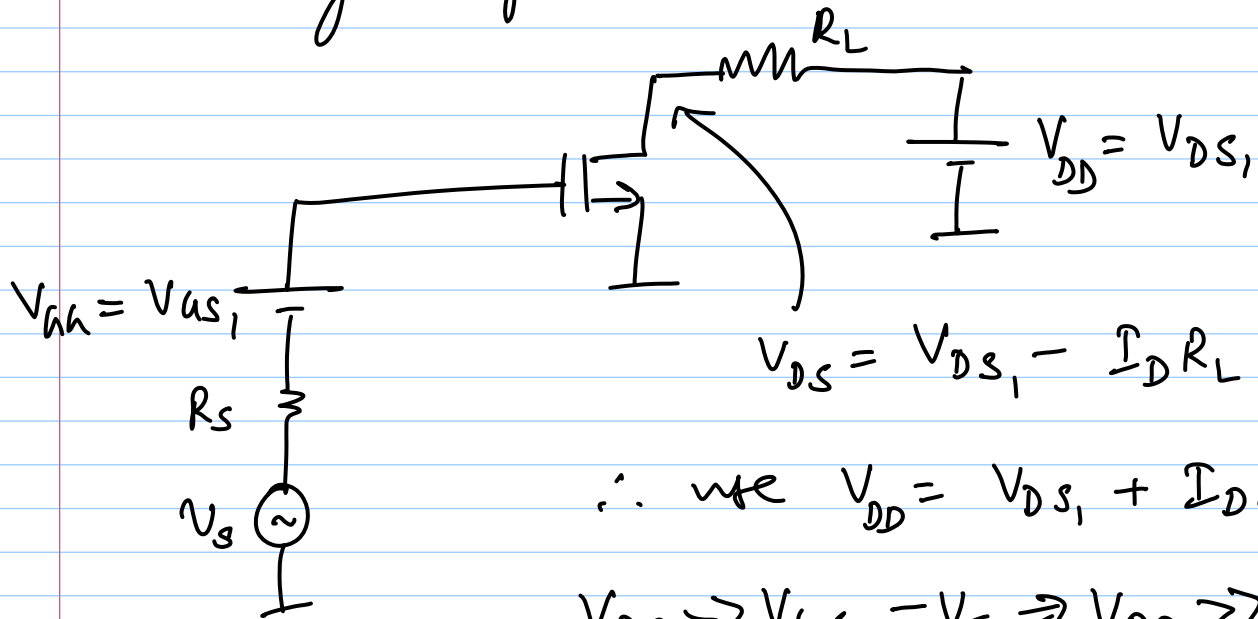

$$\therefore \text{we use } V_{DD} = V_{DS,1} + I_D R_L$$

$$V_{DS,1} > V_{Gh,1} - V_T \Rightarrow V_{DD} > V_{as,1}$$

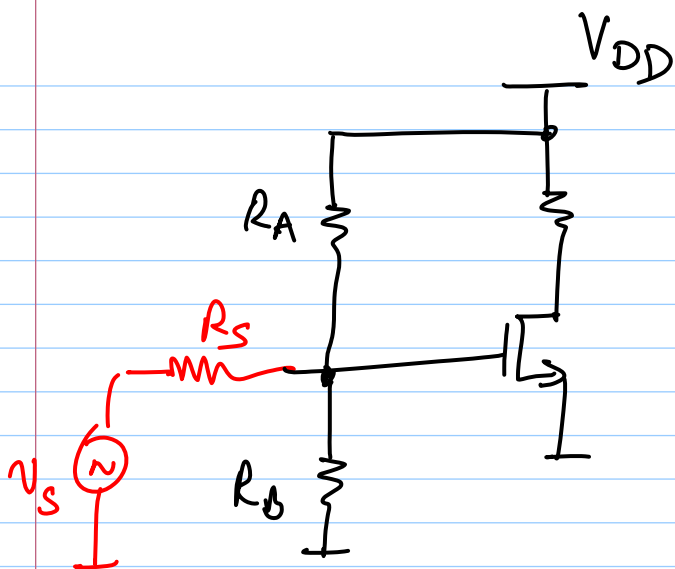* We don't want to use multiple batteries
 $\rightarrow$ generate $V_{as,1}$ from V_{DD}



$$V_{DD} \cdot \frac{R_B}{R_A + R_B} = V_{as,1}$$

increment cannot be added directly
 $\Rightarrow$ OP will change due to R_s
 e.g. if $R_s = 0 \Rightarrow V_{as,1} = 0$