
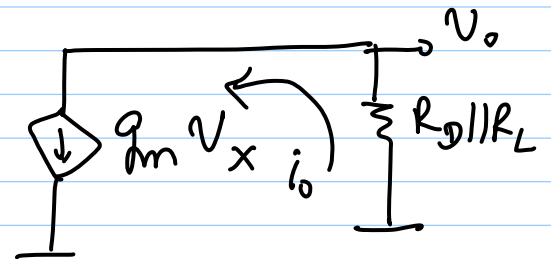
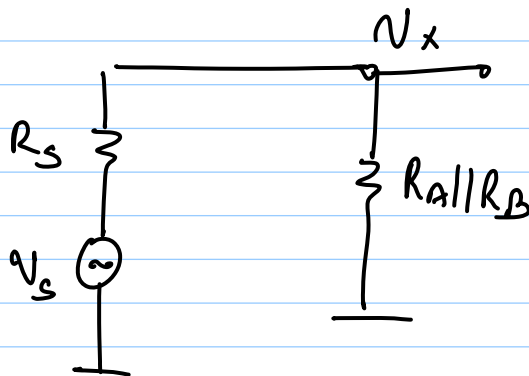




16-8-12

Lec 9

Common Source Amplifier

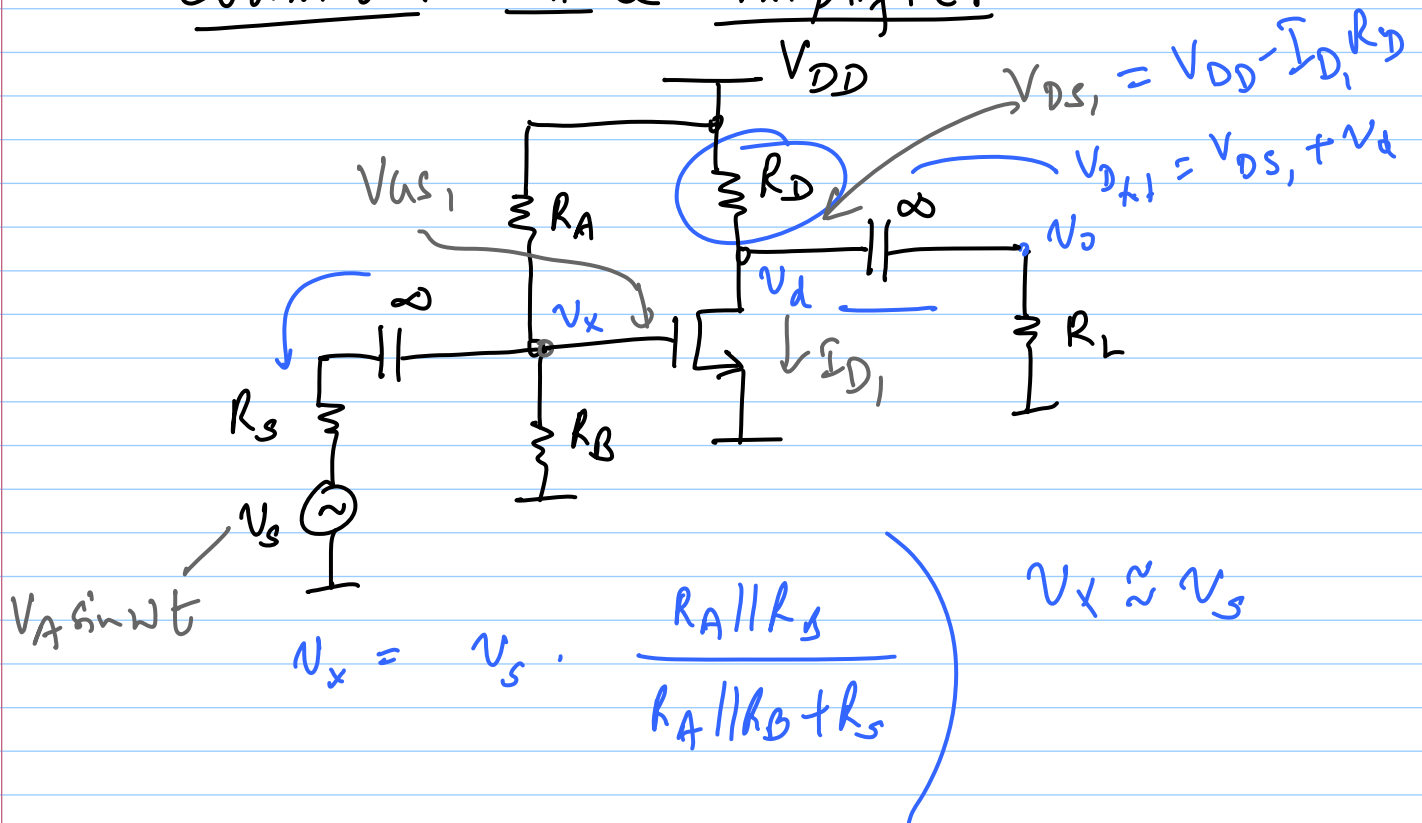

$$\begin{aligned}
 \frac{v_o}{v_s} &= \frac{v_x}{v_s} \cdot \frac{v_o}{v_x} = \frac{v_x}{v_s} \cdot \frac{i_o}{v_x} \cdot \frac{v_o}{i_o} \\
 &= \frac{R_A || R_B}{R_A || R_B + R_s} \cdot \left\{ -g_m (R_D || R_L) \right\} \\
 &\approx -g_m (R_D || R_L) = -G
 \end{aligned}$$

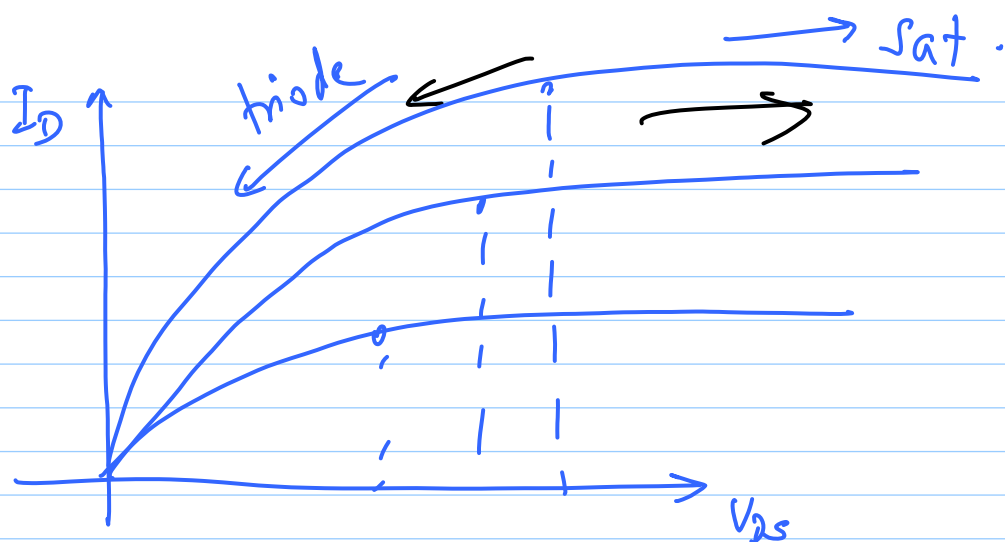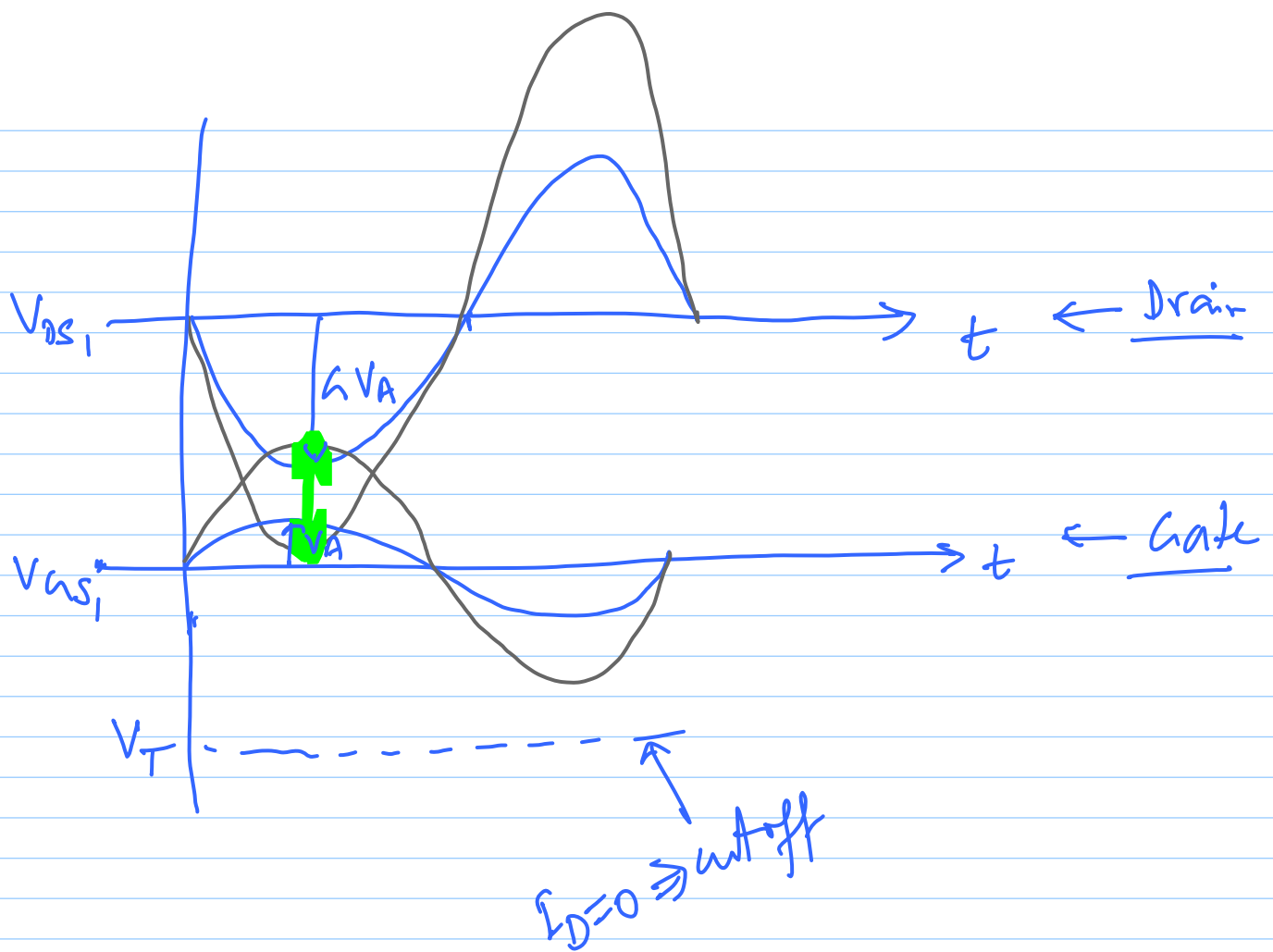

$$V_{DS} = V_{GS} - V_T$$

$$V_D - V_S = V_G - V_S - V_T$$

$$\boxed{V_D = V_G - V_T} \quad \text{limit of triode region}$$

In triode


$$I_D = \mu_n C_{ox} \left(\frac{W}{L} \right) \left[(V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right]$$

$$y = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \quad \begin{matrix} y_{11} = 0 \\ y_{12} = 0 \end{matrix}$$

$$y_{21} = \frac{\partial I_D}{\partial V_{GS}} = \mu_n C_{ox} \left(\frac{W}{L} \right) \underline{V_{DS}} = g_{m_{triode}}$$

$$g_{m_{sat.}} = \mu_n C_{ox} \left(\frac{W}{L} \right) (\underline{V_{GS} - V_T})$$
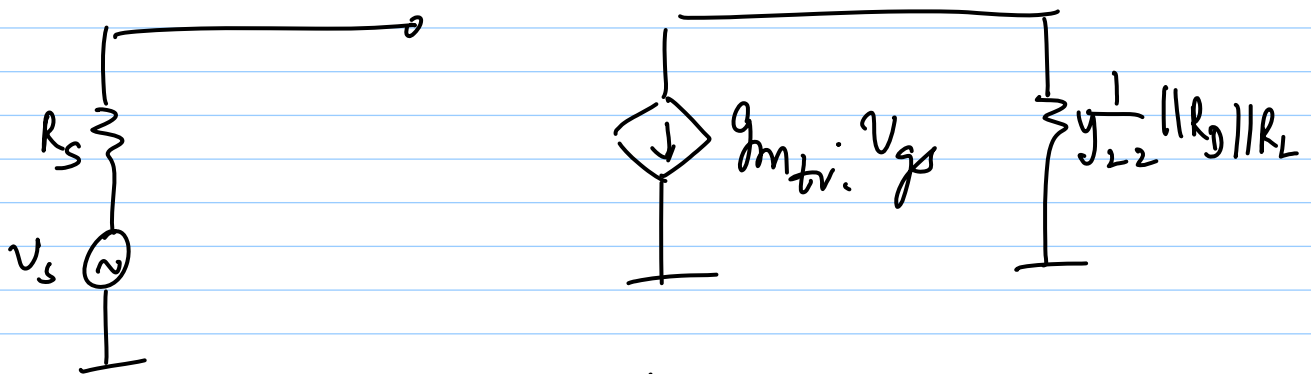
$$y_{22} = \frac{\partial I_D}{\partial V_{DS}} = \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_T - V_{DS})$$



$$\text{gain} = - \underline{g_{m_{tr.}}} \cdot \underline{\left(\frac{1}{y_{22}} \parallel R_D \parallel R_L \right)}$$

< gain in sat.

