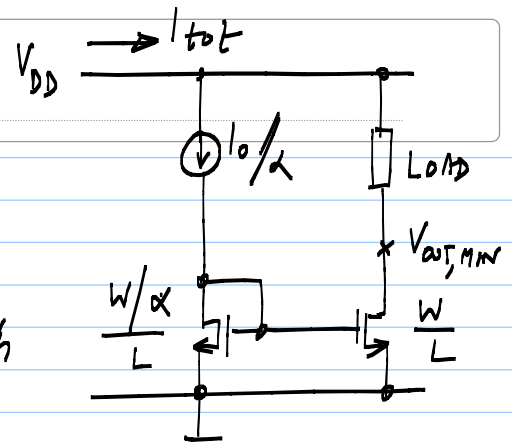


## EE5390 Assignment 1

Thursday 14/02/2013

- ① The current mirror shown on the right delivers a current  $I_0$  to the load. The reference branch current can be tailored using the parameter  $\alpha$ .




- \* The transistors must be sized to allow a minimum voltage of  $V_{out, min}$  in saturation region.
- \* The total current must be  $I_{tot}$

- \* The signal (current in the load) to the noise (rms current in a bandwidth  $f_B$ ) has to be maximized.

Determine  $W/L$ ,  $\alpha$ , output signal & noise rms in terms of the given parameters.

② In the cascode current mirror shown here, all transistors are in saturation region.

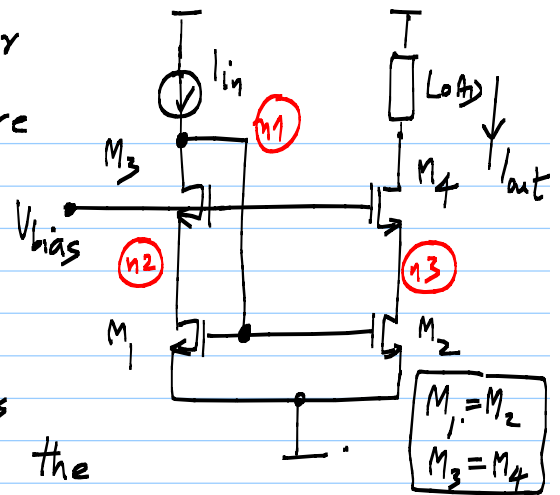Model  $M_{1,2}$  by  $g_m$ ,  $g_{ds} \rightarrow 0$   
 Model  $M_{3,4}$  by  $g_{m3}$  for all transistors



- (i) Determine the noise PSD of the output current due to each transistor separately
- (ii) Determine the current error in the output due to  $\Delta V_{T,12}$  &  $\Delta V_{T,34}$  separately


(iii) Determine  $\frac{I_{out}(s)}{I_{in}(s)}$  by including a parasitic capacitor  $C_p$  to nodes  $n1$ ,  $n2$ , and  $n3$ , one at a time

(Not to be submitted:

Reason out why the above results come out the way they do)

③ For the RC filter,

determine

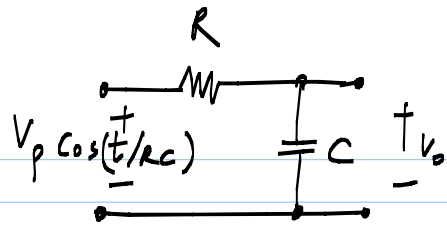

(a) Mean squared o/p signal ( $S$ )

(b) Mean squared o/p noise ( $N$ )


(c) Ratio  $S/N$

(d) Power dissipated in the resistor ( $P_d$ )

(e) Bandwidth in Hz ( $f_B$ )

Express the power dissipated ( $P_d$ ) in terms of the signal to noise ratio and the bandwidth

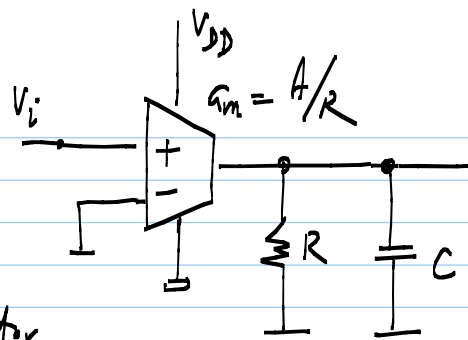
(4) (a) For the amplifier shown here, calculate the mean squared output noise voltage assuming that the transconductor



$G_m$  has an input referred noise voltage PSD of  $4kT/g_m$


(b) Assuming that  $V_i = \frac{V_p}{A} \cos \omega t$ , and a low frequency  $\omega$ , calculate the output mean squared signal voltage

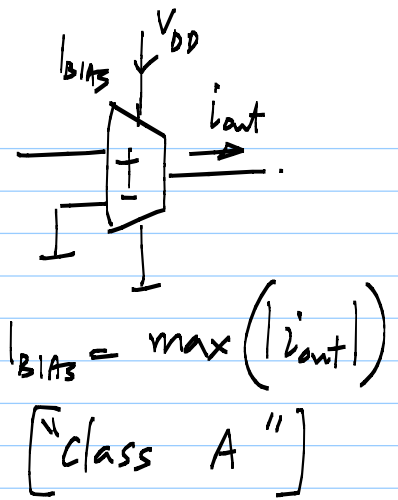- (c) Assuming a "class A" transconductor, determine the power drawn (average power over one output cycle) from the supply for the above signal



- (d) Express the power dissipated ( $P_d$ ) in terms of the signal to noise ratio and the bandwidth

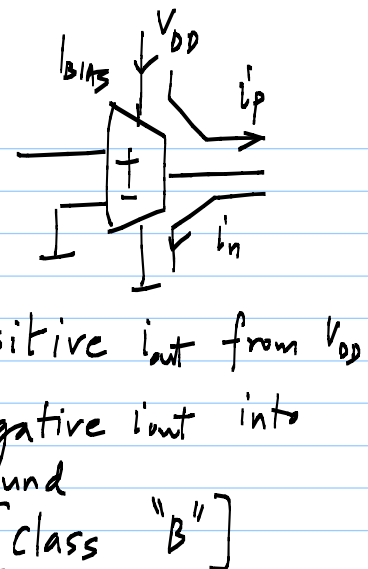- (e) Assuming a "class B" transconductor, determine the power drawn (average power over one output cycle) from the supply for the above signal



- (f) Express the power dissipated ( $P_d$ ) in terms of the signal to noise ratio and the bandwidth

(5) What do you infer from the relationships between  $P_d$ ,  $\frac{S}{N}$ , and  $f_B$  in the previous problems?

(6) Calculate the output noise PSD & the input referred noise PSD due to the opAMP noise ( $PSD = S_{V,opA}$ ), with and without  $R_2$ .

