

31/7/13

Lec 1



Resonance ← amplify only the freq. of interest

* Local Osc. — noise (LC oscillators have lower noise)

* Most RF circuits are narrowband

* Series & Parallel Resonance

1) Parallel Resonance

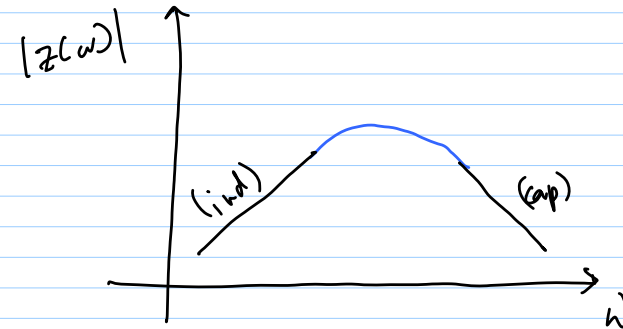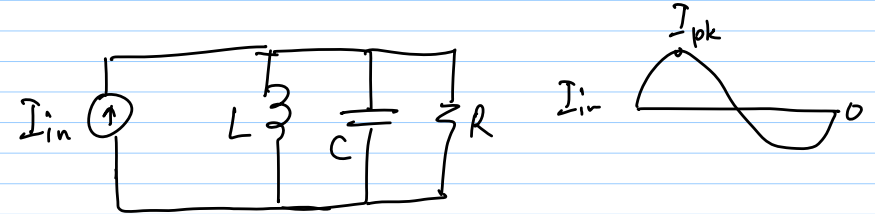



$$Y(\omega) = \frac{1}{R} + j\omega C + \frac{1}{j\omega L}$$

$$= \frac{1}{R} + j\left(\omega C - \frac{1}{\omega L}\right)$$

@ resonance (ω_0)

$$\omega_0 C = \frac{1}{\omega_0 L} \Rightarrow \boxed{\omega_0 = \frac{1}{\sqrt{LC}}}$$

$$Y(\omega_0) = \frac{1}{R}$$

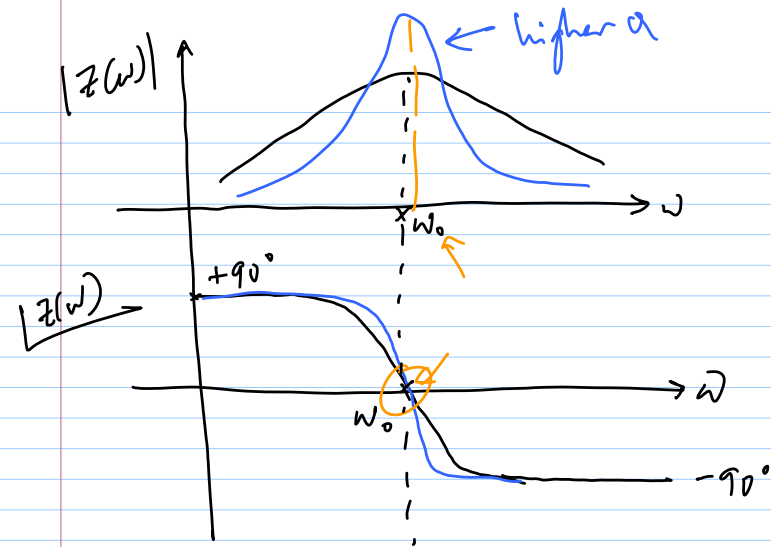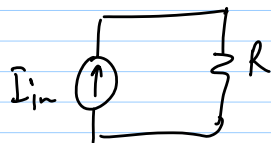

Quality Factor $\equiv Q$

$$Q \equiv \omega \cdot \frac{\text{Energy stored}}{\text{Average power dissipated}}$$

@ $\omega = \omega_0$, $V_{out} = I_{in} \cdot R$

$$V_{out\ pk} = I_{pk} \cdot R \Rightarrow E_{tot.} = \frac{1}{2} C (I_{pk} \cdot R)^2$$

$$P_{av.} = (I_{rms})^2 \cdot R = \left(\frac{I_{pk}}{\sqrt{2}}\right)^2 \cdot R = \frac{1}{2} I_{pk}^2 \cdot R$$


$$Q = \omega_0 \cdot \frac{\frac{1}{2} C I_{pk}^2 \cdot R^2}{\frac{1}{2} I_{pk}^2 \cdot R} = \omega_0 C R$$

$$Q = \omega_0 C R$$

$$= \frac{R}{\omega_0 L}$$

$$= \frac{R}{\sqrt{L/C}} \leftarrow \text{characteristic impedance}$$

@ resonance
 $|Z_L| = \omega_0 L = \sqrt{L/C} = |Z_C|$

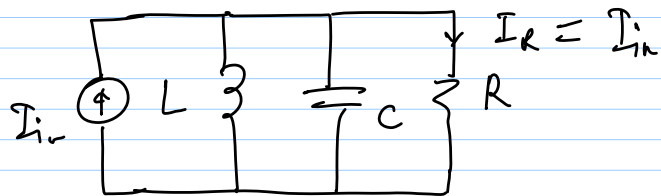

$$\begin{aligned} * |I_L| &= \frac{|V_{out}|}{\omega_0 L} = \frac{|I_{in} \cdot R|}{\omega_0 L} = Q \cdot |I_{in}| \\ &= |I_C| \quad (\text{worry about this during layout}) \end{aligned}$$

BW & Q

$$Y(\omega) = \frac{1}{R} + \frac{j}{\omega L} (\omega^2 LC - 1)$$



$$\begin{aligned} Y(\omega_0 + \Delta\omega) &= \frac{1}{R} + \frac{j}{(\omega_0 + \Delta\omega)L} \left[(\omega_0 + \Delta\omega)^2 LC - 1 \right] \\ &= \frac{1}{R} + \frac{j}{\omega_0 L \left[1 + \frac{\Delta\omega}{\omega_0} \right]} \left[\cancel{\omega_0^2 LC} + 2\omega_0 \Delta\omega LC - \cancel{\Delta\omega^2 LC} - 1 \right] \end{aligned}$$

$$= \frac{1}{R} + \frac{j}{\cancel{\omega_0 L} \left[1 + \frac{\Delta \omega}{\omega_0} \right]} \cdot \cancel{\omega_0 \Delta \omega} L \left[2 + \frac{\Delta \omega}{\omega_0} \right]$$

$$\approx \frac{1}{R} + j \Delta \omega C \left(2 + \frac{\Delta \omega}{\omega_0} \right) \left(1 - \frac{\Delta \omega}{\omega_0} \right)$$

$$= \frac{1}{R} + j \Delta \omega C \left[2 - \frac{2 \Delta \omega}{\omega_0} + \frac{\Delta \omega}{\omega_0} - \left(\frac{\Delta \omega}{\omega_0} \right)^2 \right]$$
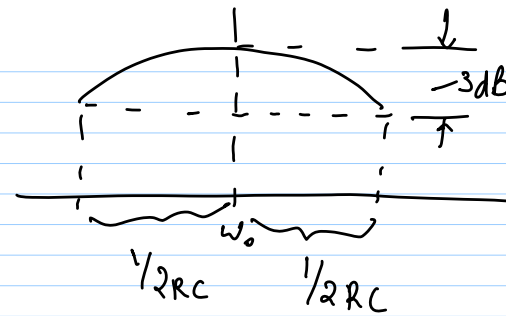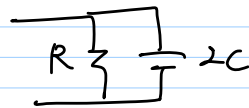
$$\approx \frac{1}{R} + j 2 \Delta \omega C$$



$$\text{total BW} = \frac{1}{RC}$$

$$\frac{\omega_0}{\text{BW}} = \frac{\omega_0}{1/RC} = \omega_0 RC \equiv Q$$

Definitions of Q

1) Physical def.

$$Q \equiv \omega_0 \frac{E_{\text{tot.}}}{P_{\text{av.}}}$$

can be used for RC, RL networks
also

2) $Q = \frac{\text{Im}(Z(\omega))}{\text{Re}(Z(\omega))}$ ← either the
w -ve part
of Im(Z(ω))

3) $Q = \frac{\omega_0}{\text{BW}}$

4) $Q = \frac{\omega_0}{2} \left| \frac{d\phi}{d\omega} \right|$
 $\phi(\omega) = \text{phase of OL TF}$