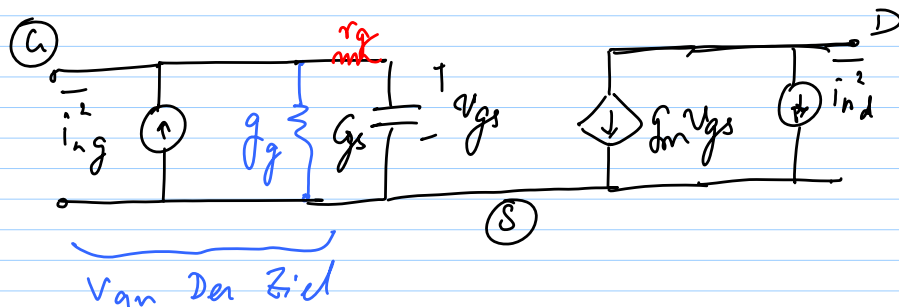


2-9-13

Lec 13

MOSFET 2-port noise parameters

* Refer to section 12.2 of T. Lee's textbook



$$\overline{i_{ng}^2} = 4kT \delta f_g \Delta f$$

$$g_g = \frac{W^2 C_{gs}^2}{5 g_{ds}} = \frac{W^2 C_{gs}}{5} \cdot \frac{C_{gs}}{g_{m/\alpha}}$$


$$= \frac{W^2 C_{gs} \cdot \alpha}{5 V_T}$$

δ = empirical value


$$\delta = 2\delta^2$$

$$* C \equiv \frac{\overline{i_{ng} \cdot i_{nd}^*}}{\sqrt{\overline{i_{ng}^2}} \sqrt{\overline{i_{nd}^2}}}$$


= j0.395 for a long-channel MOSFET

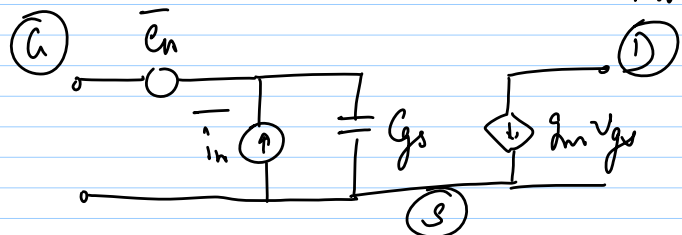

(a)

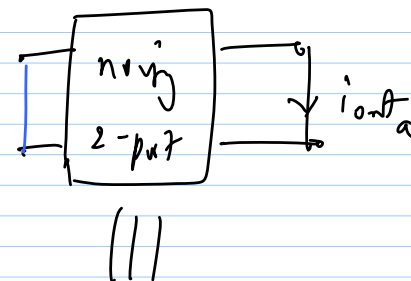


(b)

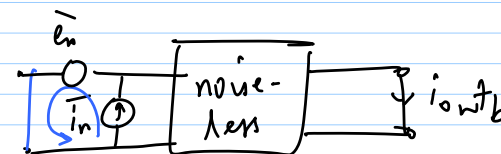


- 1) Input o.c.
- 2) " s.c.

Noise Figure

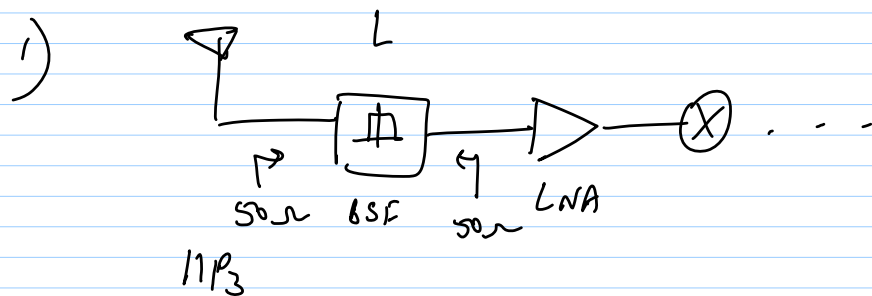

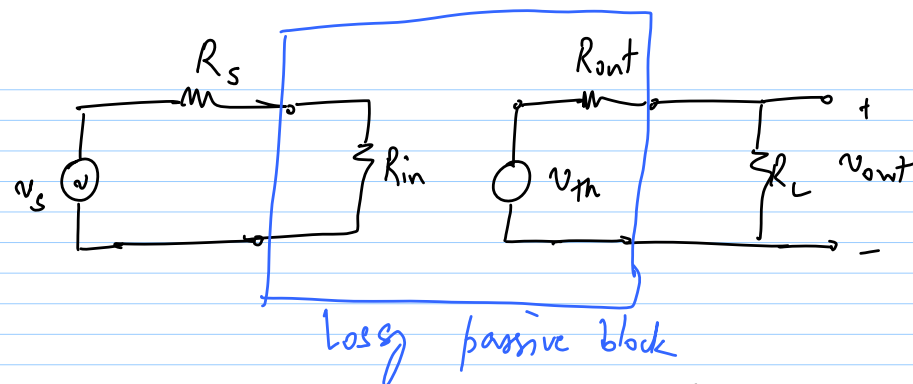
- ① SNR limited by frontend blocks
- ② NF of lossy passive block



$$L = \frac{P_{in}}{P_{out}} \quad R_s = R_{in} \quad R_{out} = R_L$$

$$L_{dB} = P_{in}/dB - P_{out}/dB$$
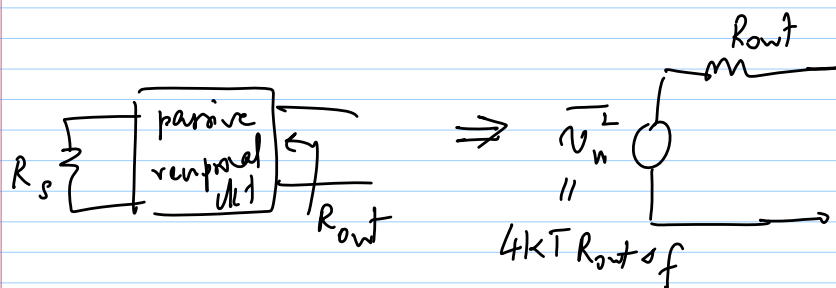
$$L = \frac{v_s^2 / 4R_s}{(v_n^2 / 4R_{out})} = \frac{v_s^2}{v_n^2} \cdot \frac{R_{out}}{R_s}$$



$$\frac{\overline{v_{n,out}^2}}{\Delta f} = 4kTR_{out} \left(\frac{R_L}{R_L + R_{out}} \right)^2$$

$$A_v = \frac{v_{th}}{v_s} \cdot \left(\frac{R_L}{R_L + R_{out}} \right)$$

$$F = \frac{\overline{v_{n,out}^2}}{\overline{v_n^2} \cdot A_v^2} = \frac{4kTR_{out} \left(\frac{R_L}{R_L + R_{out}} \right)^2}{4kTR_s \cdot \frac{v_n^2}{v_s^2} \cdot \left(\frac{R_L}{R_L + R_{out}} \right)^2}$$

$$= \frac{v_s^2}{v_n^2} \cdot \frac{R_{out}}{R_s} = L \quad \boxed{NF = L_{dB}}$$