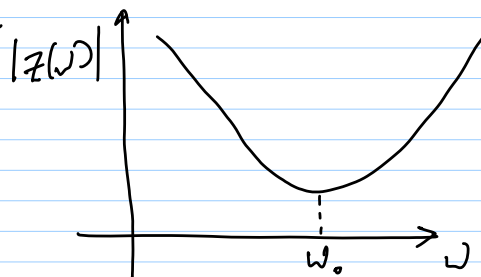
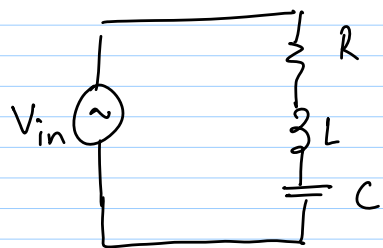


2/8/13



Lec 2Series Resonance

$$Z(\omega_0) = R \quad ; \quad Q = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 C R} \quad \checkmark$$

at resonance, $|V_L| = |V_C| = Q \cdot V_R$


Impedance Transformation

- * Minimise reflections $|\Gamma| = \left| \frac{Z_L - Z_0}{Z_L + Z_0} \right|$
- * Max power transfer $Z_L = Z_0^*$

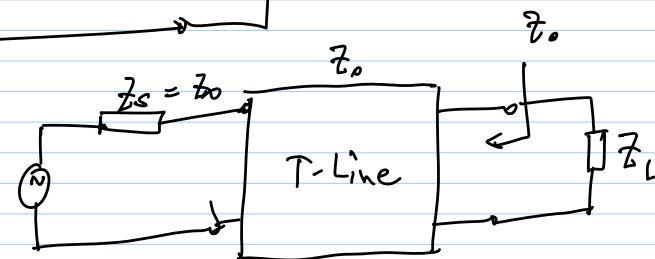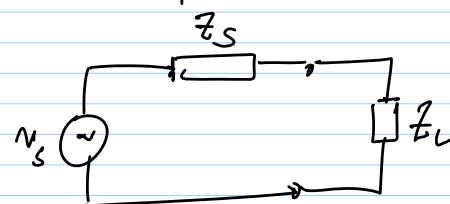

* RF impedances — 50Ω, 75Ω

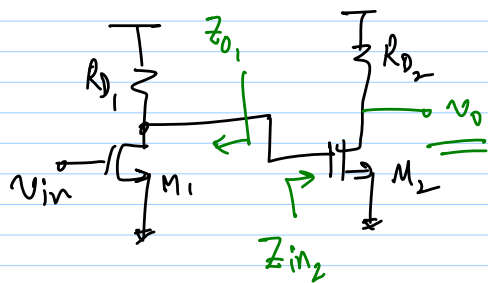- * On-chip — small distances (lumped eq.)
- small R loads (typical IC requires power $R > k\Omega$)



$$Z_{01} = R_{D1} \parallel r_{ds1} \parallel \frac{1}{j\omega C_{gs1}}$$

$$Z_{01} = Z_{in2}^*$$

$$Z_{in2} = \frac{1}{j\omega C_{gs2}}$$

$$P_{out} = \frac{|V_{rms}|^2}{R_{D2}}$$

