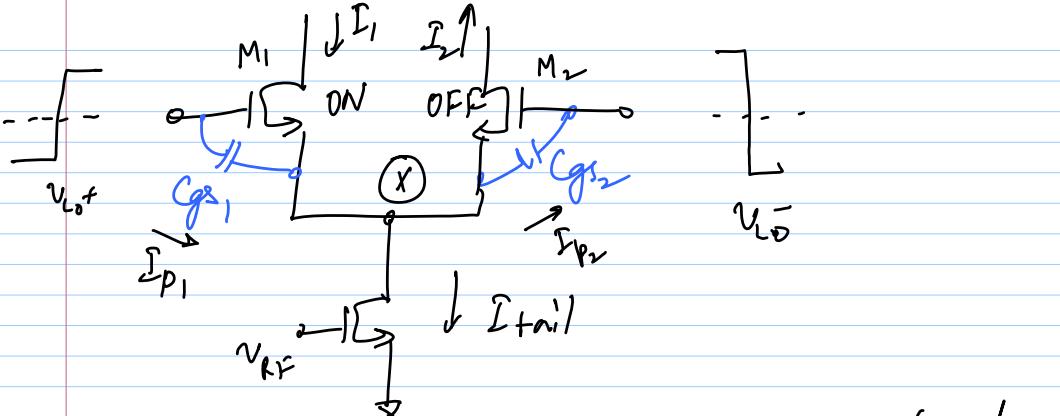
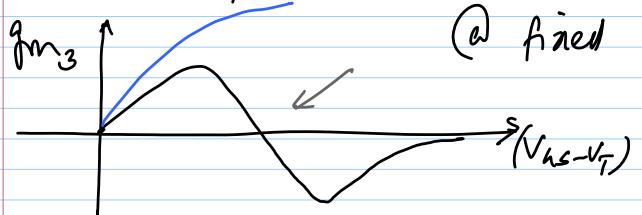


23/9/13

## Lec 22

Linearity of Gilbert Mixer1)  $G_m$ - non linearity



$$V_{RF} + V_{RF} \rightarrow I_{out} = I_{DC} + g_{m_1} V_{RF} + g_{m_2} V_{RF}^2 + g_{m_3} V_{RF}^3 + \dots$$

to improve  $IIP_3$   $\rightarrow \uparrow(V_{AS} - V_T)$ (a) fixed  $I_{DC}$ ,  $g_m \downarrow \Rightarrow h_c \downarrow \Rightarrow NF \uparrow$ 

$$C_{GS1} = \frac{2}{3} WL_Cox ; C_{GS2} = WL_D Cox \quad (\text{overlap } C_{GS})$$

KCL @ node x

$$I_1 + I_{P1} = I_2 + I_{P2} + I_T$$

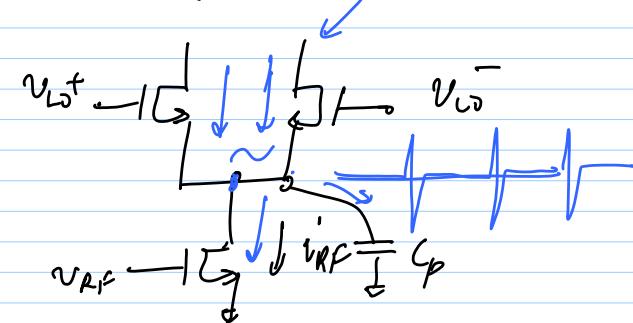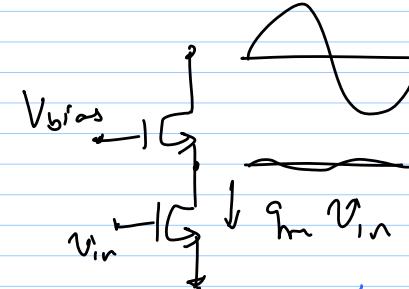
2) LO switch nonlinearity

$$\begin{aligned} I_1 &= I_T + (I_{P2} - I_{P1}) \\ &\approx I_T - I_{P1} \quad (\because I_{P1} \gg I_{P2}) \\ &= I_T - C_{GS1} \cdot \frac{d}{dt} (V_{LO} - V_X) \end{aligned}$$

displacement current

- \* If  $I_1$  becomes small enough,  $M_1$  ( $\& M_2$ ) may leave sat. region
- \*  $\frac{dV_{LO}}{dt}$  is large (i.e. LO signal has

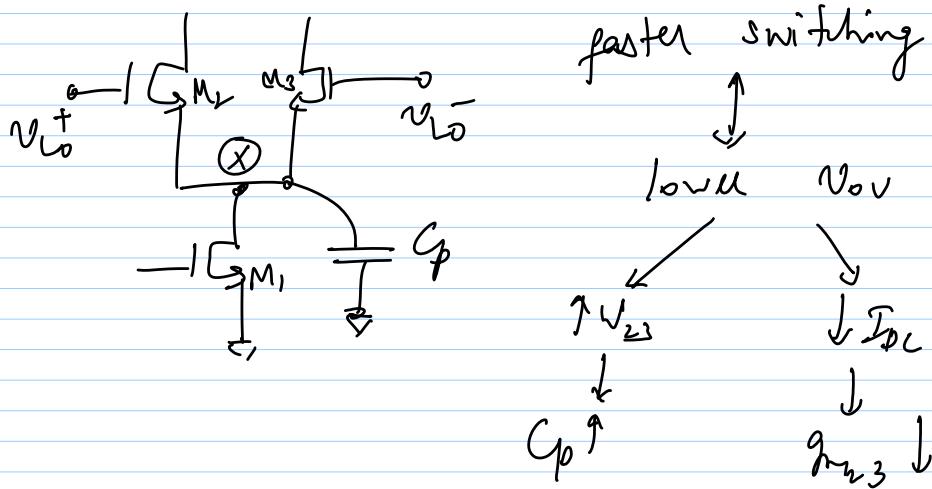
sharp edges)  $\Rightarrow$  more nonlinear




### Noise in Gilbert-cell Mixers

#### 1) Load noise

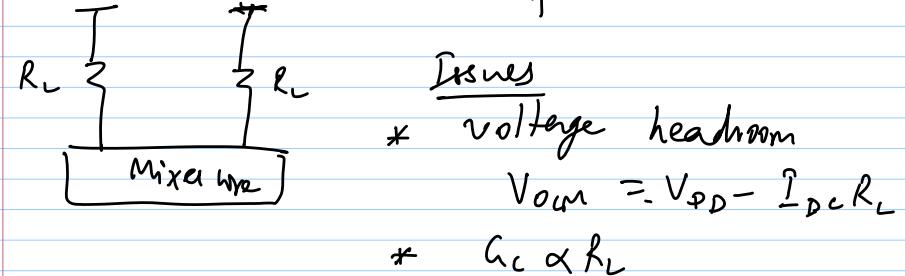a)  $R_L \times \frac{V_{on}^2}{R_L} = \delta kT R_L$   
 \* no flicker noise



#### b) PMOS loads (active load)

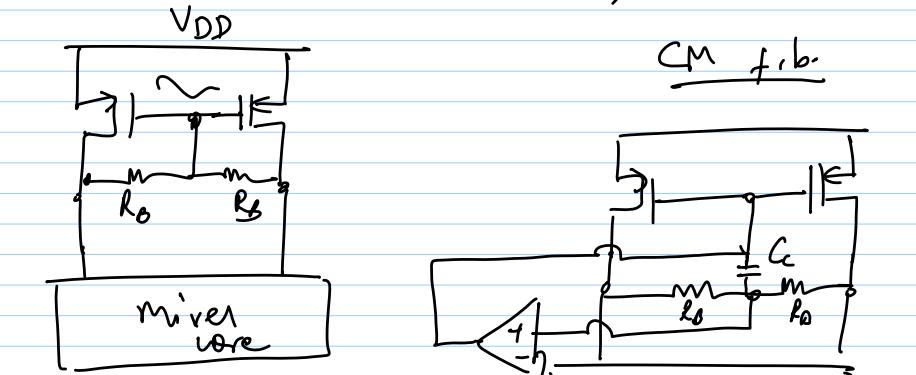

$$V_{out} = V_{DD} - V_{Asg}$$

$$L_c \propto R_S, g_{M_P}$$

$$V_{out} = V_{DD} - V_{Asg} \cdot \frac{1}{R_S}$$

$C_C$  - mixer comb cap

\* Noise from PMOS devices  
 →  $y_f$  noise & thermal noise

Large large PMOS