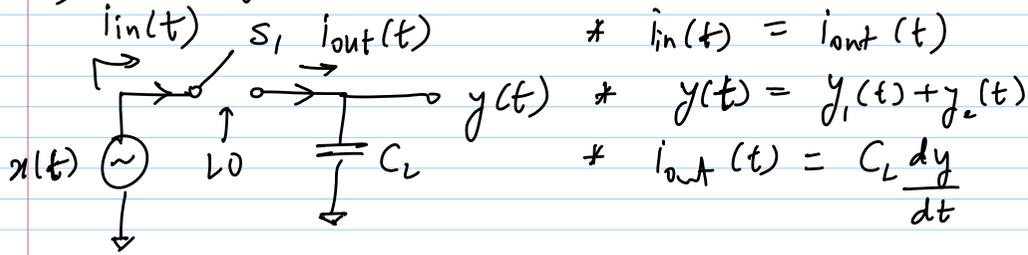


1/10/13

Lec 2b

Input impedance of PM

1) Voltage-driven PM



$$I_{in}(f) = j\omega C_L Y(f)$$

* $x(t)$ is narrowband \Rightarrow we are interested in freq. component of $I_{in}(f)$ corresponding to this

$$Y_1(f) = X(f) * \left[\frac{1}{j\omega} (1 - e^{-j\omega T_{Lo}/2}) \cdot \frac{1}{T_{Lo}} \sum_{k=-\infty}^{\infty} \delta(f - kf_{Lo}) \right]$$

$$Y_2(f) = \left[X(f) * \frac{1}{T_{Lo}} \sum_{k=-\infty}^{\infty} e^{-j\omega T_{Lo}/2} \delta(f - kf_{Lo}) \right] \cdot \frac{1}{j\omega} (1 - e^{-j\omega T_{Lo}/2})$$

* Set $k=0$ for freq. component of interest

$$Y_1(f) \rightarrow \frac{X(f)}{2}$$

$$Y_2(f) \rightarrow \frac{1}{T_{Lo}} \cdot X(f) \cdot \left[\frac{1}{j\omega} (1 - e^{-j\omega T_{Lo}/2}) \right]$$

$$Y_{in}(f) = \frac{I_{in}(f)}{X(f)} = j\omega C_L \left[\frac{1}{2} + \frac{1}{j\omega T_{Lo}} (1 - e^{-j\omega T_{Lo}/2}) \right]$$

a) $\omega \ll 2\pi f_{Lo}$
 $Y_{in}(f) = j\omega C_L$ (Tx)

b) $\omega = 2\pi f_{Lo}$ (DCR): second term = $\frac{1}{j\pi}$

$$Y_{in}(f) = j\frac{\omega C_L}{2} + 2fC_L$$

c) $\omega \gg 2\pi f_{Lo}$, second term is negligible

$$\Rightarrow Z_{in}(f) = \frac{j\omega C_L}{2}$$


Single-balanced PM, with $\omega \approx \omega_{Lo}$

$$Z_{inSB} = \frac{1}{2} \left[R_{sw} + \frac{1}{2fC_L + j\frac{\omega C_L}{2}} \right]$$

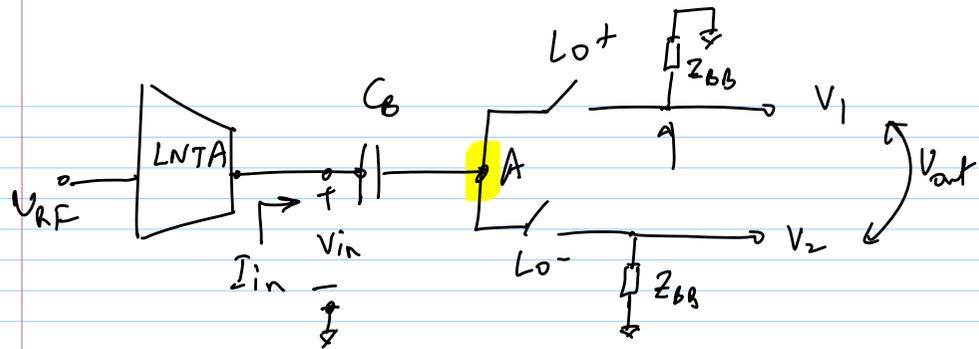2) Current mode PM


* Z_{in} could be different because the PM is time variant

$$* Z_{in}(f) = \frac{V_{in}(f)}{I_{in}(f)}$$



Z_{BB} has impulse response $h(t)$



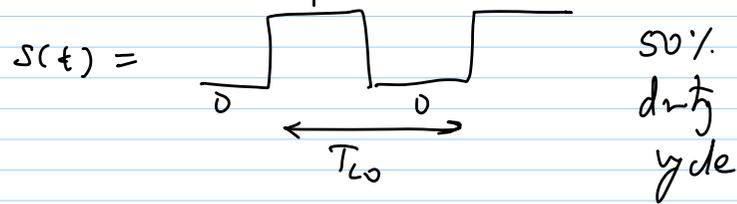
$$V_1(t) = [I_{in}(t) \times S(t)] * h(t)$$




$$V_1(f) = [I_{in}(f) * S(f)] \cdot Z_{BB}(f)$$

- * $I_{in}(f)$ convolved with 1st harmonic of $S(f)$ - freq. translation to $I_{IF}(f)$
- * $V_1(f) = I_{IF}(f) \cdot Z_{BB}(f)$
- * $V_1(t)$ & $V_2(t)$ are multiplied with $S(t)$ - up-converted to RF


$I_{in}(f)$

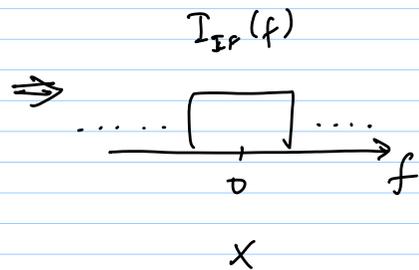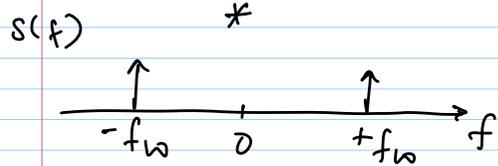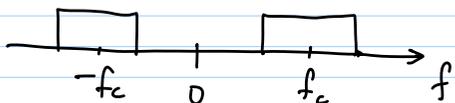

V_{in} at input node A

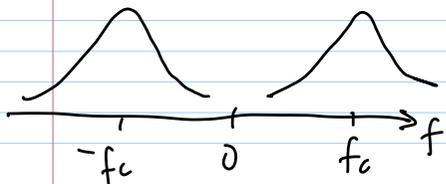

upconversion

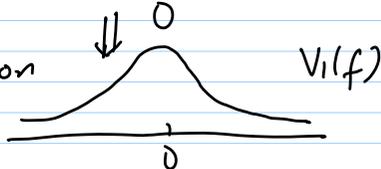

- * RF voltage spectrum is shaped by $Z_{BB}(f)$
- Lowpass - becomes Bandpass @ RF
- * Noise & linearity of current mode PM are better - because the mixer is in series with input current source

PM I_0 swing

- as large as possible (not a problem @ moderate freq.)
- 50% duty cycle

duty cycle = d ← maximise

$$I_{IP}(t) = \frac{2}{\pi} \frac{\sin(\pi d)}{2d} I_{RF0} \cos \omega_{IPT} t$$

best case - impulse sampling

- generating impulses is difficult
- 25% duty cycle is easy to generate
- gives 3dB ($\sqrt{2}$ times) more gain
- $G_c = \frac{2\sqrt{2}}{\pi}$ for $d = 0.25$
- LQ_0 & LQ_{100} and LQ_{90} & LQ_{270} are

not on simultaneously - lower noise
& NL