

5-8-13


Lec 3

* 50 Ω impedance is the RF std.

→ don't drive 50 Ω on-chip


* chip boundary - match to 50 Ω

Impedance xformation

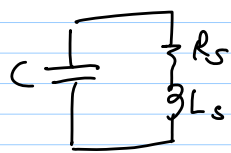

neither series nor 11^l

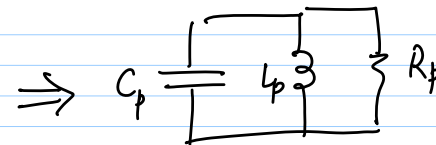@ resonance - do series to parallel conv.



$$C_p = C$$

$$R_s + j\omega_0 L_s = \frac{R_p \cdot j\omega_0 L_p}{R_p + j\omega_0 L_p}$$

$$= \frac{(\omega_0 L_p)^2 \cdot R_p + j\omega_0 L_p R_p^2}{R_p^2 + \omega_0^2 L_p^2}$$

Equate real parts


$$R_s = \frac{(\omega_0 L_p)^2 \cdot R_p}{R_p^2 + (\omega_0 L_p)^2}$$

Im part

$$\omega_0 L_s = \frac{\omega_0 L_p R_p^2}{R_p^2 + (\omega_0 L_p)^2}$$

$$Q_s = \frac{\omega_0 L_s}{R_s} ; Q_p = \frac{R_p}{\omega_0 L_p} ; Q_p = Q_s = Q$$
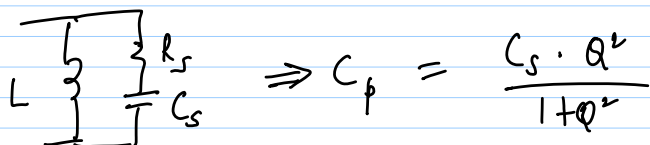
$$R_p = R_s (1 + Q^2) ; L_p = \frac{L_s (1 + Q^2)}{Q^2}$$



$$\Rightarrow C_p = \frac{C_s \cdot Q^2}{1 + Q^2}$$


Impedance matching

discrete RF


- 1) $\lambda/4$ xfmr.
- 2) Stub matching
- 3) xfmr

L-match networks

Upward xformation

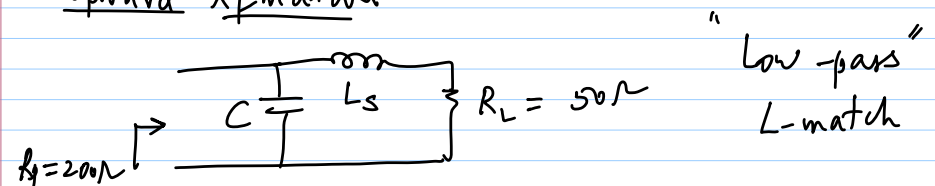

"low-pass"
L-match

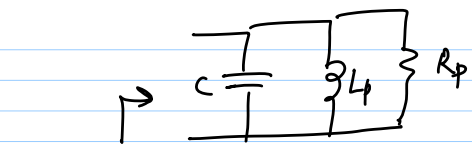

200Ω
(R_p @ resonance)

$$L_p = \frac{L_s (1 + Q^2)}{Q^2}$$





$$R_p = R_s (1 + Q^2)$$

$$Q = \sqrt{\frac{R_p}{R_s} - 1} = \sqrt{3} = 1.732$$



$\frac{\omega_0}{2\pi}$ = freq. of operation (known)

from $Q, \omega_0, R_p, R_s \Rightarrow L_s$ & L_p are known
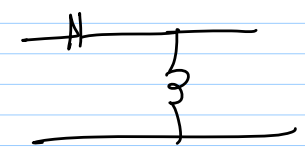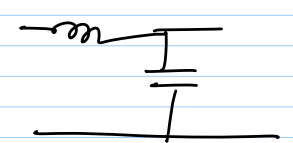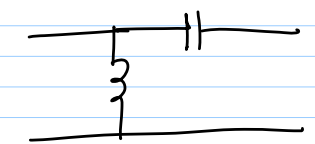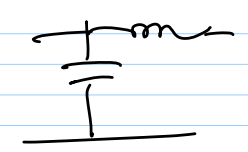
$$\omega_0 = \frac{1}{\sqrt{CL_p}} \Rightarrow \text{find } C$$



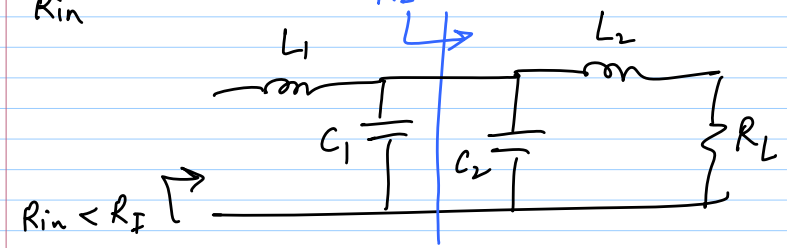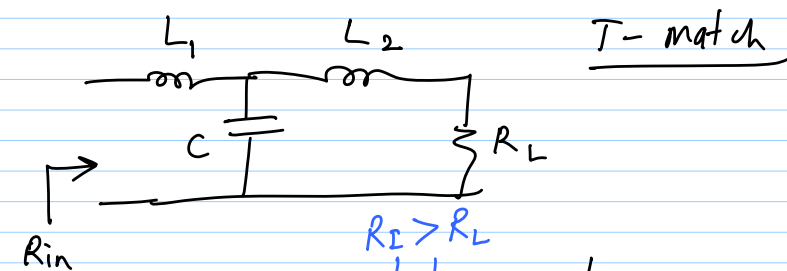
To design for BW, need 3rd degree of freedom - design for Q_s .




$\omega_0, R_{in}/R_s, Q$

$$Q = Q_L + Q_R \checkmark$$

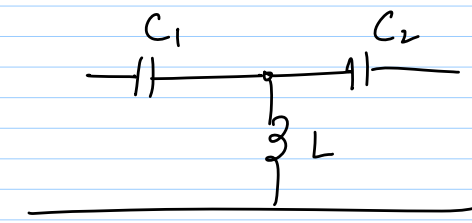
$$Q = \sqrt{\frac{R_L}{R_{in}} - 1} + \sqrt{\frac{R_L}{R_L} - 1}$$



HP T-match

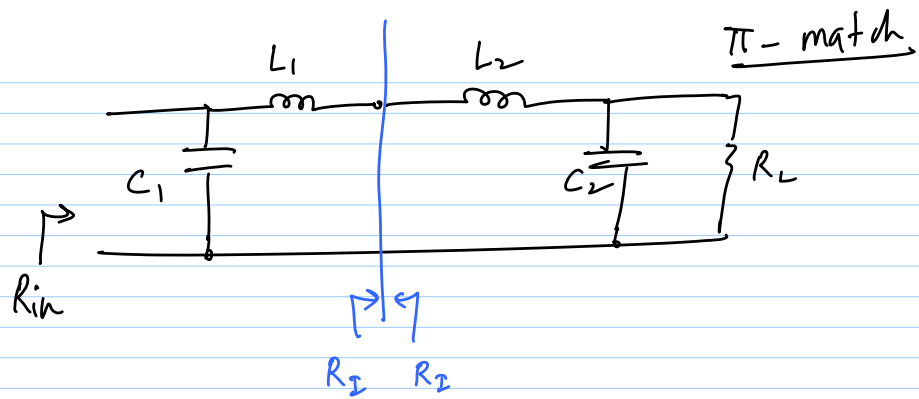

$$R_1 < R_{in} ; R_2 < R_L$$

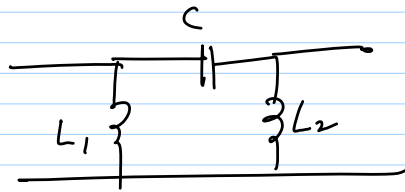

- 1) Q - choose between L & T/π
- 2) Low-pass or high-pass
- 3) Area - # of components
 - # of L 's
 - value of L 's & C 's
- 4) Insertion loss - loss in the components
 (L 's have low Q)