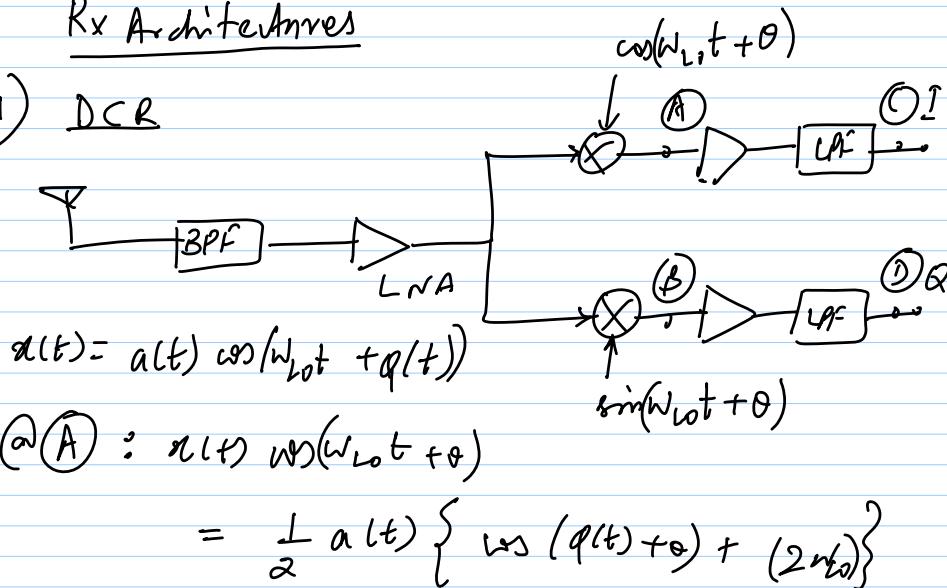


14-10-13

Lec 30

Rx Architectures

i) DCR



* Why both I & Q

a) I & Q can be independently mod.

b) $\theta \neq 0$

we are trying to transmit AM ($\varphi(t) \approx 0$)

$$\alpha(t) = a(t) \cos(\omega_{Lo}t)$$

$$\theta = 90^\circ \times$$

(C) : $\frac{1}{2} a(t) \cos \theta$

(D) : $\frac{1}{2} a(t) \sin \theta$ $\theta = 0^\circ \times$

Assume $\theta = 0$ (for now)

@ C $\Rightarrow \frac{1}{2} a(t) \cos(\varphi(t))$

@ D $\Rightarrow -\frac{1}{2} a(t) \sin \varphi(t)$

Demod. algo: $\sqrt{c^2 + d^2} = \frac{1}{2} a(t) \leftarrow \text{AM}$



from
quadrant
 $\tan^{-1} \frac{d}{c} = \varphi(t) \leftarrow \text{PM}$

c) PM

$$\alpha(t) = A \cos(\omega_{Lo}t + \varphi(t))$$

$$\alpha_I(t) = A \cos \varphi(t)$$



$$\alpha_Q(t) = A \sin \varphi(t)$$

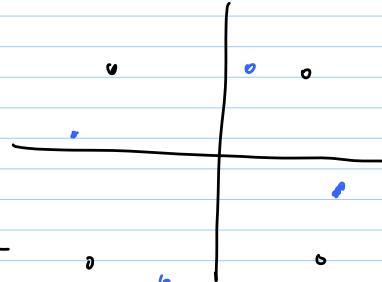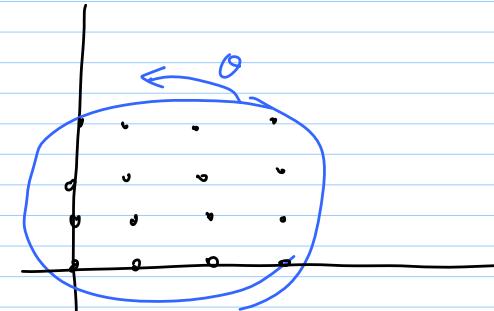

Advantages of DCR

- * Simplest Rx arch.
- * No image problem ($w_{IF} = 0$)
- * Highly integrable, no IR filter, no var drive
- * Filtering is easy
- * ADC is easy
- * Only PLL needed.

Disadvantages of DCR

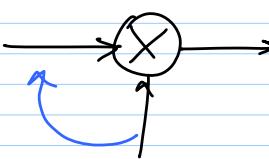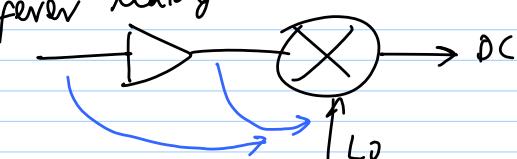- i) $y_f \text{ NOV}$ of BB blocks - large devices
- ii) DC offsets : -
- iii) RF  DC offset Lo self mixing
- iv) Interferer leakage  DC offsets

v) Lo pulling - RF signal becomes too large
& pulls Lo signal

vi) Even order Distortion

